

**Problem S4 (Signals and Systems)**

For the circuit of Problem S3, find the branch voltages and branch currents using the loop method. Of course, your answer should agree with that of Problem S3.