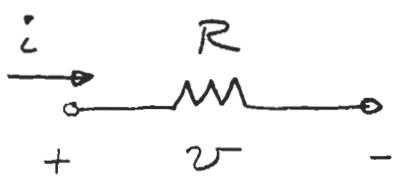


From last time:



The constitutive relation is

$$V = iR \text{ "Ohm's law"}$$

Why do we choose the sign convention this way?


If  $V > 0 \dots$

- + terminal is at higher potential than - terminal, so...
- + charges move toward lower potential,  
- charges move toward higher potential, so...

current is + if drawn as shown.

Why is Ohm's law linear? Cannot easily derive — it's an experimentally observed fact about many materials.


The battery symbol is

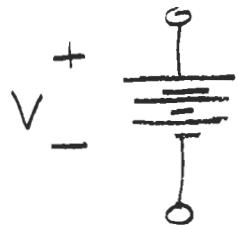

What is the constitutive relation for a battery?

(Will say more later...)

## The Voltage Source

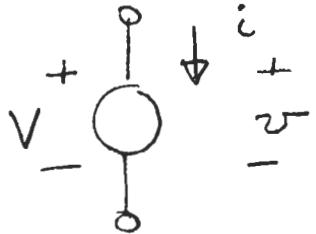

Constitutive relation:

$$v = V \text{ for all } i$$

Is this a good model for a battery?


[Do Battery Model concept test here]

Sometimes, a voltage source is a good model for a battery, sometimes it is not, depending on the current draw and the length of time it is used.


[Do Model Definition turn-to-partner exercise.]
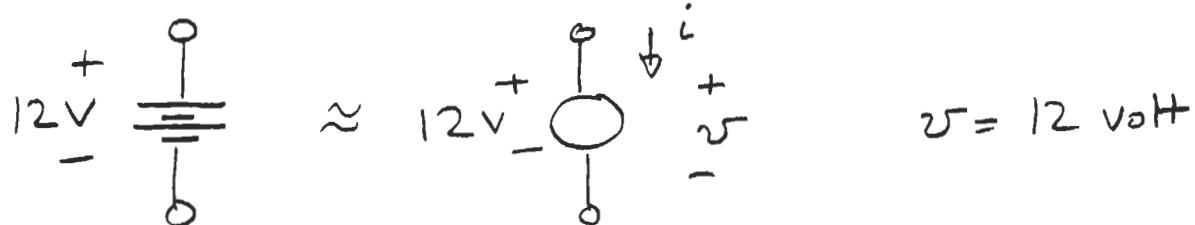
## Example Models of a battery

Case 1 Current is low enough that battery voltage is nearly constant.  
Then the model is




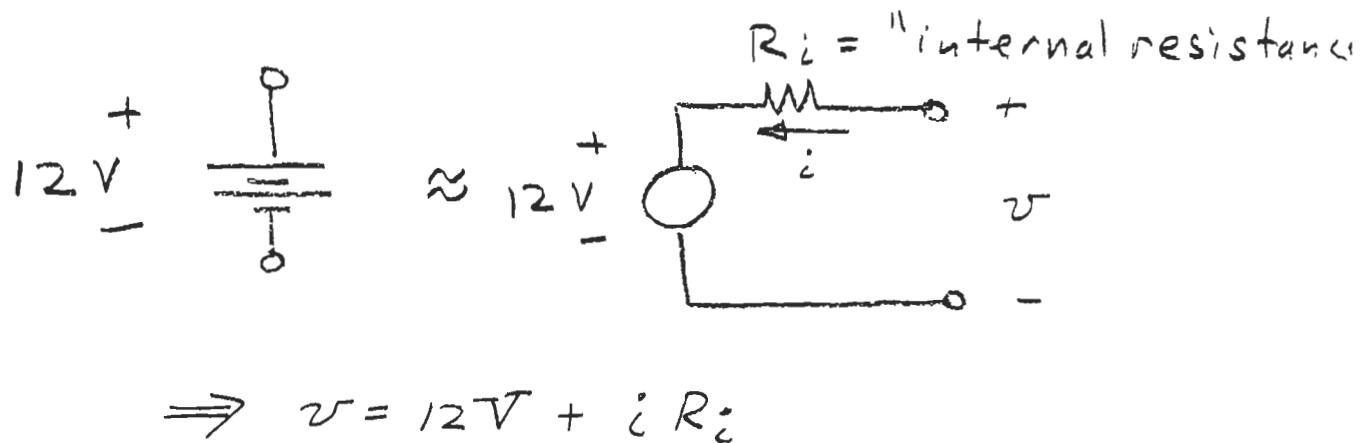Case 2 Current is significant enough that voltage varies due to current flow.



$$\Rightarrow v = 12V + iR_i$$

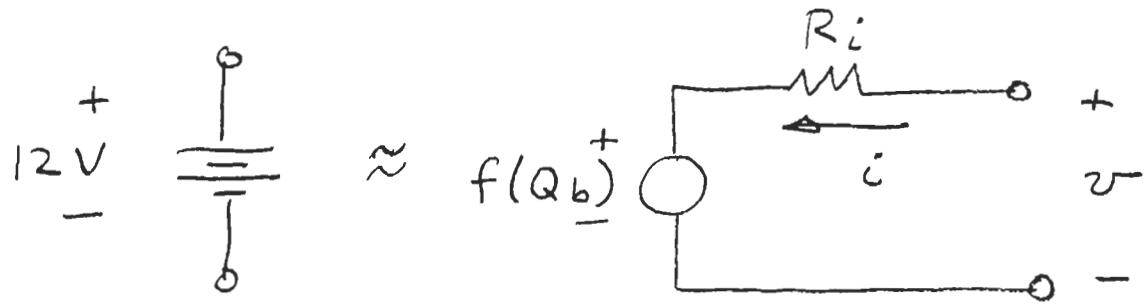Case 3 As in case 3, but battery runs long enough to be discharged, so voltage drops over time



$$v = f(Q_b) + iR_i$$


$Q_b$  = battery charge

$$= Q_i + \int_0^t i dt$$

$\uparrow$  initial charge

$R_i$  might also be a function of  $Q_b$ .

## The Current Source

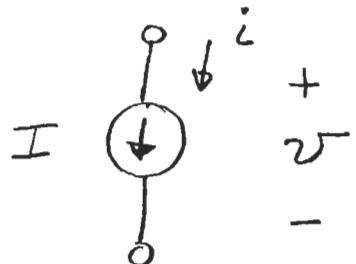


Constitutive relation:  
 $i = I$  for all  $v$

Current sources are useful idealizations of circuits that produce a nearly constant current for a range of loads. They are often seen in transistor amplifier circuits.

## Solving networks

By "solving," we mean finding all the branch currents and branch voltages in the circuit.

Simple example:

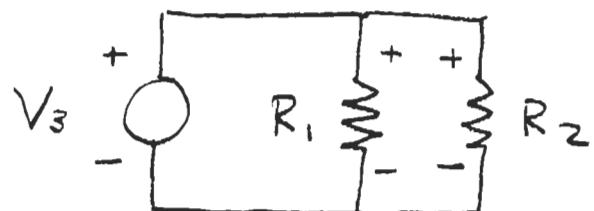

"Parallel" resistors

Find  $v_1, v_2, v_3, i_1, i_2, i_3$ :

$$V_1 = V_2 = V_3 = V_3 \quad (\text{why?}) \quad (1)$$

$$i_1 = \frac{V_1}{R_1} = \frac{V_3}{R_1} \quad (\text{constitutive relation for } R_1)$$

$$i_2 = \frac{V_2}{R_2} = \frac{V_3}{R_2} \quad (\text{constitutive relation for } R_2)$$

$$i_3 + i_1 + i_2 = 0 \quad (\text{why?}) \quad (2)$$

$$\begin{aligned} \Rightarrow i_3 &= -\left(\frac{1}{R_1} + \frac{1}{R_2}\right)V_3 \\ &= -\frac{V_3}{R} \end{aligned}$$

$$R = R_1 \parallel R_2 = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$

To solve, we used the constitutive relations for the elements, plus Kirchhoff's laws

(1) comes from Kirchhoff's Voltage Law (KVL)

(2) comes from Kirchhoff's Current Law (KCL)