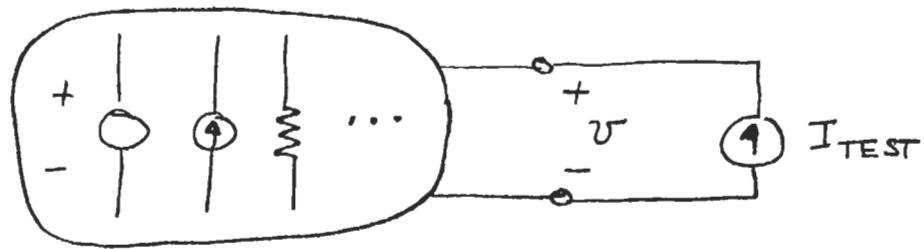


Thevenin and Norton Equivalent Networks




If we control current at terminal, what is voltage?

Analyze by superposition!

$$U = a_1 V_1 + a_2 V_2 + \dots + b_1 I_1 + b_2 I_2 + \dots + R_T I_T$$

↗ internal voltage source ↗ internal current source
 ↘ external test current

$$S_0 \quad v = V_T + R_T I_{TEST}$$

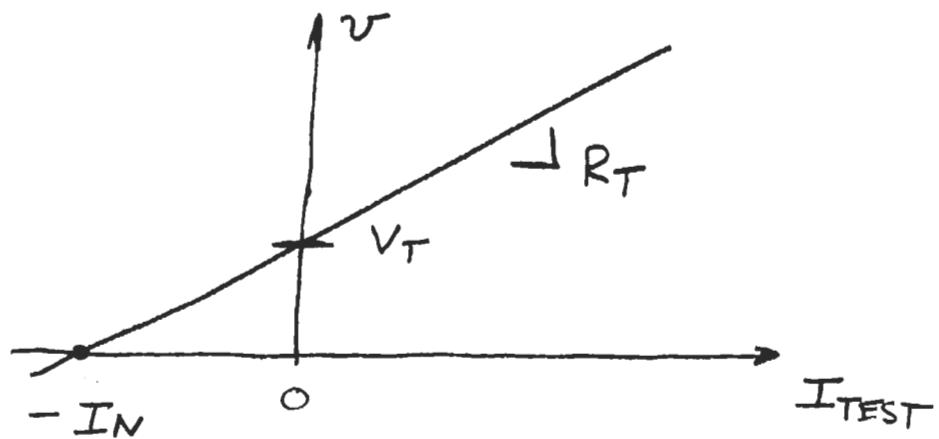

V_T = Thevinin equivalent voltage
= "open circuit voltage"


R_T = Thevinin equivalent resistance
= "output resistance" (or "impedance")

I_N = "short circuit current"

Any two of the parameters above completely characterize the behavior of the circuit at the terminals


$$R_T = V_T / I_N$$

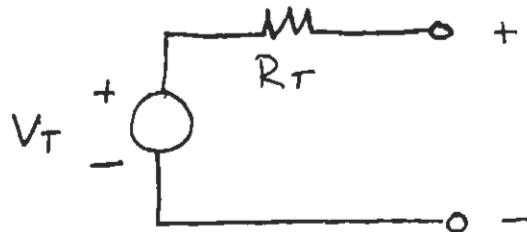Circuit with open-circuit voltage V_T , output resistance R_T :




Thevinin equivalent network

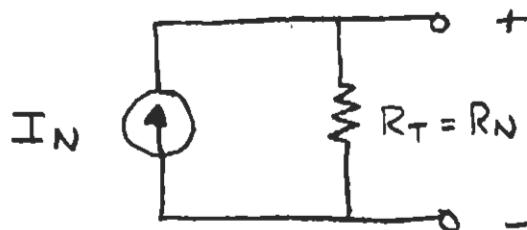Circuit with short-circuit current I_N , output resistance R_T :



Norton equivalent network

Example

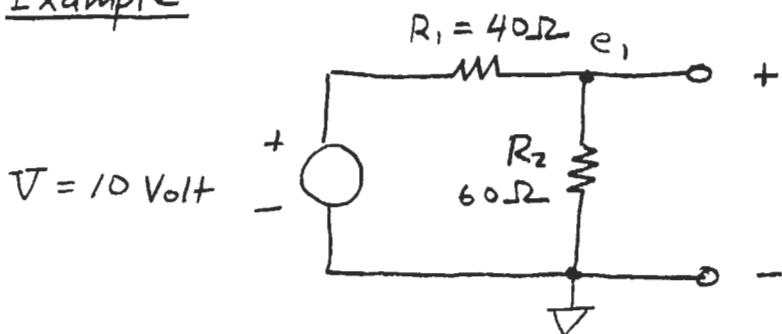

What is Thevinin equivalent?

Method 1:

Find V_T = open circuit voltage


$$= \frac{R_2}{R_1 + R_2} \cdot V$$

$$= \frac{60}{40 + 60} \cdot 10 \text{ volt} = 6 \text{ volt} \quad (\text{could use node method})$$


Find R_T = output resistance with all sources = 0

$$R_T = \frac{M}{R_2} = R_1 \parallel R_2 = \frac{40 \cdot 60}{40 + 60} = 24\Omega$$


Thevinin equivalent:

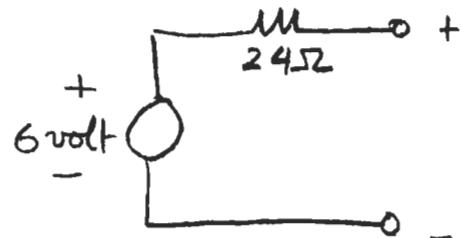

Norton Equivalent:

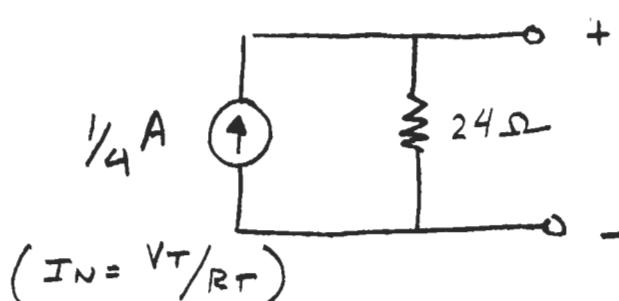

Method 2: Node method

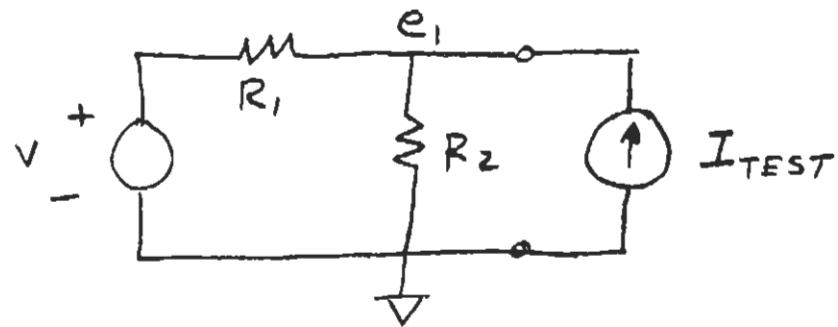

$$\left(\frac{1}{R_1} + \frac{1}{R_2} \right) e_1 - \frac{1}{R_1} V - I_{TEST} = 0$$

$$\Rightarrow e_1 = \left(\frac{1}{R_1} V + I_{TEST} \right) / \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$= \frac{R_2 V + R_1 R_2 I_{TEST}}{R_1 + R_2}$$

$$\Rightarrow V_T = \frac{R_2}{R_1 + R_2} V = 6 \text{ volt}$$

$$R_T = \frac{R_1 R_2}{R_1 + R_2} = R_1 \parallel R_2 = 24 \Omega \quad \checkmark$$