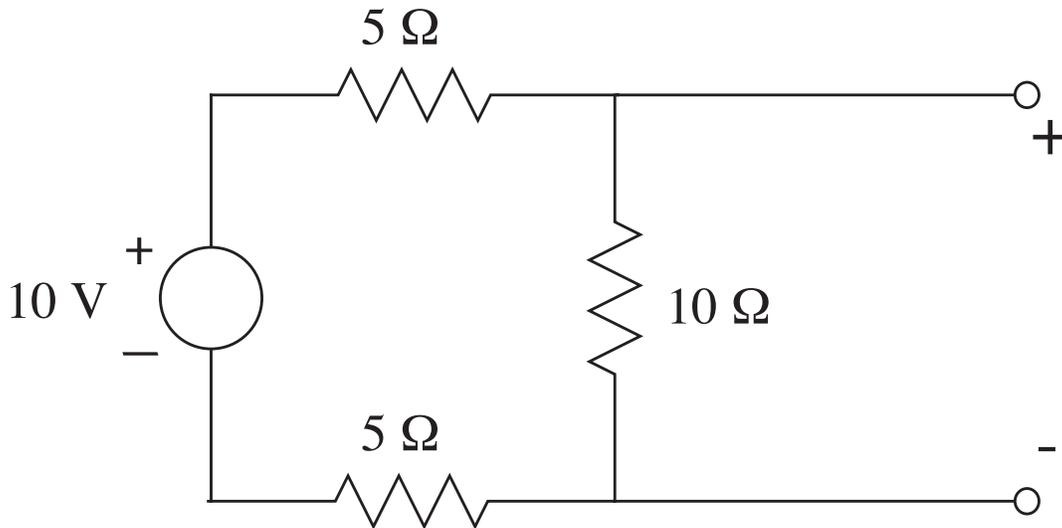




Thevenin Equivalent Circuit Concept Test



For the circuit above, the Thevenin equivalent circuit has

1. $V_T = 10 \text{ V}, R_T = 10 \Omega$
2. $V_T = 10 \text{ V}, R_T = 20 \Omega$
3. $V_T = 10 \text{ V}, R_T = 5 \Omega$
4. $V_T = 5 \text{ V}, R_T = 10 \Omega$
5. $V_T = 5 \text{ V}, R_T = 20 \Omega$
6. $V_T = 5 \text{ V}, R_T = 5 \Omega$

Thevenin Equivalent Circuit Solution

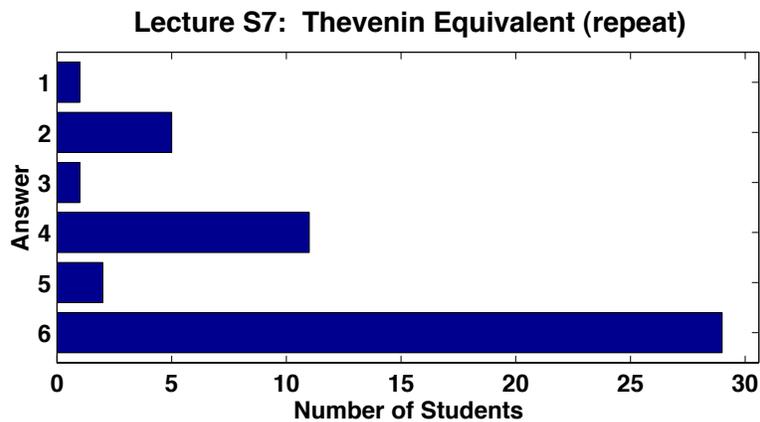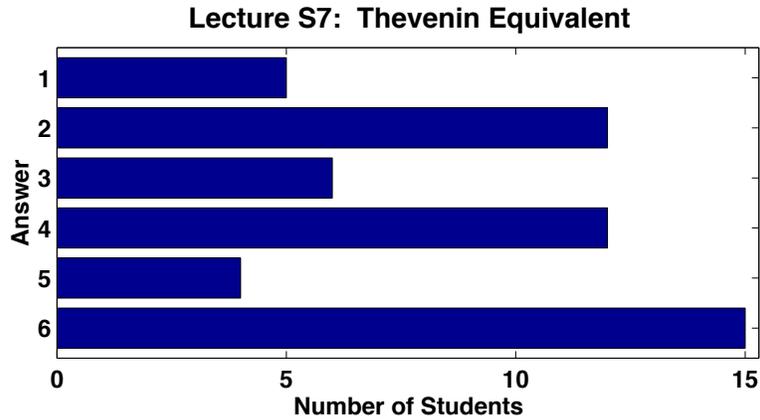

The open circuit voltage is given by

$$V_{oc} = \frac{10 \Omega}{5 \Omega + 10 \Omega + 5 \Omega} 10 \text{ V} = 5 \text{ V}$$

since the circuit is basically a voltage divider, with three resistors. Therefore,

$$V_T = V_{oc} = 5 \text{ V}$$

To find the Thevenin equivalent resistance, set all the sources to zero, and determine the resistance looking into the terminals. A voltage source of zero strength is a short circuit, so the result is that the two $5\ \Omega$ resistors are in series, forming an equivalent $10\ \Omega$. This is in turn in parallel with the $10\ \Omega$ resistor. The equivalent resistance of two $10\ \Omega$ resistors in parallel is $5\ \Omega$. Thus,

$$R_T = 5\ \Omega$$

The correct answer is therefore number 6. The class did much better on the second try.