


Lecture S7

Energy Storage Elements


- Resistive networks are static.
 Voltages and currents don't change with time, if sources are constant.
- Systems with energy storage elements are dynamic.
 Voltages and currents depend on time history of source strengths

Energy storage elements:

Capacitor:

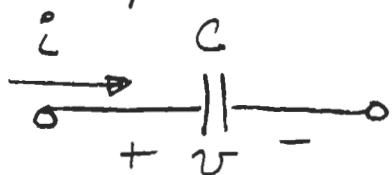

Inductor:

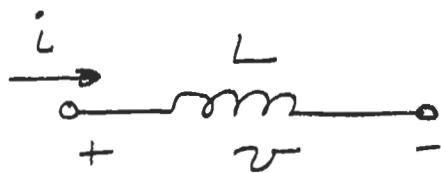

$$i = C \frac{dv}{dt}$$

$$v = L \frac{di}{dt}$$

Capacitors resist voltage change — requires current flow to change voltage

Inductors resist current change — requires voltage to change voltage

How much energy is stored?

$$\begin{aligned}\text{Energy} &= \int_{-\infty}^t \text{Power } dz \\ &= \int_{-\infty}^t i(z) v(z) dz \\ &= \int_{-\infty}^t C \frac{dv(z)}{dz} v(z) dz \\ &= \frac{1}{2} Cv^2(t)\end{aligned}$$

$$E = \frac{1}{2} Cv^2(t) \quad \text{for capacitor}$$

Similarly,


$$E = \frac{1}{2} L i^2(t) \quad \text{for inductor}$$

Our goal is to find time response
of circuits with inductors and capacitors.

Roadmap:

- RC networks
 - easily solved using node method
- RI networks
 - easily solve using loop method
- RLC networks
 - Hard to solve using either method
 - Solve by impedance or state methods

Simple RC network:

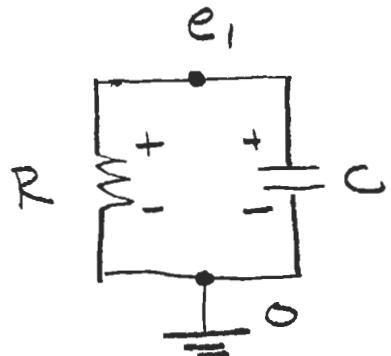

Solve by node method

KCL at node e_1 :

$$0 = i_R + i_C$$

$$= \frac{e_1 - 0}{R} + C \frac{d}{dt}(e_1 - 0)$$

$$= C \frac{d}{dt} e_1 + \frac{1}{R} e_1 = 0$$

$$\Rightarrow \boxed{\dot{e}_1(t) + \frac{1}{RC} e_1(t) = 0}$$

Solution is an exponential:

$$e_1(t) = e_1(0) e^{-t/RC}$$

(check by plugging in). Will talk more about how to solve later.