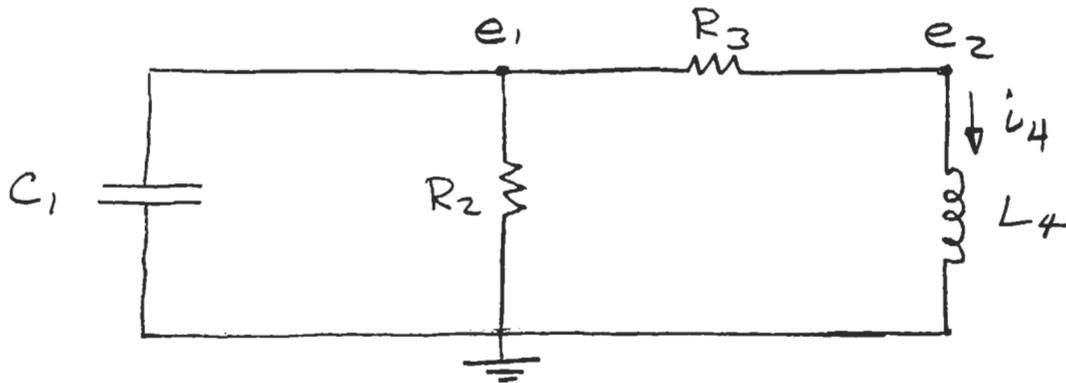


# Lecture 59

## RLC Circuits

Consider the RLC Circuit below:



$$C_1 = \frac{1}{2} \text{ F} \quad R_2 = 4 \Omega \quad R_3 = 6 \Omega \quad L_4 = 2 \text{ H}$$

Try to solve using node method:

$$e_1: \quad C_1 \frac{d}{dt} (e_1 - 0) + \frac{1}{R_2} (e_1 - 0) + \frac{1}{R_3} (e_1 - e_2) = 0$$

$\underbrace{\hspace{10em}}_{\text{current out of } e_1 \text{ through } C_1} \quad \underbrace{\hspace{10em}}_{\text{current out of } e_1 \text{ through } R_2} \quad \underbrace{\hspace{10em}}_{\text{current out of } e_1 \text{ through } R_3}$

$$\Rightarrow C_1 \dot{e}_1 + (G_2 + G_3) e_1 - G_3 e_2 = 0$$

$$e_2: \quad \frac{e_2 - e_1}{R_4} + \dot{L}_4 = 0$$

$\underbrace{\hspace{10em}}_{\text{current out of } e_2 \text{ through } R_4} \quad \underbrace{\hspace{10em}}_{\text{current out of } e_2 \text{ through } L_4}$

What is  $i_4$ ?

Constitutive law:

$$v_4 = L_4 \frac{di_4}{dt}$$

$$\Rightarrow \frac{di_4}{dt} = \frac{1}{L_4} (e_2 - 0) = \frac{1}{L_4} e_2$$

Integrating,

$$i_4(t) = \frac{1}{L_4} \int_0^t e_2(\tau) d\tau + i_4(0)$$

What a pain! We could use this,  
but it's easier to work with differential  
form:

$$e_1: C_1 \dot{e}_1 + (G_2 + G_3) e_1 - G_3 e_2 = 0$$

$$e_2: -G_3 e_1 + G_3 e_2 + \dot{i}_4 = 0$$

$$L_4: \frac{1}{L_4} e_2 - \frac{di_4}{dt} = 0$$

So we have 3 equations, 3 unknowns

Solve just like before. Assume

$$e_1(t) = E_1 e^{st}$$

$$e_2(t) = E_2 e^{st}$$

$$i_4(t) = I_4 e^{st}$$

Plug into equations:

$$e_1: (C_1 s + G_2 + G_3) E_1 - G_3 E_2 = 0$$

$$e_2: -G_3 E_1 + G_3 E_2 + I_4 = 0$$

$$L_4: \frac{1}{L_4} E_2 - s I_4 = 0$$

Eliminate  $I_4$ :

$$I_4 = \frac{1}{L_4 s} E_2$$

Therefore

$$(C_1 s + G_2 + G_3) E_1 - G_3 E_2 = 0$$

$$-G_3 E_1 + \left(G_3 + \frac{1}{L_4 s}\right) E_2 = 0$$

## Impedance and Admittance

In the example above,  $C_s$  and  $1/L_s$  played the role of conductance. To distinguish these from a true conductance, we call them "admittances." Likewise,  $1/C_s$  and  $L_s$  are "impedances," which are like resistances:

<u>Element</u>	<u>Impedance</u>	<u>Admittance</u>
Resistor	$R$	$G = 1/R$
Capacitor	$1/C_s$	$C_s$
Inductor	$L_s$	$1/L_s$
General	$Z$	$Y = 1/Z$

Can write down the equations for any RLC circuit by inspection, just by treating L's and C's like R's!