

## Lecture S11

### The Concept of State (continued)

Ways to think of the state:

- Each state variable is associated with "memory"
- Each state variable is associated with an initial condition.
- State variables are often associated with energy storage.


State variables are denoted by  $x_1, x_2 \dots$  and collected in the state vector  $\underline{x}$ :

$$\underline{x} = \begin{bmatrix} x_1 \\ x_2 \\ \vdots \\ x_n \end{bmatrix}$$

Goal is to find state equations of the form

$$\dot{\underline{x}}(t) = \frac{d\underline{x}(t)}{dt} = \underline{f}(\underline{x}(t))$$

Network from last time:

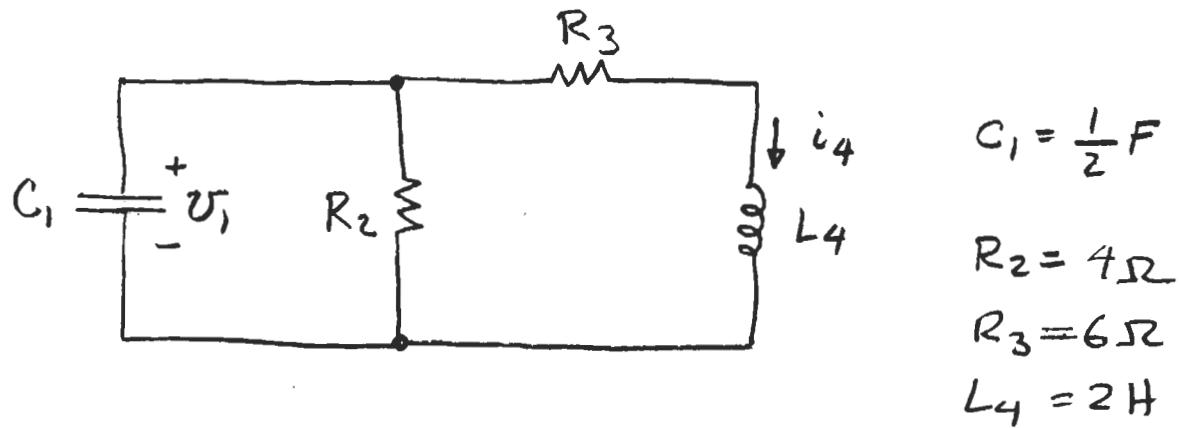

Why?

- Energy is  $\frac{1}{2} C_1 v_1^2, \frac{1}{2} L_4 i_4^2$
- Required initial conditions are  $v_1(0), i_4(0)$ .
- Differential equations are

$$\dot{v}_1 = C_1 \frac{dv_1}{dt}$$

$$v_4 = L_4 \frac{di_4}{dt}$$

Derivative terms  
are indicative of states

So state vector is

$$\underline{x} = \begin{pmatrix} x_1 \\ x_2 \end{pmatrix} = \begin{pmatrix} v_1 \\ i_4 \end{pmatrix}$$

Need to find

$$\frac{d}{dt} v_1 = f_1(v_1, i_4) \quad \left[ \dot{x}_1 = f_1(x, x_2) \right]$$


$$\frac{d}{dt} i_4 = f_2(v_1, i_4) \quad \left[ \dot{x}_2 = f_2(x_1, x_2) \right]$$

But we know that

$$\frac{d}{dt} v_1(t) = \frac{1}{C_1} i_1(t) \quad \frac{d}{dt} i_4(t) = \frac{1}{L_4} v_4(t)$$

So need to find  $i_1(t)$ ,  $v_4(t)$  in terms of  $v_1(t)$ ,  $i_4(t)$ .

Analysis circuit:

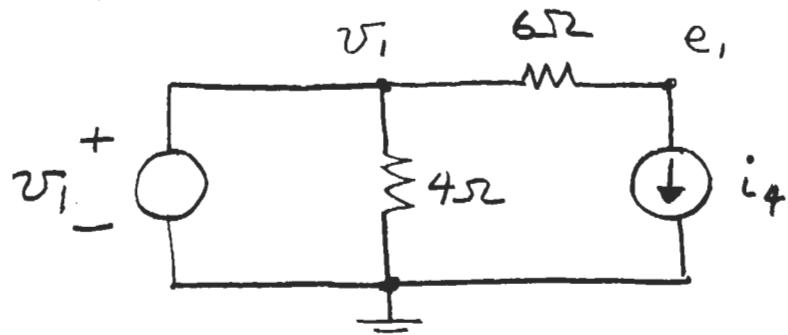

Use node method to find  $e_1 = v_4$ :

$$\frac{e_1}{6} - \frac{v_1}{C} + i_4 = 0$$

$$\Rightarrow v_4 = e_1 = v_1 - 6 i_4$$

$$\Rightarrow \frac{d}{dt} i_4 = \frac{1}{L_4} v_4 = \frac{1}{2} v_1 - 3 i_4$$

$$\boxed{\frac{d}{dt} i_4 = \frac{1}{2} v_1 - 3 i_4}$$

To find differential equation for  $v_1$ , need  $i_1$ . To find  $i_1$ , apply KCL at  $v_1$  node:

$$i_1 + v_1 \left( \frac{1}{4} + \frac{1}{6} \right) - \frac{1}{6} e_1 = 0$$

$$\Rightarrow i_1 = -\frac{5}{12} v_1 + \frac{1}{6} (v_1 - 6 i_4)$$

$$= -\frac{1}{4} v_1 - i_4 = c_1 \frac{d v_1}{dt} = \frac{1}{2} \frac{d v_1}{dt}$$

$$\Rightarrow \boxed{\frac{d}{dt} v_1 = -\frac{1}{2} v_1 - 2 i_4}$$

So state equation is

$$\frac{d}{dt} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \underbrace{\begin{bmatrix} -1/2 & -2 \\ 1/2 & -3 \end{bmatrix}}_A \underbrace{\begin{bmatrix} x_1 \\ x_2 \end{bmatrix}}_x$$

More compactly,

$$\dot{x} = Ax$$

This form of state equation is very common, and very useful. Any linear, homogeneous system can be expressed in this form.

Why use this "state-space" approach?

- Very general
- There is a very rich theory describing solutions
- Approach is central to "modern" control

We care about systems, not just circuits. Circuits are our vehicle for understanding systems.