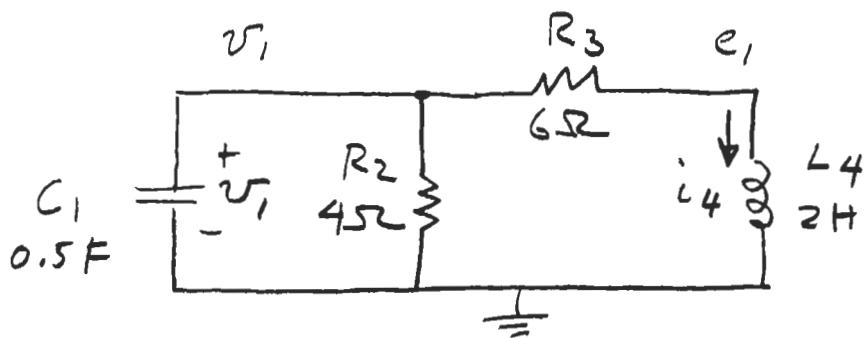


## Lecture S12

From last time:



Step 1 Identify the states. These are

$$v_1(t), i_4(t)$$

Step 2 Use constitutive laws to write differential equations for  $v_1(t)$ ,  $i_4(t)$ :

$$i_1 = C_1 \frac{dv_1}{dt} \Rightarrow \frac{dv_1}{dt} = \frac{1}{C_1} i_1$$

$$v_4 = L_4 \frac{di_4}{dt} \Rightarrow \frac{di_4}{dt} = \frac{1}{L_4} v_4$$

Step 3 Solve for  $i_1$ ,  $v_4$  using, say, node method. Treat  $v_1$  and  $i_4$  as known:

$$\frac{e_1 - v_1}{R_3} + i_4 = 0 \quad (\text{KCL at } e_1)$$

①

$$\Rightarrow e_1 = v_1 - R_3 i_4$$

But  $v_1 = e_1 - 0$ ,

$$\Rightarrow \frac{di_4}{dt} = \frac{v_4}{L_4} = \frac{v_1}{L_4} - \frac{R_3}{L_4} i_4$$

$$\frac{di_4}{dt} = \frac{1}{2}v_1 - 3i_4$$

This is in required form:

$$\frac{di_4}{dt} = \dot{x}_2 = f_2(x_1, x_2)$$

Now find  $i_1$ . [concept test here]

Solution: We have "solved" network, in that we know all the node voltages. To find current through  $C_1$ , apply KCL at  $v_1$  node, since constitutive law does not give current.

$$v_1: i_1 + \frac{v_1}{R_2} + \frac{v_1 - e_1}{R_3} = 0$$

$$\begin{aligned}
 \Rightarrow i_1 &= -\left(\frac{1}{R_2} + \frac{1}{R_3}\right)v_1 + \frac{1}{R_3}e_1 \\
 &= -\left(\frac{1}{R_2} + \frac{1}{R_3}\right)v_1 + \frac{1}{R_3}(v_1 - R_3 i_4) \\
 &= -\frac{1}{R_2}v_1 - i_4
 \end{aligned}$$

Therefore,

$$\frac{dv_1}{dt} = \frac{1}{C_1} i_1 = -\frac{1}{R_2 C_1} v_1 - \frac{1}{C_1} i_4$$

$$\boxed{\frac{dv_1}{dt} = -\frac{1}{2}v_1 - 2i_4}$$

Therefore,

$$\dot{x} = \frac{d}{dt} \begin{pmatrix} v_1 \\ i_4 \end{pmatrix} = \begin{pmatrix} -1/2 & -2 \\ 1/2 & -3 \end{pmatrix} \begin{pmatrix} v_1 \\ i_4 \end{pmatrix}$$

$$= A \underline{x}$$

$$A = \begin{bmatrix} -1/2 & -2 \\ 1/2 & -3 \end{bmatrix}$$

(5)

Note that differential equations have the form

$$\dot{\underline{x}} = A \underline{x}$$

$\underline{x}$  = state vector

$A$  = state dynamics matrix

This form of state equation is very common, and very useful. Any linear, homogeneous system has dynamics in this form.

Why use state-space approach?

- Approach is very general
- There is a rich theory describing solutions
- There are good numerical algorithms for obtaining solutions
- Approach is central to "modern" control.

So what is  $v_1(t)$ ,  $i_4(t)$ , if

$$v_1(0) = 2 \text{ V}, i_4(0) = 1 \text{ A} \quad ?$$

First, find general solution to

$$\dot{\underline{x}} = A\underline{x}$$

What is solution? Guess!

$$\underline{x} = \underline{v} e^{st}$$

Plug this in:

$$\Rightarrow \cancel{\underline{v} s e^{st}} = A \cancel{\underline{v} e^{st}}$$

$$\Rightarrow s \underline{v} = A \underline{v} \quad \text{or} \quad (sI - A) \underline{v} = \underline{0}$$

A (nontrivial) solution  $\underline{v}$  to this equation is an eigenvector; the corresponding value of  $s$  is an eigenvalue.

These are special cases of characteristic vectors and characteristic values.

[Do concept test]

(7)

To find eigenvalues, set

$$\phi(s) = \det(sI - A) = 0$$

$$\det(sI - A) = \begin{vmatrix} s + 1/2 & +2 \\ -1/2 & s+3 \end{vmatrix}$$

$$= s^2 + 3.5s + 2.5 = (s-1)(s+2.5)$$

so  $\lambda_1 = -1$   
 $\lambda_2 = -2.5$

To find eigenvectors, set  $(\lambda I - A) \underline{v} = 0$

$$\lambda_1 I - A = \begin{bmatrix} -1/2 & 2 \\ -1/2 & 2 \end{bmatrix}$$

$$(\lambda_1 I - A) \underline{v}_1 = 0 \Rightarrow \underline{v}_1 = \begin{pmatrix} 4 \\ 1 \end{pmatrix}$$

Similarly,  $\underline{v}_2 = \begin{pmatrix} 1 \\ 1 \end{pmatrix}$

So general solution is

$$\underline{x}(t) = \underline{v}_1 e^{\lambda_1 t} + \underline{v}_2 e^{\lambda_2 t}$$