

## Lecture S14

From last time, found that

$$\underline{x}(t) = \begin{bmatrix} v_1(t) \\ i_2(t) \end{bmatrix} = a_1 \begin{bmatrix} -\frac{1}{5} + \frac{3}{5}j \\ 1 \end{bmatrix} e^{(-1+3j)t} + a_2 \begin{bmatrix} -\frac{1}{5} - \frac{3}{5}j \\ 1 \end{bmatrix} e^{(-1-3j)t}$$

We want to choose  $a_1$  and  $a_2$  so that we match the initial conditions

$$v_1(0) = 1V \Rightarrow \underline{x}(0) = \begin{pmatrix} 1 \\ 1 \end{pmatrix}$$

$$\underline{x}(0) = \begin{pmatrix} 1 \\ 1 \end{pmatrix} = \begin{bmatrix} -\frac{1}{5} + \frac{3}{5}j & -\frac{1}{5} - \frac{3}{5}j \\ 1 & 1 \end{bmatrix} \begin{pmatrix} a_1 \\ a_2 \end{pmatrix}$$

$$\Rightarrow a_1 = \frac{1}{2} - \frac{1}{2}j \quad \text{ugh!}$$

$$a_2 = \frac{1}{2} + \frac{1}{2}j$$

Therefore,

$$\underline{x}(t) = \begin{bmatrix} 0.5 + 0.5j \\ 0.5 - j \end{bmatrix} e^{(-1+3j)t} + \begin{bmatrix} 0.5 - 0.5j \\ 0.5 - j \end{bmatrix} e^{(-1-3j)t}$$

Use Euler's Formula to express in terms of real variables:

$$e^{\alpha+j\beta} = e^\alpha (\cos \beta + j \sin \beta)$$

Therefore,

$$\begin{aligned} v_1(t) &= (0.5 + 0.5j)(\cos 3t + j \sin 3t) e^{-t} \\ &\quad + (0.5 - 0.5j)(\cos 3t - j \sin 3t) e^{-t} \\ &= (\cos 3t - \sin 3t) e^{-t} \end{aligned}$$

Likewise,

$$i_2(t) = (\cos 3t + 2 \sin 3t) e^{-t}$$

---

Note: There are "shortcuts" to reduce the math a little.

## Circuits with Sources

All interesting circuits have an input source:


- Antenna
- Scope probe
- Tuner
- Microphone

All interesting circuits have an output:

- Loudspeaker
- Display
- Conditioned signal

We want to be able to analyze these in terms of their input/output behavior.

## Example

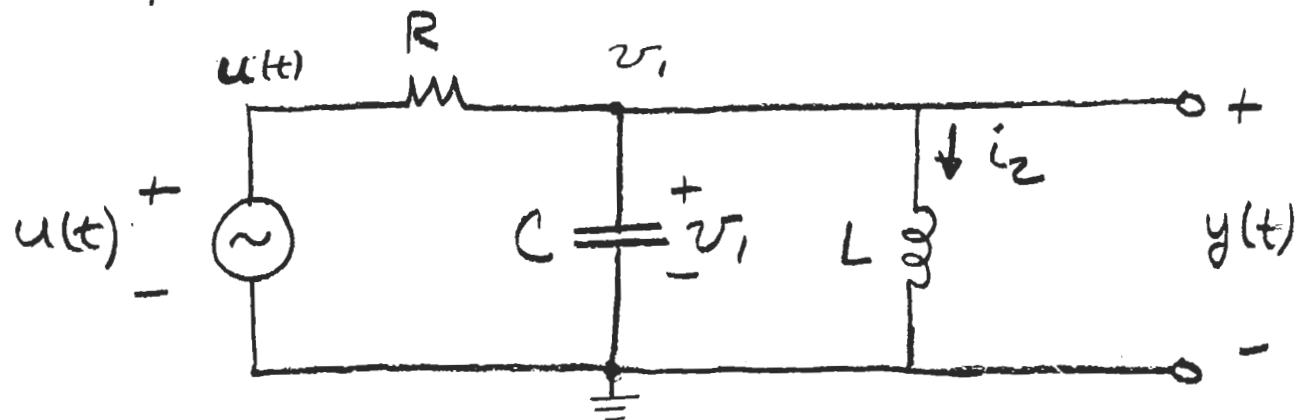

$$C = \frac{1}{2} F \quad L = \frac{1}{5} H \quad R = 1 \Omega$$

Let's find state equation:

Step 1 States are  $v_1, i_2$ .

$$\frac{d}{dt} v_1 = \frac{1}{C} i_1 \quad \text{need to find } i_1$$

$$\frac{d}{dt} i_2 = \frac{1}{L} v_2 = \frac{1}{L} v_C$$

To find  $i_1$ , apply KCL at  $v_1$ :

$$i_1 + i_2 + \frac{v_1 - u}{R} = 0$$

$$\Rightarrow i_1 = -\frac{v_1}{R} - i_2 + \frac{u}{R}$$

$$\Rightarrow \frac{d v_1}{dt} = -\frac{1}{RC} v_1 - \frac{1}{C} i_2 + \frac{1}{RC} u$$

So state equation, in matrix form, is

$$\frac{d}{dt} \begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -1/RC & -1/C \\ +1/L & 0 \end{bmatrix} \begin{bmatrix} v_C \\ i_2 \end{bmatrix} + \begin{bmatrix} 1/RC \\ 0 \end{bmatrix} u$$

$$\underline{\dot{x}}(t) = A \underline{x}(t) + B u(t)$$

The state equation in the form

$$\dot{\underline{x}} = A\underline{x} + B\underline{u}$$

is (almost) the most general form of the dynamics equation for linear systems.

Example aircraft longitudinal dynamics

states:  $h$  - altitude  
 $V$  - velocity  
 $\gamma$  - flight path angle  
 $\alpha$  - angle of attack  
 $q$  - pitch rate

inputs:  $\delta_e$  - elevator deflection  
 $\delta_f$  - flap deflection  
 $\delta_T$  - thrust level setting

So now we have state in terms of input. What is output?

$$y = \underline{v}_1 = [1 \ 0] \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = C\underline{x}$$

For some systems, can get

$$\underline{y}(t) = C \underline{x}(t) + D \underline{u}(t)$$

Again, this is the most general form.

For our example (with numbers),

$$\dot{\underline{x}} = \begin{bmatrix} -2 & -2 \\ 5 & 0 \end{bmatrix} \underline{x} + \begin{bmatrix} 2 \\ 0 \end{bmatrix} \underline{u}$$

"state eq'n."

$$y = [1 \ 0] \underline{x} + [0] \underline{u}$$

"measurement eq'n"

### The Transfer Function

Very often, we care about the response of a system to an exponential input. Why?

- Sines and cosines are exponentials, and sine waves are common signals (in testing and in practice)

$$\cos \omega t = \frac{e^{j\omega t} + e^{-j\omega t}}{2}$$