

SP.764, Practical Electronics
Dr. James A. Bales
Lecture 9: Final Project Concepts

Topics:

- 1) Concepts
 - Generate concepts
 - Explore concepts
 - Select concepts
- 2) Plan & Begin Design

Concepts:

- I. Temperature-controlled fan, w/ readout
 - a. Sense temperature
 - i. Thermistor
 - b. Display temperature
 - i. LEDs
 - ii. Comparator
 - c. Control speed of motor w/ PWM
 - i. Transistor
 - ii. 555
- II. "Color Organ"
 - a. Pick up sound
 - i. Microphone
 - ii. Amplifier
 - iii. Filter
 - b. Sense volume (Extract envelope)
 - i. Rectifier
 - ii. Low-pass Filter
 - c. Sense freq. band & volume in that band
 - d. Light LED bar

III. Sunflower

- a. Sense light
 - i. Photocells
- b. Compare intensity
 - i. Comparator
- c. Actuator
 - i. Solenoids
 - ii. Motor
- d. Motor needs to stop! (Implement "dead-band")

MIT OpenCourseWare
<http://ocw.mit.edu>

EC.S06 / EC.S11 Practical Electronics
Fall 2004

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.