

Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science

6.002 - Electronic Circuits  
Spring 2007

Homework #5  
Handout F07-028

Issued 3/8/2007 - Due 3/16/2007

Helpful Readings for this Homework: Agarwal & Lang Chapter 7.1 - 7.6

**Exercise 5.1:** Do Exercise 7.1 in Agarwal & Lang, page 390.

**Exercise 5.2:** Do Exercise 7.3 in Agarwal & Lang, page 391.

**Problem 5.1:** Determine the Thevenin equivalent of the following circuit. Note that it contains a dependent voltage source, and that the parameter  $\alpha$  has units of Ohms.

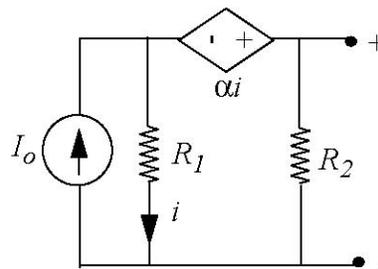


Figure for Problem 5.1

**Problem 5.2:** This problem studies the two amplifiers shown on the other side of the page. Amplifier A is a single-stage amplifier implemented with a voltage-dependent current source and a pull-up resistor. Assume that the current source parameters  $G$  and  $V_T$  satisfy  $G > 0$  and  $V_S > V_T > 0$ . Also assume that  $R_G < \frac{V_S}{V_S - V_T}$ . Amplifier B is a two-stage amplifier in which each stage is identical to Amplifier A.

- (A) Determine  $v_{OUT}$  as a function of  $v_{IN}$  for Amplifier A.
- (B) Sketch and clearly label a graph of the input-output relation found in Part (A).
- (C) Determine  $v_{OUT}$  as a function of  $v_{IN}$  for Amplifier B.
- (D) Sketch and clearly label a graph of the input-output relation found in Part (C).
- (E) Consider Amplifier A again. Show that the dependent current source sinks power for  $v_{OUT} > 0$  and sources power for  $v_{OUT} < 0$ .
- (F) Unlike the expression for the current in Amplifier A given with the figure on the next page, real-world devices do not supply additional current when  $v_{OUT} < 0$ . Instead the device saturates and the dependent current source supplies a constant current, given by  $V_S / R$ . Redo parts (A) and (B) in light of this fact. What change (if any) occurs in the input-output relation of Amplifier B?

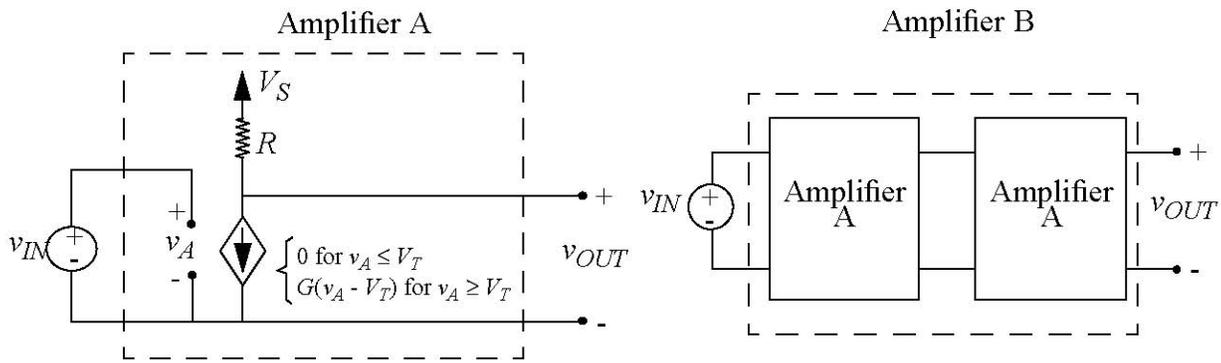


Figure for P.5.2.