
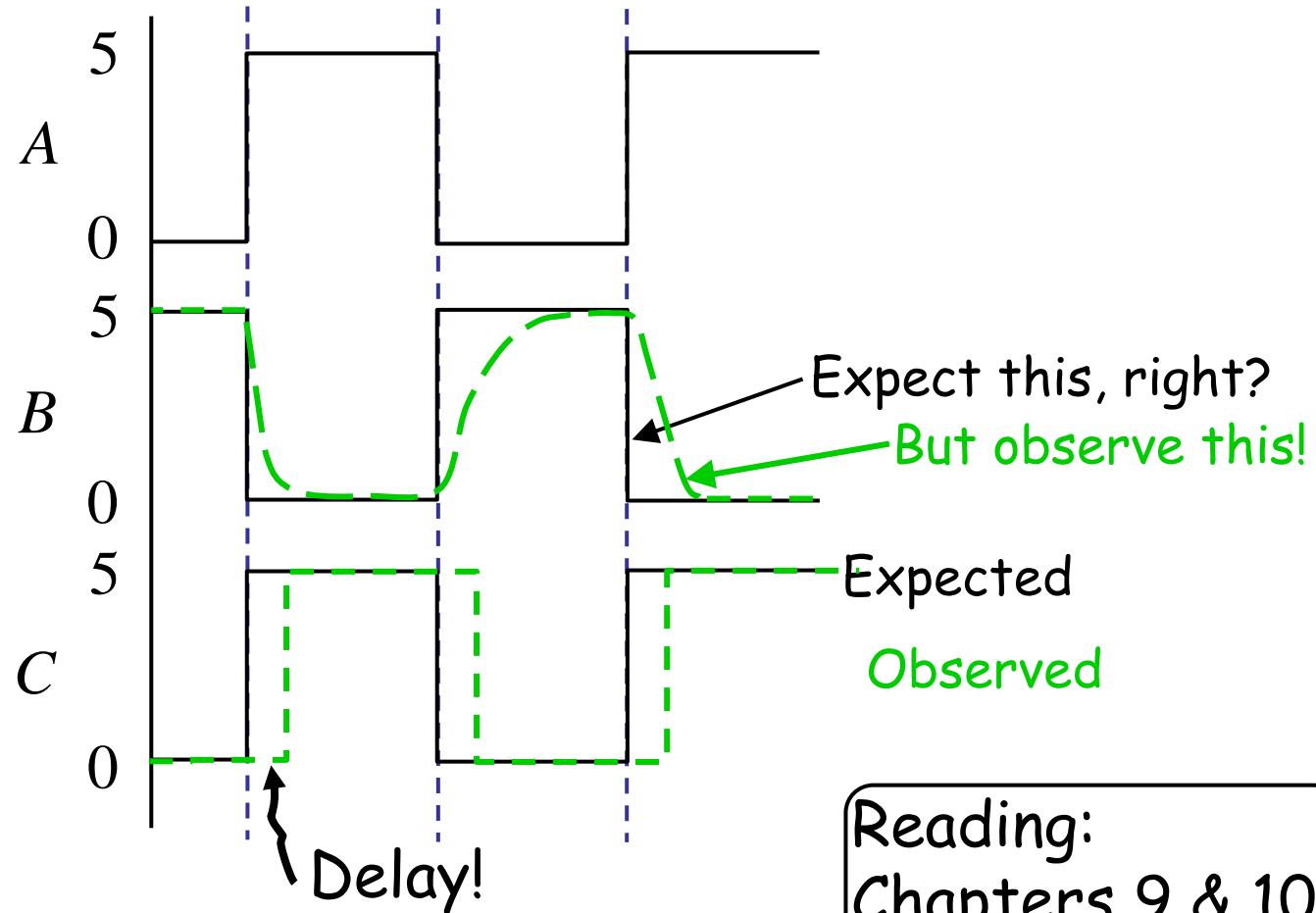


**6.002**

**CIRCUITS AND  
ELECTRONICS**


# **Capacitors and First-Order Systems**

# Motivation

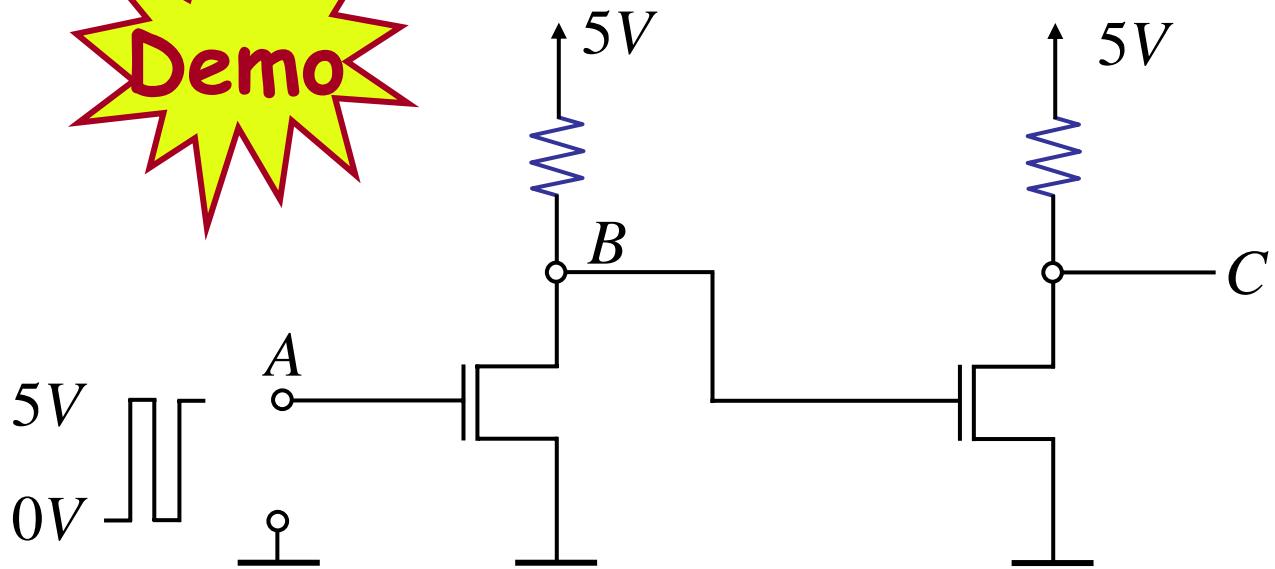


Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].


# The Capacitor

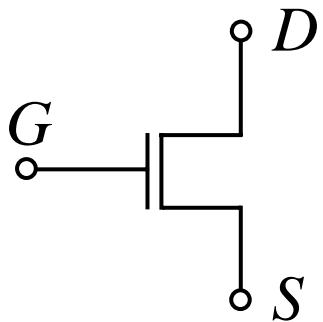

n-channel MOSFET symbol

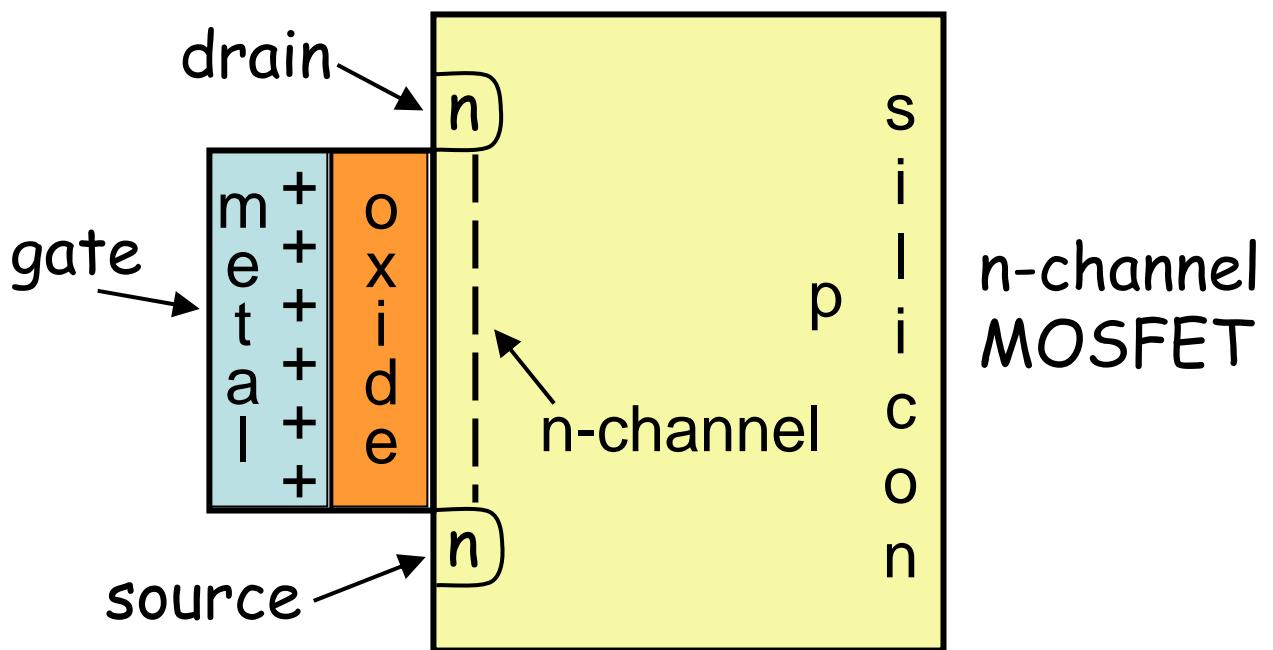


n-channel MOSFET

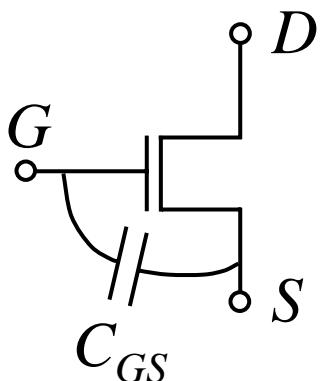

Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].


# Ideal Linear Capacitor

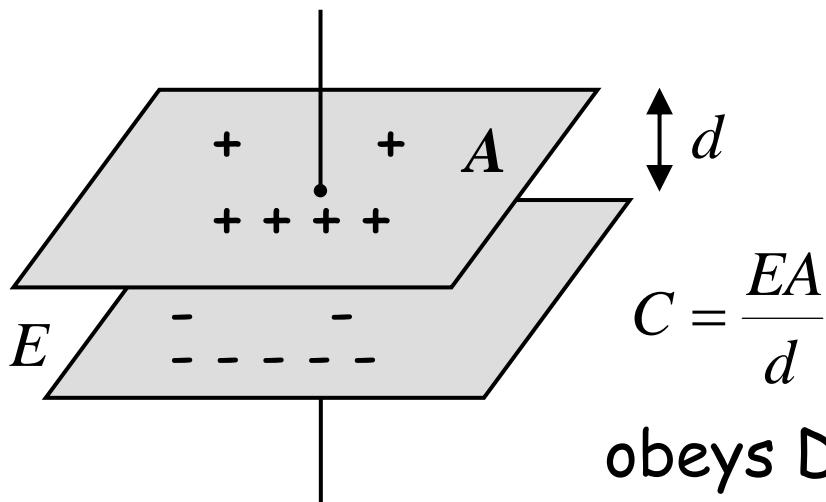

$$C = \frac{EA}{d}$$

obeys DMD!  
total charge on  
capacitor


$$= +q - q = 0$$

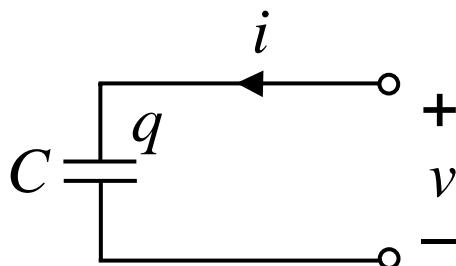

$$q = C v$$

arrows pointing from the words "coulombs", "farads", and "volts" to the variables  $q$ ,  $C$ , and  $v$  respectively.

# Ideal Linear Capacitor

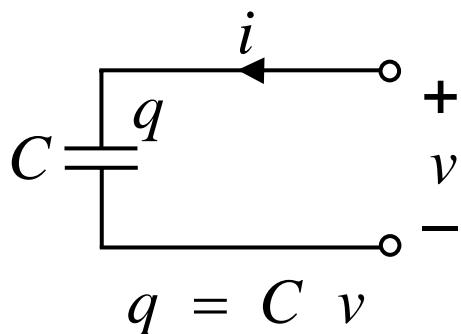


$$\begin{aligned} i &= \frac{dq}{dt} \\ &= \frac{d(Cv)}{dt} \\ &= C \frac{dv}{dt} \end{aligned}$$

$$\underbrace{\left[ E = \frac{1}{2} Cv^2 \right]}_{\text{A capacitor is an energy storage device}}$$

A capacitor is an energy storage device  
→ memory device → history matters!

# Analyzing an RC circuit

Thévenin Equivalent:

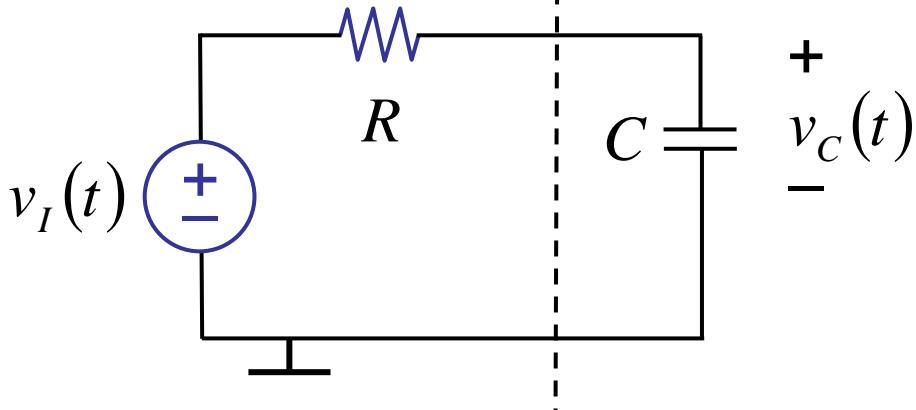


Apply node method:

$$\frac{v_C - v_I}{R} + C \frac{dv_C}{dt} = 0$$

$$(RC) \frac{dv_C}{dt} + v_C = v_I \quad \begin{cases} t \geq t_0 \\ v_C(t_0) \text{ given} \end{cases}$$

units  
of time

# Let's do an example:

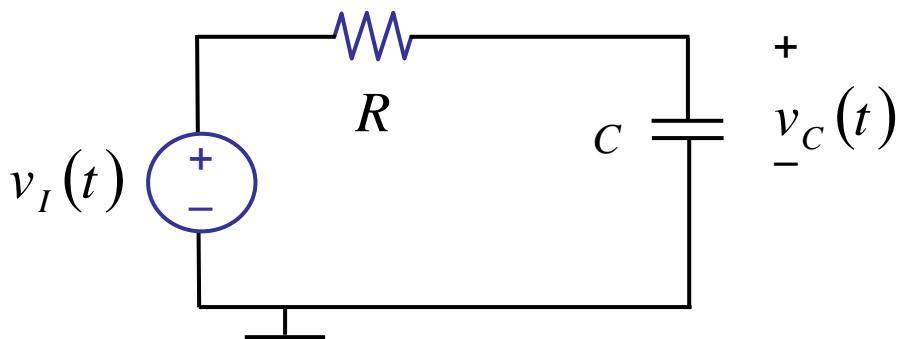

$$v_I(t) = V_I$$

$$v_C(0) = V_0 \quad \text{given}$$

$$RC \frac{dv_C}{dt} + v_C = V_I \quad \text{—————} \times$$

# Example...

$$v_I(t) = V_I$$

$$v_C(0) = V_0 \text{ given}$$

$$RC \frac{dv_C}{dt} + v_C = V_I \quad \text{—————} \times$$

$$v_C(t) = v_{CH}(t) + v_{CP}(t)$$

total homogeneous particular

## Method of homogeneous and particular solutions:

- ① Find the particular solution.
- ② Find the homogeneous solution.
- ③ The total solution is the sum of the particular and homogeneous solutions.

Use the initial conditions to solve for the remaining constants.

# ① Particular solution

$$RC \frac{dv_{CP}}{dt} + v_{CP} = V_I$$

$v_{CP} = V_I$  works

$$RC \frac{dV_I}{dt} + V_I = V_I$$

0 ↗

In general, use trial and error.

$v_{CP}$ : any solution that satisfies the original equation

2

## Homogeneous solution

$$RC \frac{dv_{CH}}{dt} + v_{CH} = 0 \quad \text{--- } \textcircled{y}$$

$v_{CH}$ : solution to the homogeneous equation  $\textcircled{y}$   
 (set drive to zero)

$v_{CH} = A e^{st}$  assume solution  
 of this form.  $A, s$  ?

$$RC \frac{dA e^{st}}{dt} + A e^{st} = 0$$

$$\cancel{RCAs e^{st}} + \cancel{Ae^{st}} = 0$$

Discard trivial  $A = 0$  solution,

$RCs + 1 = 0$  Characteristic equation

$$\rightarrow s = -\frac{1}{RC}$$

or  $v_{CH} = Ae^{\frac{-t}{RC}}$

$RC$   
 called time  
 constant  $\tau$

### ③ Total solution

$$v_C = v_{CP} + v_{CH}$$

$$v_C = V_I + A e^{\frac{-t}{RC}}$$

Find remaining unknown from initial conditions:

Given,  $v_C = V_0$  at  $t = 0$


so,  $V_0 = V_I + A$

or  $A = V_0 - V_I$



thus  $v_C = V_I + (V_0 - V_I) e^{\frac{-t}{RC}}$

also  $i_C = C \frac{dv_C}{dt} = -\frac{(V_0 - V_I)}{R} e^{\frac{-t}{RC}}$
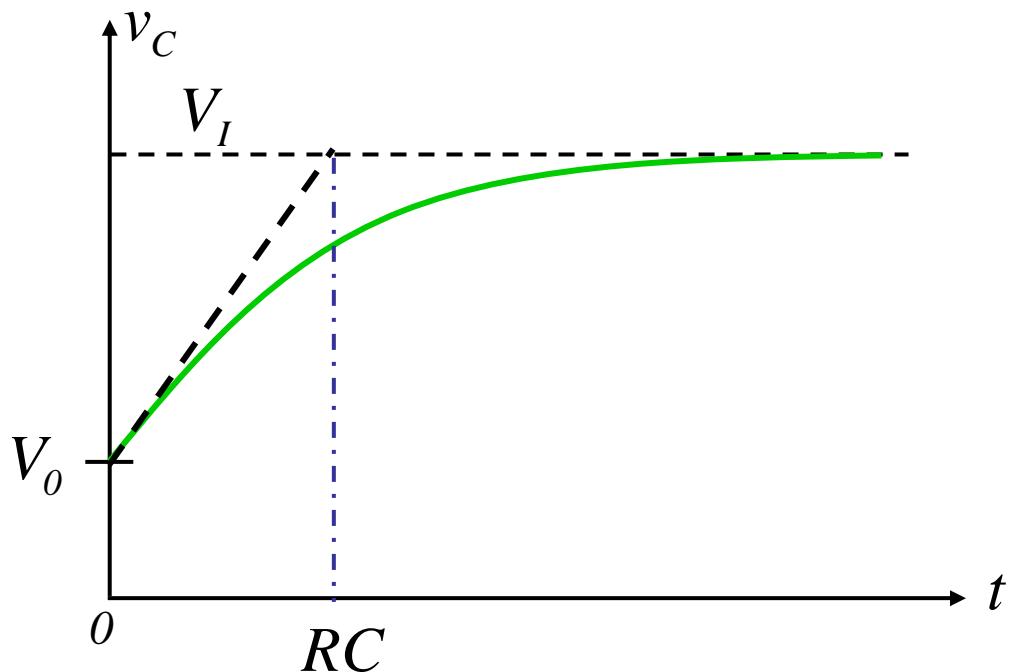
$$v_C = V_I + (V_0 - V_I) e^{\frac{-t}{RC}}$$



# Examples

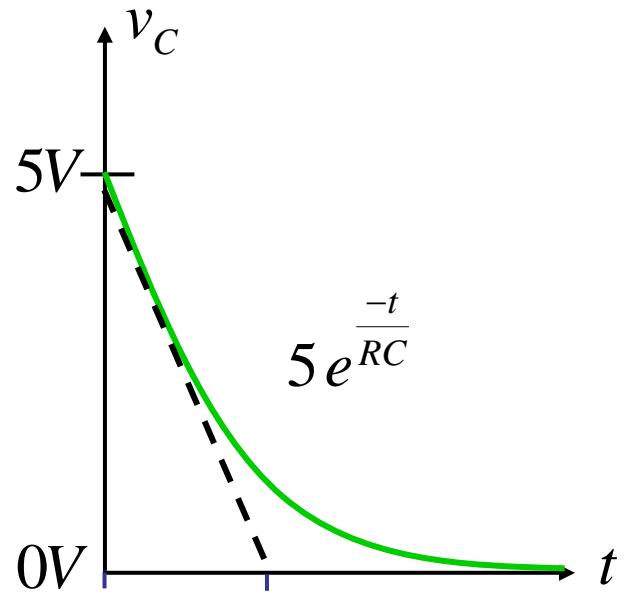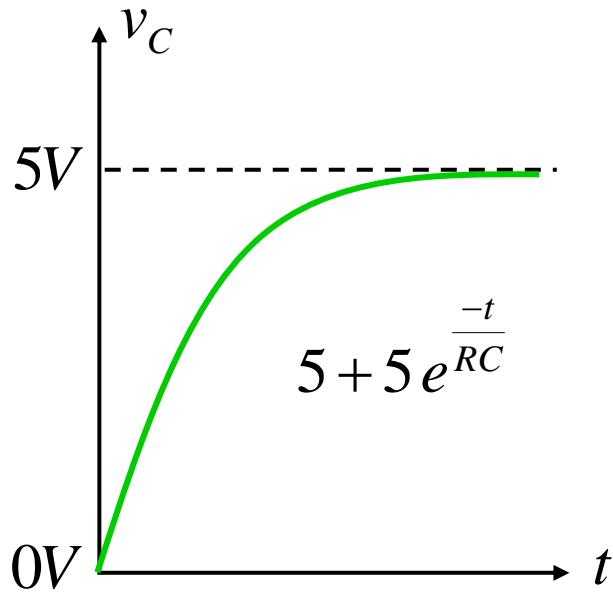

$$V_o = 0V \quad \boxed{5} \\ V_I = 5V \quad \boxed{0}$$

$$V_o = 5V \quad \boxed{5} \\ V_I = 0V \quad \boxed{0}$$

$\tau = RC$

Remember  
demo

