

**6.002**


**CIRCUITS AND  
ELECTRONICS**

# The Operational Amplifier Abstraction


Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

# Review


## ■ MOSFET amplifier – 3 ports

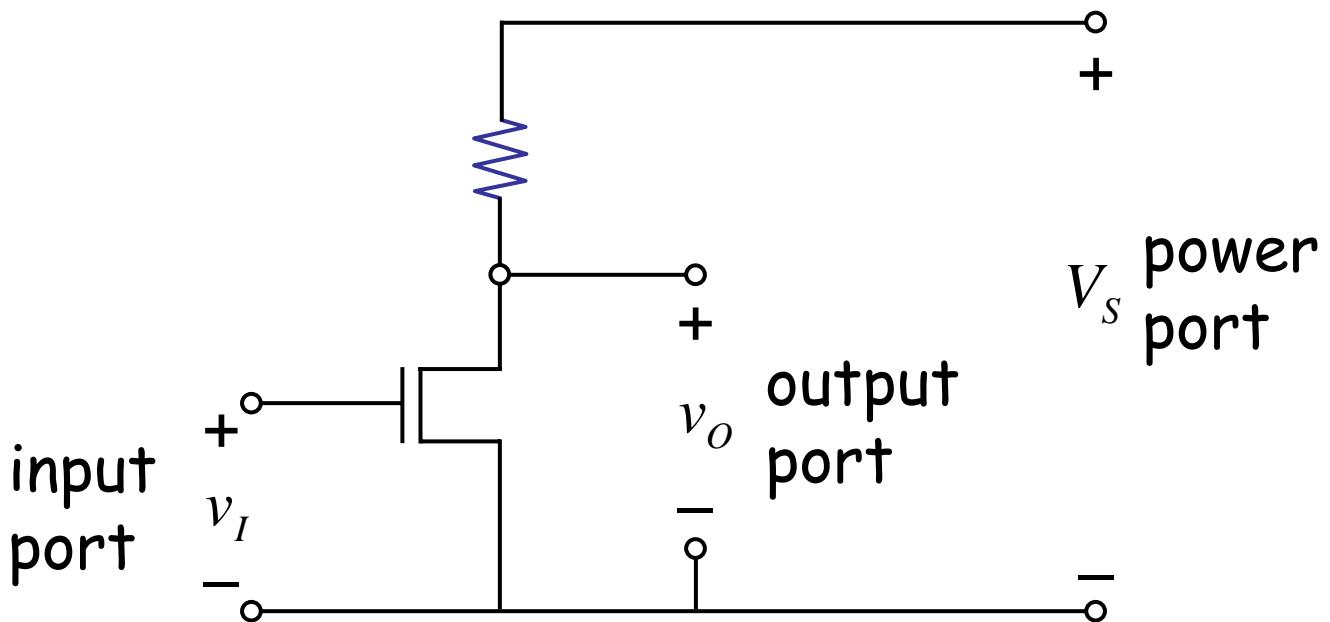

## ■ Amplifier abstraction

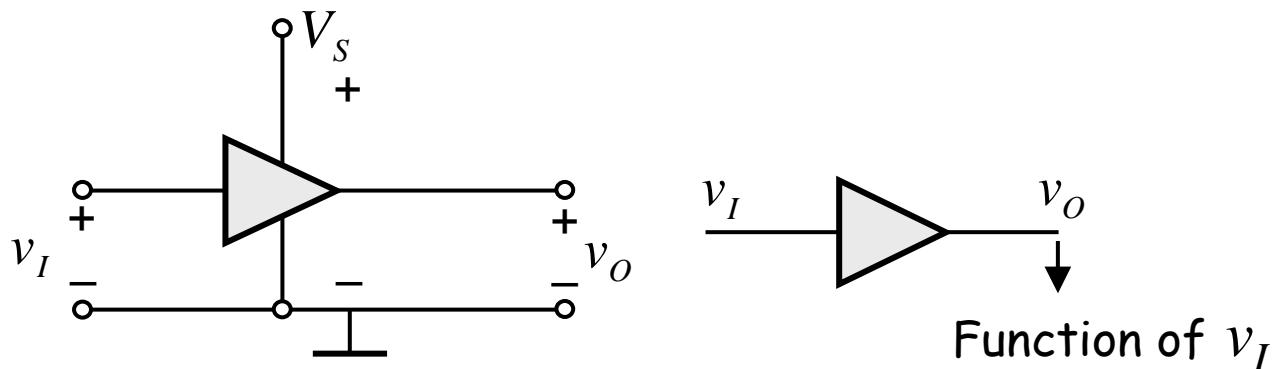


# Review

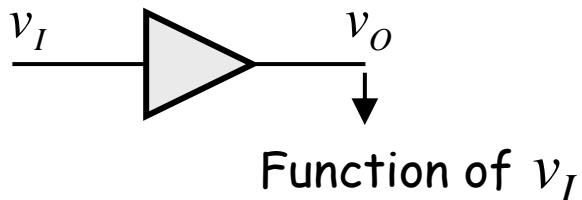


- Can use as an abstract building block for more complex circuits (of course, need to be careful about input and output).
- Today
  - Introduce a more powerful amplifier abstraction and use it to build more complex circuits.

Reading: Chapter 15 from A & L.



# Operational Amplifier Op Amp

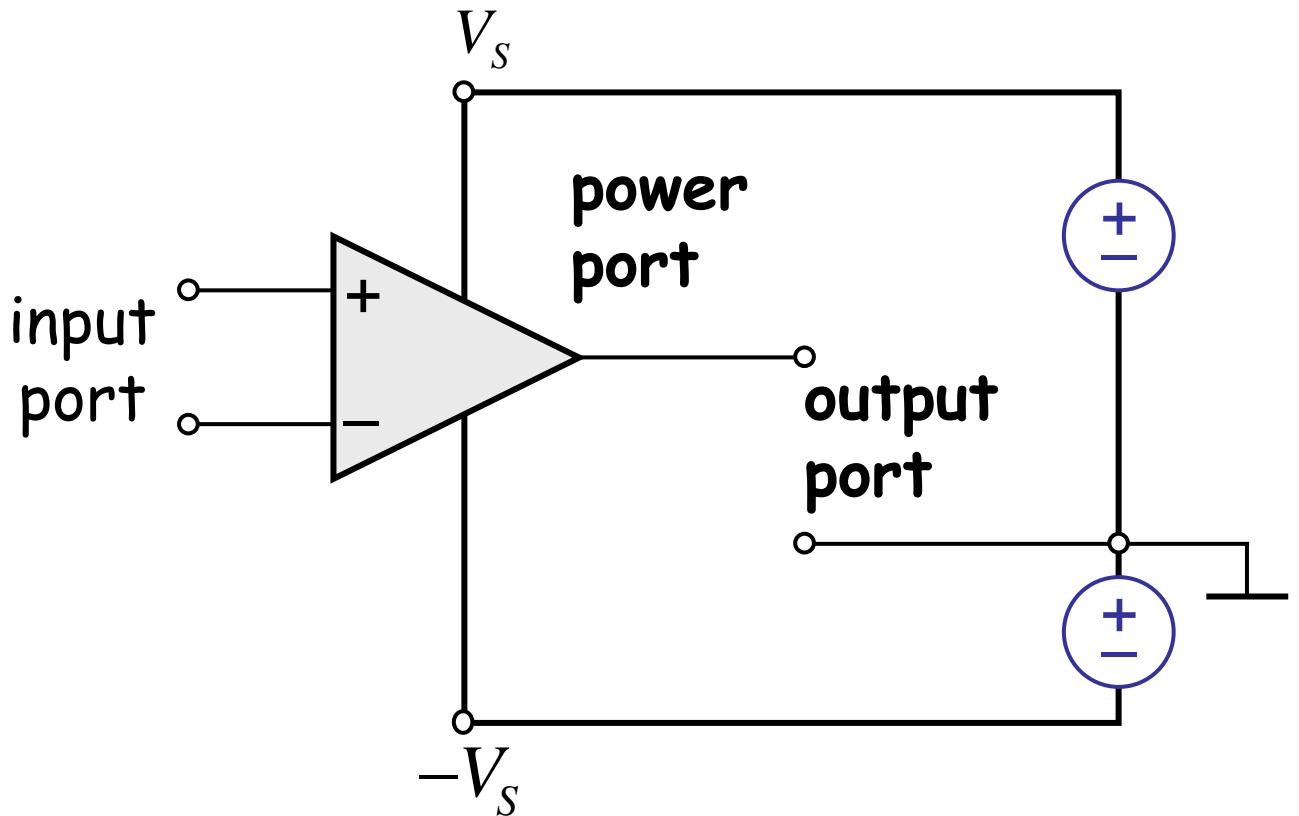

More abstract representation:

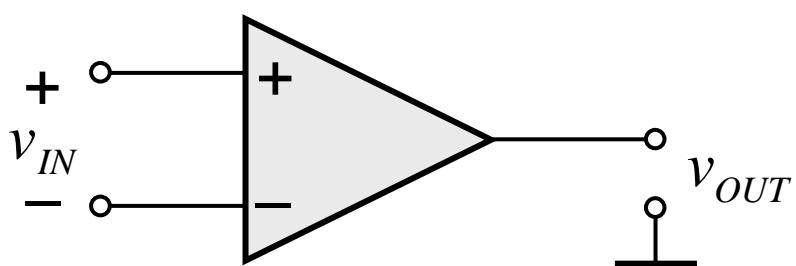


# Circuit model (ideal):

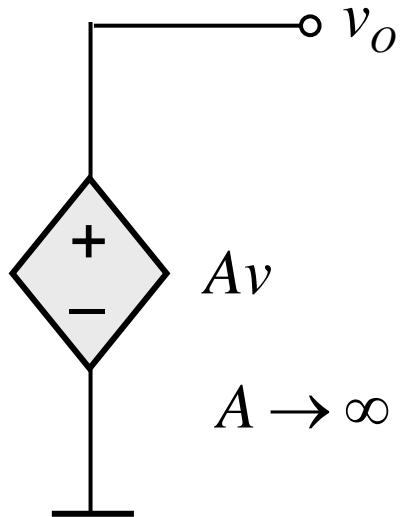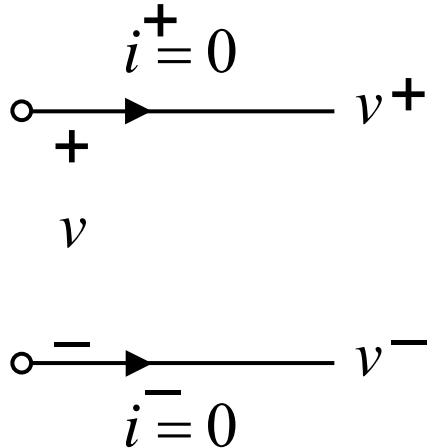


- i.e. ◆  $\infty$  input resistance
- ◆ 0 output resistance
- ◆ "A" virtually  $\infty$
- ◆ No saturation

# Using it...

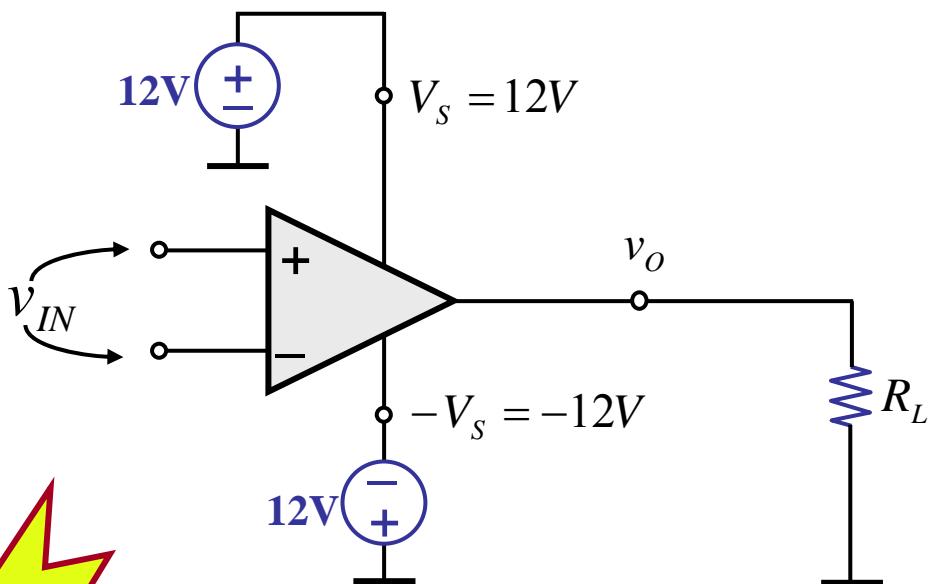

**Demo**

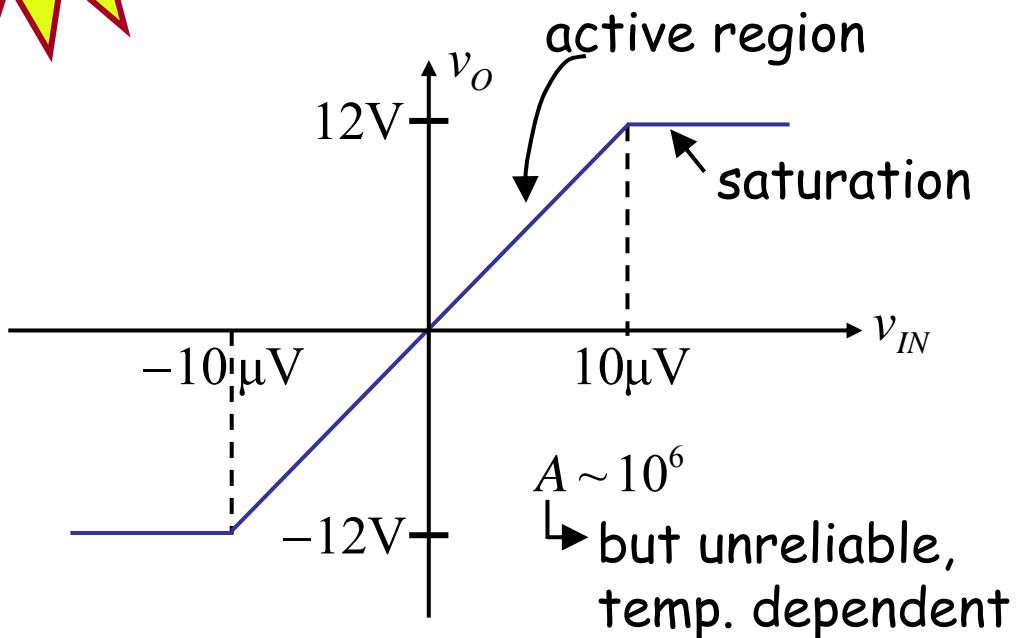


(Note: possible confusion with MOSFET saturation!)


Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

# Let us build a circuit...

## Circuit: noninverting amplifier

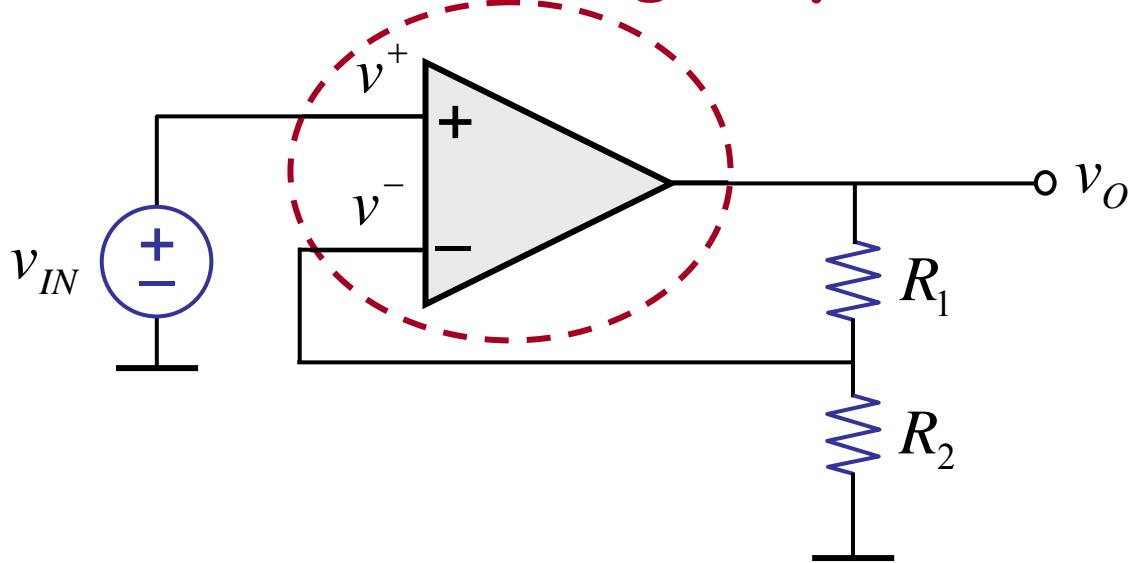

Equivalent circuit model

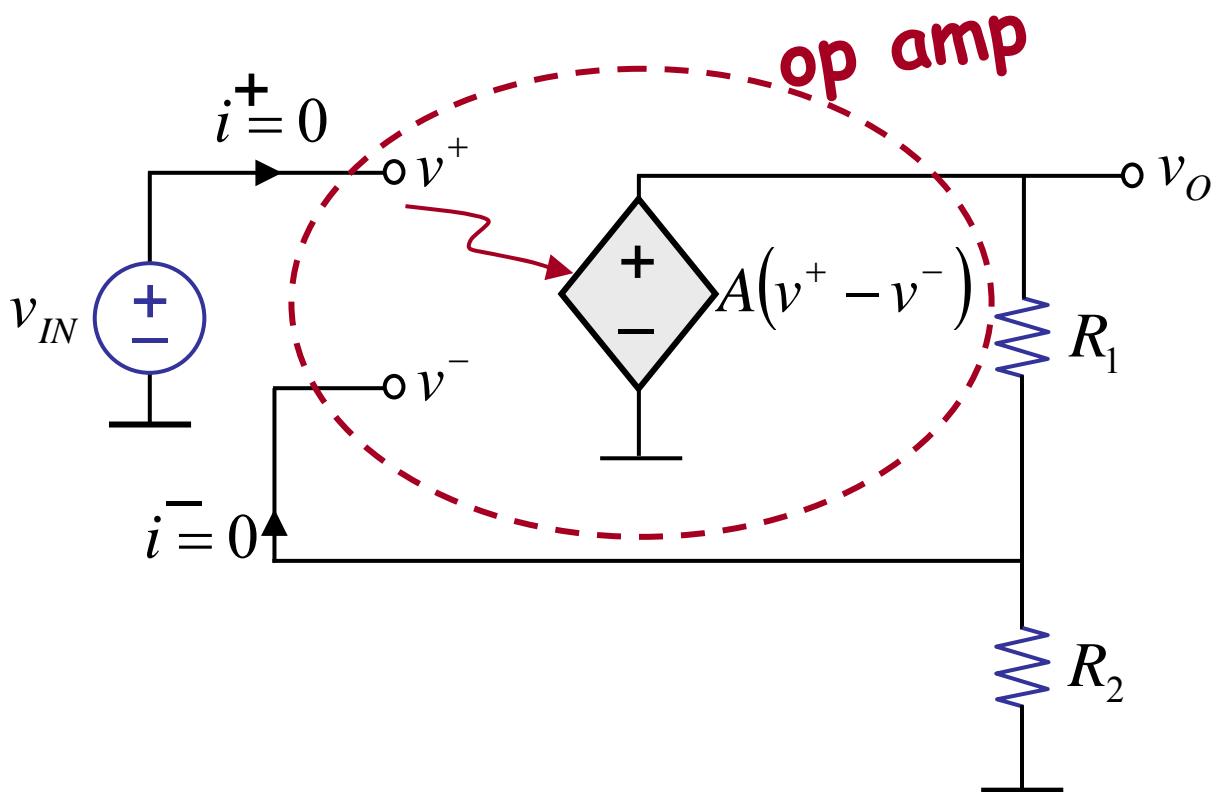

Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

# Let us analyze the circuit:

Find  $v_o$  in terms of  $v_{IN}$ , etc.

$$v_o = A(v^+ - v^-)$$

$$= A \left( v_{IN} - v_o \frac{R_2}{R_1 + R_2} \right)$$

$$v_o \left( 1 + \frac{AR_2}{R_1 + R_2} \right) = Av_{IN}$$

$$v_o = \frac{Av_{IN}}{1 + \frac{AR_2}{R_1 + R_2}}$$

What happens when "A" is very large?

# Let's see... When A is large

$$v_o = \frac{Av_{IN}}{1 + \frac{AR_2}{R_1 + R_2}} \approx \frac{\cancel{Av_{IN}}}{\cancel{AR_2}} \underbrace{\frac{(R_1 + R_2)}{R_2}}_{\text{gain}}$$

Suppose  $A = 10^6$   
 $R_1 = 9R$   
 $R_2 = R$

$$\begin{aligned} v_o &= \frac{10^6 \cdot v_{IN}}{1 + \frac{10^6 R}{9R + R}} \\ &= \frac{10^6 \cdot v_{IN}}{1 + 10^6 \cdot \frac{1}{10}} \end{aligned}$$

$$v_o \approx v_{IN} \cdot 10$$




Gain:

- determined by resistor ratio
- insensitive to  $A$ , temperature, fab variations

# Why did this happen?

Insight:

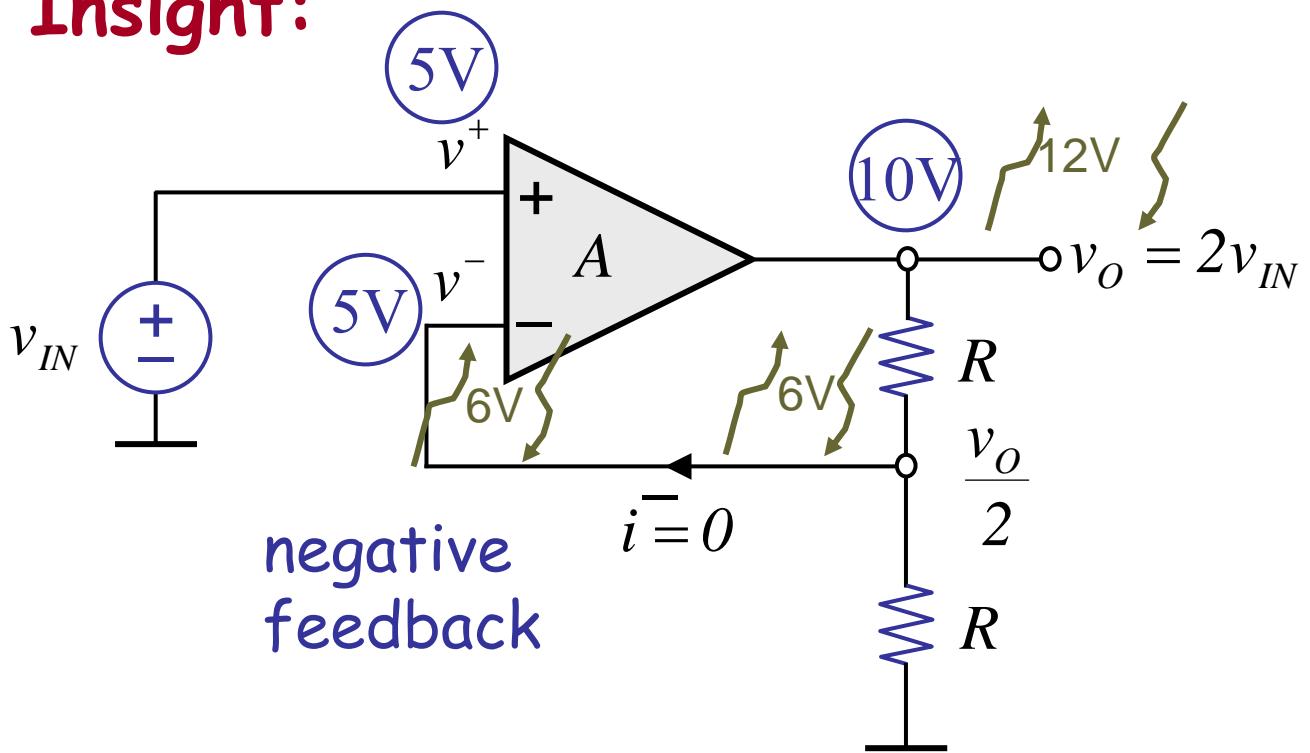

e.g.  $v_{IN} = 5V$

Suppose I perturb the circuit...

(e.g., force  $v_O$  momentarily to 12V somehow).


Stable point is when  $v^+ \approx v^-$ .

**Key:** negative feedback  $\rightarrow$  portion of output fed to  $-ve$  input.

e.g. Car antilock brakes  
 $\rightarrow$  small corrections.

# Question: How to control a high-strung device?

## Antilock brakes

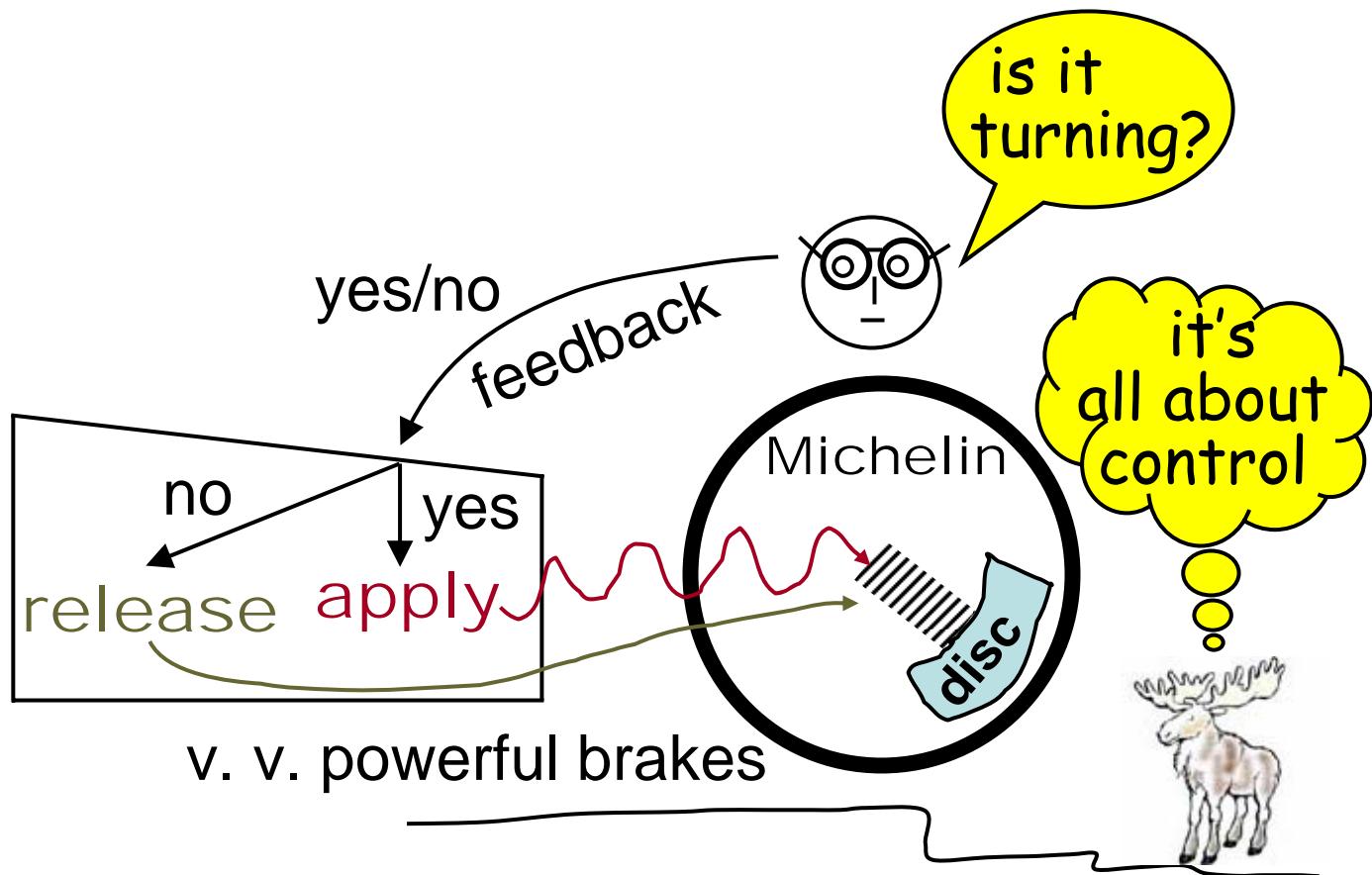

Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

# More op amp insights:

Observe, under negative feedback,

$$v^+ - v^- = \frac{v_o}{A} = \frac{\left( \frac{R_1 + R_2}{R_1} \right) v_{IN}}{A} \rightarrow 0$$

$$v^+ \approx v^-$$

We also know

$$i^+ \approx 0$$

$$i^- \approx 0$$


→ yields an easier analysis method  
(under negative feedback).

# Insightful analysis method under negative feedback


$$v^+ \approx v^-$$

$$i^+ \approx 0$$

$$i^- \approx 0$$

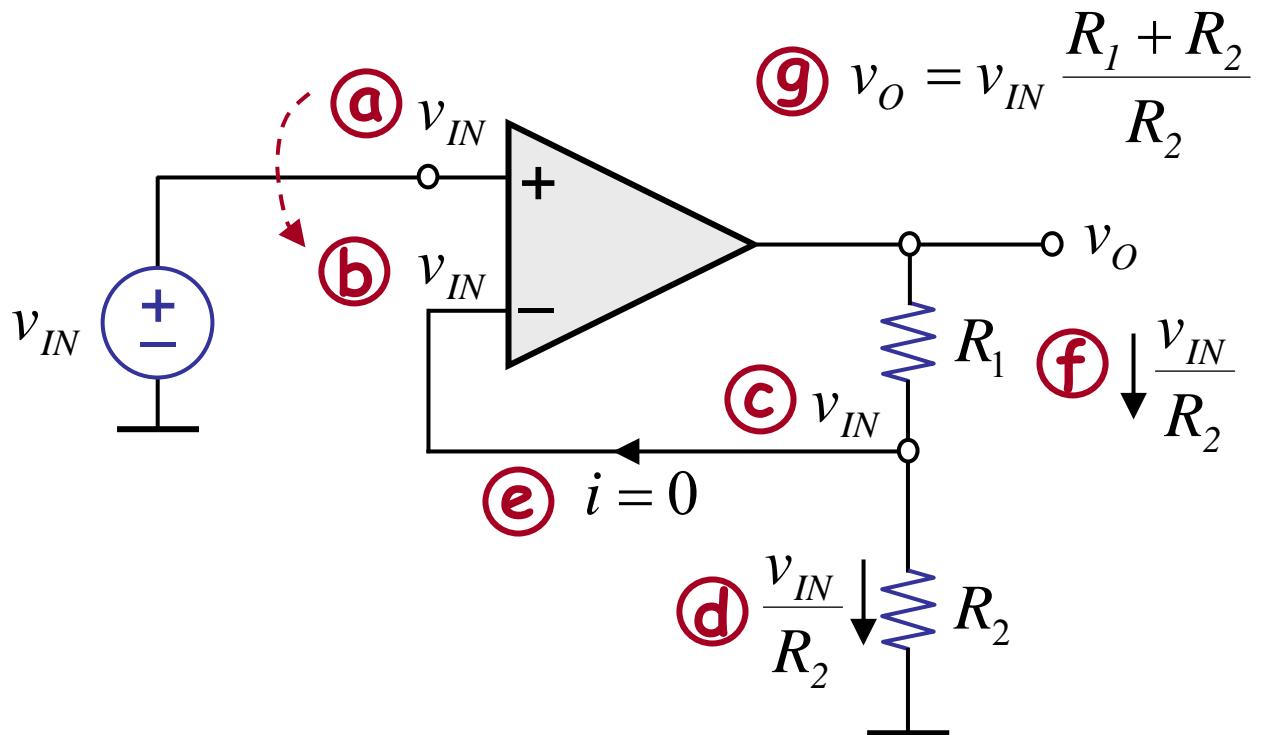

# Question:

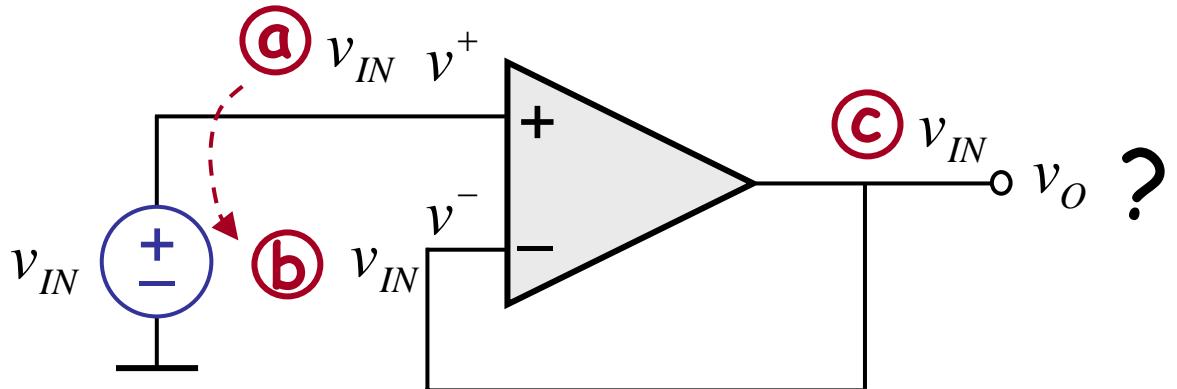


$$v_o \approx v_{IN}$$

or  $v_o = v_{IN} \frac{R_1 + R_2}{R_2}$

with  $R_1 = 0$

$$R_2 = \infty$$

# Why is this circuit useful?

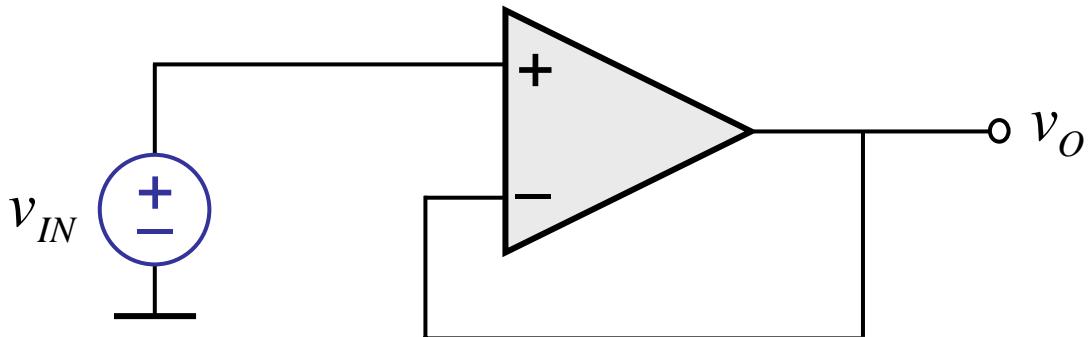

$$v_O \approx v_{IN}$$

## Buffer

voltage gain = 1  
input impedance =  $\infty$   
output impedance = 0  
current gain =  $\infty$   
power gain =  $\infty$