

6.002


**CIRCUITS AND
ELECTRONICS**

Op Amps Positive Feedback


Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

Negative vs Positive Feedback

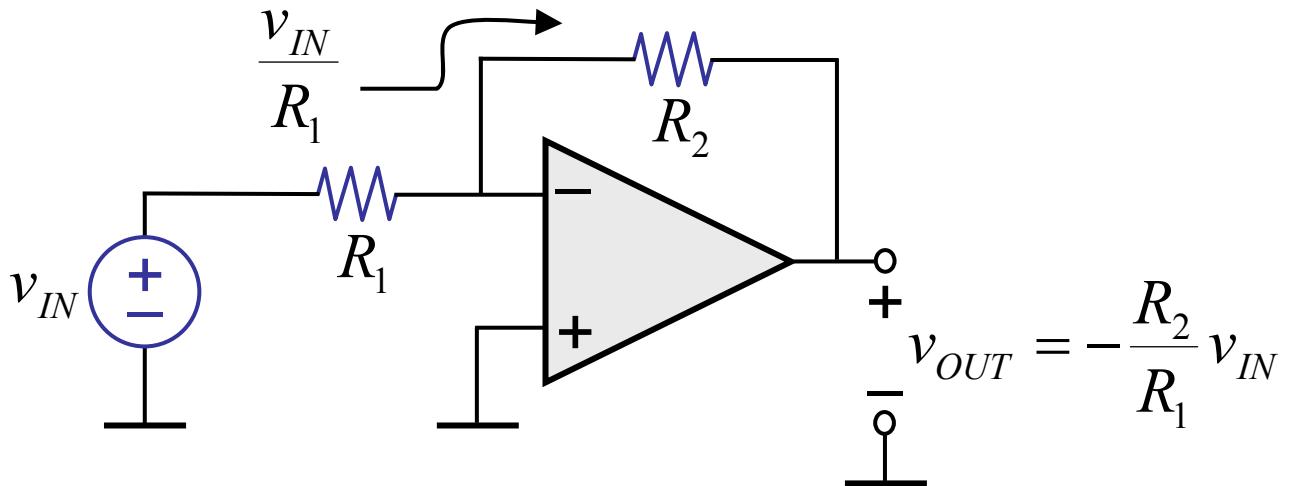Consider this circuit — negative feedback



and this — positive feedback

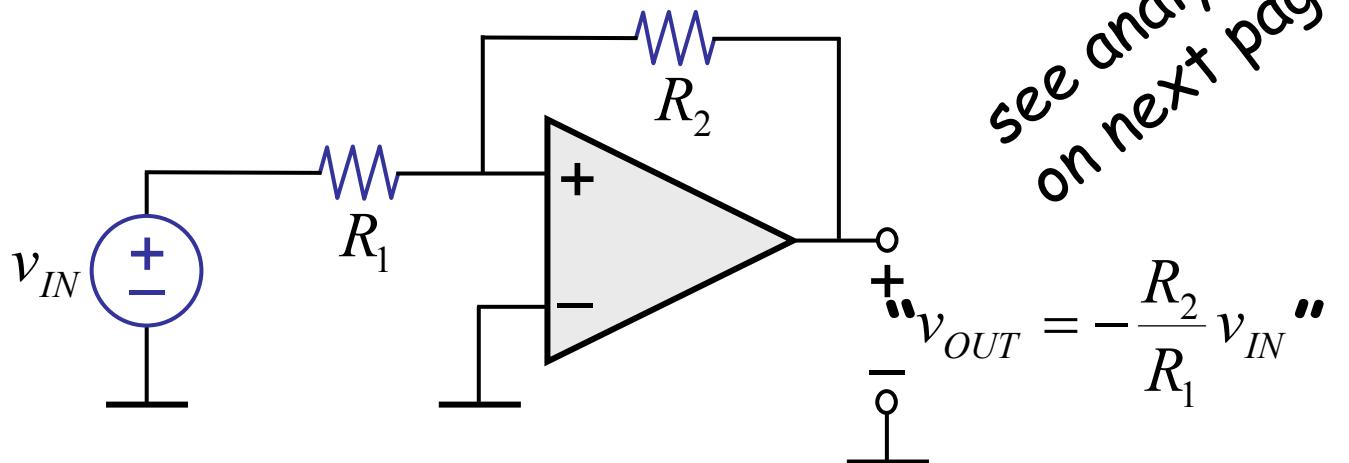


What's the difference?

Consider what happens when there is a perturbation...
Positive feedback drives op amp into saturation:

$$v_{OUT} \rightarrow \pm V_S$$


Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

Static Analysis of Positive Feedback Ckt

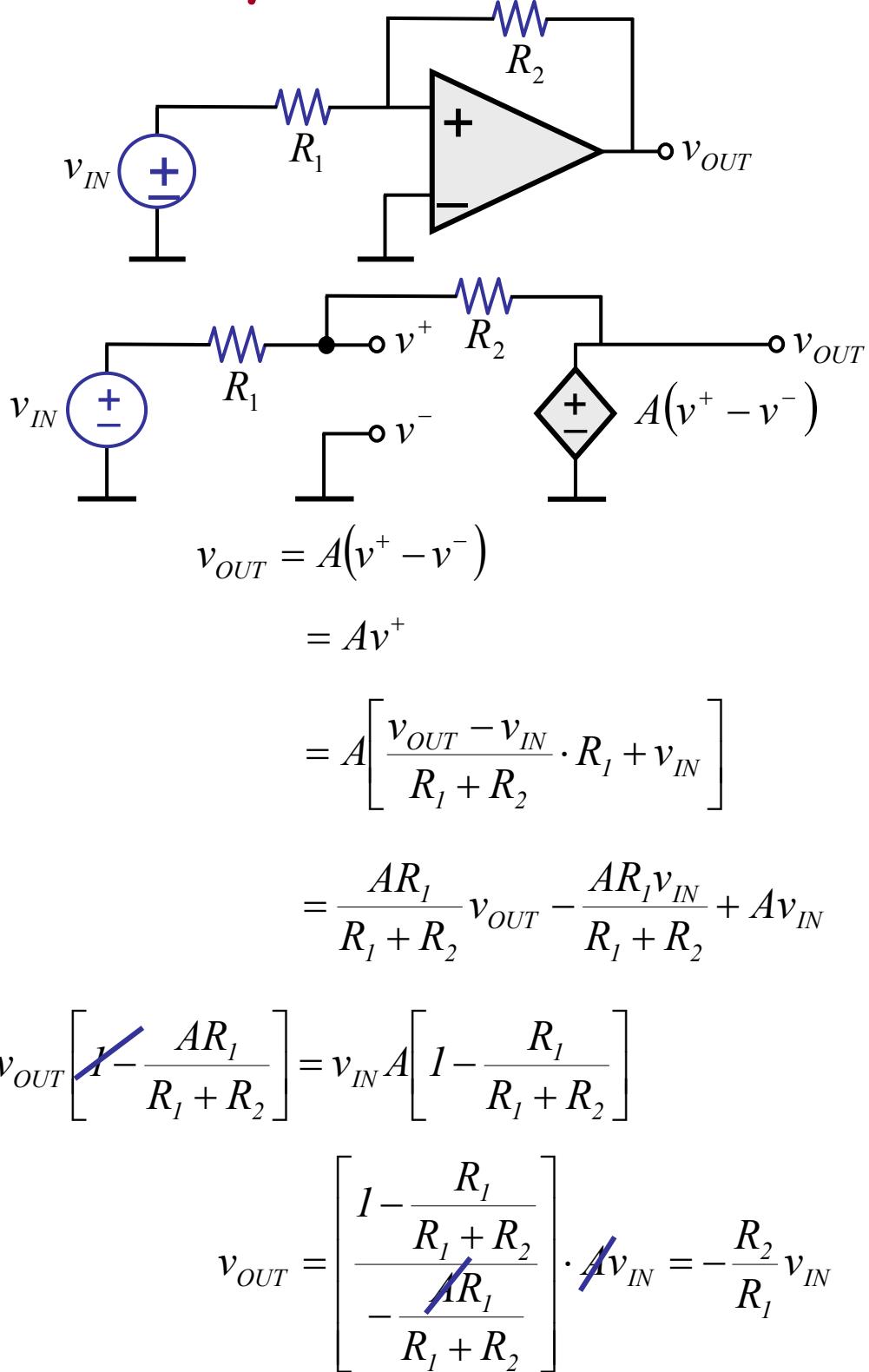

Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].


Representing dynamics of op amp...

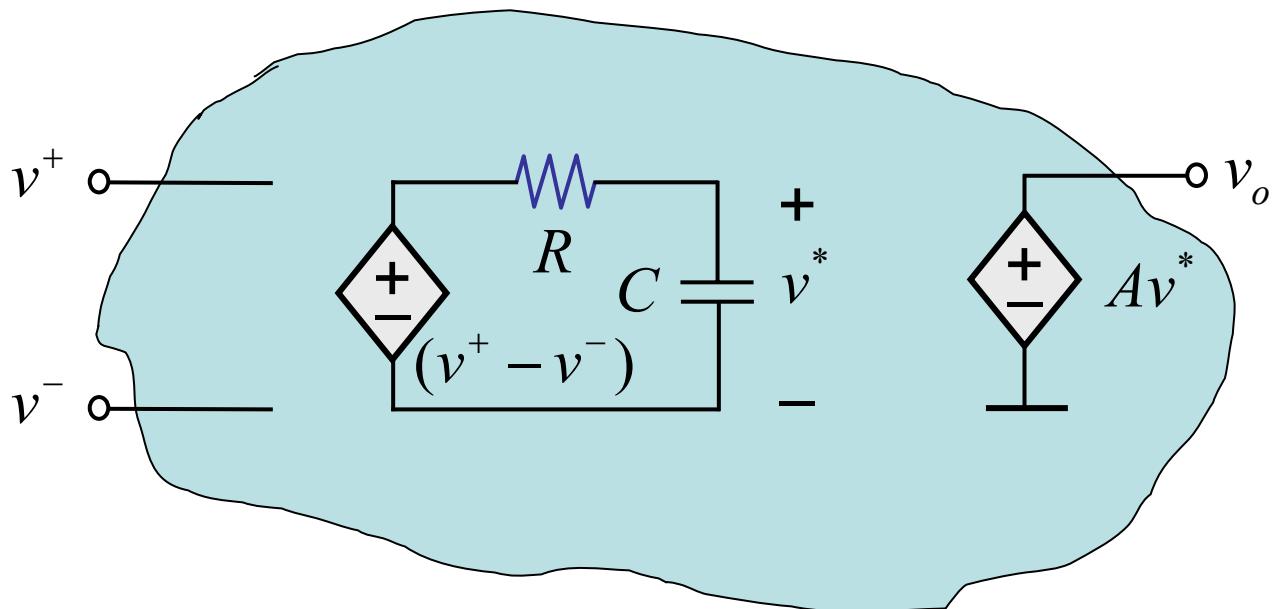


Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

Representing dynamics of op amp...

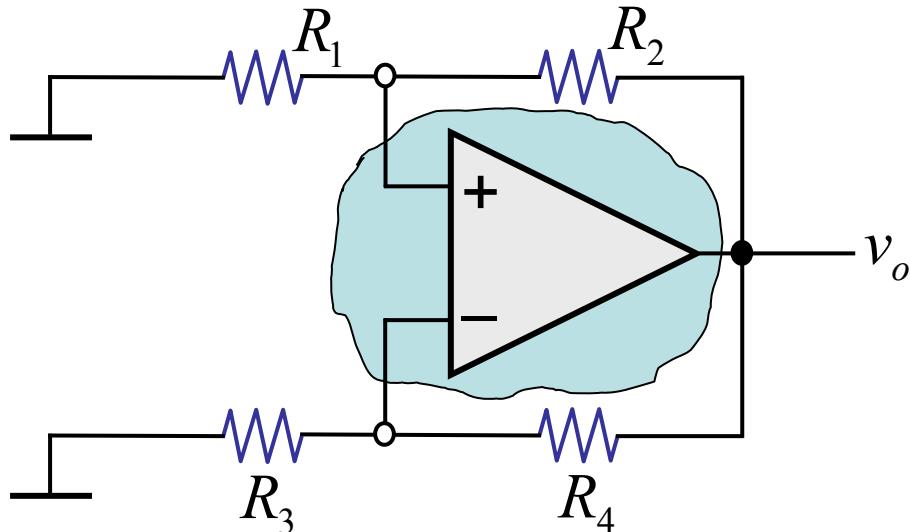Consider this circuit and let's analyze its dynamics to build insight.



Circuit model

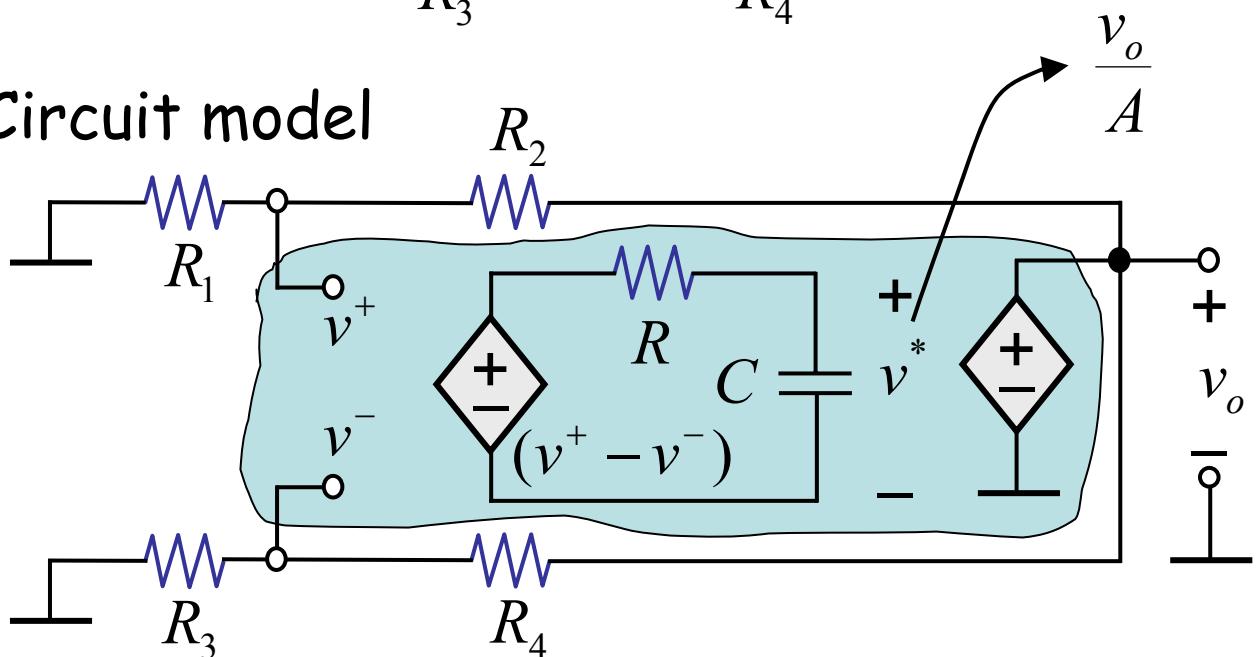

Let's develop equation representing time behavior of v_o .

Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

Dynamics of op amp...

$$v_o = Av^* \quad \text{or} \quad v^* = \frac{v_o}{A}$$

$$RC \frac{dv^*}{dt} + v^* = v^+ - v^-$$

$$\frac{RC}{A} \frac{dv_o}{dt} + \frac{v_o}{A} = v^+ - v^- \\ = (\gamma^+ - \gamma^-) v_o$$

$$\left| \begin{array}{l} v^+ = \frac{v_o R_1}{R_1 + R_2} = \gamma^+ v_o \\ v^- = \frac{v_o R_3}{R_3 + R_4} = \gamma^- v_o \end{array} \right.$$

neglect

or $\frac{dv_o}{dt} + \left[\frac{1}{RC} + \frac{A}{RC} (\gamma^- - \gamma^+) \right] v_o = 0$

$$\frac{dv_o}{dt} + \underbrace{\frac{A}{RC} (\gamma^- - \gamma^+)}_{\text{time}^{-1}} v_o = 0$$

or $\frac{dv_o}{dt} + \frac{v_o}{T} = 0 \quad \text{where } T = \frac{RC}{A(\gamma^- - \gamma^+)}$

$$v_o(0) = 0$$

Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

Consider a small disturbance to v_o (noise).

if $\bar{\gamma} > \dot{\gamma}^+$ T is positive


$$v_o = K e^{-\frac{t}{T}} \quad \text{stable}$$

if $\dot{\gamma}^+ > \bar{\gamma}$ T is negative

$$v_o = K e^{\frac{t}{|T|}} \quad \text{unstable}$$

if $\dot{\gamma}^+ = \bar{\gamma}$ T is very large




$$v_o = K \quad \text{neutral}$$

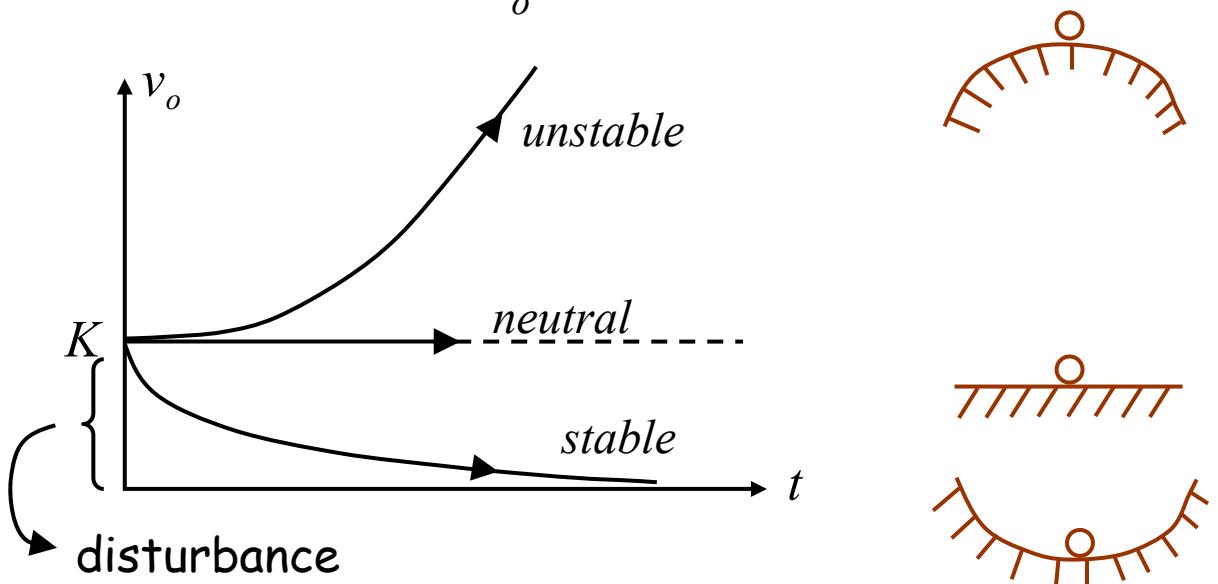

Now, let's build some useful circuits with positive feedback.



Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

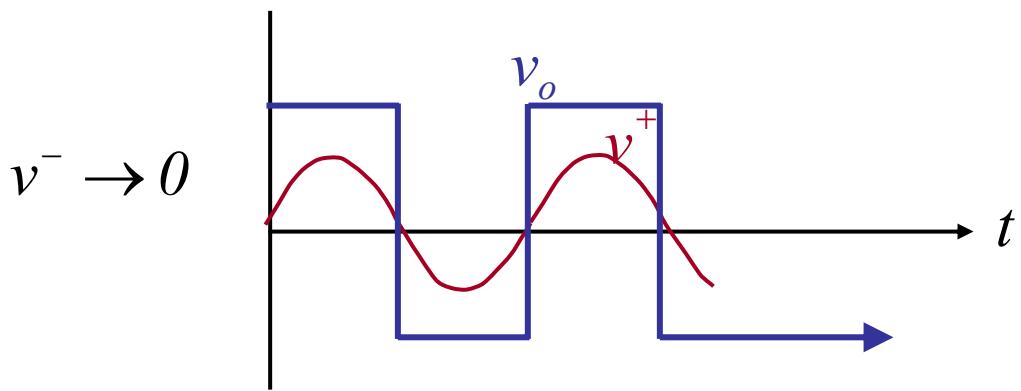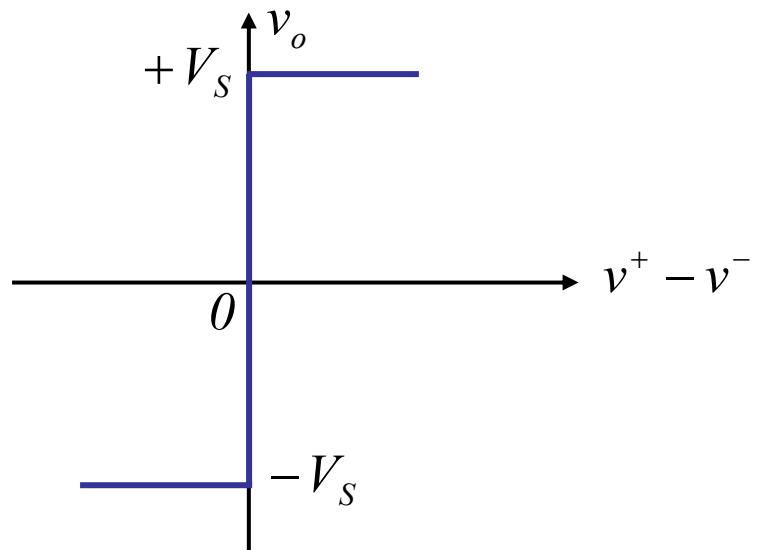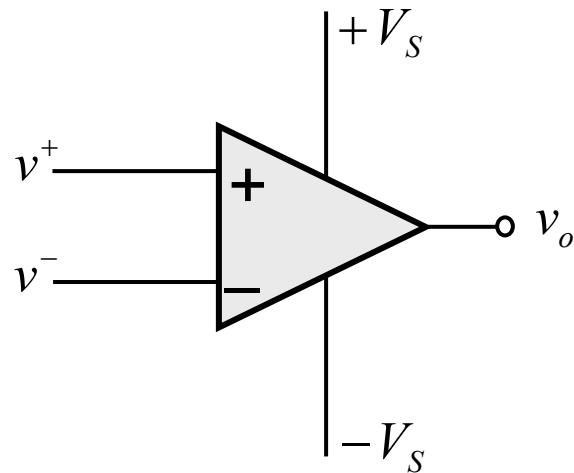One use for instability: Build on the basic op amp as a comparator





Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

Now, use positive feedback

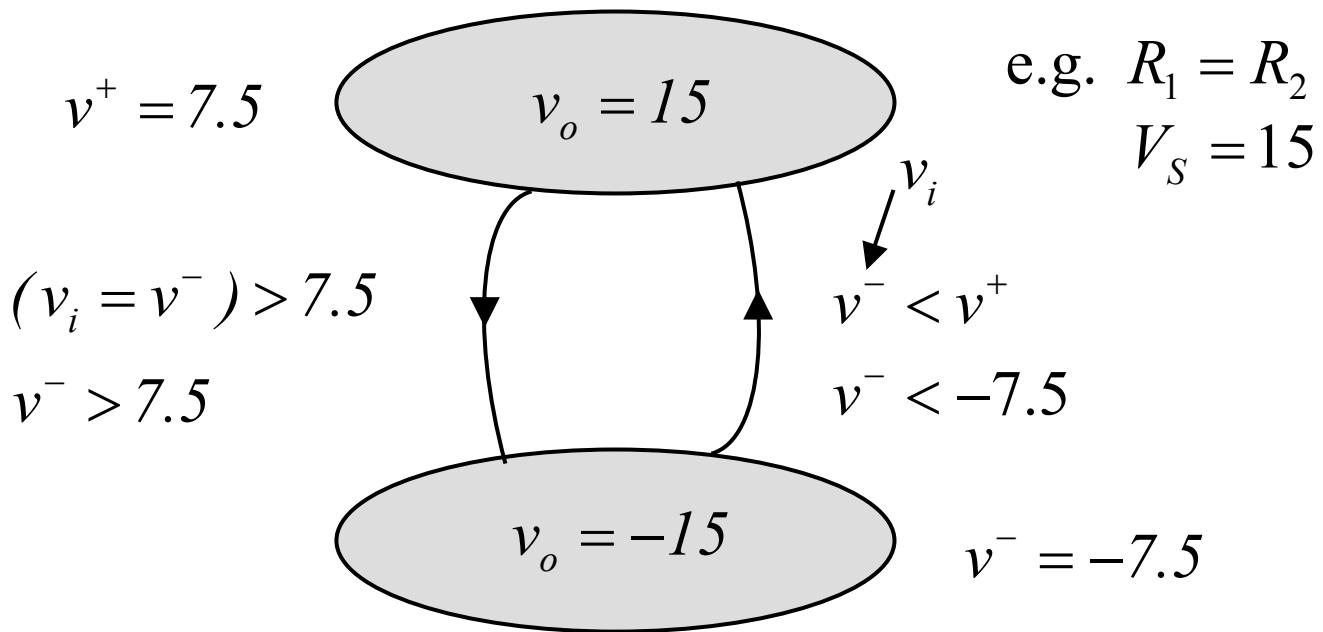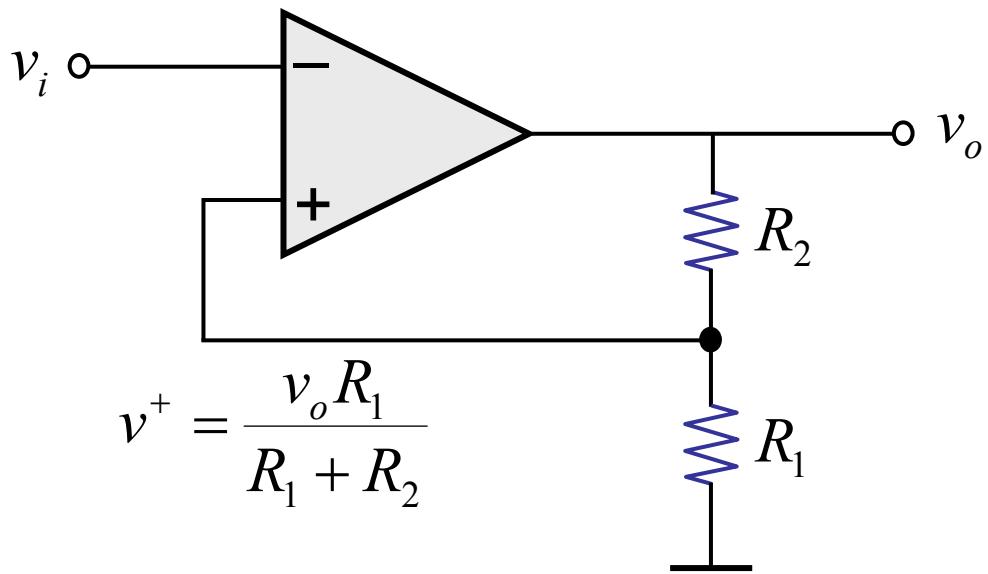


Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

Now, use positive feedback

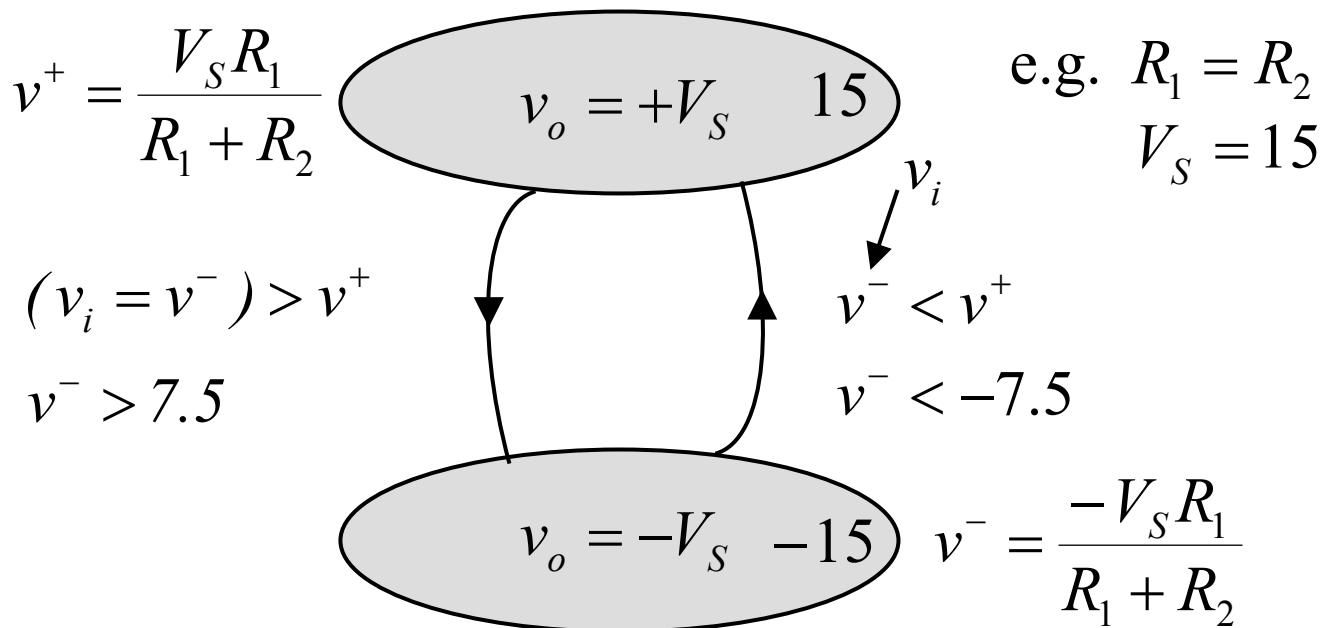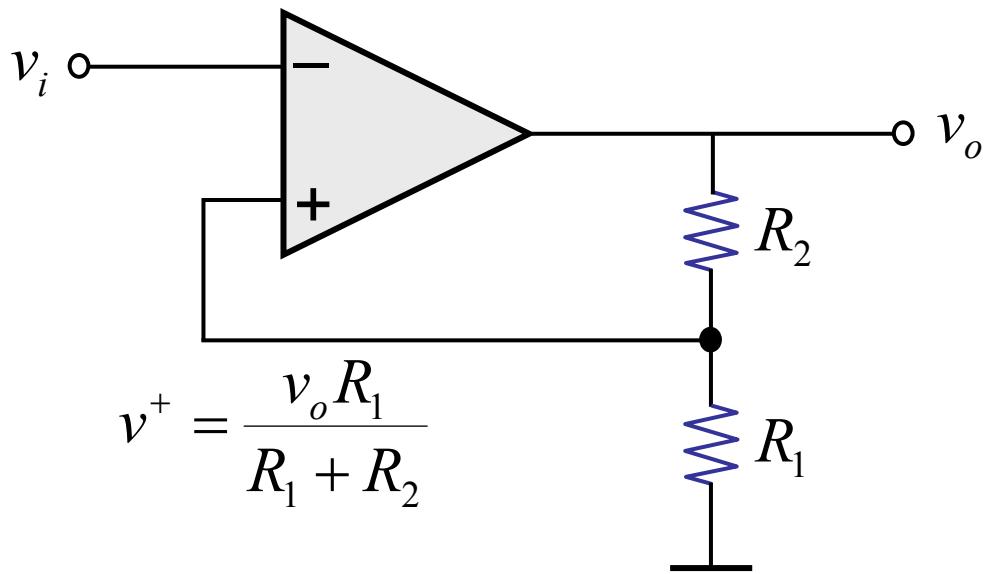

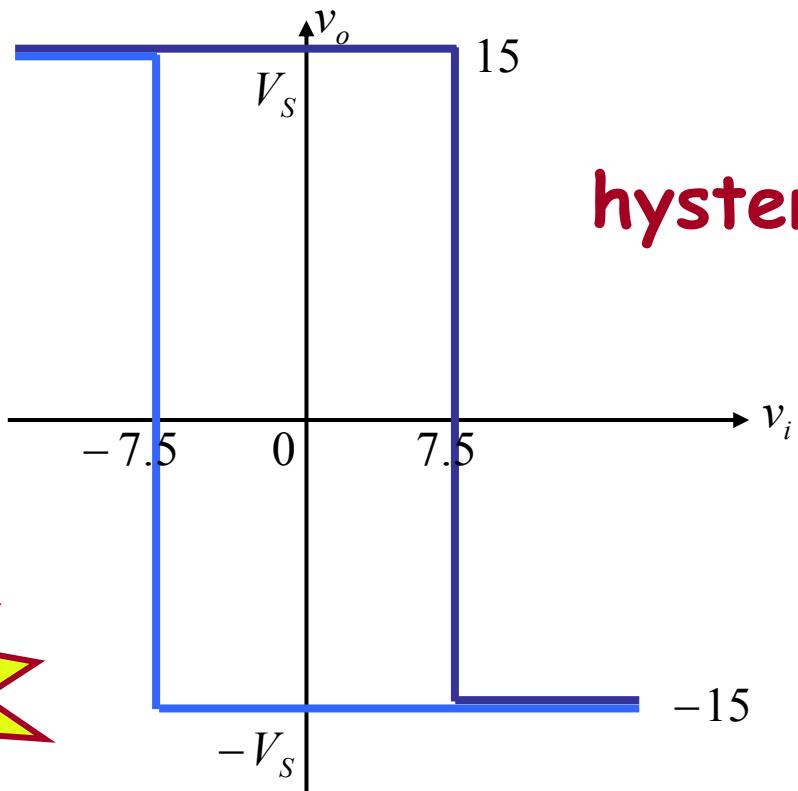Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].




hysteresis




Why is hysteresis useful?

e.g., analog
to digital

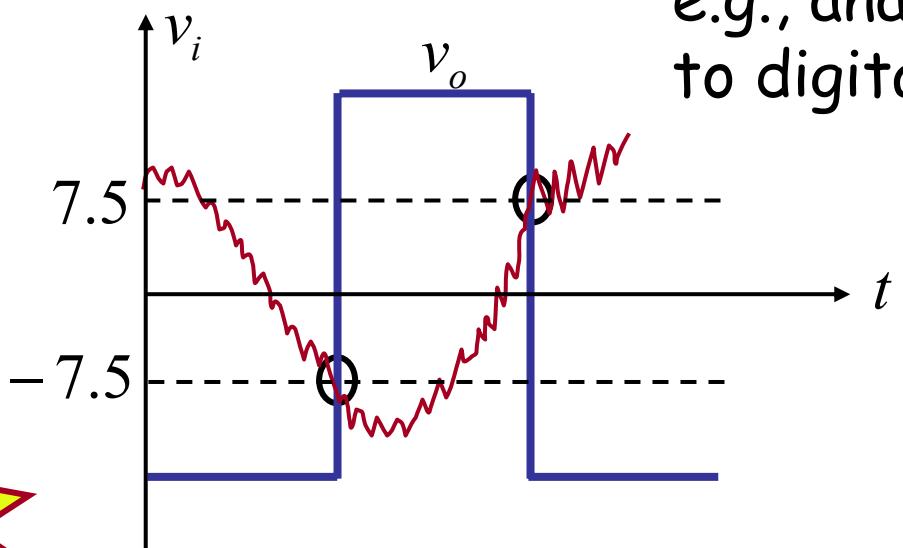


Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

Without hysteresis

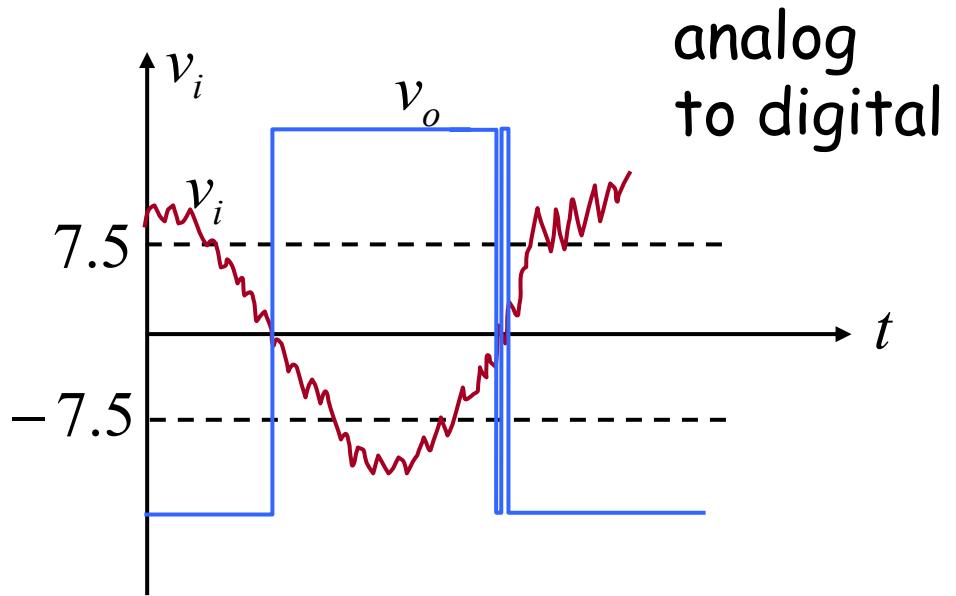

Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

Oscillator — can create a clock

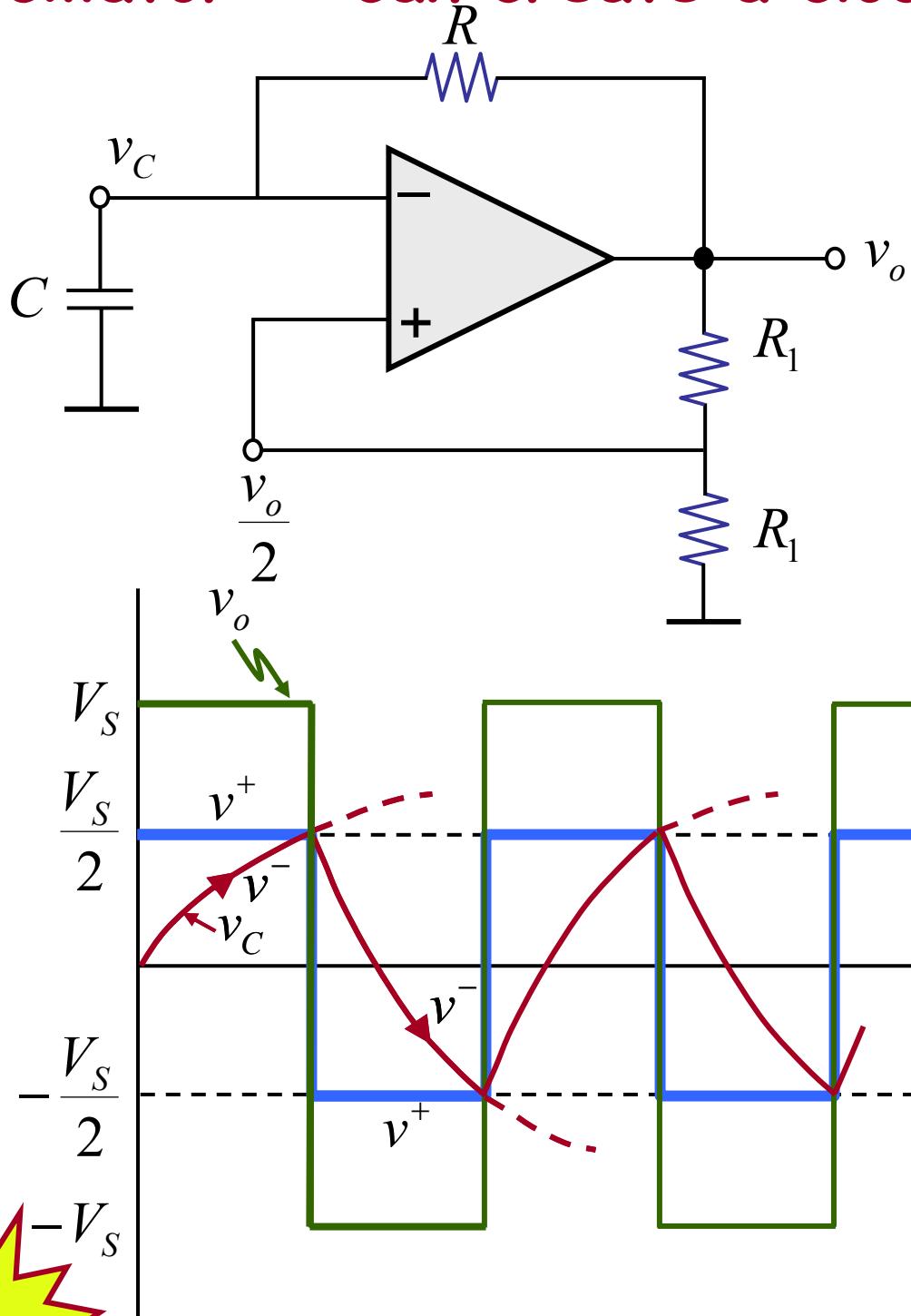


Demo

Assume $v_o = V_S$ at $t = 0$
 $v_C = 0$


Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

Clocks in Digital Systems

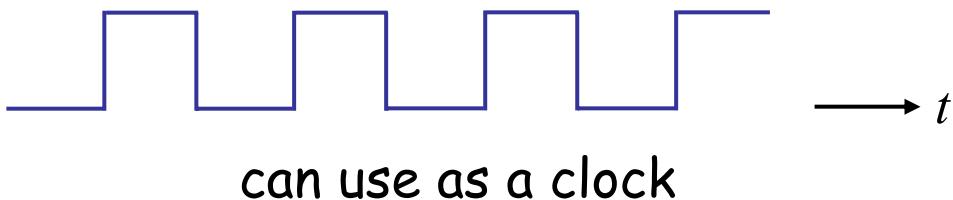- We built an oscillator using an op amp.



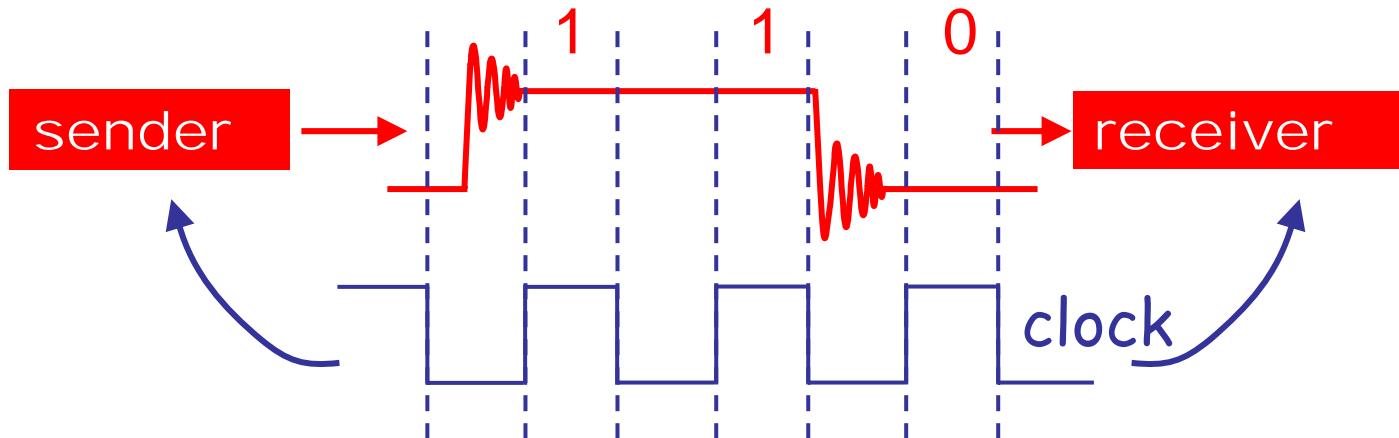- Why do we use a clock in a digital system?
(See page 735 of A & L)



- (a) 1,1,0?
- (b) When is the signal valid?
common timebase -- when to "look" at a signal
(e.g. whenever the clock is high)

→ Discretization of time
one bit of information associated with
an interval of time (cycle)

Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].