

**6.002**

**CIRCUITS AND  
ELECTRONICS**


# Nonlinear Analysis

Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

**6.002 Fall 2000 Lecture 6**


# Review

## ■ Discretize matter → LCA

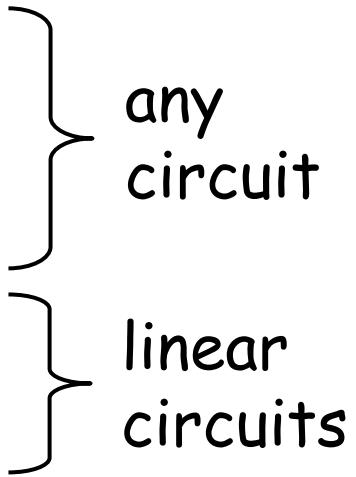- m1 ► KVL, KCL,  $i-v$
  - m2 ► Composition rules
  - m3 ► Node method
  - m4 ► Superposition
  - m5 ► Thévenin, Norton
- 
- The list of methods is grouped into two categories by curly braces on the right side:
- A brace groups m1, m2, m3, and m4, with the label "any circuit" positioned to its right.
  - A brace groups m5, with the label "linear circuits" positioned to its right.
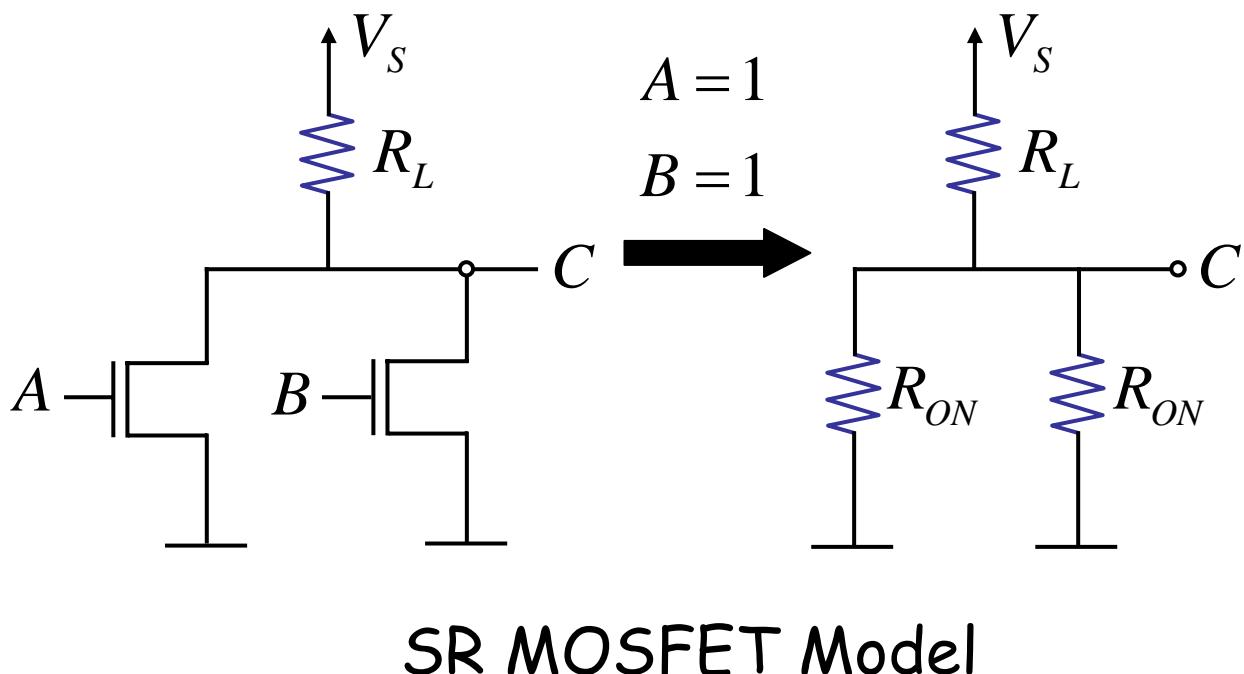
# Review

- Discretize value → Digital abstraction
  - Subcircuits for given “switch” setting are linear! So, all 5 methods ( $m_1 - m_5$ ) can be applied




# Today


## ■ Nonlinear Analysis

- ▶ Analytical method  
based on  $m_1, m_2, m_3$
- ▶ Graphical method
- ▶ Introduction to incremental analysis

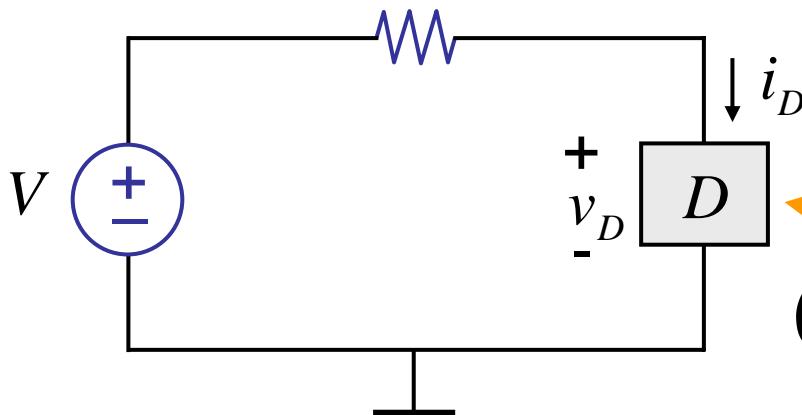
# How do we analyze nonlinear circuits, for example:



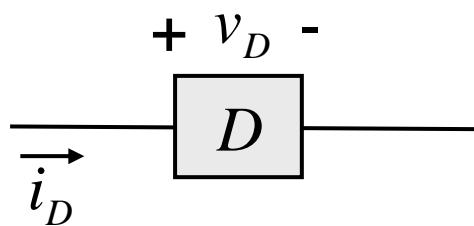Hypothetical  
nonlinear  
device  
(Expo Dweeb ☺)



$$i_D = ae^{bv_D}$$

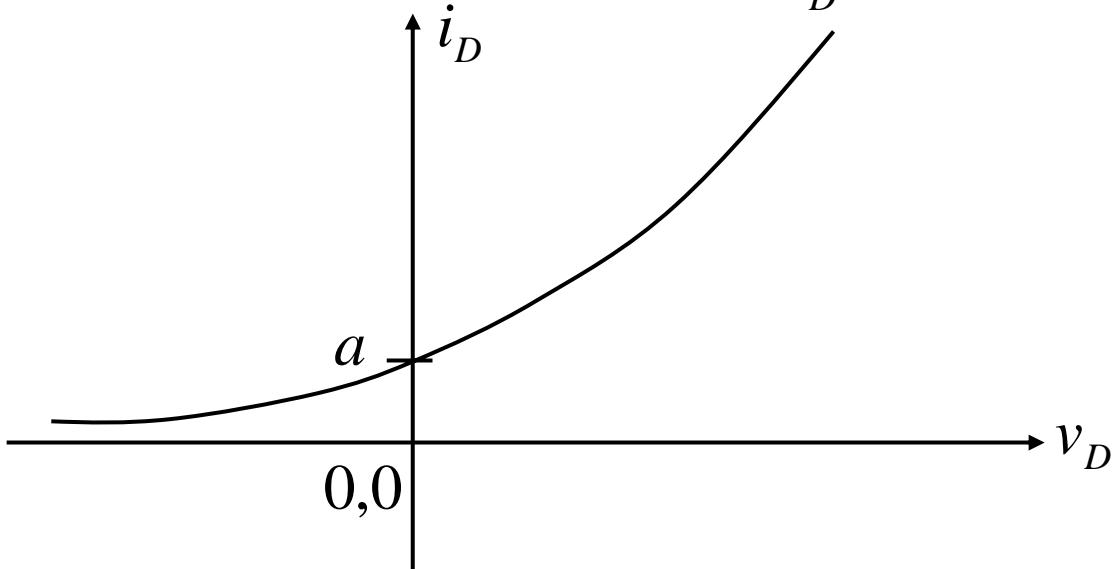

(Curiously, the device supplies power when  $v_D$  is negative)

# Method 1: Analytical Method

Using the node method,  
(remember the node method applies for linear or  
nonlinear circuits)

$$\frac{v_D - V}{R} + i_D = 0 \quad \textcircled{1}$$

$$i_D = ae^{bv_D} \quad \textcircled{2}$$

2 unknowns      2 equations



Solve the equation by

- trial and error
- numerical methods


# Method 2: Graphical Method

Notice: the solution satisfies equations

① and ②

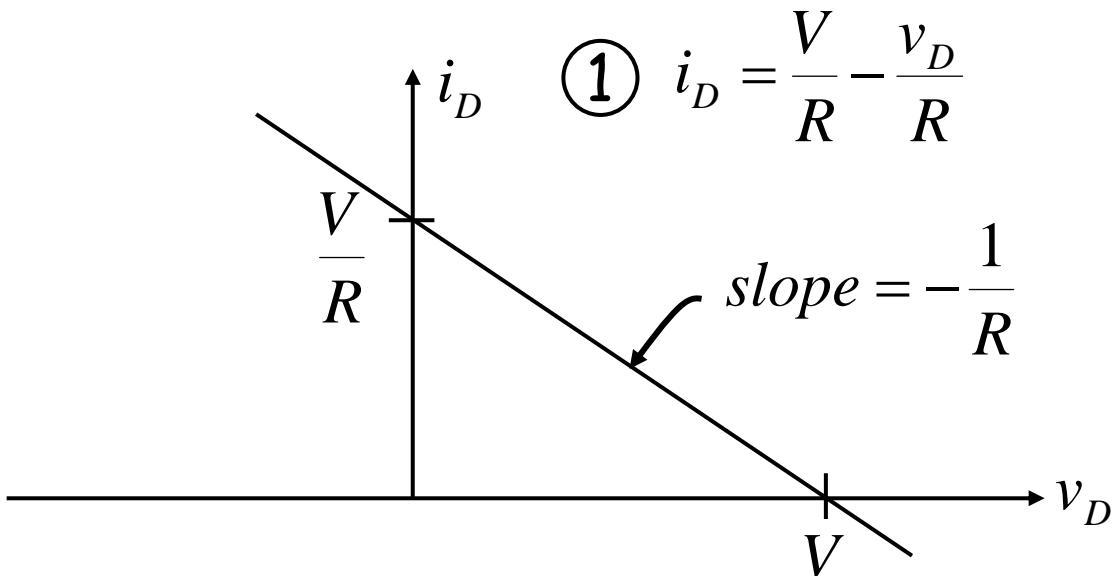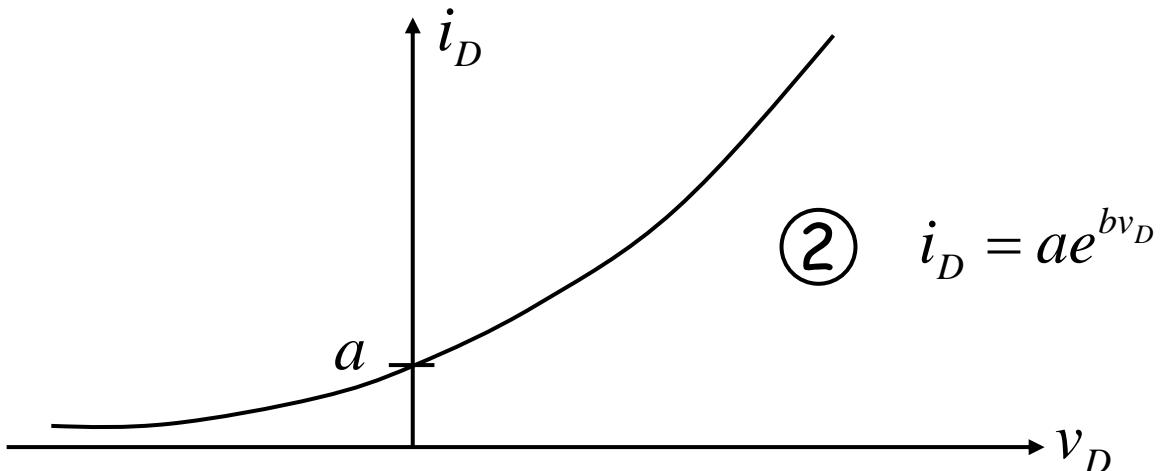

## Combine the two constraints

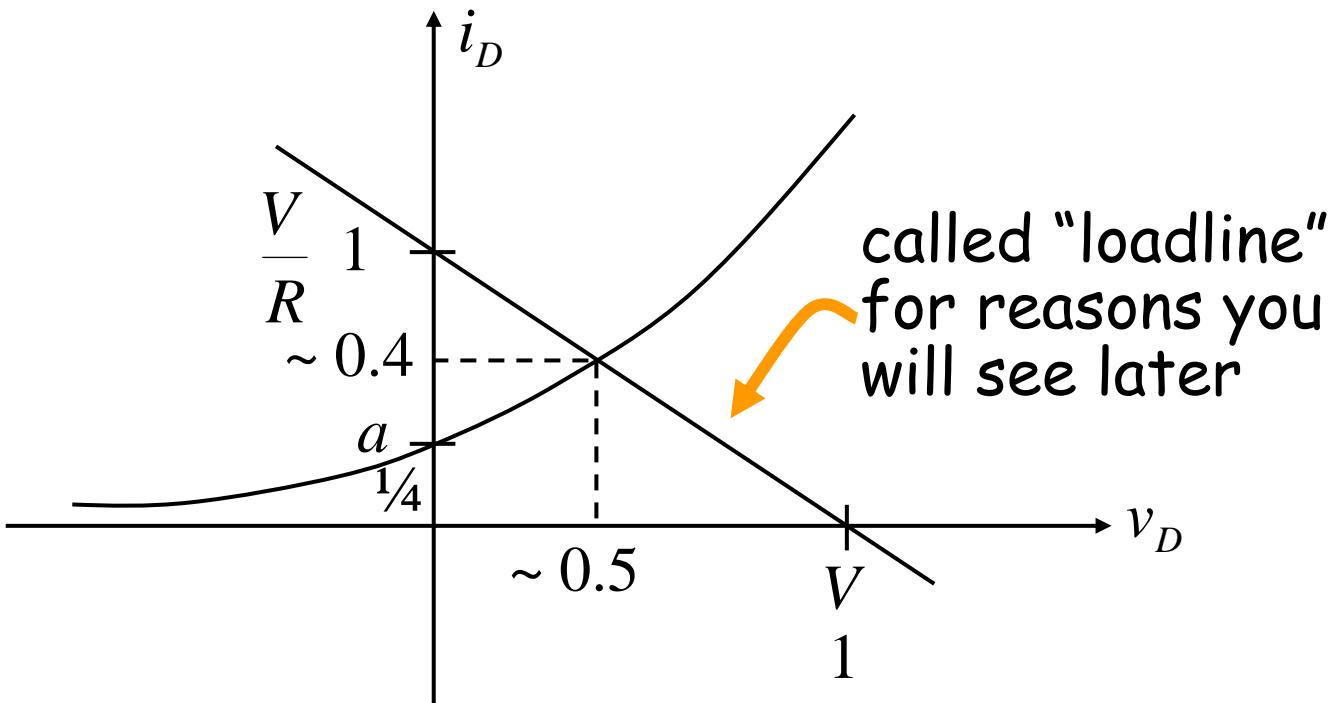

$$\text{e.g. } V = 1 \quad v_D = 0.5V$$

$$R = 1 \quad i_D = 0.4A$$



$$a = \frac{1}{4}$$

$$b = 1$$

# Method 3: Incremental Analysis


Motivation: music over a light beam

Can we pull this off?

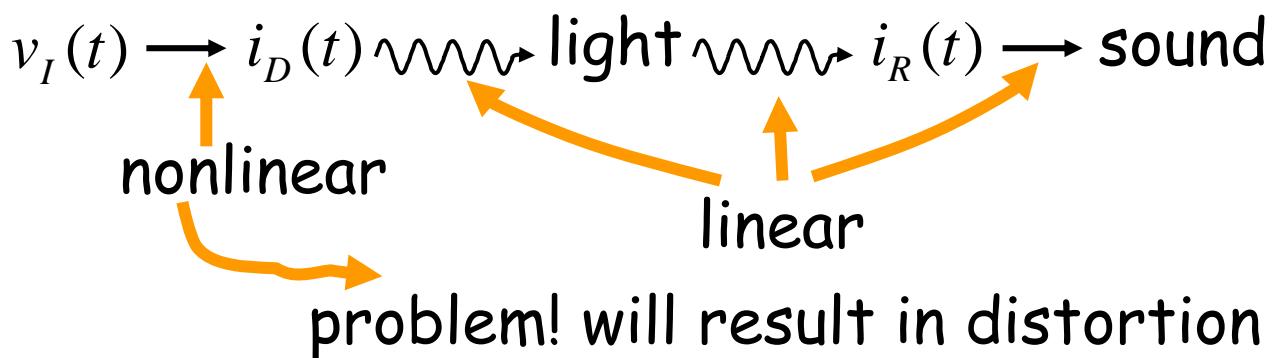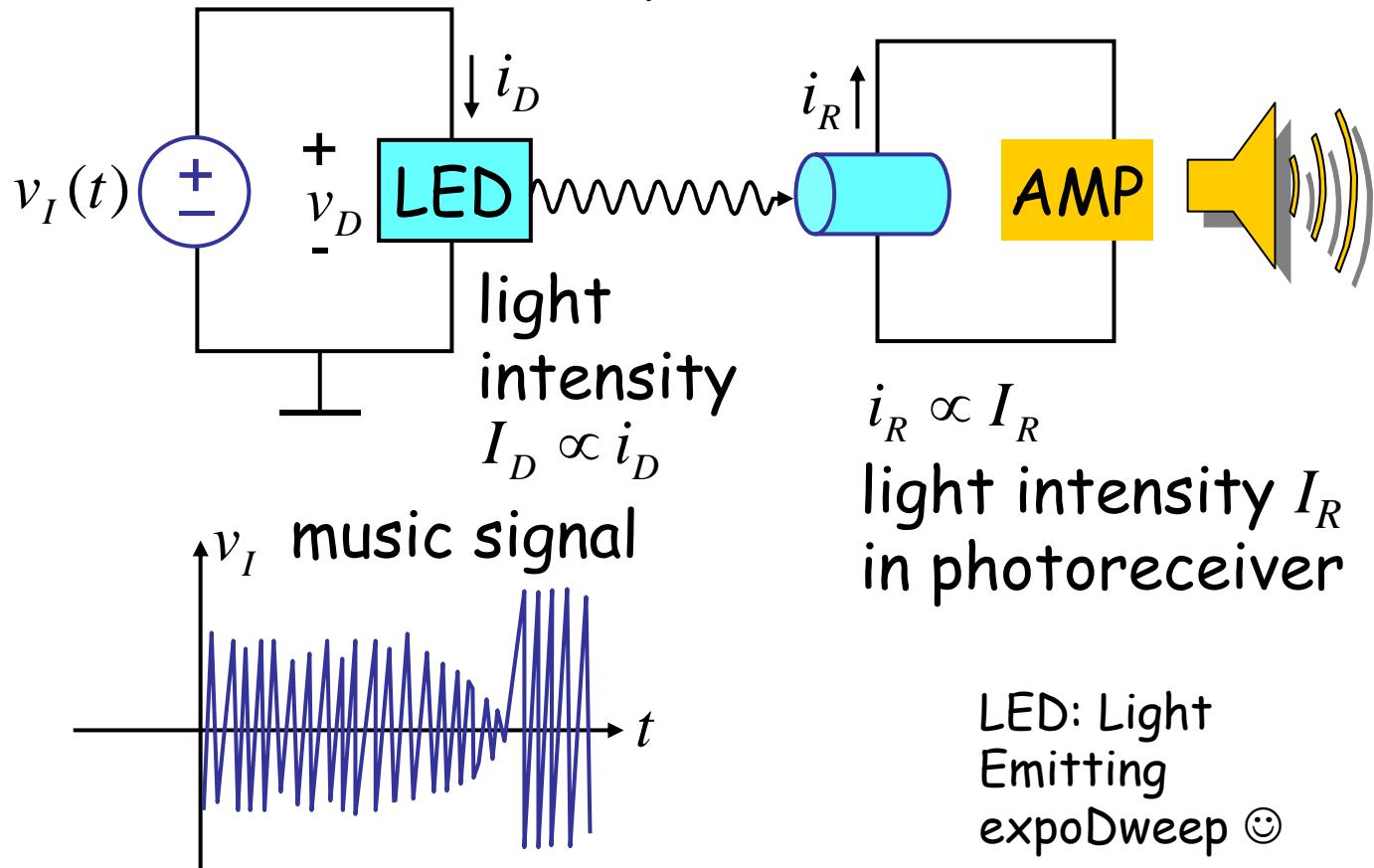

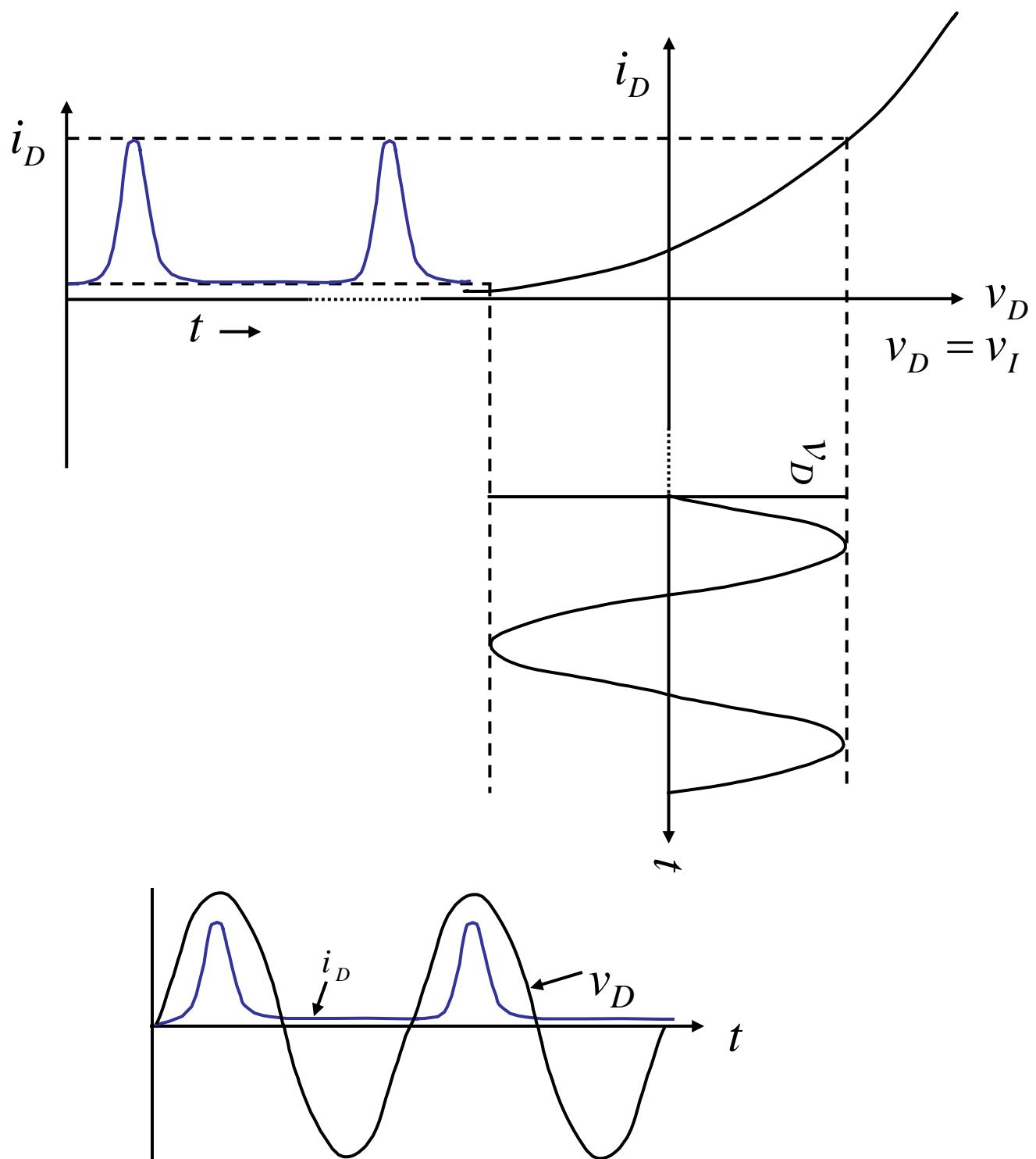
# Problem:

The LED is nonlinear  $\rightarrow$  distortion



Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

# If only it were linear ...

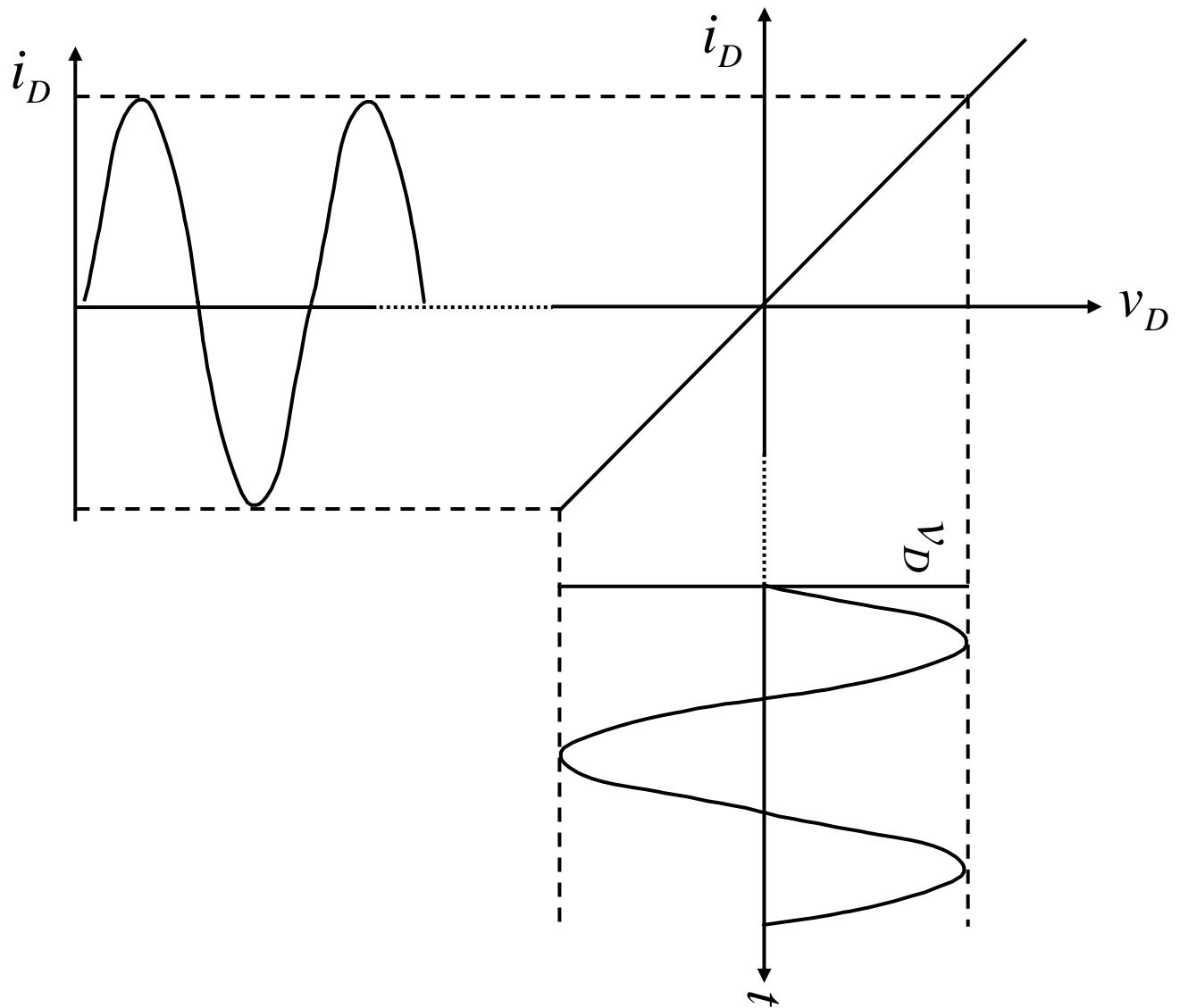

it would've been ok.

What do we do?  
Zen is the answer  
... next lecture!