

6.002

**CIRCUITS AND
ELECTRONICS**

Incremental Analysis

Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

6.002 Fall 2000 Lecture 7

Review

Nonlinear Analysis

- ▶ Analytical method
- ▶ Graphical method

Today



- ▶ Incremental analysis

Reading: Section 4.5


Method 3: Incremental Analysis

Motivation: music over a light beam

Can we pull this off?

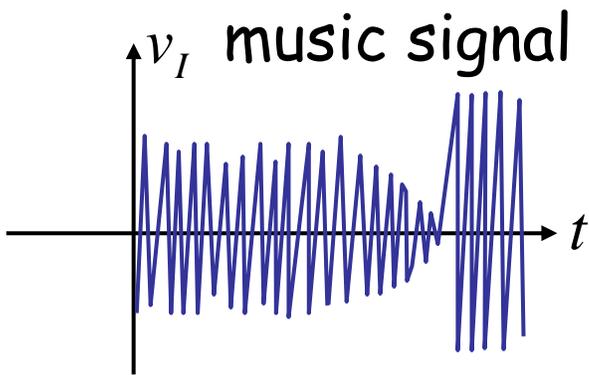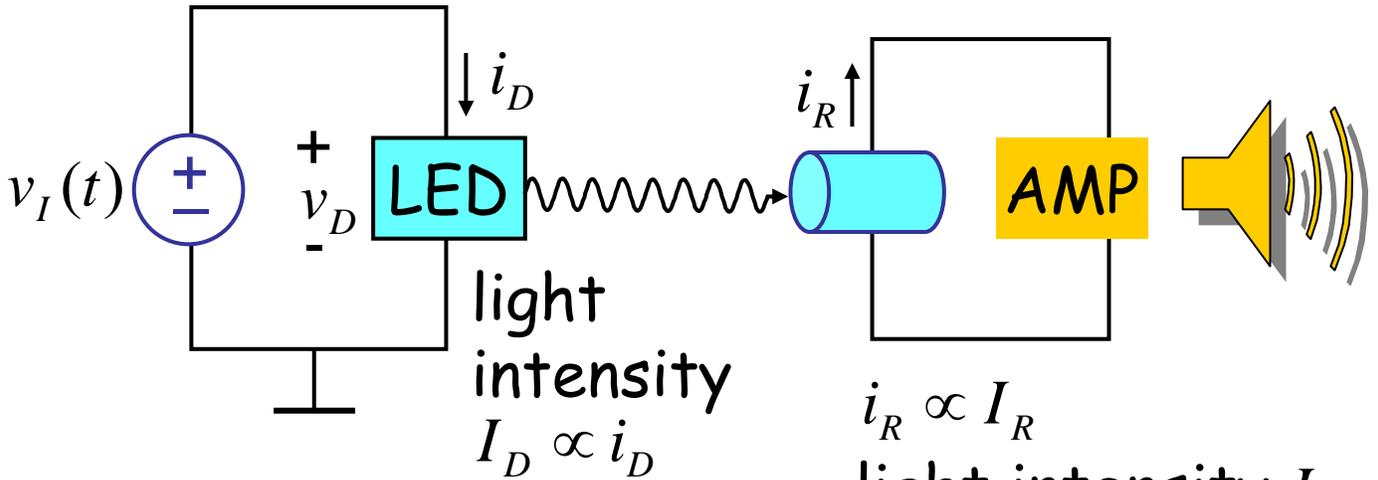


LED: Light Emitting expDweep ☺

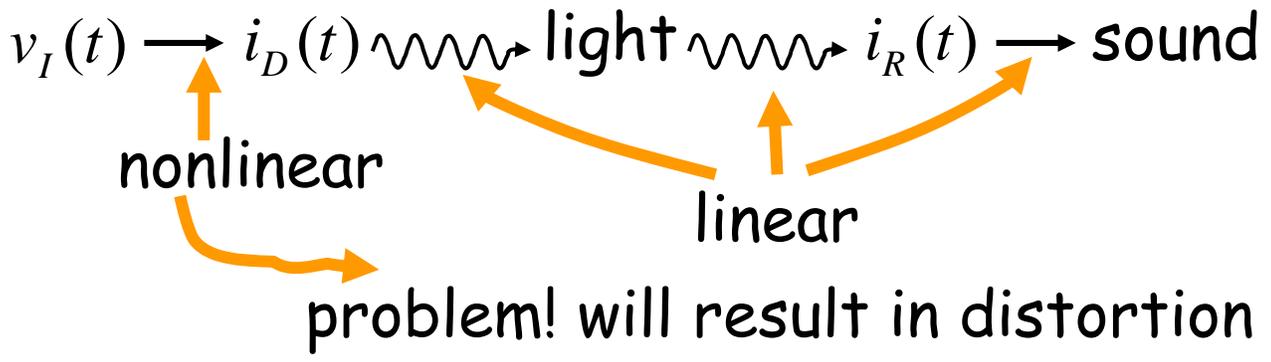

Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].

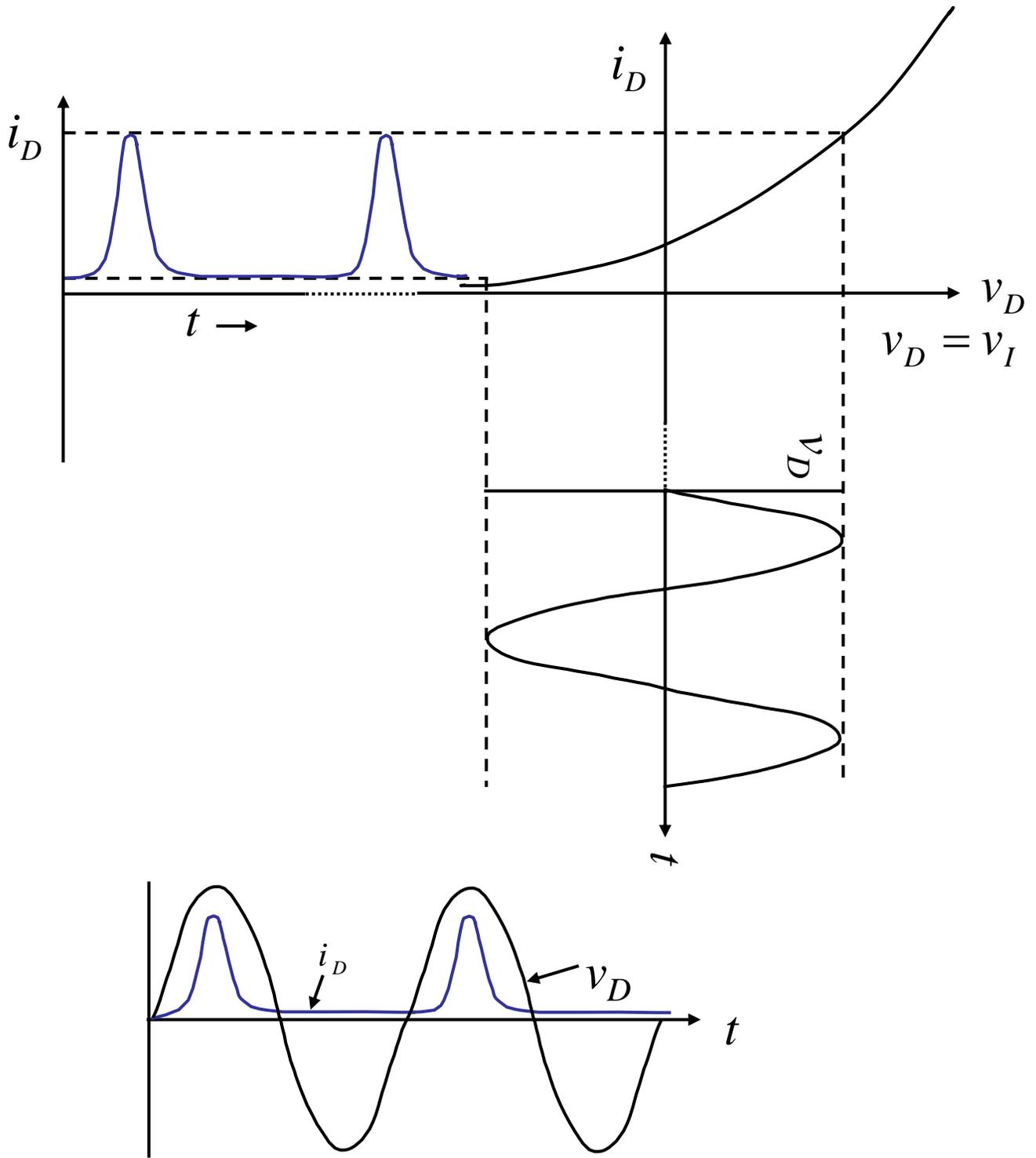
Problem:

The LED is nonlinear \rightarrow distortion




Cite as: Anant Agarwal and Jeffrey Lang, course materials for 6.002 Circuits and Electronics, Spring 2007. MIT OpenCourseWare (<http://ocw.mit.edu/>), Massachusetts Institute of Technology. Downloaded on [DD Month YYYY].


Insight:

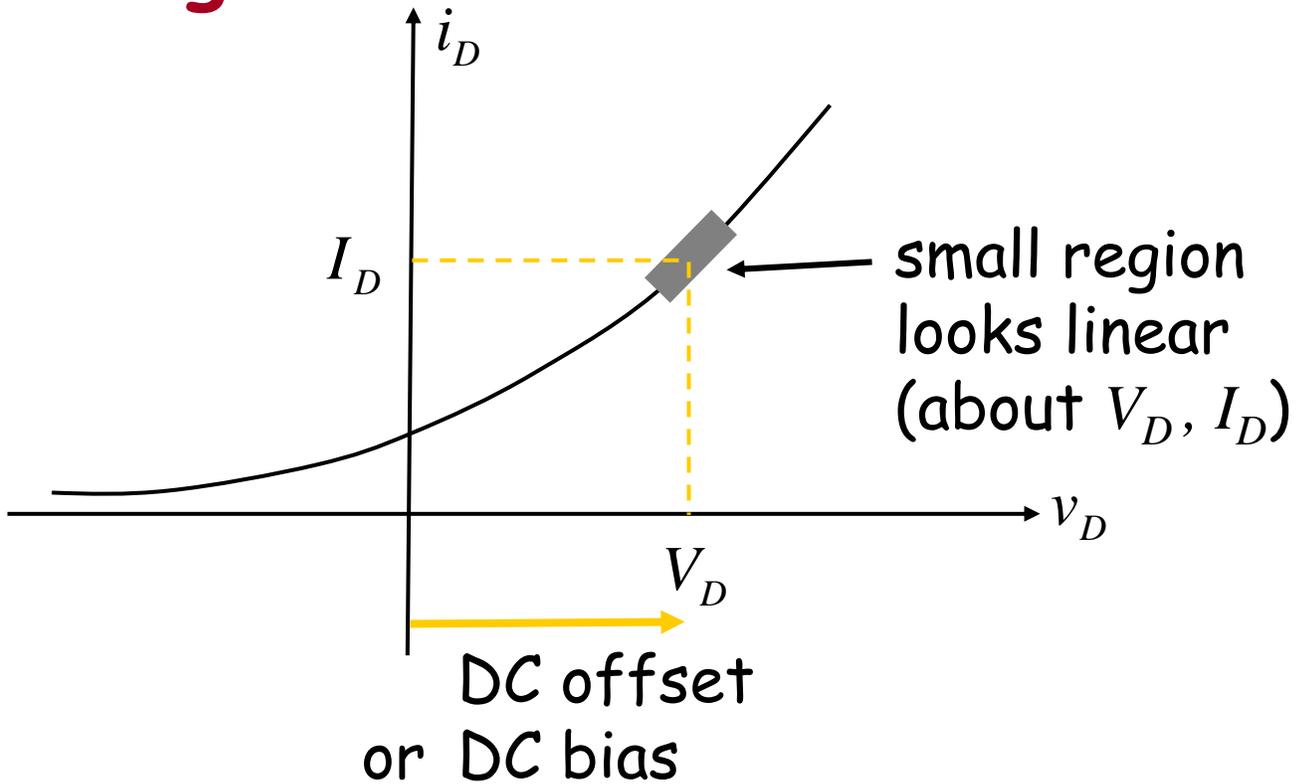



Trick:

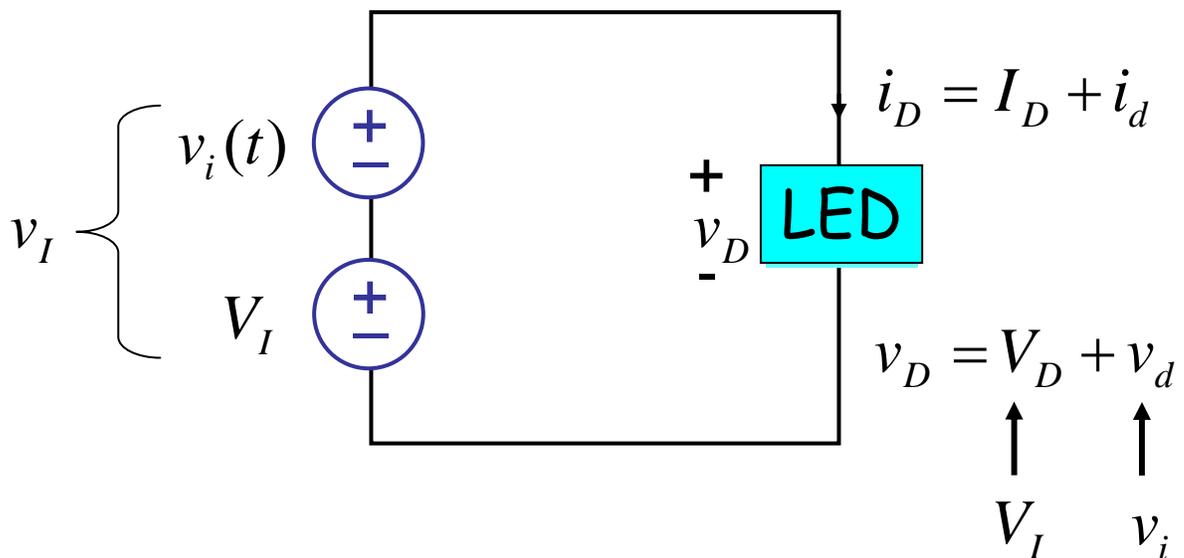

Result

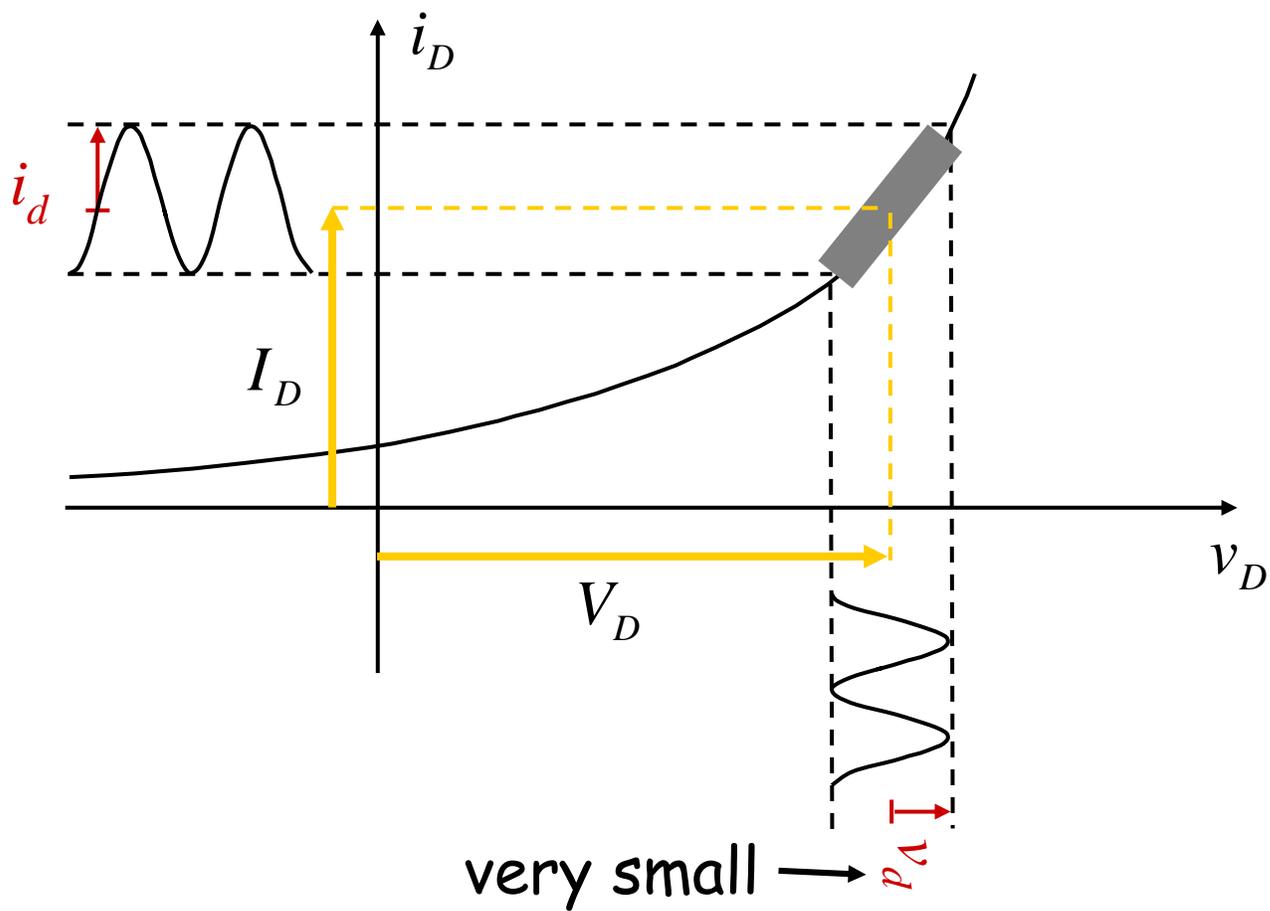

Result

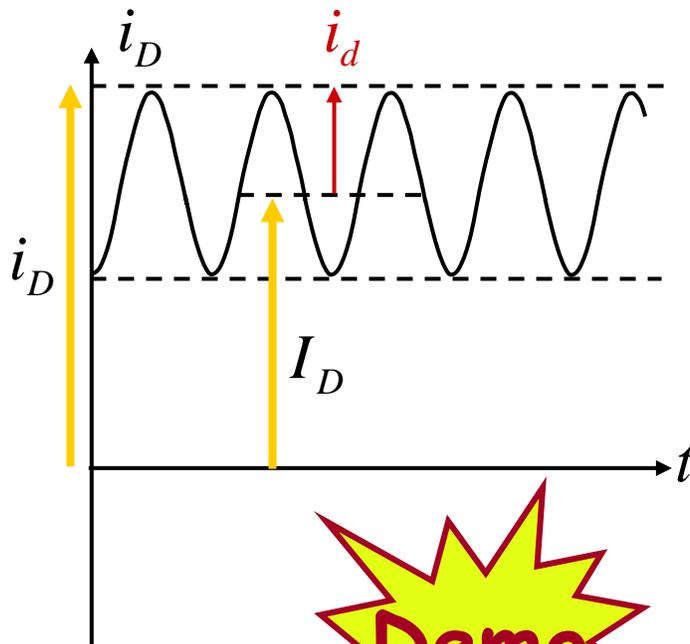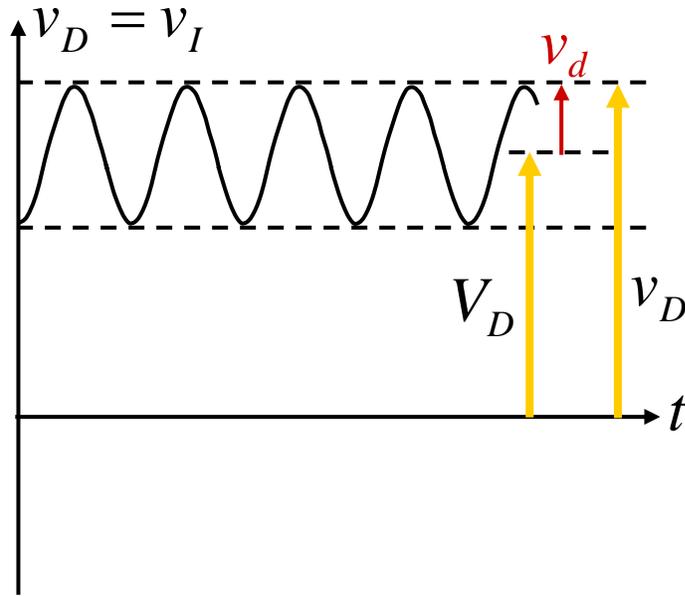

~linear!



The incremental method: (or small signal method)

1. Operate at some DC offset or bias point (V_D, I_D) .
2. Superimpose small signal (v_d) (music) on top of (V_D) .
3. Response (i_d) to small signal (v_d) is approximately linear.

Notation:

$$i_D = I_D + i_d$$

The diagram illustrates the equation $i_D = I_D + i_d$. Three yellow arrows point from the text labels below to the terms in the equation: one from 'total variable' to i_D , one from 'DC offset' to I_D , and one from 'small superimposed signal' to i_d .

total variable DC offset small superimposed signal

What does this mean mathematically?

Or, why is the small signal response linear?

We replaced

$$i_D = f(v_D)$$

nonlinear

$$v_D = V_D + \Delta v_D$$

large DC

increment about V_D

using Taylor's Expansion to expand $f(v_D)$ near $v_D = V_D$:

$$i_D = f(V_D) + \left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D} \cdot \Delta v_D + \frac{1}{2!} \left. \frac{d^2 f(v_D)}{dv_D^2} \right|_{v_D=V_D} \cdot \Delta v_D^2 + \dots$$

neglect higher order terms
because Δv_D is small

$$i_D \approx \underbrace{f(V_D)}_{\text{constant w.r.t. } \Delta v_D} + \underbrace{\left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D}}_{\text{constant w.r.t. } \Delta v_D} \cdot \Delta v_D$$

constant w.r.t. Δv_D constant w.r.t. Δv_D
slope at V_D, I_D

We can write

$$\textcircled{\times} : I_D + \Delta i_D \approx f(V_D) + \left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D} \cdot \Delta v_D$$

equating DC and time-varying parts,

$$I_D = f(V_D) \quad \longrightarrow \quad \text{operating point}$$

$$\Delta i_D = \left. \frac{df(v_D)}{dv_D} \right|_{v_D=V_D} \cdot \Delta v_D$$

constant w.r.t. Δv_D

so, $\Delta i_D \propto \Delta v_D$

By notation,

$$\Delta i_D = i_d$$

$$\Delta v_D = v_d$$

In our example,

$$i_D = a e^{bv_D}$$

From \otimes : $I_D + i_d \approx a e^{bV_D} + a e^{bV_D} \cdot b \cdot v_d$

Equate DC and incremental terms,

$$\boxed{I_D = a e^{bV_D}} \longrightarrow \begin{array}{l} \text{operating point} \\ \left[\begin{array}{l} \text{aka bias pt.} \\ \text{aka DC offset} \end{array} \right. \end{array}$$


$$i_d = \underbrace{a e^{bV_D}}_{\text{constant}} b \cdot v_d$$

$$i_d = \underbrace{I_D \cdot b}_{\text{constant}} \cdot v_d \longrightarrow \begin{array}{l} \text{small signal} \\ \text{behavior} \\ \longrightarrow \text{linear!} \end{array}$$

Graphical interpretation

$$I_D = a e^{bV_D} \quad \longrightarrow \text{operating point}$$

$$i_d = I_D \cdot b \cdot v_d$$

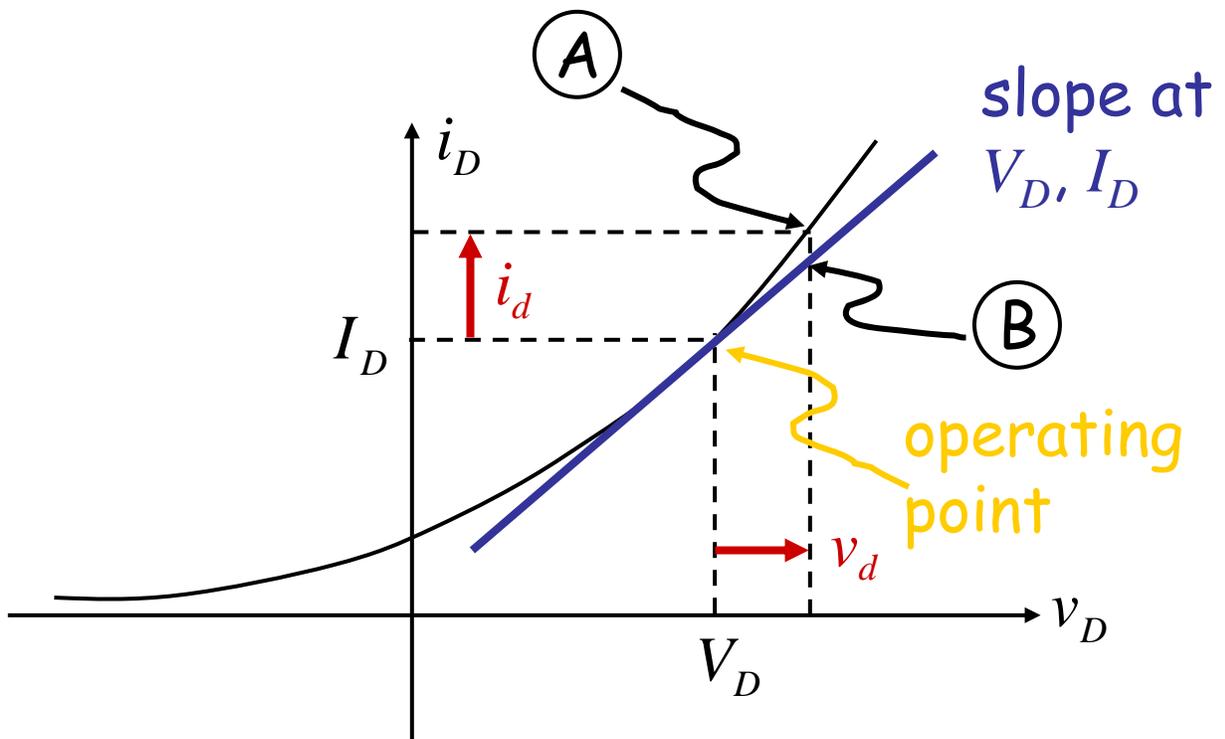


we are
approximating
(A) with (B)

We saw the small signal
}


 graphically
 mathematically
 now, circuit

Large signal circuit:

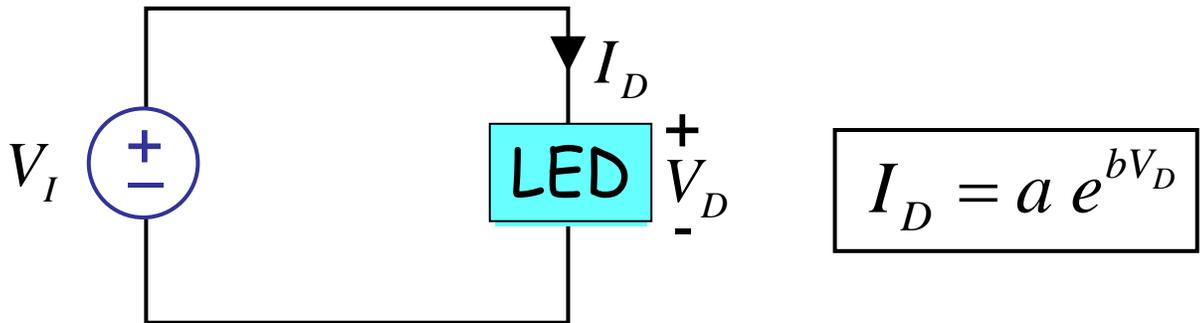


Small signal response: $i_d = I_D b v_d$

behaves like:

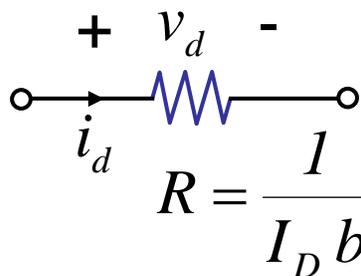

small signal circuit:

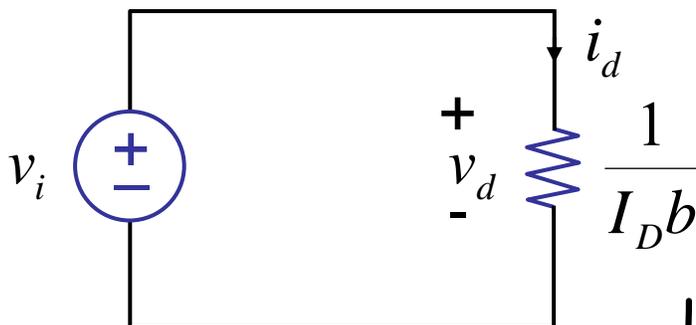

Linear!