

6.004 Computation Structures  
Spring 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.

## The Digital Abstraction

1. Making bits concrete
2. What makes a good bit
3. Getting bits under contract

Handouts: Lecture Slides

6.004 – Spring 2009

2/5/09

modified 1/30/09 11:46

LO2 - Digital Abstraction 1

## Substrates for computation

We can build upon almost any physical phenomenon...

Wait!  
Those last ones  
might have potential...

lanterns  
dominos  
engraved stone tablets  
Billiard balls  
E. Coli  
polarization of a photon

## Concrete encoding of information

To this point we've discussed encoding information using bits. But where do bits come from?

If we're going to design a machine that manipulates information, how should that information be physically encoded?

He said to his friend, "If the British march  
By land or sea from the town to-night,  
Hang a lantern aloft in the belfry arch  
Of the North Church tower as a signal light,--  
**One if by land, and two if by sea;**  
And I on the opposite shore will be,  
Ready to ride and spread the alarm  
Through every Middlesex village and farm,  
For the country folk to be up and to arm."

### What makes a good bit?

- cheap (we want a lot of them)
- stable (reliable, repeatable)
- ease of manipulation  
(access, transform, combine, transmit, store)

6.004 – Spring 2009

2/5/09

LO2 - Digital Abstraction 2

## But, since we're EE's...

Stick with things we know about:

voltages	phase
currents	frequency

This semester we'll use **voltages** to encode information. But the best choice depends on the intended application...

### Voltage pros:

- easy generation, detection
- lots of engineering knowledge
- potentially low power in steady state

**zero**

### Voltage cons:

- easily affected by environment
- DC connectivity required?
- R & C effects slow things down

6.004 – Spring 2009

2/5/09

LO2 - Digital Abstraction 4

6.004 – Spring 2009

2/5/09

LO2 - Digital Abstraction 3

## Representing information with voltage

Representation of each point ( $x, y$ ) on a B&W Picture:

0 volts: BLACK  
1 volt: WHITE  
0.37 volts: 37% Gray  
etc.



Representation of a picture:  
Scan points in some prescribed  
raster order... generate voltage  
waveform

How much information  
at each point?

6.004 - Spring 2009

2/5/09

LO2 - Digital Abstraction 5

## Information Processing = Computation

First let's introduce some processing blocks:



6.004 - Spring 2009

2/5/09

LO2 - Digital Abstraction 6

## Why have processing blocks?

The goal of modular design:

Abstraction

What does that mean anyway:

- Rules simple enough for a 6-3 to follow...
- Understanding BEHAVIOR without knowing IMPLEMENTATION
- Predictable **composition** of functions
- Tinker-toy assembly
- Guaranteed behavior, under REAL WORLD circumstances

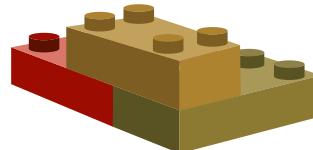


Figure by MIT OpenCourseWare.

6.004 - Spring 2009


2/5/09

LO2 - Digital Abstraction 7

## Let's build a system!



input

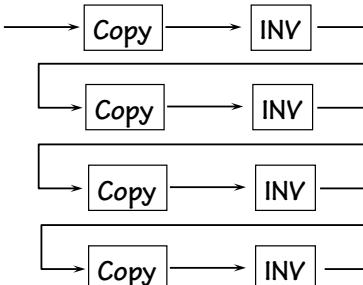

(Reality)



output

6.004 - Spring 2009

2/5/09

LO2 - Digital Abstraction 8

## Why did our system fail?

Why doesn't reality match theory?

1. COPY Operator doesn't work right
2. INVERSION Operator doesn't work right
3. Theory is imperfect
4. Reality is imperfect
5. Our system architecture stinks

ANSWER: all of the above!

Noise and inaccuracy are inevitable; we can't reliably reproduce infinite information-- we must **design our system to tolerate some amount of error** if it is to process information reliably.

## The Key to System Design

A system is a structure that is guaranteed to exhibit a specified behavior, assuming all of its components obey their specified behaviors.

How is this achieved?

### Contracts!


Every system component will have clear obligations and responsibilities. If these are maintained we have every right to expect the system to behave as planned. If contracts are violated all bets are off.

## The Digital Panacea ...

Why digital?

... because it keeps the contracts simple!


The price we pay for this robustness:

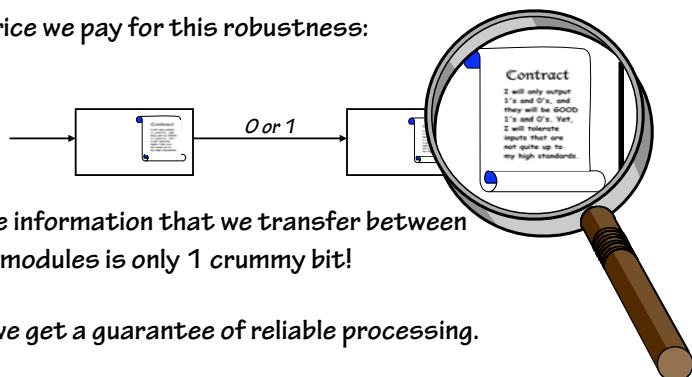

All the information that we transfer between modules is only 1 crummy bit!

But, we get a guarantee of reliable processing.


## The Digital Abstraction

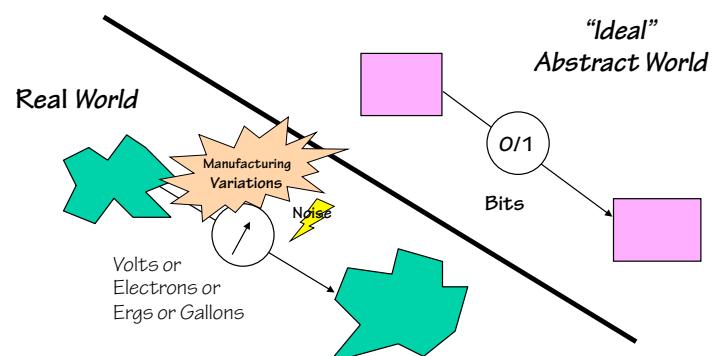

Keep in mind that the world is not digital, we would simply like to engineer it to behave that way. Furthermore, we must use **real physical phenomena to implement digital designs!**
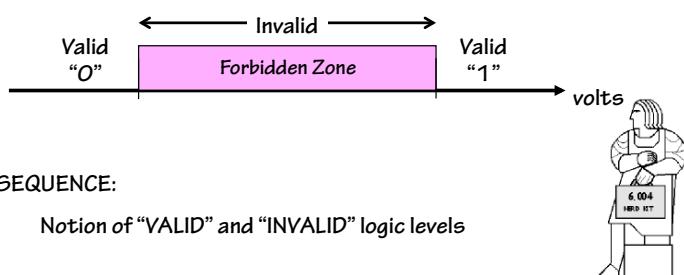
## Using Voltages “Digitally”

- Key idea: don't allow “0” to be mistaken for a “1” or vice versa
- Use the same “uniform representation convention” for every component and wire in our digital system
- To implement devices with high reliability, we outlaw “close calls” via a representation convention which forbids a range of voltages between “0” and “1”.



6.004 – Spring 2009

2/5/09

LO2 - Digital Abstraction 13


## A Digital Processing Element

A combinational device is a circuit element that has

- Static discipline
- one or more digital inputs
  - one or more digital outputs
  - a functional specification that details the value of each output for every possible combination of valid input values
  - a timing specification consisting (at minimum) of an upper bound  $t_{pd}$  on the required time for the device to compute the specified output values from an arbitrary set of stable, valid input values



6.004 – Spring 2009

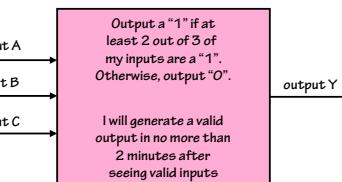

2/5/09

LO2 - Digital Abstraction 14

## A Combinational Digital System

A set of interconnected elements is a **combinational device** if



- each circuit element is combinational
- every input is connected to exactly one output or to some vast supply of constant 0's and 1's
- the circuit contains no directed cycles

Why is this true?

Given an acyclic circuit meeting the above constraints, we can derive functional and timing specs for the input/output behavior from the specs of its components!

We'll see lots of examples soon. But first, we need to build some combinational devices to work with...




6.004 – Spring 2009

2/5/09

LO2 - Digital Abstraction 15

## Wires: theory vs. practice

Does a wire obey the static discipline?

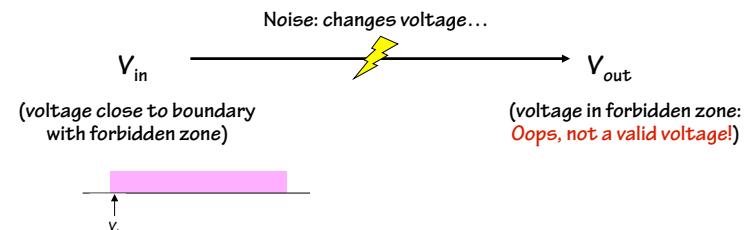

Questions to ask ourselves:


In digital systems, where does noise come from?  
How big an effect are we talking about?

6.004 – Spring 2009

2/5/09

LO2 - Digital Abstraction 16

## Power Supply Noise

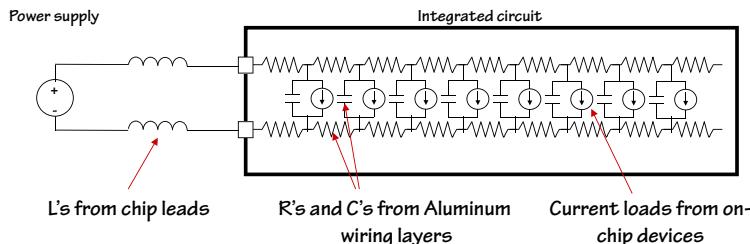

$\Delta V$  from:


- IR drop  
(between gates: 30mV, within module: 50mV, across chip: 350mV)
- L(dI/dt) drop  
(use extra pins and bypass caps to keep within 250mV)
- LC ringing triggered by current "steps"

6.004 - Spring 2009

2/5/09

LO2 - Digital Abstraction 17

## Crosstalk

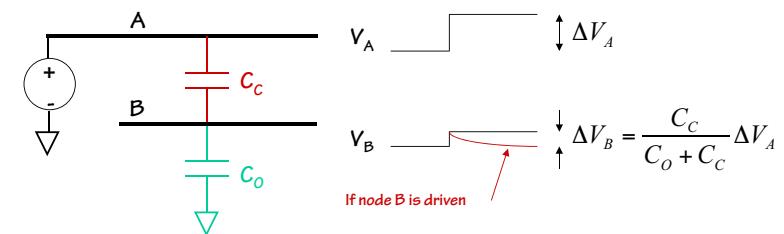

This situation frequently happens on integrated circuits where there are many overlapping wiring layers. In a modern integrated circuit  $\Delta V_A$  might be 2.5V,  $C_o = 20\text{fF}$  and  $C_c = 10\text{fF} \rightarrow \Delta V_B = 0.83\text{V}$ ! Designers often try to avoid these really bad cases by careful routing of signals, but some crosstalk is unavoidable.

6.004 - Spring 2009



2/5/09

LO2 - Digital Abstraction 18

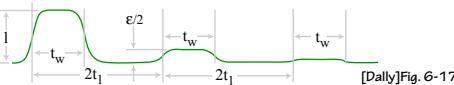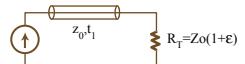
## Sequential Interference

$\Delta V$  from energy storage left over from earlier signaling on the wire:



- transmission line discontinuities  
(reflections off of impedance mismatches and terminations)



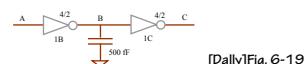- charge storage in RC circuit  
(narrow pulses are lost due to incomplete transitions)



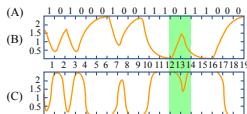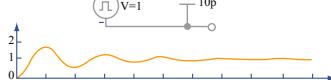- RLC ringing (triggered by voltage "steps")



Fix: slower operation, limiting voltage swings and slew rates

6.004 - Spring 2009

[Dally]Fig. 6-20


LO2 - Digital Abstraction 19
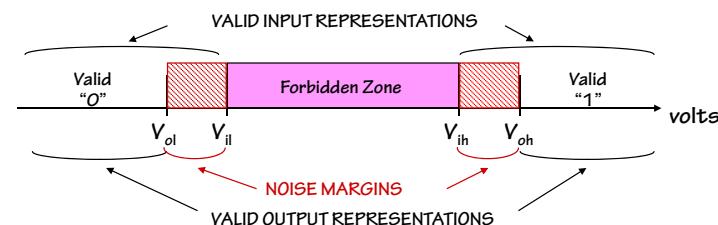
## Needed: Noise Margins!

Does a wire obey the static discipline?



No! A combinational device must restore marginally valid signals. It must accept marginal inputs and provide unquestionable outputs (i.e., to leave room for noise).



6.004 - Spring 2009


2/5/09

LO2 - Digital Abstraction 20

Figures by MIT OpenCourseWare.

## A Buffer

A simple combinational device:

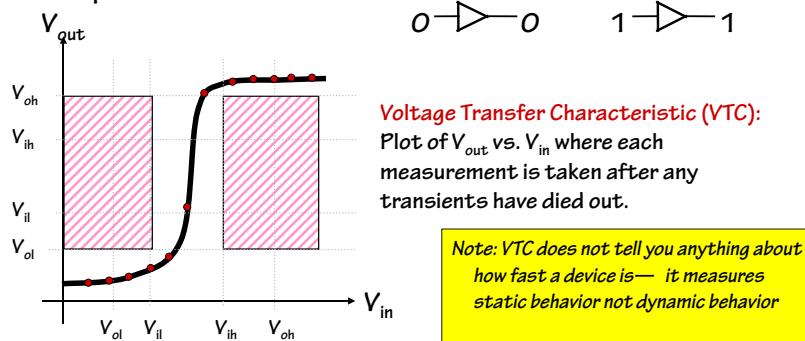

Static Discipline requires that the VTC avoid the shaded regions (aka "forbidden zones"), which correspond to valid inputs but invalid outputs.

Net result: combinational devices must have GAIN > 1 and be NONLINEAR.


6.004 – Spring 2009

2/5/09

LO2 - Digital Abstraction 21
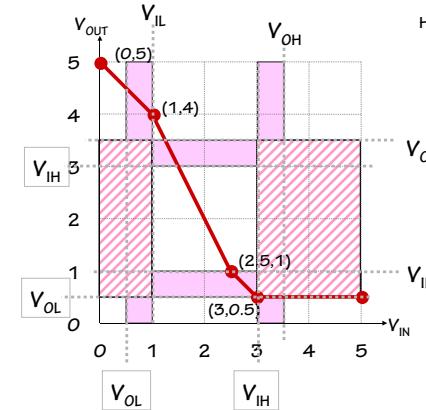
## Can this be a combinational device?

Suppose that you measured the voltage transfer curve of the device shown below.  
Could we build a logic family using it as a single-input combinational device?



Hmmm, it had better be an INVERTER...

The device must be able to actually produce the desired output level. Thus,  $V_{OL}$  can be no lower than 0.5 V.

Try  $V_{OL} = 0.5$  V

$V_{IH}$  must be high enough to produce  $V_{OL}$

Try  $V_{IH} = 3$  V

Now, choose noise margins – find an N and set  
 $V_{OH} = V_{IH} + N$   
 $V_{IL} = V_{OL} + N$   
Such that  
 $V_{IH}$  IN generates  $V_{OL}$  or less out; AND  
 $V_{IL}$  IN generates  $V_{OH}$  or more out.

Try  $N = 0.5$  V

6.004 – Spring 2009

2/5/09

LO2 - Digital Abstraction 22

## Summary

- Use voltages to encode information
- “Digital” encoding
  - valid voltage levels for representing “0” and “1”
  - forbidden zone avoids mistaking “0” for “1” and vice versa
  - gives rise to notion of signal VALIDITY.
- Noise
  - Want to tolerate real-world conditions: NOISE.
  - Key: tougher standards for output than for input
  - devices must have gain and have a non-linear VTC
- Combinational devices
  - Each logic family has Tinkertoy-set simplicity, modularity
  - predictable composition: “parts work → whole thing works”
  - static discipline
    - digital inputs, outputs; restore marginal input voltages
    - complete functional spec
    - valid inputs lead to valid outputs in bounded time

6.004 – Spring 2009

2/5/09

LO2 - Digital Abstraction 23

## Next time: Building Logic w/ Transistors



6.004 – Spring 2009

2/5/09

LO2 - Digital Abstraction 24