
 


MIT OpenCourseWare  
<http://ocw.mit.edu>

6.004 Computation Structures  
Spring 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.

# Synthesis of Combinational Logic

 


Lab 1 is due Thursday 2/19  
 Quiz 1 is a week from Friday (in section)

# Functional Specifications

There are many ways of specifying the function of a combinational device, for example:

Argh... I'm tired of word games

 

Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Concise alternatives:

**truth tables** are a concise description of the combinational system's function.

**Boolean expressions** form an algebra in whose operations are **AND** (multiplication), **OR** (addition), and **inversion** (overbar).

$$Y = \overline{C}BA + C\overline{B}A + C\overline{B}\overline{A} + CBA$$

Any combinational (Boolean) function can be specified as a truth table or an equivalent **sum-of-products** Boolean expression!

# Here's a Design Approach

Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

1) Write out our functional spec as a truth table

2) Write down a Boolean expression with terms covering each '1' in the output:

$$Y = \overline{C}BA + C\overline{B}A + C\overline{B}\overline{A} + CBA$$

3) Wire up the gates, call it a day, and declare success!

This approach will always give us Boolean expressions in a particular form: **SUM-OF-PRODUCTS**

- it's systematic!
- it works!
- it's easy!
- are we done yet???

# Straightforward Synthesis

We can implement


**SUM-OF-PRODUCTS** with just three levels of logic.

**INVERTERS/AND/OR**

Propagation delay --

No more than 3 gate delays

 (assuming gates with an arbitrary number of inputs)



# Basic Gate Repertoire

Are we sure we have all the gates we need?  
Just how many two-input gates are there?

AND		OR		NAND		NOR	
AB	Y	AB	Y	AB	Y	AB	Y
00	0	00	0	00	1	00	1
01	0	01	1	01	1	01	0
10	0	10	1	10	1	10	0
11	1	11	1	11	0	11	0

Hmmm... all of these have 2-inputs (no surprise)  
... each with 4 combinations, giving  $2^2$  output cases  
 $2^2 = 2^4 = 16$   
How many ways are there of assigning 4 outputs?

# There are only so many gates

There are only 16 possible 2-input gates  
... some we know already, others are just silly


How many of these gates can be implemented using a single CMOS gate?

I N P	Z	A A	B	X	N N	O A	N O	N B	N A	O
T	R N	>	>	O O	O O	T <=	T <=	T <=	N N	N
AB	O	D B	A A	B R	R R	R R	'B' B	'A' A	A D	E
00	0	0	0	0	0	0	0	1	1	1
01	0	0	0	0	1	1	1	0	0	1
10	0	0	1	1	0	0	1	1	0	1
11	0	1	0	1	0	1	0	1	0	1

CMOS gates are inverting; we can always respond positively to positive transitions by cascaded gates. But suppose our logic yielded cheap positive functions, while inverters were expensive...
 
# Logic Geek Party Games

You have plenty of ANDs and ORs, but only 2 inverters. Can you invert more than 2 independent inputs?



CHALLENGE: Come up with a combinational circuit using ANDs, ORs, and at most 2 inverters that inverts A, B, and C!



- Such a circuit exists. What does that mean?
- If we can invert 3 signals using 2 inverters, can we use 2 of the pseudo-inverters to invert 3 more signals?
  - Do we need only 2 inverters to make ANY combinational circuit?
- Hint: there's a subtle difference between our 3-inv device and three combinational inverters!

Is our 3-inv device LENIENT?


# Fortunately, we can get by with a few basic gates...

AND, OR, and NOT are sufficient... (cf Boolean Expressions):

B>A		XOR	
AB	Y	AB	Y
00	0	00	0
01	1	01	1
10	0	10	1
11	0	11	0

  


That is just DeMorgan's Theorem!

 

How many different gates do we really need?

## One will do!

NANDs and NORs are universal:

 

Ah!, but what if we want more than 2-inputs

## Stupid Gate Tricks

Suppose we have some 2-input XOR gates:




$$t_{pd} = 1$$

$$t_{cd} = 0$$

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

And we want an N-input XOR:

 


output = 1  
iff number of 1s  
input is ODD  
("ODD PARITY")

$$t_{pd} = O(N) \text{ -- WORST CASE.}$$

Can we compute N-input XOR faster?

 I think that I shall never see  
a circuit lovely as...



N-input TREE has  $O(\log N)$  levels...


Signal propagation takes  $O(\log N)$  gate delays.

Question: Can EVERY N-Input Boolean function be implemented as a tree of 2-input gates?

 
## Are Trees Always Best?

Alternate Plan: Large Fan-in gates

- ◆ N pulldowns with complementary pullups
- ◆ Output HIGH if any input is HIGH = "OR"



 
- ◆ Propagation delay:  $O(N)$  since each additional MOSFET adds  $C$



Don't be misled by the "big O" stuff... the constants in this case can be much smaller... so for small N this plan might be the best.

# Practical SOP Implementation


## NAND-NAND

 

$$\overline{\overline{AB}} = \overline{A+B}$$




"Pushing Bubbles"

 


$$xyz = \overline{\overline{x} + \overline{y} + \overline{z}}$$

## NOR-NOR

 
 
$$\overline{\overline{AB}} = \overline{A+B}$$



$$\overline{x + y} = \overline{\overline{x} \overline{y}}$$

You might think all these extra inverters would make this structure less attractive. However, quite the opposite is true.

# Logic Simplification

Can we implement the same function with fewer gates?

Before trying we'll add a few more tricks in our bag.

## BOOLEAN ALGEBRA:

- OR rules:  $a + 1 = 1, a + 0 = a, a + a = a$
- AND rules:  $a1 = a, a0 = 0, aa = a$
- Commutative:  $a + b = b + a, ab = ba$
- Associative:  $(a + b) + c = a + (b + c), (ab)c = a(bc)$
- Distributive:  $a(b+c) = ab + ac, a + bc = (a+b)(a+c)$
- Complements:  $a + \overline{a} = 1, a\overline{a} = 0$
- Absorption:  $a + ab = a, a + \overline{a}b = a + b$   
 $a(a+b) = a, a(\overline{a}+b) = ab$
- Reduction:  $ab + \overline{a}b = b, (a+b)(\overline{a}+b) = b$
- DeMorgan's Law:  $\overline{a+b} = \overline{a}\overline{b}, \overline{\overline{a}\overline{b}} = a+b$

# Boolean Minimization:

An Algebraic Approach

Lets (again!) simplify

$$Y = \overline{C}BA + C\overline{B}A + CBA + \overline{C}BA$$

Using the identity

$$\alpha A + \alpha \overline{A} = \alpha$$

For any expression  $\alpha$  and variable A:

$$Y = \overline{C}BA + C\overline{B}A + CBA + \overline{C}BA$$

$$Y = \overline{C}BA + CB + \overline{C}BA$$


$$Y = \overline{C}A + CB$$

Can't he come up with a new example???

Hey, I could write A program to do That!

# A Case for Non-Minimal SOP

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

$$Y = \overline{C}A + CB$$


$t_{CD} = 1 \text{ nS}$

$t_{PD} = 2 \text{ nS}$




That's what we call a "glitch" or "hazard"

 NOTE: The steady state behavior of these circuits is identical. They differ in their transient behavior.



$$Y = \overline{C}A + CB + AB$$

 

Now it's LENIENT!

## Truth Tables with "Don't Cares"

One way to reveal the opportunities for a more compact implementation is to rewrite the truth table using "don't cares" (--) to indicate when the value of a particular input is irrelevant in determining the value of the output.


C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

➔

C	B	A	Y
0	--	0	0
0	--	1	1
1	0	--	0
1	1	--	1
--	0	0	0
--	1	1	1

$\rightarrow \bar{C}A$   
 $\rightarrow CB$   
 $\rightarrow BA$

## We've been designing a "mux"

 


2-input Multiplexer


Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 MUXes can be generalized to  $2^k$  data inputs and k select inputs ...




 ... and implemented as a tree of smaller MUXes:



 
## Systematic Implementations of Combinational Logic

Consider implementation of some arbitrary Boolean function,  $F(A,B,C)$  ... using a MULTIPLEXER as the only circuit element:



## General Table Lookup Synthesis

 

Generalizing:

In theory, we can build any 1-output combinational logic block with multiplexers.

For an N-input function we need a  $2^N$  input mux.

BIG Multiplexers?

How about 10-input function? 20-input?


Muxes are UNIVERSAL!

$\frac{1}{0} \frac{0}{1} Y = A \rightarrow Y$

$\frac{0}{0} \frac{1}{1} Y = A \cdot B$


$\frac{0}{1} \frac{1}{1} Y = A \cdot B$

 In future technologies muxes might be the "natural gate".



What does that one do?

## A New Combinational Device

 

DECODER:  
 k SELECT inputs,  
 $N = 2^k$  DATA OUTPUTS.  
 Selected  $D_j$  HIGH;  
 all others LOW.


Have I mentioned that HIGH is a synonym for '1' and LOW means the same as '0'.

NOW, we are well on our way to building a general purpose table-lookup device.

We can build a 2-dimensional ARRAY of decoders and selectors as follows ...


## Read-only memories (ROMs)

### Full Adder

 

A	B	C <sub>i</sub>	S	C <sub>o</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 Each column is large fan-in "OR" as described on slide #12. Note location of pulldowns correspond to a "1" output in the truth table!




For K inputs, decoder produces  $2^K$  signals, only 1 of which is asserted at a time -- think of it as one signal for each possible product term.

One selector for each output

## Read-only memories (ROMs)


### Full Adder

 

A	B	C <sub>i</sub>	S	C <sub>o</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

LONG LINES slow down propagation times...

 The best way to improve this is to build square arrays, using some inputs to drive output selectors (MUXes):



2D Addressing: Standard for ROMs, RAMs, logic arrays...

## Logic According to ROMs

ROMs ignore the structure of combinational functions ...

- Size, layout, and design are independent of function
- Any Truth table can be "programmed" by minor reconfiguration:

- Metal layer (masked ROMs)
- Fuses (Field-programmable PROMs)
- Charge on floating gates (EPROMs)
- ... etc.

ROMs tend to generate "glitchy" outputs. WHY?

Model: LOOK UP value of function in truth table...

Inputs: "ADDRESS" of a T.T. entry

ROM SIZE = # TT entries...

... for an N-input boolean function, size =  $\frac{2^N \times \text{\#outputs}}{\text{\#inputs}}$

## Summary

- **Sum of products**
  - Any function that can be specified by a truth table or, equivalently, in terms of AND/OR/NOT (Boolean expression)
  - “3-level” implementation of any logic function
    - Limitations on number of inputs (fan-in) increases depth
  - SOP implementation methods
    - NAND-NAND, NOR-NOR
- **Muxes used to build table-lookup implementations**
  - Easy to change implemented function -- just change constants
- **ROMs**
  - Decoder logic generates all possible product terms
  - Selector logic determines which p'terms are or'ed together