


MIT OpenCourseWare
<http://ocw.mit.edu>

6.004 Computation Structures
Spring 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.

Sequential logic and memory components

 Problem 1. Consider the following diagram of a simple sequential circuit:



The components labeled CL1 and CL2 are combinational; R1 and R2 are edge-triggered flip flops. Timing parameters for each component are as noted.

- A. ★ Write the timing specifications (t_S , t_H , t_{CD} , t_{PD} , t_{CLK}) for the system as a whole using the timing specifications for the internal components that are given in the figure.

It's a good idea to check if the circuit will work for any clock period. We check this by checking if the total contamination delay from R1 to R2 is long enough to cover the hold time of R2. In other words,

$$t_{H,R2} \leq t_{CD,R1} + t_{CD,CL2}$$

$$2 \leq 1 + 1$$

$$2 \leq 2$$

The inequality is satisfied, so we can determine the timing specifications of the system.

The setup time and hold time of the system is determined by the setup time and hold time required for the signal IN, which is the input to CL1. Thus,

$$t_S = t_{PD,CL1} + t_{S,R1} = 6, \text{ and}$$

$$t_H = t_{H,R1} - t_{CD,CL1} = 1.$$

The contamination and propagation delay of the system is determined by the contamination and

propagation delay of the signal OUT, which is the output of register R2. Thus,

$$t_{CD} = t_{CD,R2} = 2, \text{ and}$$

$$t_{PD} = t_{PD,R2} = 8.$$

The clock period for the system is determined by adding all the propagation delays from R1 to R2, and the setup time for R2.

$$t_{CLK} \geq t_{PD,R1} + t_{PD,CL2} + t_{S,R2}$$


$$t_{CLK} \geq 2 + 5 + 4$$

$$t_{CLK} \geq 11$$

- B. ★ Suppose you had available a faster version of CL2 having a propagation delay of 3 and a contamination delay of zero. Could you substitute the faster CL2 for the one shown in the diagram? Explain.

You could not substitute the faster CL2 because our hold time constraint for R2 would not be met. The sum of the contamination delays between R1 and R2 must be greater than the hold time of R2. Using the faster CL2 would reduce the contamination delay sum to 1 which is not greater than the hold time, 2, of R2.

 - C. We've been treating wires as idealized components that introduce no delay of their own. In the real world, wires have resistance, capacitance and inductance that will cause different frequencies to propagate along the wire at different rates. This means that wires will delay the arrival of sharp rising and falling transitions (which you'll remember from Fourier analysis have signal components at many different frequencies). This effect is particularly bothersome in connection with clock signals since the clock may arrive at separate parts of the circuit at slightly different times. This difference in arrival times of the clock is called **clock skew**, which we'll model in our simple circuit above as explicit delays along each clock path:



- D. Rewrite the timing specifications for the system as a whole taking into account d_1 and d_2 . Don't

make any assumption about the relative sizes of the two delays.

The delay d_1 causes all timing specifications associated with register R1 to be shifted later in time by d_1 . Likewise the delay d_2 causes all timing specifications associated with register R2 to be shifted later in time by d_2 . Note that we still use the original clock signal as our reference for the system, so the setup times for the registers R1 and R2 become shorter by d_1 and d_2 , respectively, and the hold times for R1 and R2 become longer by d_1 and d_2 .

The timing specifications of the system, taking d_1 and d_2 into account, are:

$$\begin{aligned}t_S &= t_{PD,CL1} + t_{S,R1} - d_1 = 6 - d_1 \\t_H &= t_{H,R1} - t_{CD,CL1} + d_1 = 1 + d_1 \\t_{CD} &= t_{CD,R2} + d_2 = 2 + d_2 \\t_{PD} &= t_{PD,R2} + d_2 = 8 + d_2\end{aligned}$$

Finally,

$$\begin{aligned}t_{CLK} &\geq t_{PD,R1} + t_{PD,CL2} + t_{S,R2} \\t_{CLK} &\geq 2 + d_1 + 5 + 4 - d_2 \\t_{CLK} &\geq 11 + d_1 - d_2\end{aligned}$$

- E. The relative clock skew ($d_2 - d_1$) between two registers connected in a "pipeline" - where the output of the first register is connected, usually through logic, to the input of the second register - can also affect the design of a circuit. Explain how relative clock skew affects the maximum clock frequency of the circuit shown above. Remember that the relative skew might be positive or negative.

As shown in part (C), $t_{CLK} \geq 11 - (d_2 - d_1)$, rewritten to show the relative clock skew term.

One can see that as the relative clock skew becomes positive, the maximum clock frequency increases. Conversely, as the relative clock skew becomes negative, the maximum clock frequency decreases.

- F. [Why clock skew keeps integrated circuit designers awake at night.] If $d_2 > d_1$, the circuit shown above will not operate correctly. Explain why. Will changing the frequency of CLK solve the problem? Why or why not?

Let's revisit the constraint that the contamination delay from R1 to R2 must cover the hold time of R2:

$$\begin{aligned}t_{H,R2} &\leq t_{CD,R1} + t_{CD,logic} \\2 + d_2 &\leq 1 + d_1 + 1\end{aligned}$$


$$d2 \leq d1$$

Thus, if $d2 > d1$, then the hold time of R2 is no longer being satisfied. Lengthening the clock period doesn't change the fact that the hold time constraint isn't met. The clock period doesn't even enter our equations above.

- G. Suggest a way for the designer to change his circuit to guarantee correct operation given an upper bound, $t_{skew} > \text{abs}(d2 - d1)$, on the maximum relative clock skew. Assume that the timing parameters of the registers cannot be adjusted.

Adding additional contamination delay, such as a buffer between R1 and R2, will work. This leads to a circuit which has a larger clock period overall.

 Problem 2. The following circuit diagram implements a sequential circuit with two state bits, S0 and S1:



inverter: $t_{CD}=1\text{ ns}$, $t_{PD}=2\text{ ns}$

nor2: $t_{CD}=1.5\text{ ns}$, $t_{PD}=2\text{ ns}$

D register: $t_{CD}=0\text{ ns}$, $t_{PD}=2\text{ ns}$, $t_H=1\text{ ns}$, $t_S=3\text{ ns}$

- A. ★ What is the smallest clock period for which the circuit still operates correctly?

There are two constraints to check:

$$t_{PD,REG} + t_{PD,INV} + t_{PD,INV} + t_{S,REG} \leq t_{CLK}$$

$$t_{PD,REG} + t_{PD,NOR2} + t_{S,REG} \leq t_{CLK}$$

The first constraint requires $t_{CLK} \geq 9\text{ ns}$.

- B. ★ A sharp-eyed student suggests optimizing the circuit by removing the pair of inverters and connecting the Q output of the left register directly to the D input of the right register. If the clock period could be adjusted appropriately, would the optimized circuit operate correctly? If yes, explain the adjustment to the clock period that would be needed.

No, the circuit won't operate correctly since $t_{CD,REG} < t_{HOLD,REG}$, i.e., the output of the left register doesn't meet the required hold time when connected directly to the input of the right register.

C. ★ When the RESET signal is set to "1" for several cycles, what values are S0 and S1 set to?

$S0 = 0, S1 = 0.$


D. ★ Assuming the RESET signal has been set to "0" and will stay that way, what is the state following $S0=1$ and $S1=1$?

$S0 = 1, S1 = 0.$

E. ★ Now suppose there is *skew* in the CLK signal such that the rising edge of CLK always arrives at the left register exactly 1ns before it arrives at the right register. What is the smallest clock period for which the circuit still operates correctly?

Fortunately the skew doesn't introduce any hold time problems with the input to the right register. t_{CLK} can now be as small as 8ns (both paths between registers fit exactly).

 Problem 3. A possible implementation of a sequential circuit with one input and one output is shown below.




- A. What is the smallest value for the ROM's contamination delay that ensures the necessary timing specifications are met?

$$t_{CD,REG} + t_{CD,ROM} \geq t_{H,REG}, \text{ so } t_{CD,ROM} \geq 0.75 \text{ ns.}$$

 - B. Assume that the ROM's $t_{CD} = 3 \text{ ns}$. What is the smallest clock period that ensures that the necessary timing specifications are met.

$$t_{PD,REG} + t_{PD,ROM} + t_{S,REG} = 2 + 5 + 1 = 8 \text{ ns.}$$

The following schematic has two flip-flops and two blocks of combinational logic with the indicated timing specifications. Assume that the flip-flops are identical and that the clock has zero rise and fall time.




- C. Assuming that the clock period is 25ns , what is the maximum setup time for the flip-flops for which this circuit will operate correctly?

$$t_S \leq t_{\text{CLK}} - t_{PD,\text{REG}} - t_{PD,\text{LOGIC}} = 25 - 6 - \max(11, 9) = 8\text{ns}.$$

- D. Assuming that the clock period is 25ns , what is the maximum hold time for the flip-flops for which this circuit will operate correctly?

$$t_H \leq t_{CD,\text{REG}} + t_{CD,\text{LOGIC}} = 2 + \min(4, 5) = 6\text{ns}.$$

 Problem 4. In lecture, you saw a static latch constructed from a 2-input lenient MUX as shown in the diagram below.



Recall that the MUX selects the Q output when $G=0$, and the D input when $G=1$. The plan is that when $G=1$, the Q output will follow D after a short delay; when $G=0$, the current Q output will be "latched" via the feedback path. In this problem we explore assumptions necessary to construct an informal proof that the latch behaves as proposed. Assume, in each of the following, that the MUX is a well-behaved lenient combinational device with a propagation delay of t_{pd} .

Recall that the lenience of the MUX allows us to assume that if any two of its inputs sufficient to determine its output are stable and valid for at least t_{pd} , then the MUX output will be stable and valid.

- A. Specify constraints on the two data inputs of the MUX sufficient to guarantee that its output will be stable and valid independently of the value on the select input.

When both data inputs are equal, valid and stable for t_{pd} , the output is valid and stable independent of the select signal.

- B. Specify constraints on a single data input and the select input of the MUX sufficient to guarantee stable and valid output independently of the value on the remaining data input.

When G is 0 and both G and Q are stable and valid for t_{pd} or when G is 1 and both G and D are stable and valid for t_{pd} , the MUX will have a valid and stable output independent of the other data input.

- C. Now we explore the scenario where $G=1$ and D has been stable and valid for t_s seconds prior to a 1-to-0 transition on G, and remains stable and valid until t_h seconds after the transition on G. Our goal is to establish that, for sufficiently large values of t_s and t_h , the latch behaves as advertised.

Consider the initial interval in the above scenario where $G=1$. At what point is $Q=D$ guaranteed? Explain why in a sentence or two.

After G and D have been stable and valid for t_{pd} , the output Q will equal the data input D.

- D. Explain why, for sufficiently large values of t_s the output Q remains stable despite invalid voltages on G. What is the setup time required to guarantee output validity during the transition on G?

Part C tells us that Q will equal D t_{pd} after D becomes valid. According to the leniency requirement, the output will be guaranteed valid and stable t_{pd} after the inputs necessary to determine the output become valid and stable. In this case, both Q and D must be valid and stable t_{pd} in order to ensure Q remains stable and valid independent of transitions on G. Thus t_s must be greater than $2 \cdot t_{pd}$.

- E. Now assume that D changes t_h seconds after the transition on G. Explain why, for a sufficiently

large value of t_H , the Q output will remain stable independently of D.

In order to ensure the Q remains stable and valid independent of D, G must be set to a valid logic "0" for t_{pd} before D transitions. Thus, t_H must be greater than t_{pd} .

- F. Identify which of your previous answers is dependent on the MUX being lenient, giving a single-sentence description of the dependence.

All of the previous answers are dependent on the MUX being lenient. In each case we discuss the necessity for two inputs to be valid and stable for t_{pd} in order to ensure the output is valid and stable. If the MUX were not lenient, all three inputs would have to be valid and stable for t_{pd} in order for the output to be guaranteed valid and stable.

- G. Does the operation of the above latch depend on the contamination delay of the MUX? Explain.

The latch does not depend on contamination delay. It only depends on the leniency of the MUX and that t_S and t_H requirements are met.

- H. Your analysis has established setup and hold time requirements necessary to guarantee proper operation of the latch. Suppose, in the above scenario, the setup or hold time requirement is violated? What can you say about the value on Q?

If the setup and hold times are violated, the value of the output cannot be determined.