

MIT OpenCourseWare
<http://ocw.mit.edu>

6.004 Computation Structures
Spring 2009


For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.

Finite State Machines

Problem 1. The ACME Company has recently received an order from a Mr. Wiley E. Coyote for their all-digital Perfectly Perplexing Padlock. The P3 has two buttons ("0" and "1") that when pressed cause the FSM controlling the lock to advance to a new state. In addition to advancing the FSM, each button press is encoded on the B signal (B=0 for button "0", B=1 for button "1"). The padlock unlocks when the FSM sets the UNLOCK output signal to 1, which it does whenever the last N button presses correspond to the unique N-digit combination.

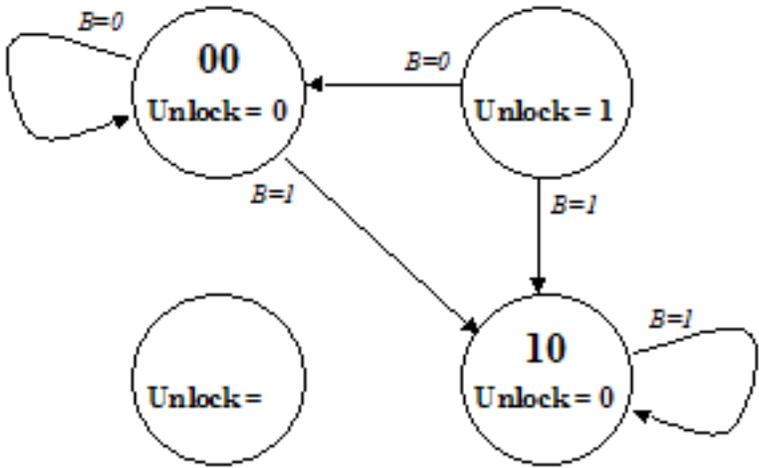A. **★** Unfortunately the design notes for the P3 are incomplete. Using the specification above and clues gleaned from the partially completed diagrams below fill in the information that is missing from the state transition diagram with its accompanying truth table. When done

- each state in the transition diagram should be assigned a 2-bit state name S₁S₀ (note that in this design the state name is not derived from the combination that opens the lock),
- the arcs leaving each state should be mutually exclusive and collectively exhaustive,
- the value for UNLOCK should be specified for each state, and
- the truth table should be completed.



S ₁	S ₀	B	S' ₁	S' ₀	UNLOCK
0	0	0	0	0	
0	0	1	1	0	
0	1	0	1	1	0
0	1	1			0
1	0	0	0	1	
1	0	1			
1	1	0			1
1	1	1			1



B. ★ Construct a truth table for the FSM logic. Inputs include the state bits and the next bit of the number; outputs include the next state bits and the control for the light.

S1	S0	b	S1'	S0'	light
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	0	0
1	0	0	0	1	0
1	0	1	1	0	0

C. Draw a logic schematic for the FSM.

$$\text{light} = \overline{S1} * \overline{S0}$$

$$S1' = \overline{S1} * \overline{S0} * b + \overline{S1} * S0 * \overline{b}$$

$$S0' = \overline{S1} * \overline{S0} * \overline{b} + \overline{S1} * S0 * b$$

Problem 3.

A. An FSM, M, is constructed by connecting the output of a 3-state FSM to the inputs of an 9-state FSM. M is then reimplemented using a state register with the minimum number of bits. What is the maximum number of bits that may be needed to reimplement M?


M has 27 states which require a total of 5 bits in the state register (not 2 + 4 bits!).

B. You connect M N-state FSMs, each have 1 input and 1 output, in series. What's an upper bound on the number of states in the resulting FSM?

Each FSM can in theory be in one of its N states, so an upper bound on the number of states in

the combined machine is N^M .

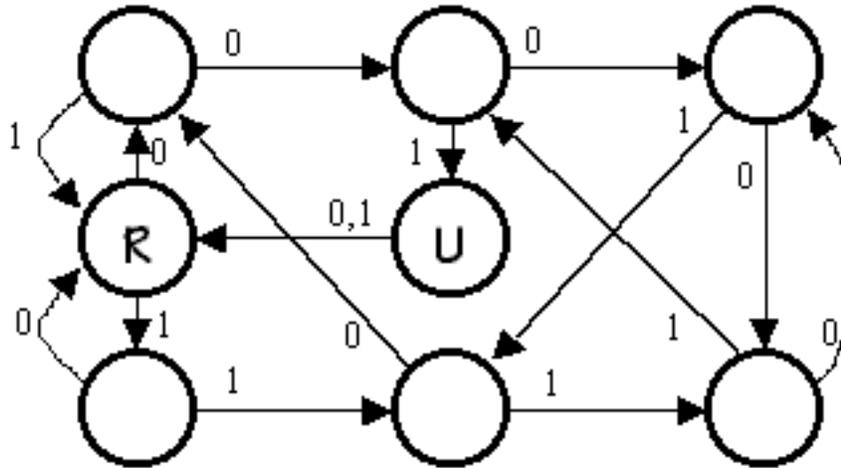Problem 4. Ben Bitdiddle has designed an electronic lock with three buttons: "reset", "0" and "1". He has provided the following state transition diagram showing how the lock responds to a sequence of inputs.



The lock makes a transition from its current state to a new state whenever one of the three buttons is pressed and released. It ignores its inputs if more than one button is pressed. Pressing "reset" returns the lock to the state marked "R" in the diagram (arcs showing the transitions to the reset state have been omitted from the diagram to make it easier to read). Pressing "0" or "1" will cause the lock to follow the appropriately labeled transition from its current state. The lock opens if it reaches the state marked "U".

- A. After pressing the "reset" button what is the length of the shortest sequence of button presses that will open the lock?

3 button presses will open the lock: 0, 0, 1.

- B. After pressing the "reset" button what is the length of the longest sequence of button presses that will cause the lock to open after the last button in the sequence is pressed but not open any earlier in the sequence?

The longest such sequence is unbounded: at least four 0's followed by 11 or 1111 will cause the lock to open for the first time.

- C. After much use, the "reset" button breaks. Is it still possible to open the lock using only the "0" and "1" buttons assuming you know nothing about the lock's state (except that its locked!) when you start?


Yes. A sequence of 1's will open the lock. You have to try the lock after each press of "1" since a

different number of 1's is required depending on the starting state.

- D. Suppose Ben wanted to design a lock that required exactly 10 button presses to open after pressing "reset". Not counting the "reset" and "unlock" states, what is the minimum number of state his FSM would need need?

His FSM would need 9 states in addition to "reset" and "unlock".

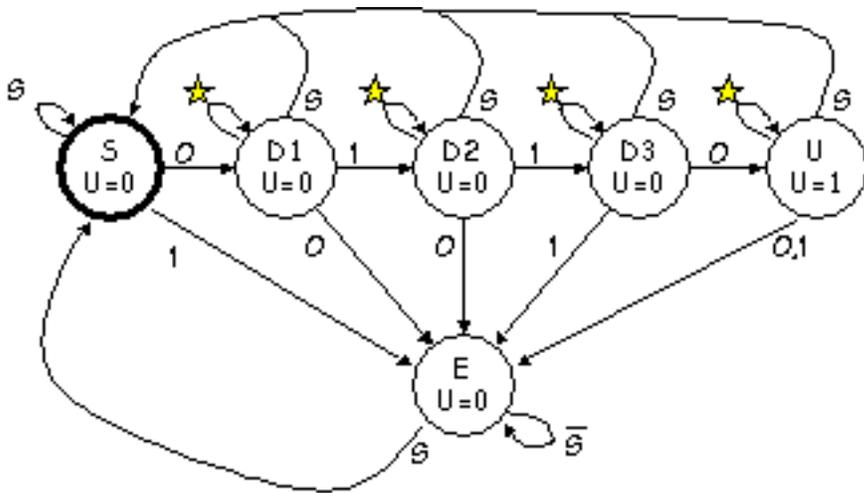Problem 5. Stimulated by Tuesday's lecture, you have decided to cover MIT's steep tuition costs by selling simple digital locks based on the neat six-state FSM used as an example:




★ = no buttons pressed

Recall that this design has three buttons labeled "0", "1", and "Start", and generates an unlock signal $U=1$ when the user presses Start followed by the sequence 0,1,1,0.

Unfortunately your partner, Mark Ting, insists that the 6.004 design is way too complex for normal users to understand. After asking you to help figure out how to make his watch stop beeping ("I never could figure out how to operate this damned thing"), Mark questions the need for a Start button. If 0110 is the combination, he argues, why can't I just walk up and enter 0,1,1,0 and have the lock open? After some reflection, you conclude that he may have a point.

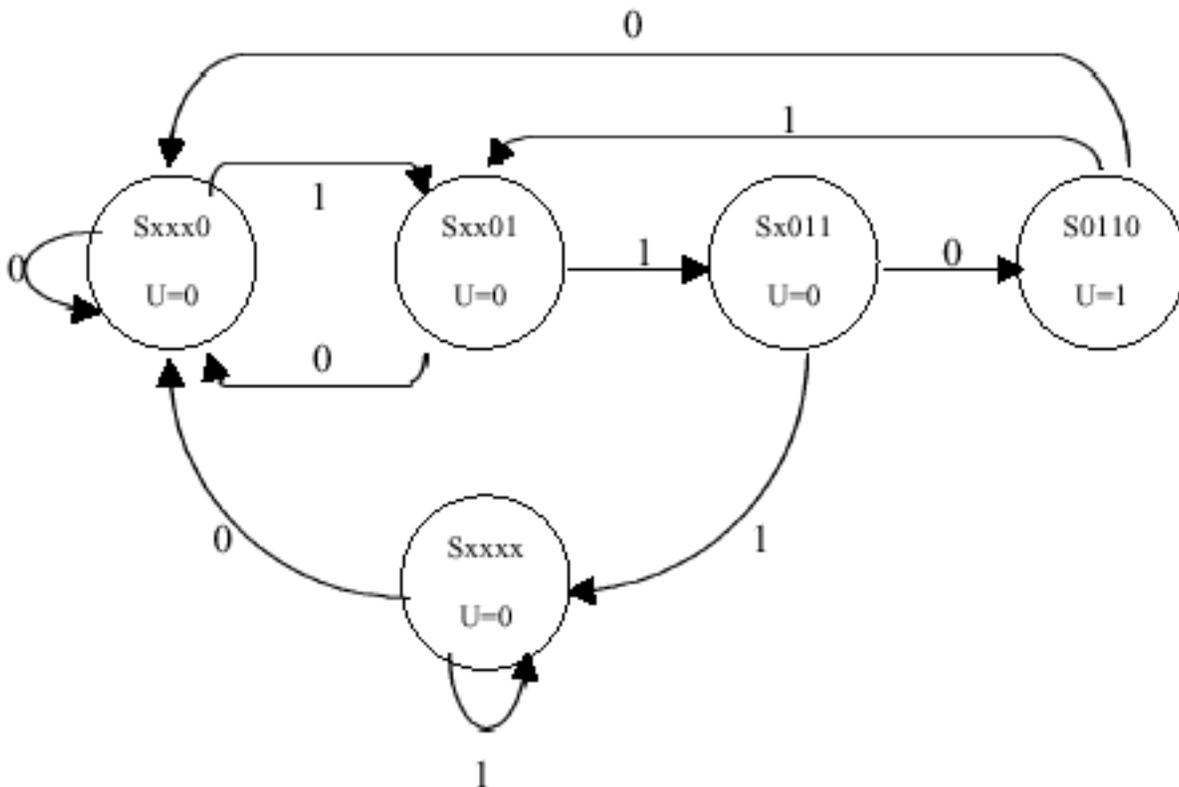- A. Design a FSM whose inputs are simply "0" and "1" buttons, whose output is the U (unlock) signal, and which has the property that $U=1$ if and only if the last four button presses correspond to the sequence 0,1,1,0. Show the state transition diagram corresponding to your design. [HINT: 5 states are sufficient].



The name of each state represents how many digits in the sequence have been input. State Sxxxx indicates that the sequences has not begun, Sxxx0 indicates that the first 0 has been input, etc.

B. Is it possible that an equivalent FSM might be implemented in fewer than 5 states? Explain.

Since 4 transitions are required for 4 button pushes, at least 5 states are needed to implement the FSM. Having only 4 states would make 3 the minimum number of transitions to the unlock state.


C. The flip flops used to hold your FSM state contain random values when power is first applied to your lock. Does this constrain your handling of unused states? Explain.

Since we have 5 states, 3 bits are required to encode the states, resulting in 3 unused states. If during power up it is possible to begin in an unknown state, our FSM must include transitions from unknown states to known states. If the machine begins in an unknown state and a 0 in input, we should transition to state Sxxx0; if a 1 is input, we should transition to Sxxxx.


D. In a table (similar to that shown in lecture), give the contents of a ROM that might be used in an implementation of your design. Completely specify the ROM contents, including those corresponding to unused states.

Current State	Input	Next State	Output
000	0	001	0
000	1	000	0
001	0	001	0
001	1	010	0
010	0	011	0
010	1	001	0
011	0	100	0
011	1	000	0
100	0	001	1
100	1	010	1
101	0	001	0
101	1	000	0
110	0	001	0
110	1	000	0
111	0	001	0
111	1	000	0

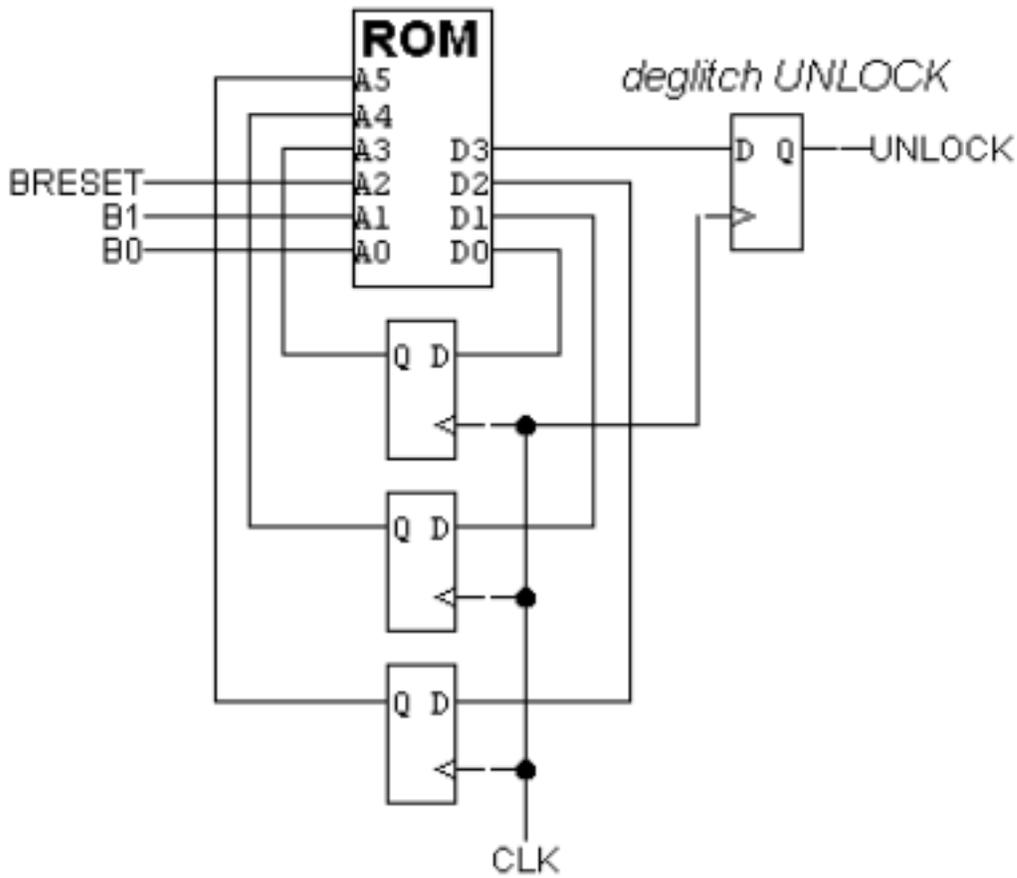Problem 6. Ben Bitdiddle has designed an electronic lock with three buttons: "Breset", "B0" and "B1". He has provided the following circuit diagram showing how the lock is implemented from a ROM and 3 flip-flops.



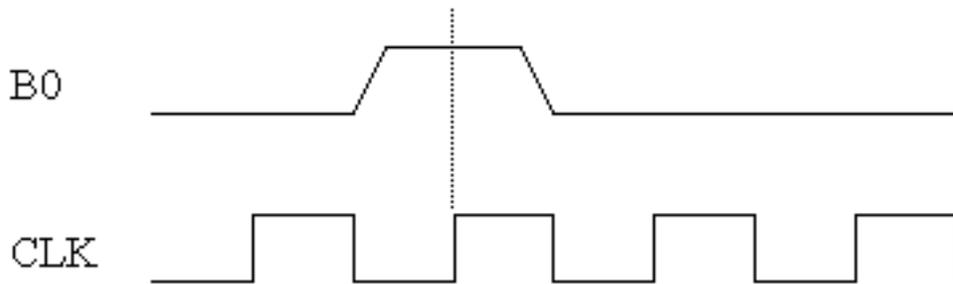The button circuitry converts each button press into a single pulse guaranteed to be stable the required amount of time before and after the rising edge of the clock. For example, pressing "B0" once produces the following waveform:



In answering the questions below, assume that the value of the UNLOCK output is only a function of the current state.

A. What is the total number of bits in the ROM?

256 bits total: 2^6 locations, 4 bits wide.

B. The timing specifications for components are:

ROM: $t_{CD}=3\text{ns}$, $t_{PD}=11\text{ns}$

D flip-flop: $t_{CD}=2\text{ns}$, $t_{PD}=4\text{ns}$, $t_S=3\text{ns}$, $t_H=3\text{ns}$

How long before the rising edge of CLK must the button circuitry guarantee that the button signals are stable?

$t_{PD,ROM} + t_S = 14\text{ns}$.

- C. Assume that all combinations start with pressing the "Breset" button. Ben wants to program the lock with the longest possible combination. Not counting the "Breset" button press, what is the longest combination Ben can achieve?

7 assuming no looping combinations.

- D. If the lock is programmed not to change state if no buttons are pressed, what is the next state field of ROM location 48 (i.e., the location corresponding to $A_5, A_4, A_3, A_2, A_1, A_0 = 110000$)?

The current state appears on $A_5, A_4, A_3 = 110$. So we want the next state field of the ROM (D_2, D_1, D_0) to specify the same state = 110.

- E. The following table shows one possible contents of the first 32 locations of the ROM; assume that all other locations have the value "0010". The location is listed as $A_5, A_4, A_3, A_2, A_1, A_0$, the data is listed as D_3, D_2, D_1, D_0 .

Location	Data
000000	0000
000001	0011
000010	0000
000011	0000
000100	0010
000101	0010
000110	0010
000111	0010
001000	1001
001001	1001
001010	1001
001011	1001
001100	1010
001101	1010
001110	1010
001111	1010

Location	Data
010000	0010
010001	0011
010010	0000
010011	0010
010100	0010
010101	0010
010110	0010
010111	0010
011000	0011
011001	0010
011010	0001
011011	0011
011100	0010
011101	0010
011110	0010
011111	0010

If the lock is programmed with this ROM data, what happens when "B0" and "B1" are pressed at the same time? Assume that "Breset" is not pressed.

State stays the same since all addresses of the form XXX011 transition to state XXX.


F. If the lock is programmed with this ROM data, what is the shortest combination that opens the lock after "Breset" has been pressed?

press B0, then B1.

G. Suppose that the "Breset" button breaks while the lock is locked. Is it still possible to open the lock using a predetermined sequence of presses of the "B0" and "B1" buttons? Assume you know nothing about the lock's state (except that it's locked!) when you start.

Yes, you can open the lock. Noting that the UNLOCK state loops to itself, B1-B0-B1 is one of many sequences that takes us from any state to UNLOCK.

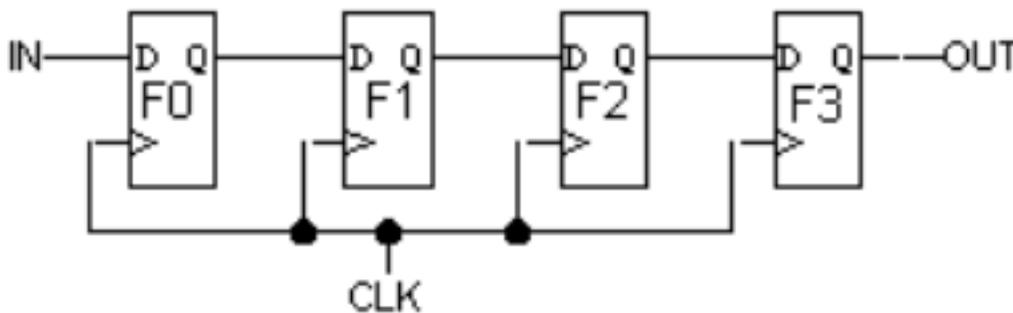Problem 7. Use the following circuit in answering the questions below.



Each of the edge-triggered D flip-flops has a setup time of t_S , a hold time of t_H , a propagation delay of t_{PD} and a contamination delay of t_{CD} . Assume that IN is stable t_S before the rising edge of CLK and t_H after the rising edge of CLK.

A. In order for the circuit shown above to operate correctly what constraints on t_H and t_S are necessary? Express them in terms of t_{CD} , t_{PD} and the clock period.

ensure hold time is met at each register: $t_H \leq t_{CD}$


B. What is the minimum clock period at which this circuit can be clocked and still be guaranteed to work? Express your answer in terms of t_H , t_S , t_{CD} and t_{PD} . Assume that timing constraints that do not depend on the clock period are met.

ensure setup time is met at each register: $t_{PD} + t_S \leq t_{CLK}$

- C. For just this question suppose there is skew in the CLK signal such that the rising edge of CLK arrives at the flip-flop labeled F1 1ns before it arrives at the other three flip-flops. Assume that hold times are not violated. How does this change the minimum clock period at which the circuit above can be clocked and still be guaranteed to work?

The minimum clock period increases by 1ns, i.e., we have to have an extra 1ns between clock edges to ensure that the setup time at F1 is met.

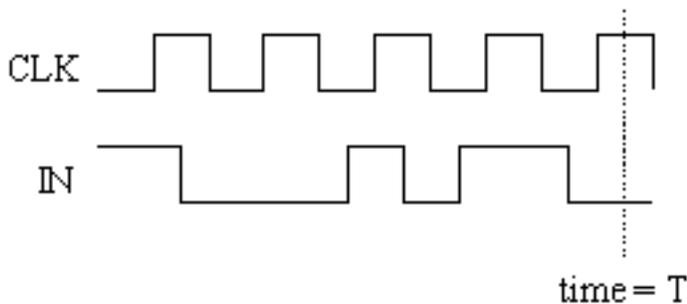- D. Consider following waveform plot for the circuit above. Assume that IN is stable t_S before the rising edge of CLK and t_H after the rising edge of CLK and that time T is more than t_{PD} after the preceding rising edge of CLK.




What is the value of OUT at time T?

At time T, $OUT = 0$ (ie, the value of IN four clock edges earlier).

- E. View the circuit above as an FSM with one input and one output. How many non-equivalent states does it have?

4 bits of state give us $2^4 = 16$ states.

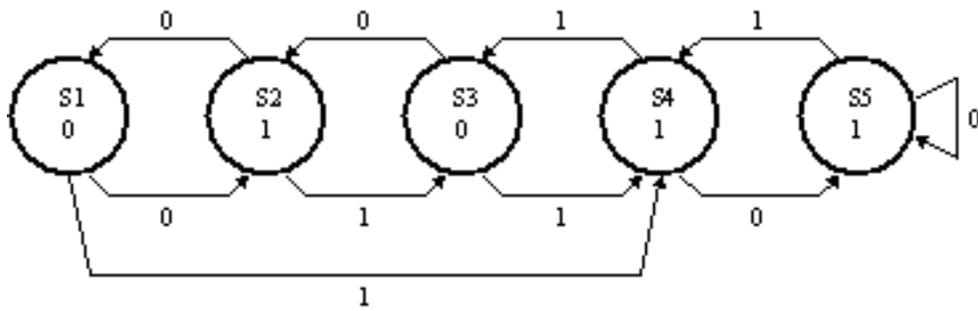Problem 8. Consider the following FSM state transition diagram:



Let's see if there is an equivalent state machine with fewer states by checking to see if any states in the diagram above are equivalent. Two states are equivalent if (1) they have identical outputs and (2) for each possible combination of inputs they transition to equivalent states.

- A. Start by filling in a "compatibility table" like the one shown below. Place an "X" in square (SI,SJ) if SI produces a different output from SJ.

all but first state	S2				
	S3				
	S4	X			
	S5	X			
		S1	S2	S3	S4
		all but last state			

S2	X			
S3		X		
S4	X		X	
S5	X		X	
	S1	S2	S3	S4

- B. For each non-X square (SI,SJ) write in pairs of states that have to be equivalent in order for SI and SJ to be equivalent. For example, for S2 to be equivalent to S5, then S1 (where S2 goes with

a "0" input) has to be equivalent to S5 (where S5 goes with a "0" input).

S2				
S3				
S4	X			
S5	X	S1,S5		
	S1	S2	S3	S4

S2	X			
S3	S2,S2 S4,S4	X		
S4	X	S1,S5 S3,S3	X	
S5	X	S1,S5 S3,S4	X	S5,S5 S3,S4
	S1	S2	S3	S4

C. Finally, look at an entry (SI,SJ). If entry is "SM,SN" and if (SM,SN) has an "X", put an "X" in square (SI,SJ). Repeat until no more squares can be X'ed out. The remaining squares indicate equivalent states. Show the final state (no pun intended) of your compatibility table.

S2	X			
S3	S2,S2 S4,S4	X		
S4	X	S1,S5 S3,S3	X	
S5	X	S1,S5 S3,S4	X	S5,S5 S3,S4
	S1	S2	S3	S4

D. Draw the state transition diagram for the simplified FSM.

Here's the state transition diagram for the simplified FSM (w/o state 3).

