

**Homework #10 - December 2, 2005**

Optional homework. No due date. Do not turn in.

In Howe & Sodini, please note difference between Exercises, labeled Ex.y, and Problems, labeled Px.y.

1. Problem P9.3 of Howe & Sodini.
2. Problem P9.14 of Howe & Sodini. Assume  $L$  is same for all transistors. Also, this question is about the  $W/L$  ratio of transistor  $M_2$  and not  $M_{2B}$ .
3. Problem P9.19 of Howe & Sodini. Ignore question (b).