

Lecture 24 - Frequency Response of Amplifiers (II)

OPEN-CIRCUIT TIME-CONSTANT TECHNIQUE

December 6, 2005

Contents:

1. Open-circuit time-constant technique
2. Application of OCT to common-source amplifier
3. Frequency response of common-gate amplifier

Reading assignment:

Howe and Sodini, Ch. 10, §§10.4.4-10.4.5. 10.6

Key questions

- Is there a fast way to assess the frequency response of an amplifier?
- Do all amplifiers suffer from the Miller effect?

1. Open-Circuit Time-Constant Technique

Simple technique to *estimate* bandwidth of an amplifier.

Method works well if amplifier transfer function has:


- a *dominant pole* that dominates the bandwidth
- no zeroes, or zeroes at frequencies much higher than that of dominant pole

Transfer function of form:

$$\frac{V_{out}}{V_s} = \frac{A_{vo}}{(1 + j\frac{\omega}{\omega_1})(1 + j\frac{\omega}{\omega_2})(1 + j\frac{\omega}{\omega_3})\dots}$$

with
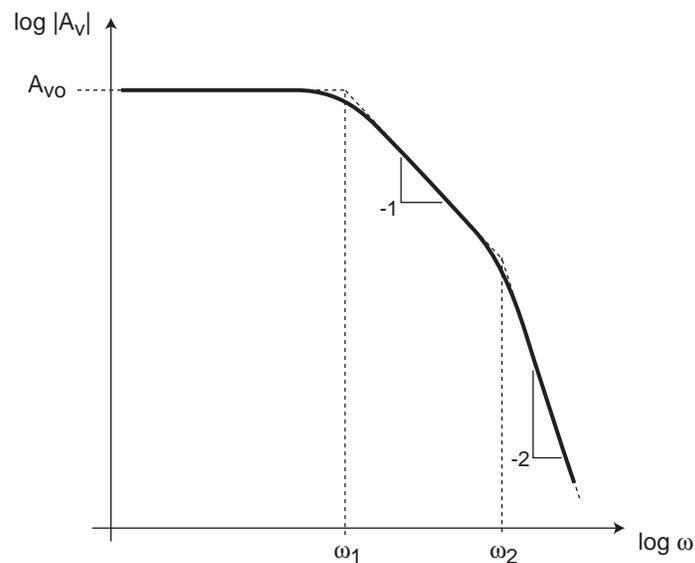
$$\omega_1 \ll \omega_2, \omega_3, \dots$$



$$\frac{V_{out}}{V_s} = \frac{A_{vo}}{(1 + j\frac{\omega}{\omega_1})(1 + j\frac{\omega}{\omega_2})(1 + j\frac{\omega}{\omega_3})\dots}$$

Multiply out the denominator:

$$\frac{V_{out}}{V_s} = \frac{A_{vo}}{1 + j\omega b_1 + (j\omega)^2 b_2 + (j\omega)^3 b_3 \dots}$$

where:


$$b_1 = \frac{1}{\omega_1} + \frac{1}{\omega_2} + \frac{1}{\omega_3} + \dots$$

If there is a dominant pole, the low frequency behavior well described by:

$$\frac{V_{out}}{V_s} \simeq \frac{A_{vo}}{1 + j\omega b_1} = \frac{A_{vo}}{1 + j\frac{\omega}{\omega_H}}$$

Bandwidth then:

$$\omega_H \simeq \frac{1}{b_1}$$

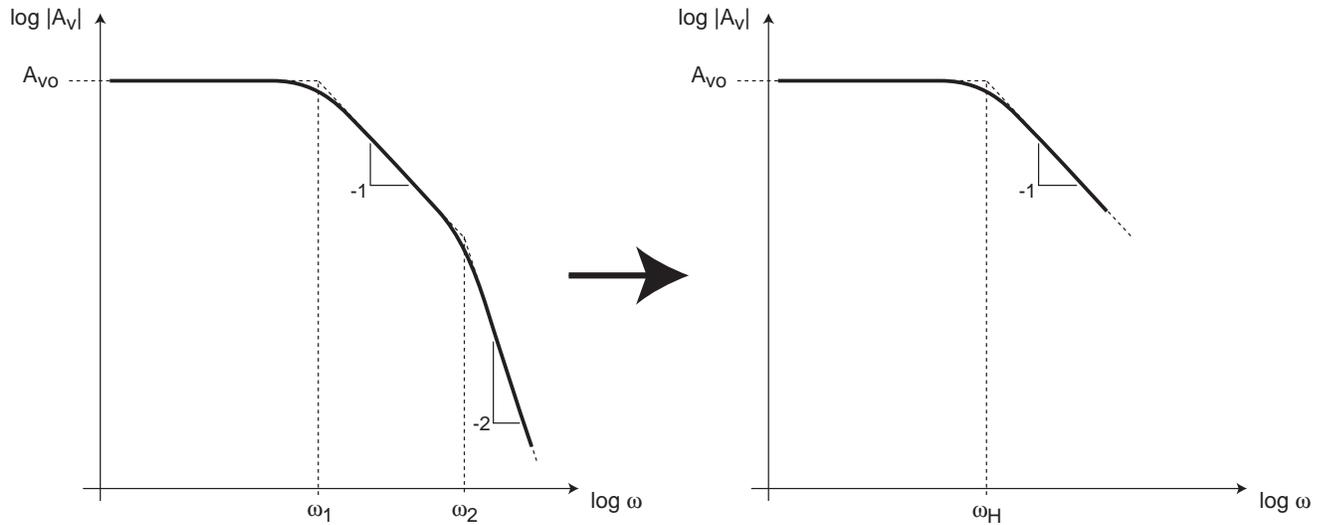

It can be shown (see Gray & Meyer, 3rd ed., p. 502) that coefficient b_1 can be found exactly through:

$$b_1 = \sum_{i=1}^n \tau_i = \sum_{i=1}^n R_{Ti} C_i$$

where:

τ_i is *open-circuit time constant* for capacitor C_i

R_{Ti} is Thevenin resistance across C_i

(with all other capacitors open-circuited)

Bandwidth then:

$$\omega_H \simeq \frac{1}{b_1} = \frac{1}{\sum_{i=1}^n \tau_i} = \frac{1}{\sum_{i=1}^n R_{Ti} C_i}$$

Summary of open-circuit time constant technique:

1. shut-off all independent sources
2. compute Thevenin resistance R_{Ti} seen by each C_i with all other C 's open
3. compute open-circuit time constant for C_i as


$$\tau_i = R_{Ti}C_i$$

4. conservative estimate of bandwidth:


$$\omega_H \simeq \frac{1}{\sum \tau_i}$$

Works also with other transfer functions: $\frac{I_{out}}{V_s}$, $\frac{V_{out}}{I_s}$, $\frac{I_{out}}{I_s}$.

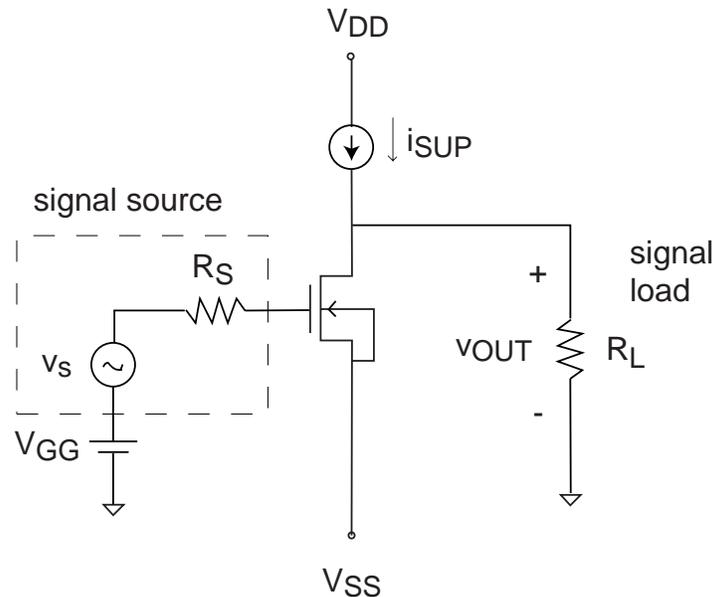2. Application of OCT to evaluate bandwidth of common source amplifier




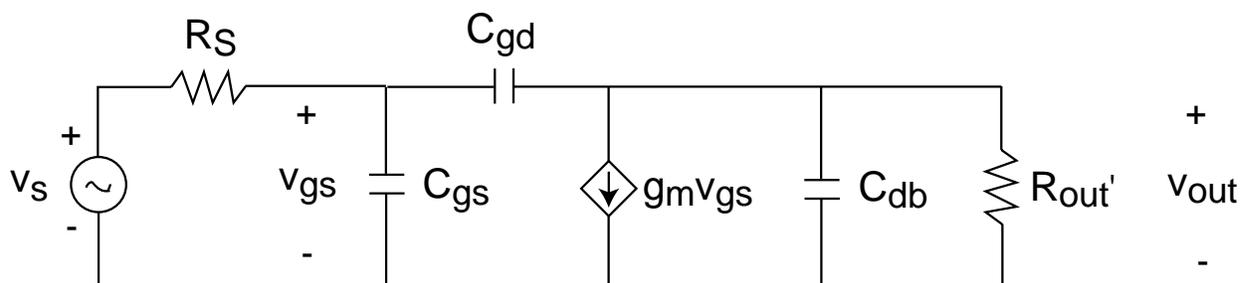Small-signal equivalent circuit model (assuming current source has no parasitic capacitance):




Three capacitors \Rightarrow three time constants

□ First, short v_s :

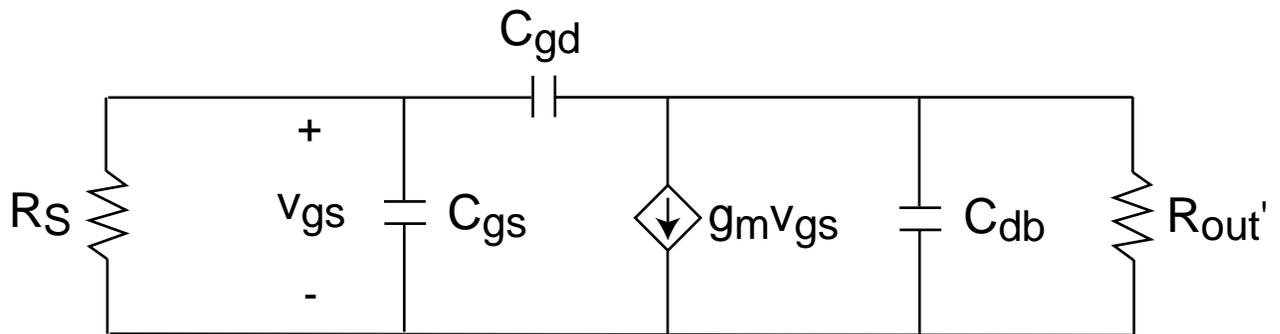

□ Time constant associated with C_{gs}

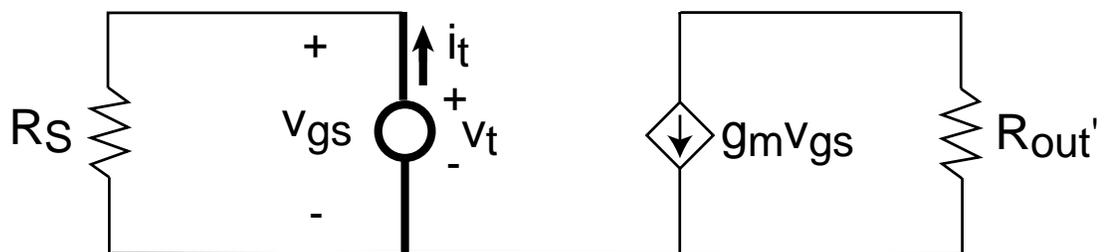


Clearly:

$$R_{T_{gs}} = R_S$$

and time constant associated with C_{gs} is:

$$\tau_{gs} = R_S C_{gs}$$

□ Time constant associated with C_{db} :

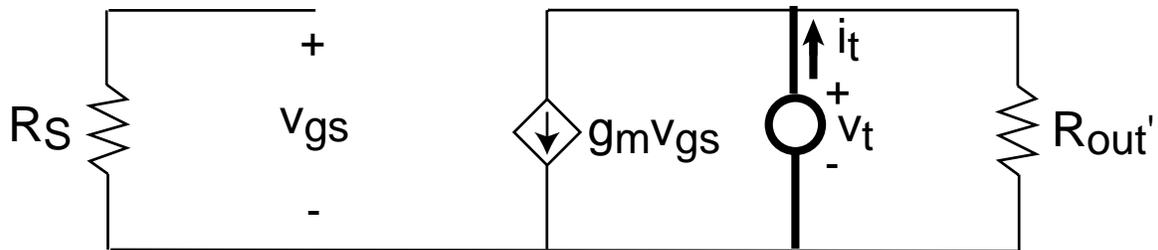

Note:

$$v_{gs} = 0$$


Then:

$$R_{Tdb} = R'_{out}$$

and time constant associated with C_{gs} is:

$$\tau_{gs} = R'_{out} C_{db}$$

Time constant associated with C_{gd} :

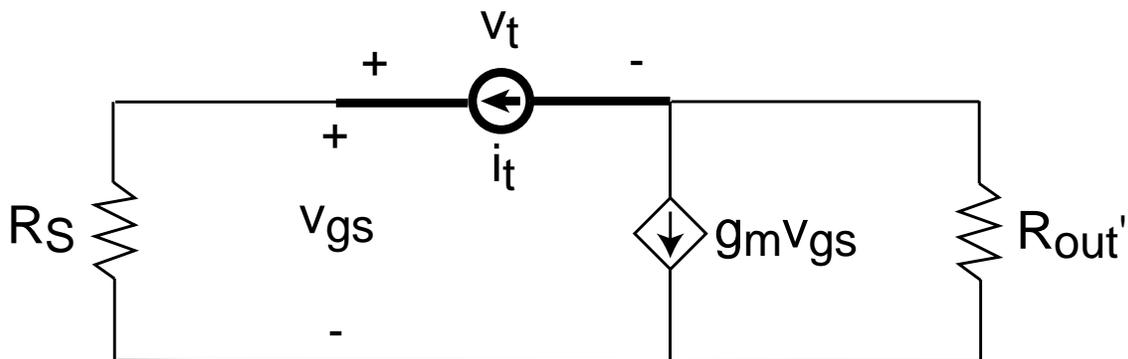

Note:

$$v_{gs} = i_t R_S$$

Also:

$$v_t = v_{gs} + (g_m v_{gs} + i_t) R_{out}'$$

Putting it all together, we have:

$$v_t = i_t [R_S + R_{out}'(1 + g_m R_S)]$$

Then:

$$R_{Tgd} = R_S + R_{out}'(1 + g_m R_S) = R_{out}' + R_S(1 + g_m R_{out}')$$

and time constant associated with C_{gd} :

$$\tau_{gd} = [R_{out}' + R_S(1 + g_m R_{out}')] C_{gd}$$


The bandwidth is then:

$$\omega_H \simeq \frac{1}{\sum \tau_i} = \frac{1}{R_S C_{gs} + [R'_{out} + R_S(1 + g_m R'_{out})]C_{gd} + R'_{out}C_{db}}$$

Identical result as in last lecture.

Open circuit time constant technique evaluates bandwidth neglecting $-\omega^2$ term in the denominator of A_v
 \Rightarrow conservative estimate of ω_H .

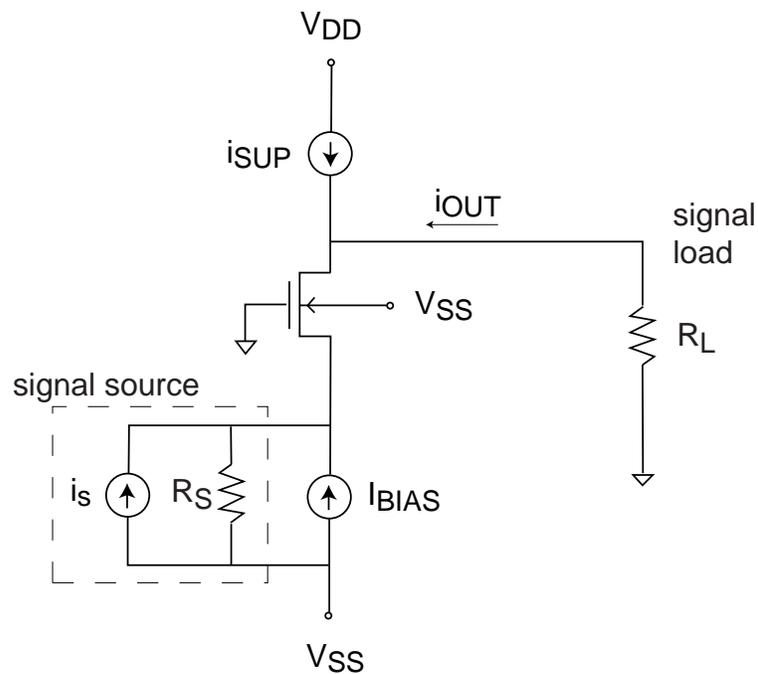
3. Frequency response of common-gate amplifier




Features:

- current gain $\simeq 1$
- low input resistance
- high output resistance
- \Rightarrow good current buffer


Small-signal equivalent circuit model:

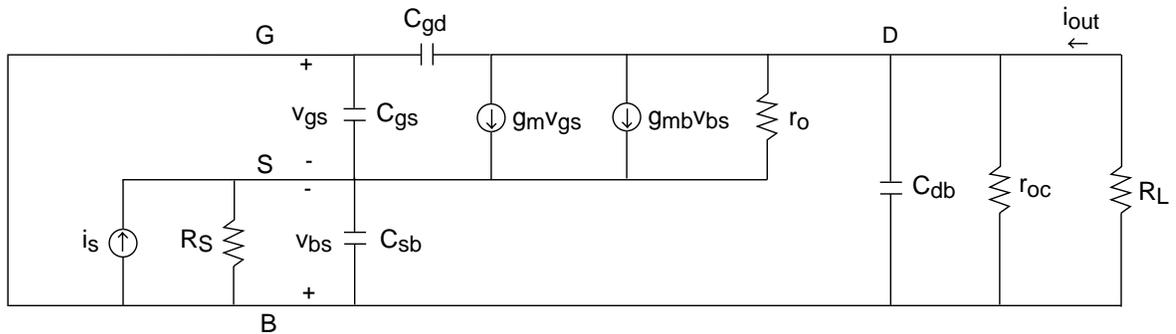


$v_{gs} = v_{bs}$

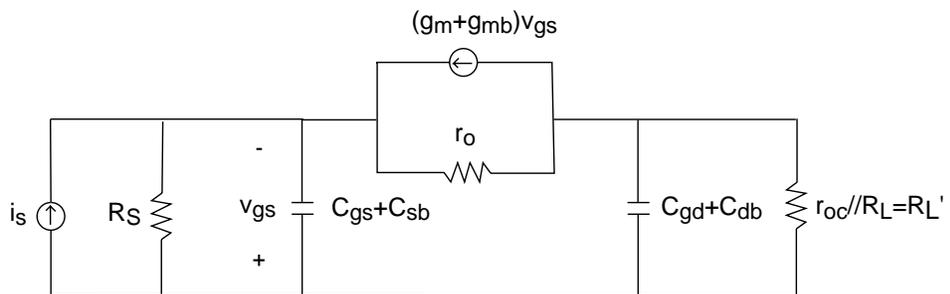

□ Frequency analysis: first, open i_s :

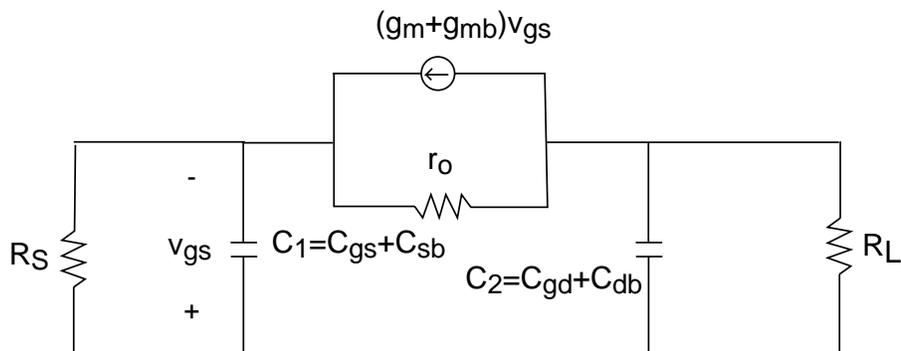

□ Time constant associated with C_1 :

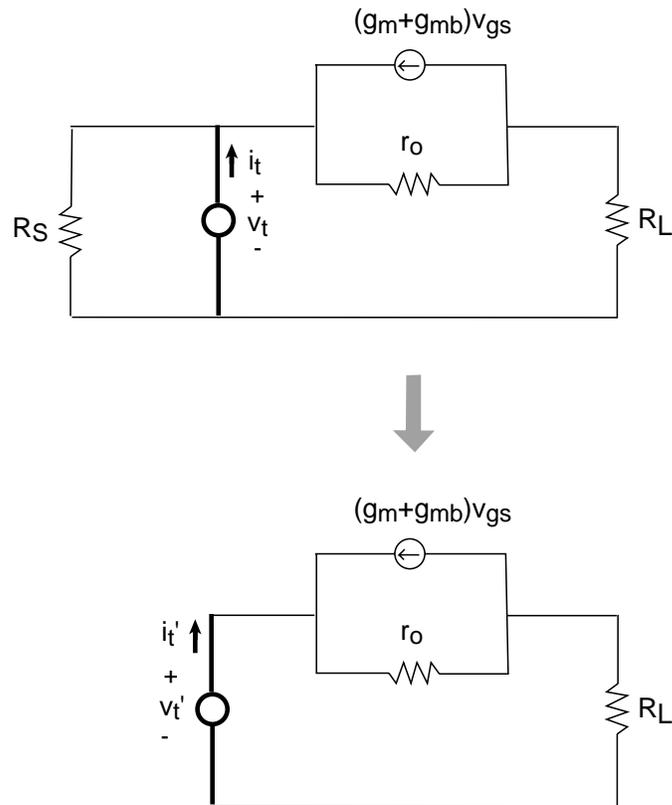

Don't need to solve:


- test probe is in parallel with R_S ,
- test probe looks into input of amplifier \Rightarrow sees R_{in} !

$$R_{T1} = R_S // R_{in}$$

And:

$$\tau_1 = (C_{gs} + C_{sb})(R_S // R_{in})$$

□ Time constant associated with C_2 :

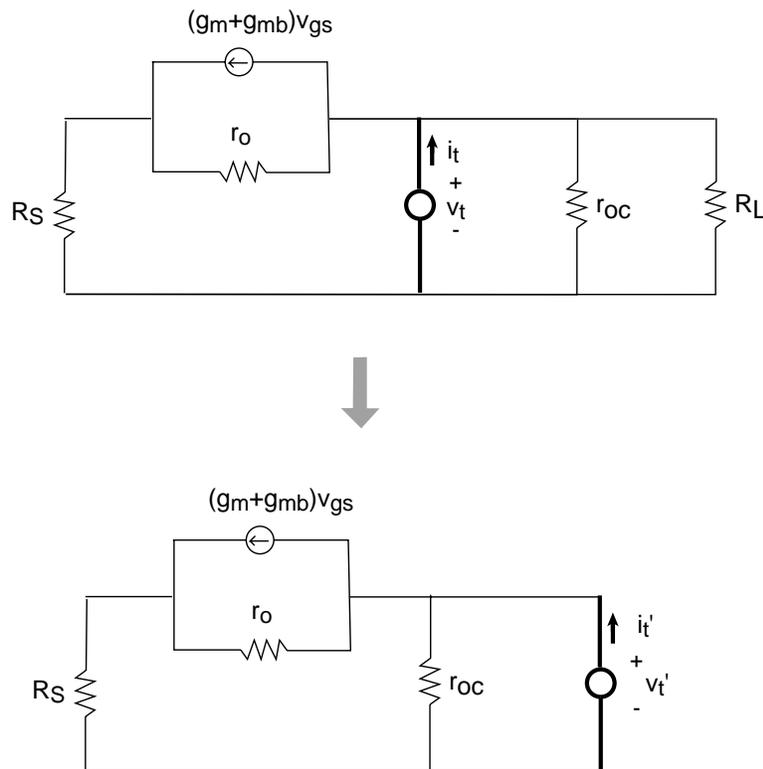

Again, don't need to solve:

- test probe is in parallel with R_L ,
- test probe looks into output of amplifier \Rightarrow sees R_{out} !

$$R_{T2} = R_L // R_{out}$$

And:

$$\tau_2 = (C_{gd} + C_{db})(R_L // R_{out})$$

□ Bandwidth:

$$\omega_H \simeq \frac{1}{(C_{gs} + C_{sb})(R_S // R_{in}) + (C_{gd} + C_{db})(R_L // R_{out})}$$

No capacitor in Miller position \rightarrow no Miller-like term.

Simplify:

- In a current amplifier, $R_S \gg R_{in}$:

$$R_{T1} = R_S // R_{in} \simeq R_{in} \simeq \frac{1}{g_m + g_{mb}} \simeq \frac{1}{g_m}$$

- At output:

$$R_{T2} = R_L // R_{out} = R_L // r_{oc} // \left\{ r_o \left[1 + R_S \left(g_m + g_{mb} + \frac{1}{r_o} \right) \right] \right\}$$

or

$$R_{T2} \simeq R_L // r_{oc} // [r_o(1 + g_m R_S)] \simeq R_L$$

Then:

$$\omega_H \simeq \frac{1}{(C_{gs} + C_{sb})\frac{1}{g_m} + (C_{gd} + C_{db})R_L}$$

If R_L is not too high, bandwidth can be rather high (and approach ω_T).

Key conclusions

- Open-circuit time-constant technique: simple and powerful method to estimate bandwidth of amplifiers.
- Common-gate amplifier:
 - no capacitor in Miller position \Rightarrow no Miller effect
 - if R_L is not too high, CG amp has high bandwidth
- R_S , R_L affect bandwidth of amplifier