

Lecture 20 - Transistor Amplifiers (II)

OTHER AMPLIFIER STAGES

November 17, 2005

Contents:

1. Common-source amplifier (*cont.*)
2. Common-drain amplifier
3. Common-gate amplifier


Reading assignment:

Howe and Sodini, Ch. 8, §§8.7-8.9


Key questions

- What other amplifier stages can one build with a single MOSFET and a current source?
- What is the uniqueness of these other stages?

 1. Common-source amplifier with current-source supply



Loadline view:

 


Current source characterized by high output resistance:
 r_{oc} .

Then, unloaded voltage gain of common-source stage:

$$|A_{vo}| = g_m(r_o // r_{oc})$$

significantly higher than amplifier with resistive supply.

 Can implement current source supply by means of p-channel MOSFET:



*upswing limited
by pMOS entering
linear regime*

$$v_{out,max} = V_B - V_{TP}$$

- Relationship between circuit figures of merit and device parameters

Remember:

$$g_m = \sqrt{2 \frac{W}{L} \mu_n C_{ox} I_D}$$

$$r_o \simeq \frac{1}{\lambda_n I_D} \propto \frac{L}{I_D}$$

Then:


Device * Parameters	Circuit Parameters		
	$ A_{vo} $	R_{in}	R_{out}
	$g_m(r_o//r_{oc})$	∞	$r_o//r_{oc}$
$I_{SUP} \uparrow$	\downarrow	-	\downarrow
$W \uparrow$	\uparrow	-	-
$\mu_n C_{ox} \uparrow$	\uparrow	-	-
$L \uparrow$	\uparrow	-	\uparrow

* adjustments are made to V_{GG} so
none of the other parameters change


CS amp with current supply source is good voltage amplifier (R_{in} high and $|A_v|$ high), but R_{out} high too \Rightarrow voltage gain degraded if $R_L \ll r_o//r_{oc}$.

Common-source amplifier is acceptable voltage amplifier
 (want high R_{in} , high A_{vo} , low R_{out}):

this is the problem

 

 ... but excellent *transconductance* amplifier
 (want high R_{in} , high G_{mo} , high R_{out}):




For common-source amplifier:

$$G_{mo} = g_m$$

Common-source amplifier does not work as *transresistance* amplifier (want low R_{in} , high R_{mo} , low R_{out}):


key problem

 

nor as *current amplifier*


(want low R_{in} , high A_{io} , high R_{out}):

key problem

 

Need new amplifier configurations.

2. Common-drain amplifier

 



How does it work?

- V_{GG} , I_{SUP} , and W/L selected to bias MOSFET in saturation, obtain desired output bias point, and desired output swing.
- $v_G \uparrow \Rightarrow i_D$ can't change $\Rightarrow v_{OUT} \uparrow$
(source follower)
- to first order, no voltage gain: $v_{out} \simeq v_s$
- but R_{out} small: effective *voltage buffer* stage
(good for making voltage amp in combination with common-source stage).

can also see that $R_{out} \propto \frac{1}{g_m}$

□ Small-signal analysis

  Unloaded small-signal equivalent circuit model:



$$v_{in} = v_{gs} + v_{out}$$


$$v_{out} = g_m v_{gs} (r_o // r_{oc})$$

Then:

$$A_{vo} = \frac{g_m}{g_m + \frac{1}{r_o // r_{oc}}} \simeq 1$$


Input impedance: $R_{in} = \infty$

Output impedance:

 

$$\downarrow \\ v_{gs} = -v_t$$

effectively:
resistance of
value $1/g_m$

 

$$R_{out} = \frac{1}{g_m + \frac{1}{r_o // r_{oc}}} \simeq \frac{1}{g_m}$$


small!

Loaded voltage gain:

$$A_v = A_{vo} \frac{R_L}{R_L + R_{out}} \simeq \frac{R_L}{R_L + \frac{1}{g_m}} \simeq 1$$

□ Effect of back bias:

 If MOSFET not fabricated on isolated p-well, then body is tied up to wafer substrate (connected to V_{SS}):
must be




Two consequences:


- Bias affected: V_T depends on $V_{BS} = V_{SS} - V_{OUT} \neq 0$
- Small-signal figures of merit affected: signal shows up between B and S ($v_{bs} = -v_{out}$).

does this help or hurt?

Small-signal equivalent circuit model:

 

$$\downarrow \quad v_{bs} = -v_{out}$$

 

$$A_{vo} = \frac{g_m}{g_m + g_{mb} + \frac{1}{r_o//r_{oc}}} \simeq \frac{g_m}{g_m + g_{mb}} < 1$$

Also:

$$R_{out} = \frac{1}{g_m + g_{mb} + \frac{1}{r_o//r_{oc}}} \simeq \frac{1}{g_m + g_{mb}}$$

- Relationship between circuit figures of merit and device parameters:

$$g_m = \sqrt{2 \frac{W}{L} \mu_n C_{ox} I_D}$$

$$g_{mb} = \frac{\gamma}{2\sqrt{-2\phi_p - V_{BS}}} g_m$$


Device * Parameters	Circuit Parameters		
	$ A_{vo} $	R_{in}	R_{out}
	$\frac{g_m}{g_m + g_{mb}}$	∞	$\frac{1}{g_m + g_{mb}}$
$I_{SUP} \uparrow$	-	-	\downarrow
$W \uparrow$	-	-	\downarrow
$\mu_n C_{ox} \uparrow$	-	-	\downarrow
$L \uparrow$	-	-	\uparrow

* adjustments are made to V_{GG} so
none of the other parameters change

CD amp useful as a **voltage buffer** to drive small loads
(in a multistage amp, other stages will be used to provide
voltage gain).

 3. Common-gate amplifier

Need to handle current-mode signal sources:




How does it work?

C_{sb}

- since source is signal ~~input~~ terminal, body cannot be tied up to source (*C_{sb}* is significant)
- i_{SUP} , I_{BIAS} , and W/L selected to bias MOSFET in saturation, obtain desired output bias point, and desired output swing
- $i_s \uparrow \Rightarrow i_D \downarrow \Rightarrow i_{OUT} \downarrow$
- no current gain: $i_s = -i_{out}$ (*current buffer*)

 - *Bias:* select I_{SUP} , I_{BIAS} , and W/L to get proper quiescent I_{OUT} and keep MOSFET in saturation.



$$I_{SUP} + I_{OUT} + I_{BIAS} = 0$$

Select bias so that $I_{OUT} = 0 \Rightarrow V_{OUT} = 0$.

Assume MOSFET in saturation (no channel modulation):


$$I_D = \frac{W}{2L} \mu_n C_{ox} (V_{GS} - V_T)^2 = I_{SUP} = -I_{BIAS}$$

but V_T depends on V_{BS} :



$$V_T = V_{To} + \gamma_n (\sqrt{-2\phi_p - V_{BS}} - \sqrt{-2\phi_p})$$

Must solve these two equations iteratively to get V_S .

 - *output shorted*
- Small-signal circuit (unloaded)




$$\downarrow \quad v_{bs} = v_{gs}$$

  


$$i_s = -i_{out} \Rightarrow A_{io} = -\frac{i_{out}}{i_s} = -1$$

Not surprising, since in a MOSFET: $i_g = 0$.

Input resistance:

 

$$\downarrow \quad v_{gs} = -v_t$$

 

Do KCL on input node:


$$i_t - g_m v_t - g_{mb} v_t - \frac{v_t - (r_{oc}/R_L) i_t}{r_o} = 0$$

Then:

$$R_{in} = \frac{1 + \frac{r_{oc}/R_L}{r_o}}{g_m + g_{mb} + \frac{1}{r_o}} \simeq \frac{1}{g_m + g_{mb}}$$

Very small.

Output resistance:

 

Do KCL on input node:

$$i'_t - g_m v_{gs} - g_{mb} v_{gs} - \frac{v'_t + v_{gs}}{r_o} = 0$$

Notice also:

$$v_{gs} = -i'_t R_S$$

Then:

$$R_{out} = r_{oc} // \left\{ r_o \left[1 + R_S \left(g_m + g_{mb} + \frac{1}{r_o} \right) \right] \right\} \simeq r_{oc} // [r_o (1 + g_m R_S)]$$

Very large, because of the feedback effect of R_S .

Summary of MOSFET amplifier stages:

stage	A_{vo}, G_{mo}, A_{io}	R_{in}	R_{out}	key function
common source	$G_{mo} = g_m$	∞	$r_o // r_{oc}$	transconductance amp.
common drain	$A_{vo} \simeq \frac{g_m}{g_m + g_{mb}}$	∞	$\frac{1}{g_m + g_{mb}}$	voltage buffer
common gate	$A_{io} \simeq -1$	$\frac{1}{g_m + g_{mb}}$	$r_{oc} // [r_o(1 + g_m R_S)]$	current buffer

In order to design amplifiers with suitable performance,
need to combine these stages \Rightarrow **multistage amplifiers**

Key conclusions

Different MOSFET stages designed to accomplish different goals:

- *Common-source stage:*
 - large voltage gain and transconductance, high input resistance, large output resistance
 - excellent transconductance amplifier, reasonable voltage amplifier
- *Common-drain stage:*
 - no voltage gain, but high input resistance and low output resistance
 - good voltage buffer
- *Common-gate stage:*
 - no current gain, but low input resistance and high output resistance
 - good current buffer