

Lecture 21 - Multistage Amplifiers (I)

MULTISTAGE AMPLIFIERS

November 22, 2005

Contents:

1. Introduction
2. CMOS multistage voltage amplifier
3. BiCMOS multistage voltage amplifier
4. BiCMOS current buffer
5. Coupling amplifier stages

Reading assignment:

Howe and Sodini, Ch. 9, §§9.1-9.3

Key questions


- How can one build a wide range of high-performance amplifiers using the single-transistor stages studied so far?
- What are the most important considerations when assembling multistage amplifiers:
 - regarding interstage loading?
 - regarding interstage biasing?

1. Introduction

Amplifier requirements are often demanding:

- must adapt to specific kinds of signal source and load,
- must deliver sufficient gain

 Single-transistor amplifier stages are very limited in what they can accomplish \Rightarrow *multistage amplifier*.



Issues:

- What amplifying stages should be used and in what order?
- What devices should be used, BJT or MOSFET?
- How is biasing to be done?

- Summary of single stage characteristics:

stage	A_{vo}, G_{mo}, A_{io}	R_{in}	R_{out}	key function
CS	$G_{mo} = g_m$	∞	$r_o // r_{oc}$	transcond. amp.
CD	$A_{vo} \simeq \frac{g_m}{g_m + g_{mb}}$	∞	$\frac{1}{g_m + g_{mb}}$	voltage buffer
CG	$A_{io} \simeq -1$	$\frac{1}{g_m + g_{mb}}$	$r_{oc} // [r_o(1 + g_m R_S)]$	current buffer
CE	$G_{mo} \simeq g_m$	r_π	$r_o // r_{oc}$	transcond. amp.
CC	$A_{vo} \simeq 1$	$r_\pi + \beta(r_o // r_{oc} // R_L)$	$\frac{1}{g_m} + \frac{R_S}{\beta}$	voltage buffer
CB	$A_{io} \simeq -1$	$\frac{1}{g_m}$	$r_{oc} // \{r_o[1 + g_m(r_\pi // R_S)]\}$	current buffer

- Key differences between BJT's and MOSFETs:

BJT	MOSFET
$I_B = \frac{I_C}{\beta} \gg I_G = 0$	

$$g_m = \frac{qI_C}{kT} > g_m = \sqrt{2\frac{W}{L}\mu C_{ox}I_D}$$


$$r_o = \frac{V_A}{I_C} > r_o = \frac{1}{\lambda I_D}$$

2. CMOS multistage voltage amplifier

□ Goals:

- high voltage gain
- high R_{in}
- low R_{out}

□ Good starting point: CS stage

 


✓ • $R_{in} = \infty$ excellent!

• $A_{vo} = -g_m(r_o//r_{oc})$, probably insufficient


• $R_{out} = r_o//r_{oc}$, too high

- Add second CS stage to get more gain:

 

- ✓ • $R_{in} = \infty$
- ✓ • $A_{vo} = g_m1(r_{o1}/\parallel r_{oc1})g_m2(r_{o2}/\parallel r_{oc2})$
- but $R_{out} = r_{o2}/\parallel r_{oc2}$, still high

- Add CD stage at output:

 


- ✓ • $R_{in} = \infty$
- ✓ • $A_{vo} = g_m1(r_{o1}/\parallel r_{oc1})g_m2(r_{o2}/\parallel r_{oc2})\frac{g_{m3}}{g_{m3}+g_{mb3}}$, still high
- ✓ • $R_{out} = \frac{1}{g_{m3}+g_{mb3}}$, now small

3. BiCMOS multistage voltage amplifier

- $A_{vo}(CE) > A_{vo}(CS)$ because $r_o(BJT) > r_o(MOSFET)$ and $g_m(BJT) > g_m(MOSFET)$ but...

CS stage is best first stage, since $R_{in} = \infty$.

- Add CE stage following CS stage?

 

Trouble is interstage loading degrades gain:


$$R_{out1} = r_{o1} // r_{oc1} \gg R_{in2} = r_{\pi2}$$

Voltage divider between stages:

$$\frac{R_{in2}}{R_{out1} + R_{in2}} = \frac{r_{\pi2}}{r_{o1} // r_{oc1} + r_{\pi2}} \simeq \frac{r_{\pi2}}{r_{o1} // r_{oc1}} \ll 1$$

Additional gain provided by CE stage more than lost in interstage loading.

 - Use two CS stages, but add CC stage at output:



Interstage loading:

$$R_{out2} = r_{o2} \parallel r_{oc2}, \quad R_{in3} = r_{\pi3} + \beta_3(r_{o3} \parallel r_{oc3} \parallel R_L)$$

Then, interstage loss:

$$\frac{R_{in3}}{R_{out2} + R_{in3}} = \frac{r_{\pi3} + \beta_3(r_{o3} \parallel r_{oc3} \parallel R_L)}{r_{o2} \parallel r_{oc2} + r_{\pi3} + \beta_3(r_{o3} \parallel r_{oc3} \parallel R_L)}$$

better than trying to use a CE stage, but still pretty bad.


Benefit is that \$R_{out}\$ has improved:

$$R_{out} = R_{out3} = \frac{1}{g_{m3}} + \frac{R_{out2}}{\beta_3} = \frac{1}{g_{m3}} + \frac{r_{o2} \parallel r_{oc2}}{\beta_3}$$

Since, in general, \$g_m(BJT) > g_m(MOSFET)\$, \$R_{out}\$ could be better than CD output stage if \$r_{o2} \parallel r_{oc2}\$ is not too large. Otherwise, CD stage output is better.

- Better voltage buffer: cascade CC and CD output stages.

 What is best order? Since $R_{in}(CD) = \infty$, best to place CD first:



Interstage loading:

$$\frac{R_{in3}}{R_{out2} + R_{in3}} = 1$$

$$\frac{R_{in4}}{R_{out3} + R_{in4}} = \frac{r_{\pi4} + \beta_4(r_{o4}/r_{oc4}/R_L)}{\frac{1}{g_{m3}+g_{mb3}} + r_{\pi4} + \beta_4(r_{o4}/r_{oc4}/R_L)} \approx 1$$

and excellent output resistance:


$$R_{out} = R_{out4} = \frac{1}{g_{m4}} + \frac{R_{out3}}{\beta_4} = \frac{1}{g_{m4}} + \frac{1}{\beta_4(g_{m3} + g_{mb3})}$$

4. BiCMOS current buffer

□ Goals:

- Unity current gain
- very low R_{in}
- very high R_{out}

Start with common-base stage:

 


- ✓ • $A_{io} = -1$
- ✓ • $R_{in} = \frac{1}{g_m}$
- $R_{out} = r_{oc} // \{r_o[1 + g_m(r_\pi // R_S)]\}$

Note that if R_S is not too low, $R_{out} \simeq r_{oc} // (\beta r_o)$.

Can we further increase R_{out} by adding a second CB stage?

□ CB-CB current buffer:

 

Now

$$R_{out} = R_{out2} = r_{oc2} // \{r_{o2}[1 + g_{m2}(r_{\pi2} // R_{out1})]\}$$

Plugging in $R_{out1} \simeq r_{oc1} // (\beta_1 r_{o1})$,

$$R_{out} = r_{oc2} // \{r_{o2}[1 + g_{m2}(r_{\pi2} // r_{oc1} // \beta_1 r_{o1})]\}$$


But, since $r_{\pi2} \ll r_{oc1} // (\beta_1 r_{o1})$, then

$$R_{out} \simeq r_{oc2} // [r_{o2}(1 + g_{m2}r_{\pi2})] \simeq r_{oc2} // (\beta_2 r_{o2})$$

Did not improve anything! The base current limits the number of CB stages that improve R_{out} to just one.

Since CG stage has no gate current, cascade it behind CB stage.

□ CB-CG current buffer:

 

$$R_{out} = R_{out2} = r_{oc2} // [r_{o2}(1 + g_{m2}R_{out1})]$$

with $R_{out1} \simeq r_{oc1} // (\beta_1 r_{o1})$,

$$R_{out} = r_{oc2} // [r_{o2}g_{m2}(r_{oc1} // \beta_1 r_{o1})]$$


✓ Now R_{out} has improved by about $g_{m2}r_{o2}$, but only to the extent that r_{oc2} is high enough...

5. Coupling amplifier stages

□ CAPACITIVE COUPLING

Capacitors of large enough value behave as AC short, so signal goes through but bias is independent for each stage.

Example, CD-CC voltage buffer:

 

- Advantages:


- can select bias point for optimum operation
- can select bias point close to middle of rails for maximum signal swing

- Disadvantages:

- to approximate AC short, need large capacitors that consume significant area


- DIRECT COUPLING: share bias points across stages.

Example, CD-CC voltage buffer:

 

- Advantages:
 - no capacitors: compact
- Disadvantages:
 - bias point shared: constrains design
 - bias shifts from stage to stage and can stray too far from center of range

Solution: use PMOS CD stage:

 













Trade-off: $g_m(\text{PMOS}) < g_m(\text{NMOS}) \rightarrow \text{higher } R_{out}$

In BiCMOS voltage amplifier:

$$R_{out} = \frac{1}{g_{m4}} + \frac{1}{\beta_4(g_{m3} + g_{mb3})}$$

smaller using PMos

- Summary of DC shifts through amplifier stages:

            Amplifier Type	Transistor Type			
	NMOS	PMOS	npn	pnp
Common Source/ Common Emitter (CS/CE)	 i_{SUP} at V^+	 i_{SUP} at V^+	 i_{SUP} at V^+	 i_{SUP} at V^+
Common Gate/ Common Base (CG/CB)	 i_{SUP} at V^+	 i_{SUP} at V^+	 i_{SUP} at V^+	 i_{SUP} at V^+
Common Drain/ Common Collector (CD/CC)	 i_{SUP} at V^+	 i_{SUP} at V^+	 i_{SUP} at V^+	 i_{SUP} at V^+

Important difference in bias shift between stages in BJT and MOSFET amps:

- In BJT (for npn):


$$V_{BE} \simeq V_{BE,on}$$

rather independent of transistor size and current level.

- In MOSFET (for nMOSFET):

$$V_{GS} = V_T + \sqrt{\frac{2I_D}{\mu_n C_{ox}} \frac{L}{W}}$$

 Can be engineered through bias current and transistor geometry.



Assumes $V_{BE} = 0.7$ V
 $V_{GS} = 1.5$ V

Key conclusions

- To achieve amplifier design goals, several stages often needed.
- In multistage amplifiers, different stages used to accomplish different goals:
 - voltage gain: common-source, common emitter
 - voltage buffer: common-drain, common collector
 - current buffer: common-gate, common base
- In multistage amplifiers must pay attention to inter-stage loading to avoid unnecessary losses.
- In *direct-coupled* amplifiers, bias is shared between adjoining stages:
 - must select compromise bias,
 - must pay attention to bias shift from stage to stage.