

6.012 MICROELECTRONIC DEVICES AND CIRCUITS


Answers to Exam 2 - Spring 2008

Problem 1: Graded by Prof. Fonstad

- a) i) n-channel MOSFET: Enhancement mode because  $V_T \geq 0$ , which for an n-channel MOSFET means that with  $v_{GS} = 0$  there is no channel.  
 p-channel MOSFET: Depletion mode because  $V_T \geq 0$ , which for a p-channel MOSFET means that with  $v_{GS} = 0$  there is already a channel.
- ii) Negative because there is a hole inversion layer in the p-channel device, i.e. electrons depleted from the area near the interface and holes attracted to the interface, even with  $v_{GS} = 0$ . Concurrently, it takes more gate voltage to invert the channel of the n-channel device, meaning more positive charge must be put on the gate electrode which is balanced by negative ions at the interface.
- iii) Larger, because the charging current is the current in saturation through the p-channel device, and since the current in saturation for both of the devices is proportional to  $(V_{DD} - |V_T|)^2$ , this current is larger for the p-channel device since for it  $|V_T|$  is smaller.
- iv) Larger, because for both devices  $|V_T| = |V_{FB}| + |2\phi_{Si}| + (t_{ox}/\epsilon_{ox})(\dots)^{1/2}$ . Thus making  $t_{ox}$  thicker, makes  $|V_T|$  larger.

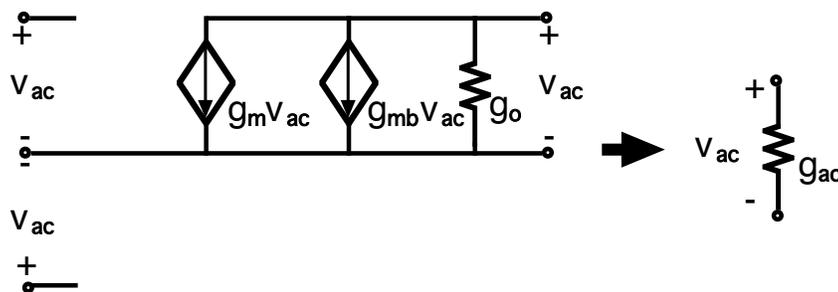- b) i)  $V_{GS}: \underline{2V}$        $V_{BS}: \underline{-1V}$        $V_{DS}: \underline{2V}$   
 $v_{gs}: \underline{V_{AC}}$        $v_{ds}: \underline{V_{AC}}$        $v_{bs}: \underline{V_{AC}}$

The LEC is a single resistor:  $r_{ac} = 1/g_{ac} = 1/[g_m + g_{mb} + g_o] = 1/[g_m(1+\eta) + g_o]$



LEC:

- ii) n-channel, because for a transistor in strong inversion and biased in saturation,  $g_m = (2KI_D)^{1/2}$  and we can assume that  $K_n > K_p$  because in general  $\mu_e > \mu_h$ .
- iii) Similar, because for a transistor operating sub-threshold  $g_m = qI_D/nkT$ , and the  $I_D$ 's are equal and the n's will be similar.
- iv) In the linear region  $i_D = K(v_{GS} - V_T - v_{DS}/2)v_{DS}$   
 Transconductance:  $g_m = \partial i_D / \partial v_{GS} |_Q = KV_{DS}$   
 Output conductance:  $g_o = \partial i_D / \partial v_{DS} |_Q = [K(v_{GS} - V_T - v_{DS}/2) - Kv_{DS}/2] |_Q = K(v_{GS} - V_T - v_{DS})$

**Problem 2:** Graded by Prof. Palacios

- a) The  $i_D$ - $v_{DS}$  plot shows us that for the gate voltage applied the MOSFET saturates at a  $v_{DS}$  of 5 V. We can find out what the gate voltage is using:  $V_{DS,sat} = V_{GS} - V_T$ :

$$V_{GS} = V_{DS,sat} + V_T = 5 \text{ V} + 1 \text{ V} = 6 \text{ V}$$

- b) Near the origin,  $i_D = K(v_{GS} - V_T - v_{DS}/2)v_{DS}$  and the slope is  $K(v_{GS} - V_T - v_{DS})$ . Evaluating this at the origin, we find that

$$\partial i_D / \partial v_{DS} (@ V_{DS} = 0) = K(V_{GS} - V_T) = KV_{DS,sat}$$

where  $(V_{GS} - V_T) = 5 \text{ V}$ . To find K and evaluate this we can use the saturation current, 10 mA, and saturation voltage, 5 V, in  $i_{D,sat} = K(V_{GS} - V_T)^2/2 = K(V_{DS,sat})^2/2$  to find:

$$K = 2i_{D,sat} / (V_{DS,sat})^2 = 2 (0.01 / 25) = 0.0008 \text{ A/V}^2$$

With this the slope,  $KV_{DS,sat}$  is:  $8 \times 10^{-4} \times 5 = 4 \times 10^{-3} \text{ S}$

- c) At any point in the channel,  $q_N^*(y) = -(\epsilon_{ox}/t_{ox})(V_{GS} - V_T) = -(\epsilon_{ox}/t_{ox})(V_{GS} - V_{CS} - V_T)$

- i) At the source end of the channel,  $V_{CS} = 0$ , and we find:

$$q_N^*(0) = -(\epsilon_{ox}/t_{ox})(V_{GS} - V_T) = -(3.5 \times 10^{-13} / 10^{-6})5 = -1.75 \times 10^{-6} \text{ C/cm}^2$$

- ii) At the drain end of the channel,  $V_{CS} = V_{DS} = 2.5 \text{ V}$ , and we find:

$$q_N^*(L) = -(\epsilon_{ox}/t_{ox})(V_{GS} - V_{DS} - V_T) = -(3.5 \times 10^{-13} / 10^{-6}) 2.5 = -8.75 \times 10^{-7} \text{ C/cm}^2$$

- d) The drift velocity can be found by remembering that  $i_D$  is the channel current and that the current at any point  $y$  along the channel is the sheet charge density in the channel,  $q_N^*(y)$ , times the drift velocity of the carriers composing this charge, times the width of the channel:  $i_D = -W q_N^*(y) s_{e-Drift}(y)$ . Thus:  $s_{e-Drift}(y) = -i_D / W q_N^*(y)$

- i) At the source end of the channel we find:

$$s_{e-Drift}(0) = i_D / W q_N^*(y) = 7.5 \times 10^{-3} / 5 \times 10^{-3} \times 1.75 \times 10^{-6} = 8.57 \times 10^5 \text{ cm/s}$$

- ii) At the drain end of the channel we find:

$$s_{e-Drift}(L) = i_D / W q_N^*(y) = 7.5 \times 10^{-3} / 5 \times 10^{-3} \times 8.75 \times 10^{-7} = 1.71 \times 10^6 \text{ cm/s}$$

- e) Now the relationship between the drain current and the charge density at  $y = L$  must be  $i_D = -W q_N^*(L) s_{sat}(y)$ . We want the charge density, so we solve for that:

$$q_N^*(L) = -i_D / W s_{sat}(y) = -10^{-2} / 5 \times 10^{-3} \times 10^7 = -2 \times 10^{-7} \text{ C/cm}^2$$

- f) This is a difficult question and almost nobody got it correct. This was anticipated before the exam, but we decided to leave the question in with a precautionary note added, just to see if anyone could do it. That said, the idea is to go back to the expression for  $i_D$  along the channel, and to integrate it from  $y = 0$  to  $y = L/2$ , the point along the channel at which we want to know  $v_{CS}$ . Since we know  $i_D$  already, we can find  $v_{CS}(L/2)$ . The sequence leading to the expression sought is:


$$i_{D,sat} = -W q_N^*(y) \mu_e dv_{CS} / dy = W (\epsilon_{ox} / t_{ox}) [V_{GS} - v_{CS}(y) - V_T] \mu_e dv_{CS} / dy$$

$$i_{D,sat} dy = W (\epsilon_{ox} / t_{ox}) [V_{GS} - v_{CS}(y) - V_T] \mu_e dv_{CS}$$


$$\int_0^y i_{D,sat} dy = i_{D,sat} y = \int_0^{v_{CS}(y)} W (\epsilon_{ox} / t_{ox}) [V_{GS} - v_{CS} - V_T] \mu_e dv_{CS}$$

**Problem 3:** Graded by Prof. Palacios


a) i)

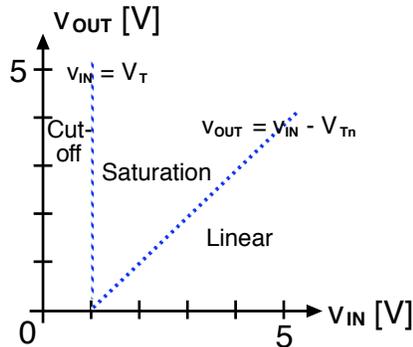

ii)

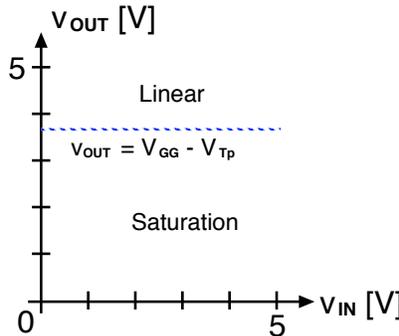

b)

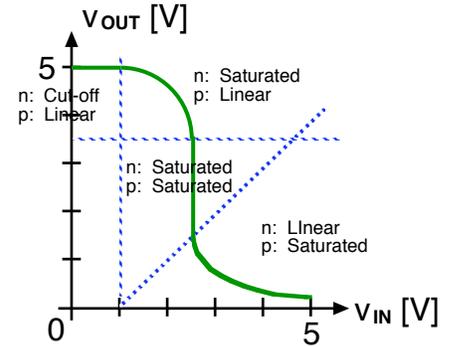


c) The threshold point occurs where both transistors are in saturation. The equation for the curve there is:

$$I_{D-sat n} = (K_n/2)(V_{GSn} - V_{Tn})^2 = I_{D-sat p} = (K_p/2)(V_{SGp} - |V_{Tp}|)^2$$

We know  $K_n = K_p$ ,  $V_{Tn} = |V_{Tp}|$ ,  $V_{SGp} = V_{DD} - V_{GG}$ , and  $V_{GSn} = V_{IN} = V_{DD}/2$ , so we find

$$V_{DD}/2 - V_{Tn} = V_{DD} - V_{GG} - |V_{Tp}| \Rightarrow V_{GG} = V_{DD}/2 = 2.5 \text{ V}$$

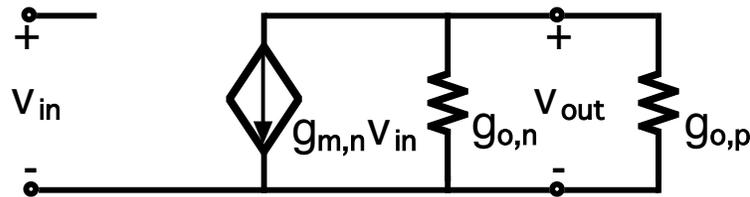d) When both devices are in saturation at this bias point, the LEC is:



We find  $A_v = -g_{mn}/(g_{on} + g_{op})$ . There are several ways to write  $g_m$  in terms of the bias current and voltages, but the most useful here is  $g_{mn} = 2I_{Dn}/(V_{GSn} - V_{Tn})$ . This along with  $g_{on} = \lambda_n I_{Dn}$  and  $g_{op} = \lambda_p I_{Dp}$ , and using  $I_{Dn} = I_{Dp} = I_D$ ,  $\lambda_n = \lambda_p = 0.1 \text{ V}^{-1}$ ,  $V_{Tn} = 1 \text{ V}$ , and  $V_{GSn} = 2.5 \text{ V}$ , lead us to:

$$A_v = -g_{mn}/(g_{on} + g_{op}) = 2/[(V_{GSn} - V_{Tn})(\lambda_n + \lambda_p)] = 2/(1.5 \times 0.2) = -6.6$$

e) When  $V_{IN} = 5 \text{ V}$  the n-channel device is on, and the p-channel device is saturated with  $I_D = K_p(V_{DD} - V_{GG} - |V_{Tp}|)^2/2$ . The corresponding static power dissipation is  $I_D V_{DD}$ . Working through this we find

$$P_{Static}(V_{IN} = 5\text{V}) = I_D V_{DD} = [(W_p/L_p)\mu_h C_{ox}^*(V_{DD} - V_{GG} - |V_{Tp}|)^2/2] \times V_{DD} \\ = (25 \times 200 \times 6 \times 10^{-7} \times 1.5^2) \times 5/2 = 16.8 \times 10^{-3} \text{ W} = 16.8 \text{ mW}$$

You did not have to include channel length modulation in this sub-section, but if you did you had an additional term  $[1 + \lambda(V_{DS} - V_{DS,sat})] = 1 + 0.1(5 - 1.5) = 1.35$  multiplying the current, and found:

$$P_{Static}(V_{IN} = 5\text{V}) = 16.8 \times 1.35 = 22.7 \text{ mW}$$

f) When  $V_{IN} = 5 \text{ V}$  the n-channel device is off, and the only static power dissipation is due to the sub-threshold current,  $I_{D,s-t}$  and is  $I_{D,s-t} V_{DD}$ . This is probably negligible, but just to be sure, we start by calculating the sub-threshold current when  $v_{GS} = 0$ :

$$\begin{aligned}
 i_{D,s-t} &= [(W_N/L_N)\mu_e C_{ox}^*] (kT/q)^2 (n-1) \exp(-qV_T/nkT) \\
 &= (10 \times 5 \times 10^2 \times 6 \times 10^{-7}) (2.5 \times 10^{-2})^2 (1.5 - 1) \exp[-1/(1.5 \times 0.025)] \\
 &\approx 9.3 \times 10^{-7} e^{-27} \text{ A} \approx 9.3 \times 10^{-7} \times 1.6 \times 10^{-12} \approx 1.5 \times 10^{-18}
 \end{aligned}$$

From this we have  $P_{\text{Static}} (V_{\text{IN}} = 0V) = 1.5 \times 10^{-18} \times 5 \approx 10^{-17} \text{ W} \approx 0$ .

- g) The low to high transition time is due to charging through the p-channel device with its saturation current,  $I_D = K_p(V_{DD} - V_{GG} - |V_{Tp}|)^2/2$  [= 3.36 mA from Part (e)], so we have:

$$\tau_{\text{Lo-Hi}} = C_L V_{DD} / [K_p(V_{DD} - V_{GG} - |V_{Tp}|)^2/2] = 10^{-13} \times 5 / (3.36 \times 10^{-3}) = 1.48 \times 10^{-10} \text{ s}$$


### Exam Statistics

Average/Standard deviation:	Problem 1	26.6	6.9
	Problem 2	21.7	6.6
	<u>Problem 3</u>	<u>22.0</u>	<u>6.9</u>
	Total	70.3	16.6

**Class median: 73**

**Distribution to nearest 5:**

Find your face in this picture

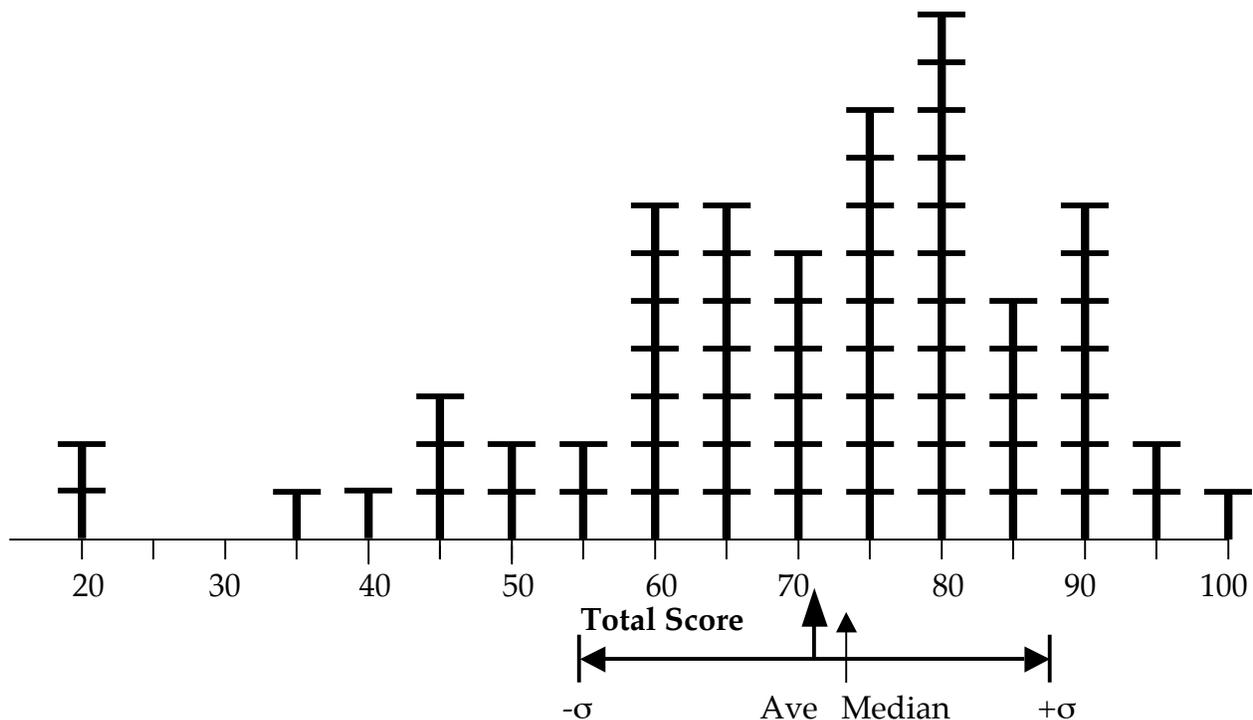

MIT OpenCourseWare  
<http://ocw.mit.edu>

6.012 Microelectronic Devices and Circuits  
Fall 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.