

MASSACHUSETTS INSTITUTE OF TECHNOLOGY
Department of Electrical Engineering and Computer Science

6.012 MICROELECTRONIC DEVICES AND CIRCUITS

Answers to Exam 2 - Fall 2009

Problem 1: Graded by Prof. Fonstad

- a) i) Applying $v_{GS} > V_T$ to an n-channel MOSFET accumulates additional holes at the interface. The additional amount of interface charge is $-WLC_{ox}^*(v_{GS} - V_T) = -5 \times 10^{-4} \times 2 \times 10^{-5} \times 10^{-8} \times 1 = 10^{-16}$ Coul.
- ii) The additional holes come from the p-type bulk region.
- iii) Applying $v_{GS} < V_{FB}$ to an n-channel MOSFET increases the number of inversion layer electrons at the interface. The additional charge is $-WLC_{ox}^*(v_{GS} - V_{FB}) = 5 \times 10^{-4} \times 2 \times 10^{-5} \times 10^{-8} \times 1 = 10^{-16}$ Coul.
- iv) The additional electrons come from the n-type source and drain regions.

- b) i) One of the n+ regions (source or drain) is the emitter, the other n+ region is the collector, and the base is the p-region, or substrate. To bias an npn BJT in its forward active region requires $V_{CE} \geq 0.2$ V and $V_{BE} \approx 0.6$ to 0.7 V. Saying both had to be greater than zero was accepted and earned most of the points.

- ii) The forward current gain, β_F , is low because a large fraction of the electrons injected across the emitter-base diode into the p-region are directed vertically and not laterally toward the collector.

The early voltage is low, and thus there is a significant amount of base width modulation, because the collector is more heavily doped than the base, meaning that the depletion region at the collector-base junction extends primarily into the base side of the junction.


- iii) Adding a heavily doped p-type region under the n+ regions reduces the vertical injection of electrons across the emitter-base junction and the junction current is now predominantly electrons flowing laterally across the junction and toward the relatively close collector. This makes β_F much larger.

- c) i) Doing a Taylor's Series expansion about Q , and isolating the small signal terms:

$$i_d = (di_D/dv_{GS})|_Q v_{gs} + (di_D/dv_{DS})|_Q v_{ds}$$

$$= (W/L) \mu_e [C_{ox}^* V_{DS} v_{gs} + (C_{ox}^* V_{GS} + \alpha) v_{ds}]$$

 - ii) The small signal linear equivalent circuit is:




with $g_m = (W/L) \mu_e C_{ox}^* V_{DS}$ and $g_o = (W/L) \mu_e (C_{ox}^* V_{GS} + \alpha)$

 - iii) To find R_L we first find $I_D = 10^{-7} (10 V_{GS} + 1) V_{DS}$ with $V_{GS} = 1$ V and $V_{DS} = 1.5$ V, or $I_D = 1.65 \times 10^{-6}$ Amps. The voltage drop across R_L must be 1.5 V, so

$$R_L = 1.5 / (1.65 \times 10^{-6}) \approx 900,000 \text{ Ohms}$$


We can now use this result and our linear equivalent circuit to draw the linear equivalent circuit for the full circuit, and from that we find the voltage gain:



We find $g_m = 1.5 \times 10^{-6}$ mho and $g_o = 1.1 \times 10^{-6}$ mho, and using the R_L above we have $1/R_L = G_L = 1.1 \times 10^{-6}$ mho. Thus, $A_v = v_{out}/v_{in} = -g_m/(g_o + G_L) \approx -0.7$.

Problem 2: Graded by Prof. Weinstein

 - a) In flatband there is no depletion region, $\phi(0) = \phi_n$, and there is no voltage drop across the dielectric.




As indicated in the figure, $V_{FB} = 1.5 \phi_n$.

 
- b) At flatband the hole and electron populations are the same as they are in the bulk of the semiconductor. Thus, $n(x = 0^+) = N_D$, and $p(x = 0^+) = n_i^2/N_D$.
- c) At the onset of threshold $\phi(0) = -\phi_n$, the depletion region accommodates a change in potential of $2 \phi_n$ and thus $X_D = [2\epsilon_{Si} (2 \phi_n) / qN_D]^{1/2}$. The potential drop across the dielectric $qN_D X_D t_{hi} / \epsilon_{hi}$, and $V_T - V_{FB} = -2 \phi_n - (t_{hi} / \epsilon_{hi}) [2\epsilon_{Si} (2 \phi_n) qN_D]^{1/2}$.

$$\begin{aligned} \text{With these results, we find } V_T &= V_{FB} - 2 \phi_n - (t_{hi} / \epsilon_{hi}) [2\epsilon_{Si} (2 \phi_n) qN_D]^{1/2} \\ &= -0.5 \phi_n - (t_{hi} / \epsilon_{hi}) [2\epsilon_{Si} (2 \phi_n) qN_D]^{1/2} \end{aligned}$$

The electrostatic potential profile at the onset of inversion:



 The net charge distribution at the onset of inversion:



- d) At the onset of inversion, the hole density at the interface is N_D , i.e. $p(x = 0^+) = N_D$, and $n(x = 0^+) = n_i^2/N_D$.
- e) If there is a net sheet charge density, σ_v , at the interface, then at flatband there is a net sheet charge density, $-\sigma_v$, on the gate, and no other charge in semiconductor up to the interface. The voltage drop across the gate dielectric is $\sigma_i(t_{hi}/\epsilon_{hi})$, and the flatband voltage must be more negative by this amount, $\Delta V_{FB} = -\sigma_i(t_{hi}/\epsilon_{hi})$. The threshold voltage will be more negative by this same amount: $\Delta V_T = -\sigma_i(t_{hi}/\epsilon_{hi})$.
- f) With an additional dielectric layer under the gate, there is additional voltage drop across the insulator for the same charge on the gate: ΔV (w.o. SiO_2) = $Q_G(t_{hi}/\epsilon_{hi})$ and ΔV (w. SiO_2) = $Q_G(t_{hi}/\epsilon_{hi}) + Q_G(t_{ox}/\epsilon_{ox})$. $C_G = Q_G/\Delta V = 1/(t_{hi}/\epsilon_{hi} + t_{ox}/\epsilon_{ox}) = \epsilon_{hi}/2t_{hi}$. Thus $C_G(\text{w. SiO}_2)/C_G(\text{w.o. SiO}_2) = 1/2$.

Problem 3: Graded by Prof. Palacios

- a) $I_{D,sat} = (W_{min}/2L_{min})\mu_e(\epsilon_{ox}/t_{ox})(V_{GS} - V_T)^2[1 + \lambda_n(V_{DS} - V_{DS,sat})]$
 $= [135/(2 \times 35)] \times 500 \times (3.5 \times 10^{-13}/10^{-7}) (0.6)^2 (1 + 0.001(1 - 0.4)) \approx 1.2 \text{ mA}$
- b) $r_o = 1/g_o = 1/\lambda_n I_D = 1/(10^{-3} \times 1.2 \times 10^{-3}) = 10^6/1.2 \approx 800,000 \text{ Ohms}$
- c)

V_{IN1}	V_{IN2}	V_{OUT}
0 V	0 V	1 V
0 V	1 V	1 V
1 V	0 V	1 V
1 V	1 V	0 V
- d) $W_{n,Inverter} = 1 W_{min}$ and $W_{p,Inverter} = (\mu_e/\mu_h) W_{n,Inverter} = (500/200) W_{min} = 2.5 W_{min}$
- e) We want the n-MOSFETs to each be minimum length since the effective length will be the sum of the lengths of two n-MOSFETs: $L_{n,NAND} = 1 L_{min}$, and $L_{n,Eff} = 2 L_{min}$. To minimize the delay, we will require the same current capability as in a standard inverter. To achieve this with an effective gate length $L_{n,Eff} = 2 L_{min}$, the width needs to be $W_{n,NAND} = 2 W_{min}$.
- As the current capability of the n-MOS branch is the same as in an inverter, the p-MOS branch can be sized as in the inverter in question d). Thus $C_{IN,NAND} = 2.5W_{min}L_{min} + 2W_{min}L_{min} = 4.5 W_{min}L_{min}$. $C_{IN,Inverter} = W_{min}L_{min} + 2.5 W_{min}L_{min} = 3.5 W_{min}L_{min}$, so $C_{IN,NAND} = 1.29 C_{IN,Inverter}$.
- f) The question speaks of inverter equivalents. The inverters have 15nA leakage if their output is high (n-MOS off), and 37.5 nA leakage if their output is low (p-MOS, which is 2.5 x as wide, off) so the static power dissipation is 15 nA/gate x $1 \text{ V} \times 10^9 \text{ gates} + 37.5 \text{ nA/gate} \times 1 \text{ V} \times 10^9 \text{ gates} = 47.5 \text{ Watts!}$

If you did the problem assuming 10^9 NAND gates, then the output is low, we have subthreshold current coming from each one of the two p-MOSFETs, which are connected in parallel. Therefore, the power dissipation is: 2 transistors/gate \times 15 nA/transistor \times 1 V \times (1×10^9) gates = 30 Watts. When the output is high, the leakage current is due to the subthreshold current through the n-MOSFETs, which are connected in series and the current is dominated by one of them (i.e. they share the same current). Thus, the power dissipation in this state is: 1 transistor/gate \times 15 nA/transistor \times 1 V \times (1×10^9) gates = 15 Watts. By adding the two contributions, the total dissipated power is: 30 W + 15W = 45 W

- g) i) $E_{ave} = 1 \text{ V} / (35 \times 10^{-7} \text{ cm}) \approx 3 \times 10^5 \text{ V/cm}$
- ii) The average sheet charge density is $q_n^* = C_{ox}^* (v_{GS} - V_T) = 0.6 (\epsilon_{ox} / t_{ox}) = 0.6 \times 3.5 \times 10^{-6} = 2.1 \times 10^{-6} \text{ coul/cm}^2$. The current, $i_D = W q_n^* s_{ch,ave}$. Assuming $i_D = 250 \mu\text{A}$, we have: $s_{ch,ave} = i_D / (W q_n^*) = 2.5 \times 10^{-4} / (1.35 \times 10^{-5} \times 2.1 \times 10^{-6}) \approx 0.88 \times 10^7 \text{ cm/s}$. Assuming $i_D = 1.2 \text{ mA}$ as found in part (a), we find: $s_{ch,ave} \approx 4.2 \times 10^7 \text{ cm/s}$.
- iii) The current is almost 5 times smaller than the low field constant mobility model predicts because the velocity saturates at just under 10^7 V/cm .


Exam Statistics

Average/Standard deviation:	Problem 1	21.5	5.3
	Problem 2	19.2	7.6
	<u>Problem 3</u>	<u>25.1</u>	<u>5.5</u>
	Total	65.8	14.9

Class median: 65

Distribution to nearest 5:

Find your face in this picture

 

MIT OpenCourseWare
<http://ocw.mit.edu>

6.012 Microelectronic Devices and Circuits
Fall 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.