

Lecture 21

Frequency Response of Amplifiers

(I)

Common-Emitter Amplifier

Outline

- Review frequency domain analysis
- BJT and MOSFET models for frequency response
- Frequency Response of Intrinsic Common-Emitter Amplifier
- Effect of transistor parameters on f_T


Reading Assignment:

Howe and Sodini, Chapter 10, Sections 10.1-10.4

I. Frequency Response Review

Phasor Analysis of the Low-Pass Filter

- Example:

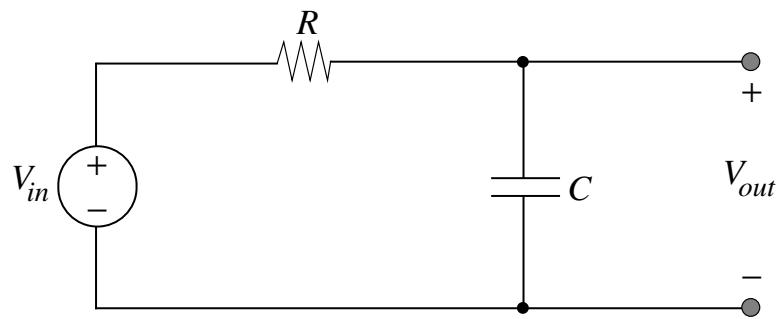

- Replacing the capacitor by its impedance, $1 / (j\omega C)$, we can solve for the ratio of the phasors V_{out}/V_{in}


$$\frac{V_{out}}{V_{in}} = \frac{1/j\omega C}{R + 1/j\omega C}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega RC}$$

- $V_{out} \equiv$ Phasor notation

Magnitude Plot of LPF


- $\left| \frac{V_{out}}{V_{in}} \right| \rightarrow 1$ for “low” frequencies
- $\left| \frac{V_{out}}{V_{in}} \right| \rightarrow 0$ for “high” frequencies

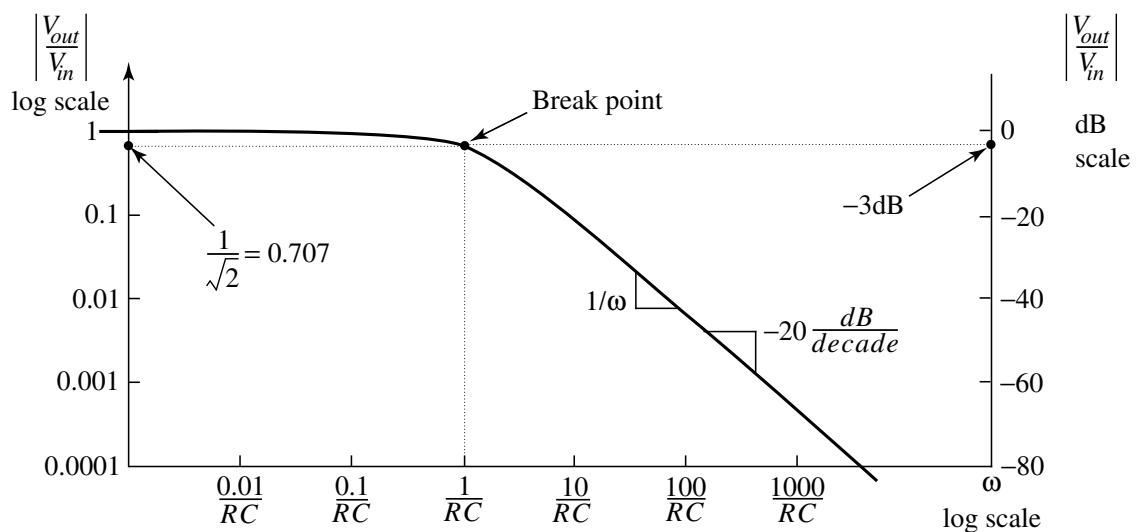

- The “break point” is when the frequency is equal to $\omega_o = 1 / RC$
- The break frequency defines “low” and “high” frequencies.
- $\text{dB} \equiv 20 \log x \rightarrow 20\text{dB} = 10, 40\text{dB} = 100, -40\text{dB} = .01$
- At ω_o the ratio of phasors has a magnitude of - 3 dB.

Phase Plot of LPF

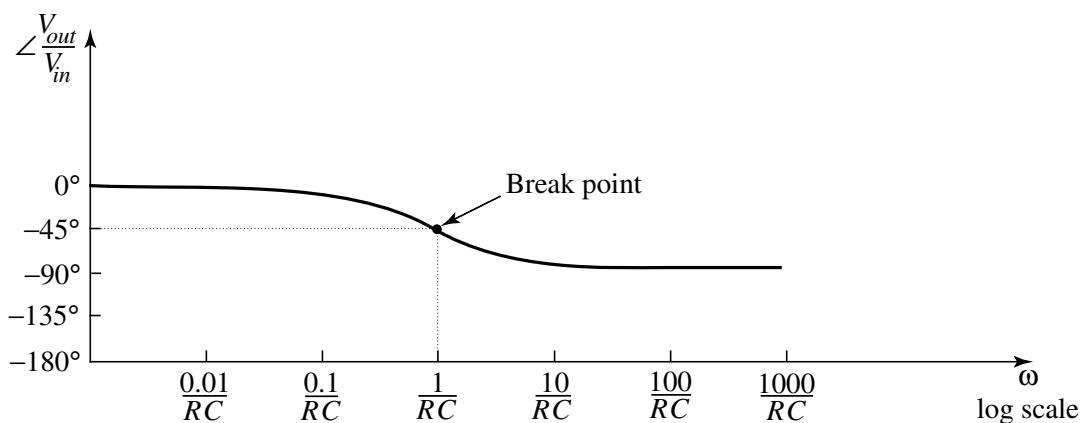- Phase $(V_{out} / V_{in}) = 0^\circ$ for low frequencies
- Phase $(V_{out} / V_{in}) = -90^\circ$ high frequencies.




- Transition region extends from $\omega_0 / 10$ to $10 \omega_0$
- At ω_0 Phase = -45°


Review of Frequency Domain Analysis [Chap 10.1](#)

II. Small Signal Models for Frequency Response

Bipolar Transistor

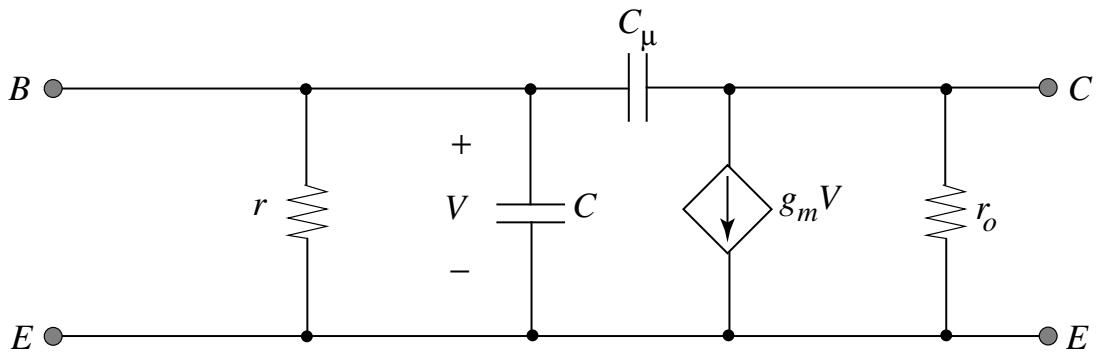

MOS Transistor - $V_{SB} = 0$

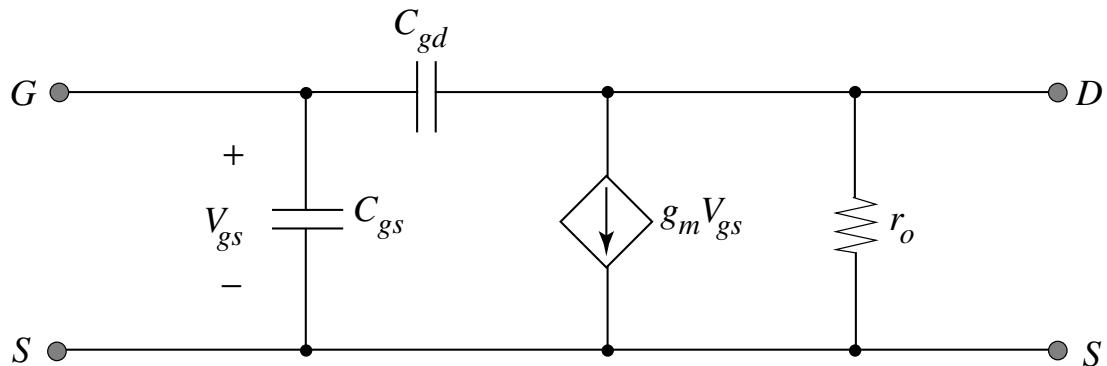


- Replace C_{gs} for C_π
- Replace C_{gd} for C_μ
- Let $r_\pi \rightarrow \infty$

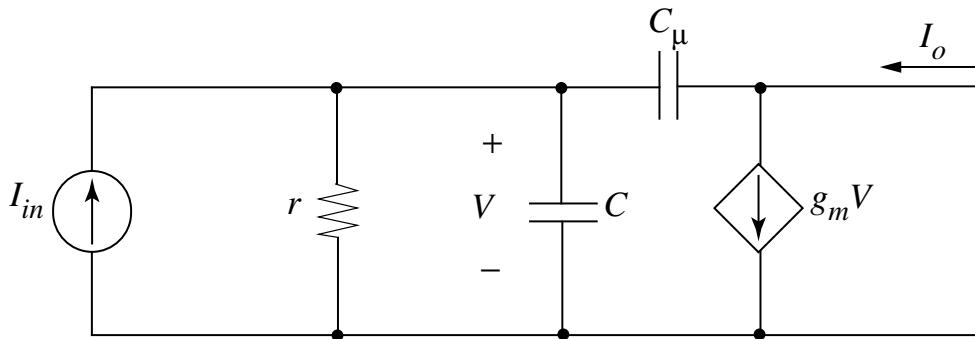III. Frequency Response of Intrinsic CE Current Amplifier

$$R_S \rightarrow \infty \text{ & } R_L = 0$$

Circuit analysis - Short Circuit Current Gain I_o/I_{in}



- KCL at the output node:

$$I_o = g_m V_\pi - V_\pi j \omega C_\mu$$

- KCL at the input node:



$$I_{in} = \frac{V_\pi}{Z_\pi} + V_\pi j \omega C_\mu \quad \text{where} \quad Z_\pi = r_\pi \left| \left(\frac{1}{j \omega C_\pi} \right) \right|$$

- After Algebra

$$\frac{I_o}{I_{in}} = \frac{g_m r_\pi \left(1 - \frac{j \omega C_\mu}{g_m} \right)}{1 + j \omega r_\pi (C_\pi + C_\mu)} = \frac{\beta_o \left(1 - \frac{j \omega C_\mu}{g_m} \right)}{1 + j \omega r_\pi (C_\pi + C_\mu)} = \beta_o \begin{vmatrix} 1 - j \frac{\omega}{\omega_z} \\ 1 + j \frac{\omega}{\omega_p} \end{vmatrix}$$

$$\omega_z = \frac{g_m}{C_\mu} \quad \omega_p = \frac{1}{r_\pi (C_\pi + C_\mu)}$$

Bode Plot of Short-Circuit Current Gain

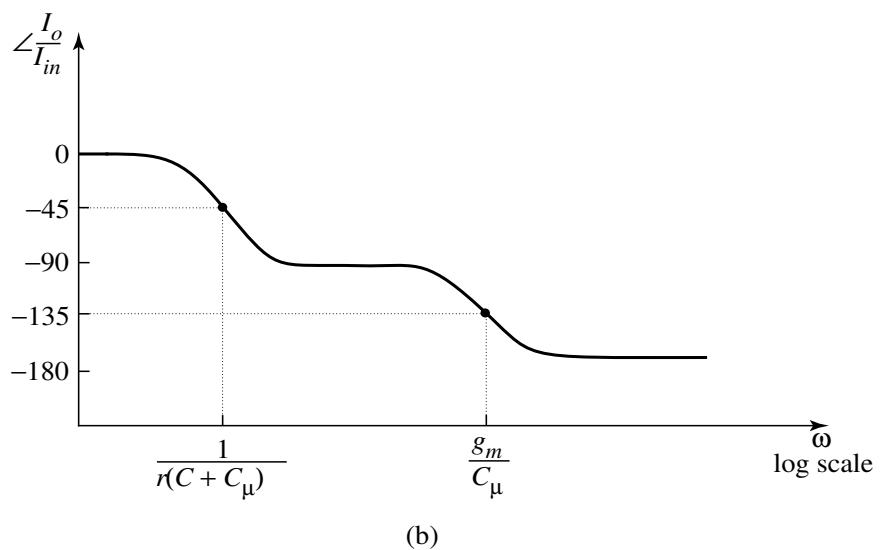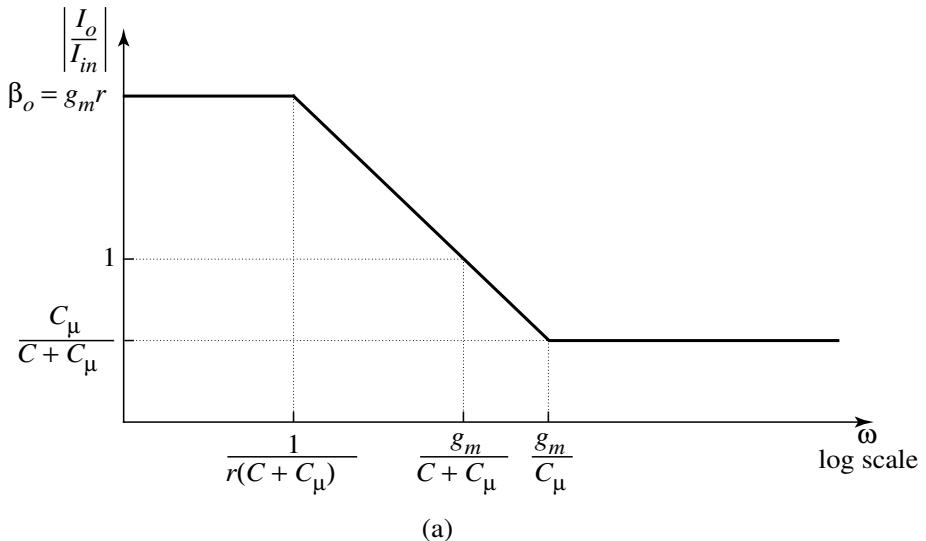


- Frequency at which current gain is reduced to 0 dB is defined at f_T :

$$f_T = \left(\frac{1}{2\pi} \right) \frac{g_m}{(C_\pi + C_\mu)}$$

Gain-Bandwidth Product

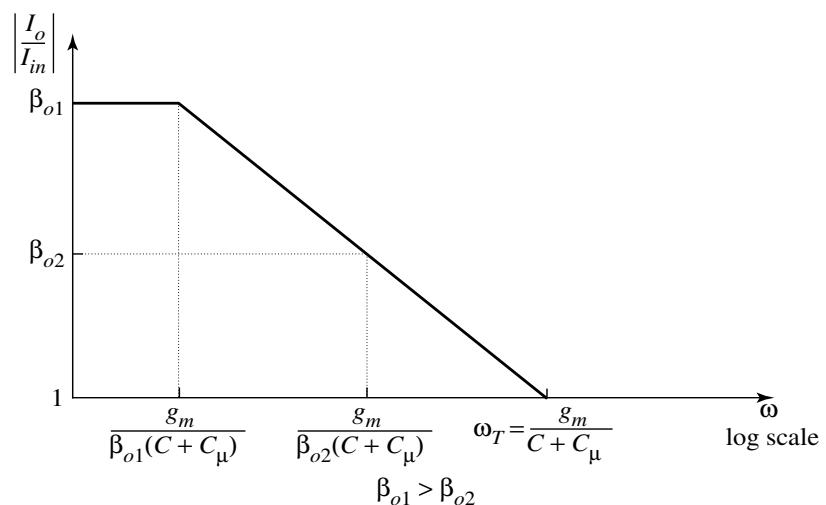- When we increase β_o we increase r_π BUT we decrease the pole frequency---> Unity Gain Frequency remains the same



Examine how transistor parameters affect ω_T


- Recall

$$C_\pi = C_{je} + g_m \tau_F$$

- The unity gain frequency is

$$\omega_T = \frac{I_C / V_{th}}{(I_C / V_{th}) \tau_F + C_{je} + C_\mu}$$
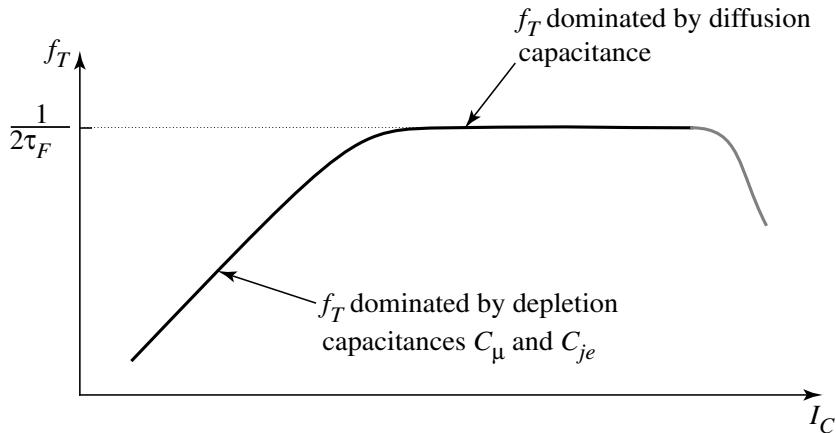
$$\omega_T = \frac{I_C / V_{th}}{(I_C / V_{th})\tau_F + C_{je} + C_\mu}$$



- At low collector current f_T is dominated by depletion capacitances at the base-emitter and base-collector junctions
- As the current increases the diffusion capacitance, $g_m \tau_F$, becomes dominant
- Fundamental Limit for the frequency response of a bipolar transistor is set by

$$\tau_F = \frac{W_B^2}{2 D n, p}$$

To Increase f_T

- High Current - Diffusion capacitance limited - Shrink basewidth
- Low Current - Depletion capacitance limited - Shrink emitter area and collector area - (geometries)

MIT OpenCourseWare
<http://ocw.mit.edu>

6.012 Microelectronic Devices and Circuits
Spring 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.