

# Lecture 26

## Analyzing Complex Amplifiers

### Outline


- Two-port hand analysis
- Examples
- What's Next?

# Multi-Stage Amplifier Analysis


- Draw circuit such that signal stages and biasing devices can be easily identified.
- Identify signal path and establish amplifier parameters.
- Determine function of all other transistors-usually current or voltage sources.
- Find high impedance nodes to estimate frequency response.

# Can now understand more complex circuits?



## Examples:

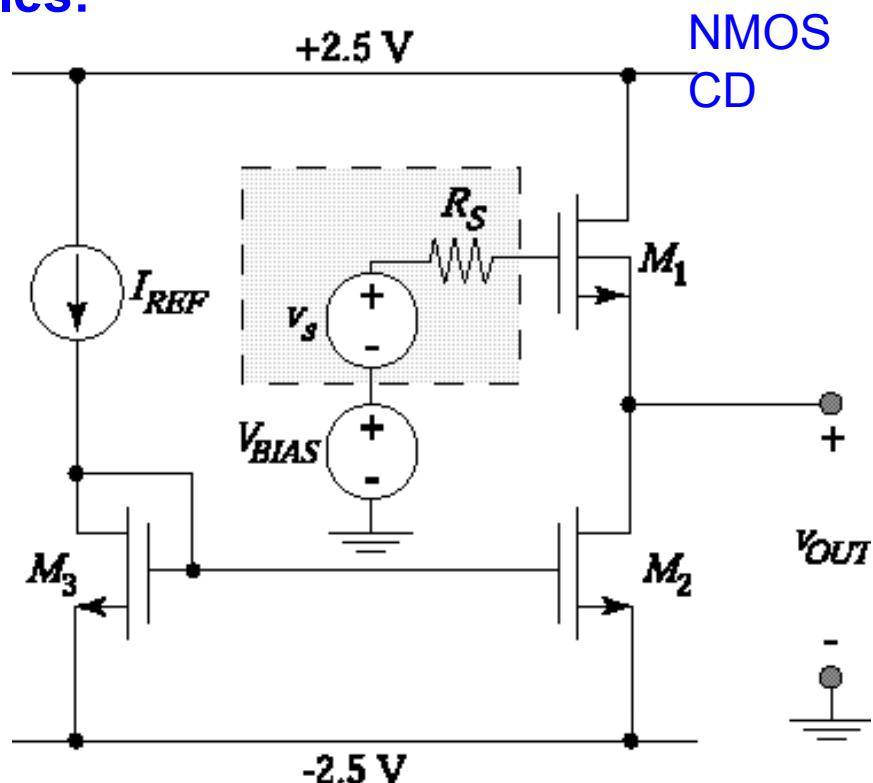


# NMOS CS - PMOS CD

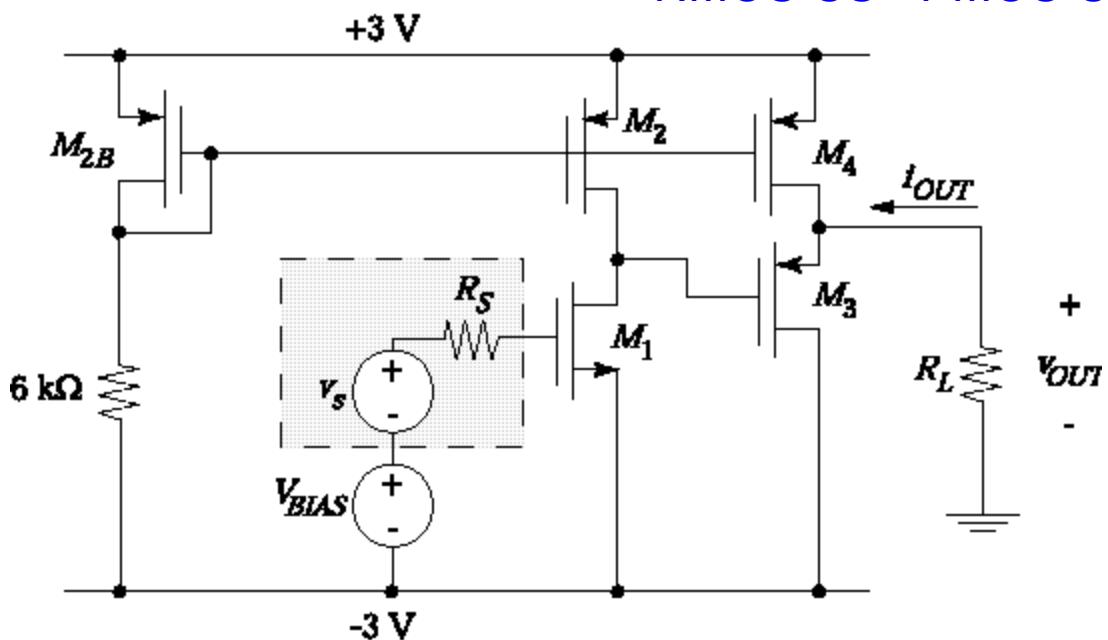
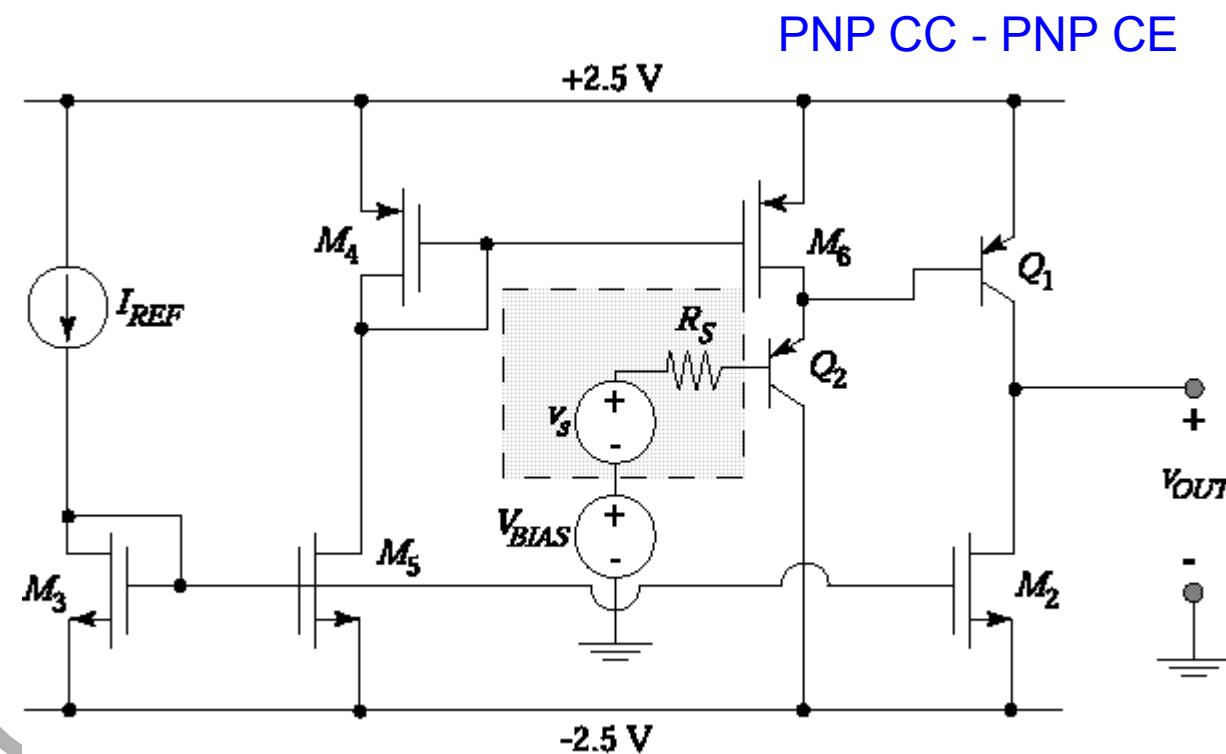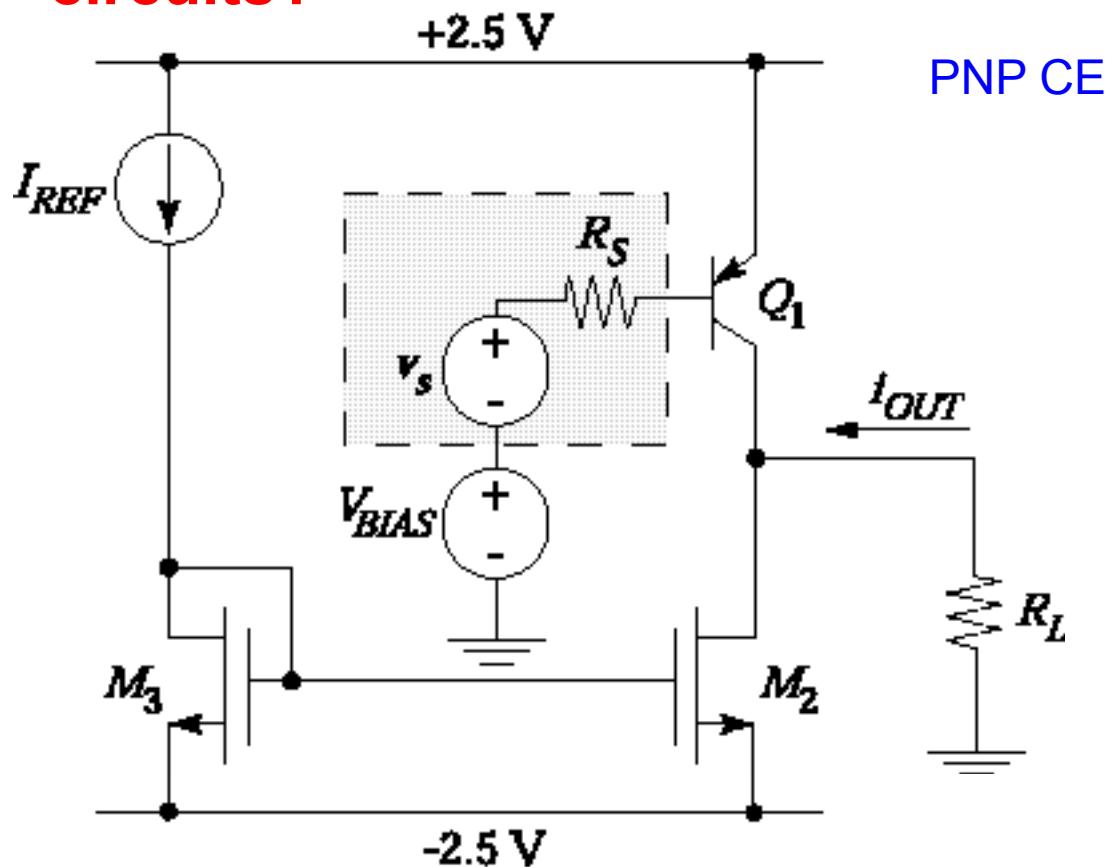
## Can now understand more complex circuits?



# BiCMOS Voltage Amplifier

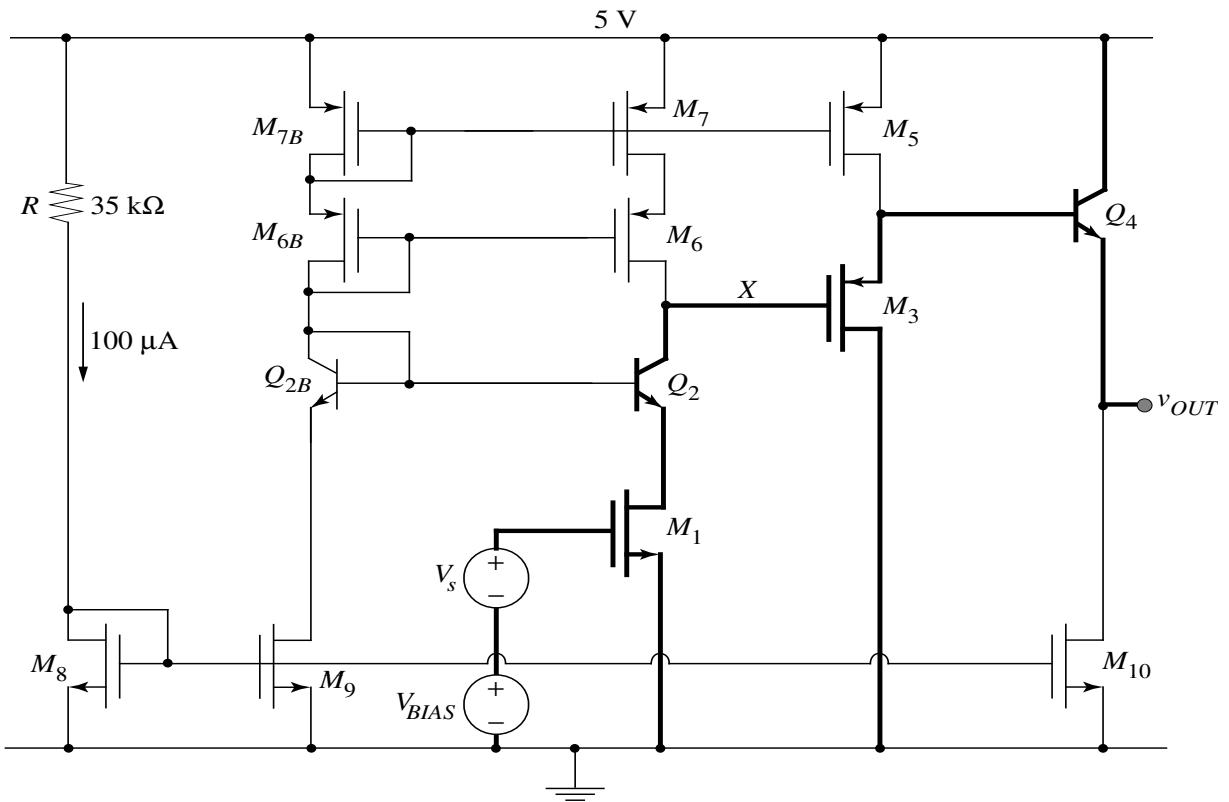


## Qualitative View

- Identify signal path and establish amplifier parameters
- CS-CB-CD-CC - Good voltage amplifier
- Determine function of all other transistors-usually current or voltage sources
- Find high impedance nodes to estimate frequency response

# Small Signal Voltage Gain Cascode+Voltage Buffer


- Cascode-CS-CB
- $R_{in} = \infty$

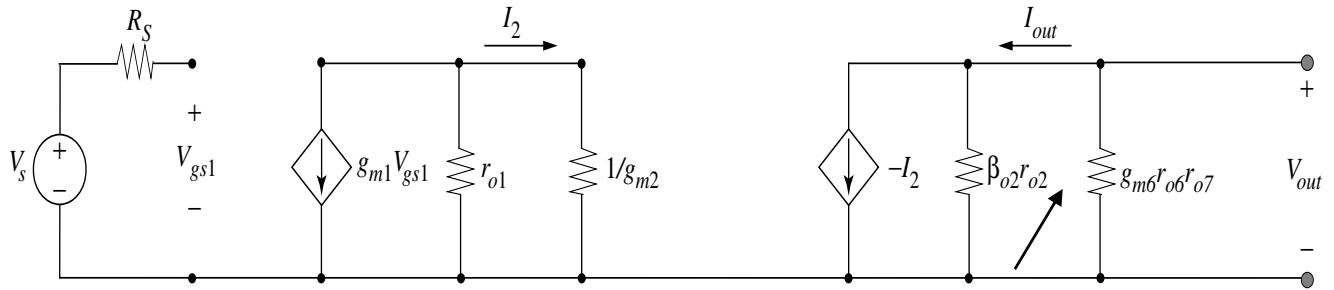

$$R_{out} = \beta_{o2} r_{o2} \| g_{m6} r_{o6} r_{o7}$$

$$A_{vo} = \frac{v_{out}}{v_s} = -g_{m1} (\beta_{o2} r_{o2} \| g_{m6} r_{o6} r_{o7}) \approx \frac{v_{out}}{v_s}$$


- Voltage buffer CD-CC

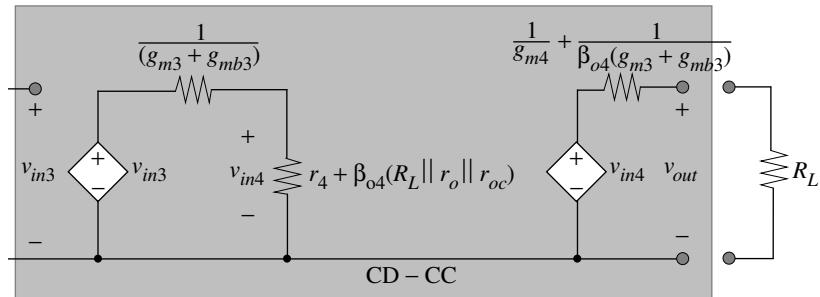

$$R_{in}' \rightarrow \infty \quad A_v \approx 1$$

$$R_{out} = \frac{1}{g_{m4}} + \frac{1}{\beta_{o4}(g_{m3} + g_{mb3})}$$

# Frequency Response

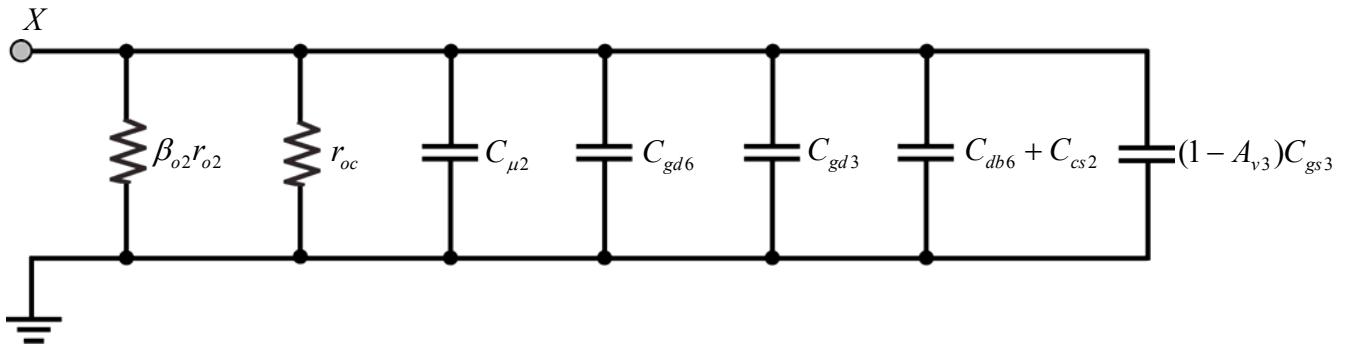


$$A_{vo} = \frac{V_{out2}}{V_s} = -g_{m1} (\beta_{o2}r_{o2} \| g_{m6}r_{o6}r_{o7}) \approx \frac{V_{out}}{V_s}$$

$$\omega_{3dB} = \left| \frac{1}{(\beta_{o2}r_{o2} \| g_{m6}r_{o6}r_{o7})} \right|$$

$$\left[ \frac{1}{(C_{\mu 2} + C_{gd6} + C_{gd3} + (1 - A_v)C_{gs3}) + C_{db6} + C_{cs2}} \right]$$

# Bode Plot

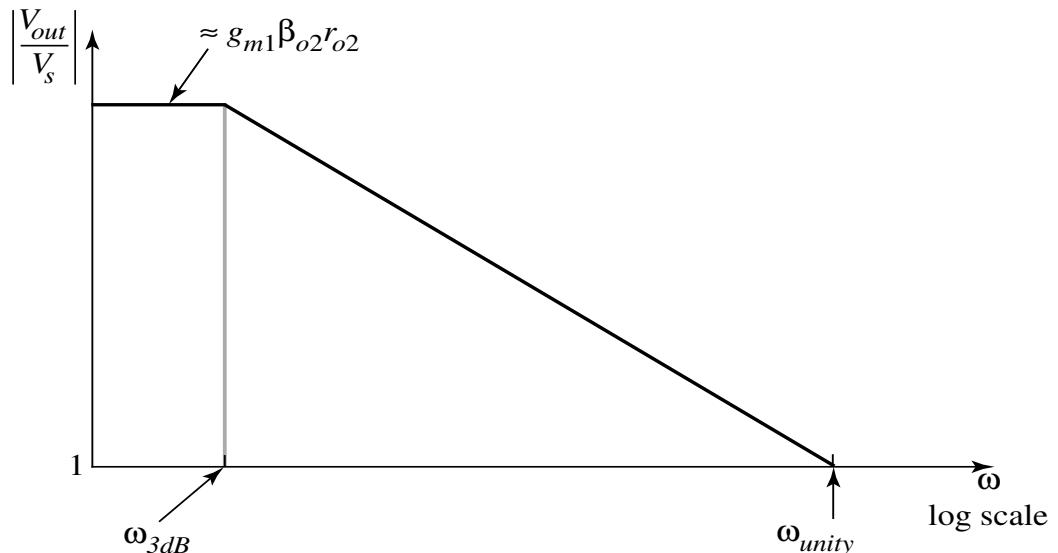

$$\omega_{3dB} = \sqrt{\frac{1}{(\beta_{o2} r_{o2} \| g_{m6} r_{o6} r_{o7})}}$$

$$= \sqrt{\frac{1}{(C_{\mu 2} + C_{gd6} + C_{gd3} + (1 - A_v C_{gs3}) C_{gs3} + C_{db6} + C_{cs2})}}$$


$$\omega_{unity} = A_{vo} * \omega_{3dB}$$

$$= \frac{g_{m1}}{(C_{\mu 2} + C_{gd6} + C_{gd3} + (1 - A_v C_{gs3}) C_{gs3} + C_{db6} + C_{cs2})}$$

# Large Signal DC Analysis

- Assume  $V_{BE} = 0.7V$

$$V_{GS} = 1.5V$$

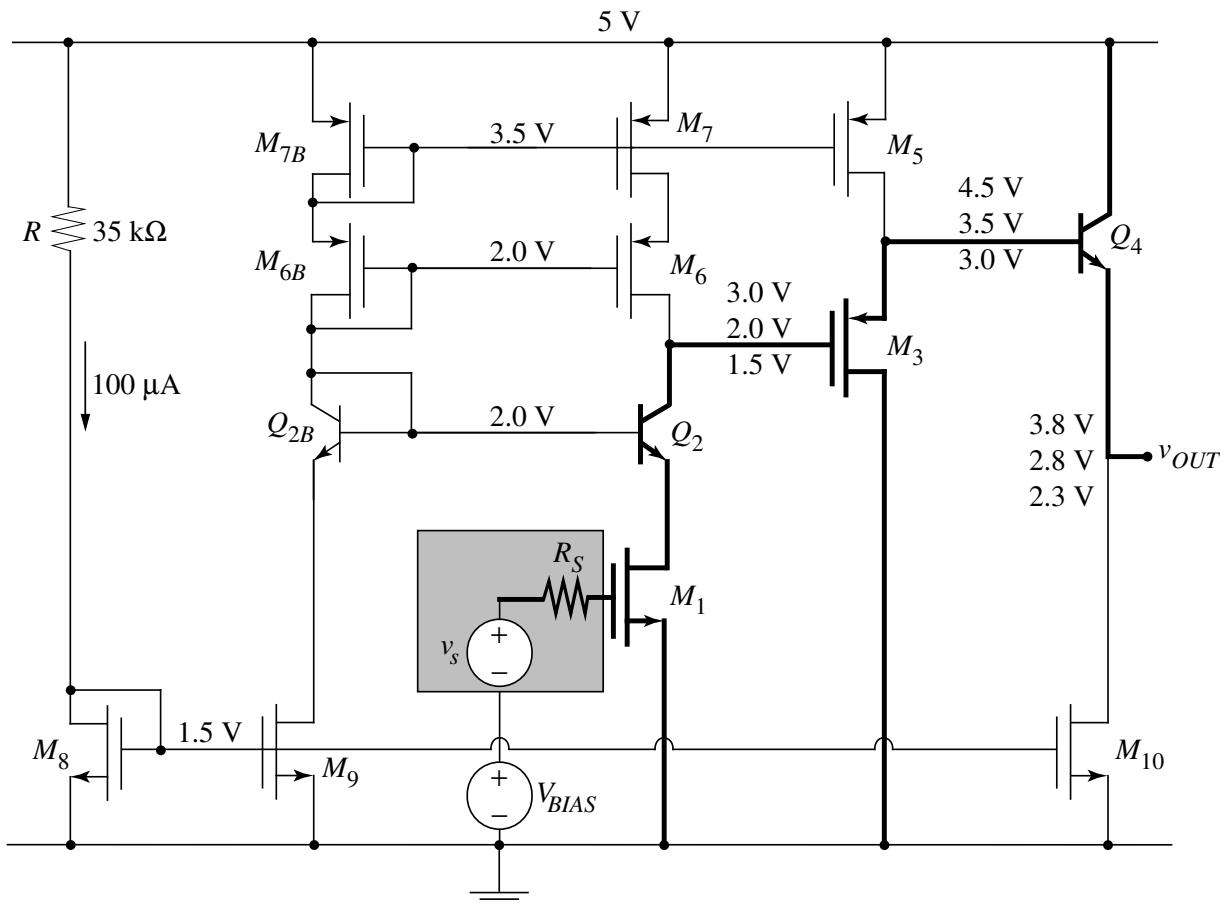

# Wrap-up of 6.012

6.012: Introductory subject to *microelectronic* devices and circuits

- MICROELECTRONIC DEVICES
  - Semiconductor physics: **electrons/holes and drift/diffusion, carrier concentration controlled by doping or electrostatically**
  - Metal-oxide-semiconductor field-effect transistors (MOSFETs): **drift of carriers in inversion layer**
  - Bipolar junction transistors (BJTs): **minority carrier diffusion**
- MICROELECTRONIC CIRCUITS
  - Digital circuits (mainly CMOS): **no static power dissipation; power ↓, delay ↓ & density ↑ as W & L ↓**
  - Analog circuits (BJT and CMOS):  **$f_t \uparrow$  and  $g_m \uparrow$  as L ↓; however,  $A_{vomax} \downarrow$  as L ↓**

## Follow-on Courses

- **6.152J** — Microelectronics Processing Technology
- **6.720J** — Integrated Microelectronic Devices
- **6.301** — Solid State Circuits
- **6.374** — Analysis and Design of Digital ICs
- **6.775** — Design of Analog MOS ICs

MIT OpenCourseWare  
<http://ocw.mit.edu>

6.012 Microelectronic Devices and Circuits  
Spring 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.