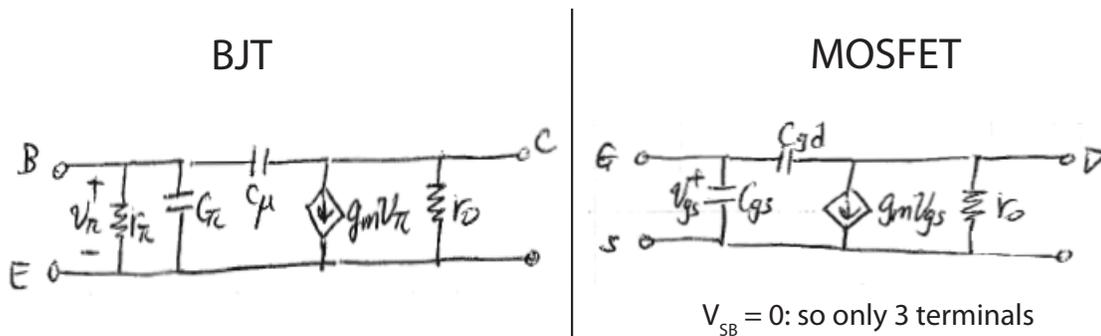


## Recitation 21: Intrinsic Frequency Response of CS & CE Amplifier



Yesterday, we discussed the intrinsic frequency response of the CE Amplifier. Since there is an analogy between MOSFET & BJT, today we will look at the intrinsic frequency response of a CS Amplifier and compare them.

### Small Signal Model





BJT	MOSFET
$C_\pi = C_{je} + C_b = C_{je} + g_m \tau_F = C_{je} + g_m \left( \frac{w_B^2}{2D_n} \right)$	$C_{gs} = \frac{2}{3} w L C_{ox} + w C_{ov}$
$C_\mu$ : depletion capacitance only	$C_{gd} = w C_{ov}$

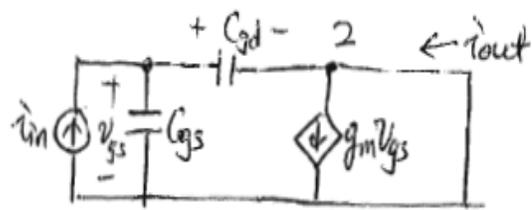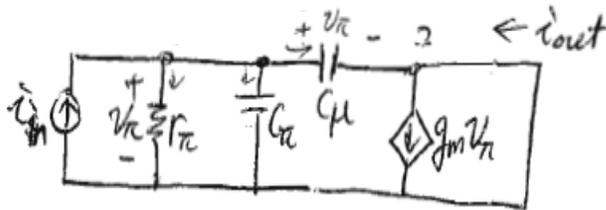**Intrinsic Frequency Response:**  $R_s \rightarrow \infty$   $R_L = 0$





BJT	MOSFET
Node 1: $i_{in} = \frac{v_{\pi}}{\gamma_{\pi}} + j\omega C_{\pi} \cdot v_{\pi} + j\omega C_{\mu} v_{\pi}$	Node 1: $i_{in} = j\omega C_{gs} \cdot V_{gs} + j\omega C_{gd} V_{gs}$
Node 2: $i_{out} = g_m v_{\pi} - j\omega C_{\mu} v_{\pi}$	Node 2: $i_{out} = g_m v_{\pi} - j\omega$
$\frac{i_{out}}{i_{in}} = \frac{g_m \gamma_{\pi} \left(1 - \frac{j\omega C_{\mu}}{g_m}\right)}{1 + j\omega \gamma_{\pi} (C_{\pi} + C_{\mu})}$	$\frac{i_{out}}{i_{in}} = \frac{g_m - j\omega C_{gd}}{j\omega (C_{gs} + C_{gd})}$
$= \frac{\beta_o \left(1 - \frac{j\omega C_{\mu}}{g_m}\right)}{1 + j\omega \gamma_{\pi} (C_{\pi} + C_{\mu})}$	

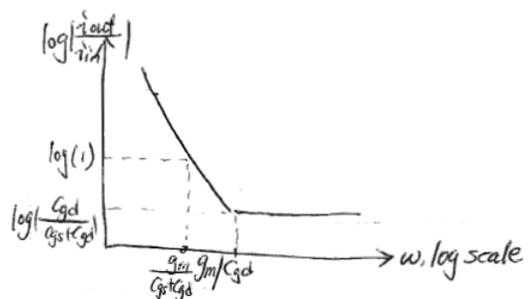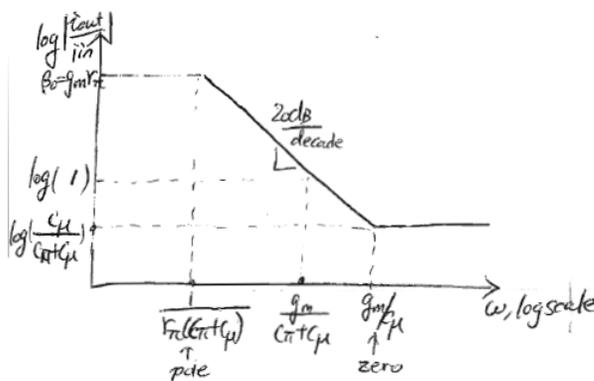

## Unit Gain Frequency, $f_T$

BJT	MOSFET
$f_T = \frac{1}{2\pi} \omega_T = \frac{1}{2\pi} \frac{g_m}{C_\mu + C_\pi}$ <p>Frequency at which the current gain is reduced to 1(0 dB)</p> <p>This is obtained by:</p> $\left  \frac{i_{out}}{i_{in}} \right  = \left  \frac{\beta_o \left( 1 - \frac{j\omega C_\mu}{g_m} \right)}{1 + j\omega \gamma_\pi (C_\mu + C_\pi)} \right  = 1$ <p>ignoring the zero on top, <math>\because \frac{g_m}{C_\mu} \gg \omega_T</math></p> $\left  \frac{\beta_o}{1 + j\omega \gamma_\pi (C_\mu + C_\pi)} \right  = 1$ $\because \omega_T \gg \frac{1}{\gamma_\pi (C_\mu + C_\pi)} \quad \therefore \omega_T \gamma_\pi (C_\mu + C_\pi) \gg 1$ $\left  \frac{\beta_o}{j\omega \gamma_\pi (C_\mu + C_\pi)} \right  = 1 \implies \omega_T = \frac{g_m}{C_\mu + C_\pi}$	$f_T = \frac{1}{2\pi} \frac{g_m}{C_{gs} + C_{gd}}$ <p>(this can be derived similar to the BJT case)</p> <p>Physical interpretation:</p> $f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$ $\simeq \frac{1}{2\pi} \frac{g_m}{C_{gs}} \simeq \frac{1}{2\pi} \frac{w/L \mu_n C_{ox} (V_{GS} - 1)}{2/3 w L C_{ox}}$ $\frac{1}{2\pi} \frac{3 \mu_n (V_{GS} - V_T)}{2 L^2} = \frac{3 \mu_n V_{D,SAT}}{2 L^2} \frac{1}{2\pi}$ <p><math>\frac{\mu_n V_{DSAT}}{L} \sim</math> velocity of carrier</p> $\frac{\mu_n V_{DSAT}}{L} / L \sim 1/\tau_T = \tau_T = L / \text{velocity}$ <p><math>\tau_T</math> is transit time from source to drain</p>
$f_T = \frac{1}{2\pi} \frac{I_c/V_{th}}{I_c/V_{th} \cdot \tau_F} + C_{je} + C_\mu \quad (\because g_m = \frac{I_c}{V_{th}})$	<p><math>f_T</math> is independent of <math>V</math>.</p> <p>For high frequency performance, NMOS &gt; PMOS.</p> <p>Scale <math>L</math> as short as possible</p>

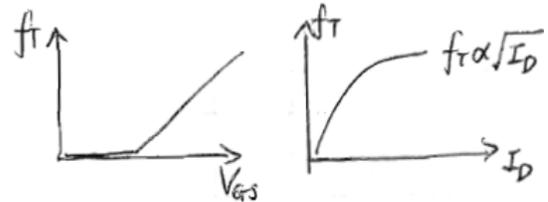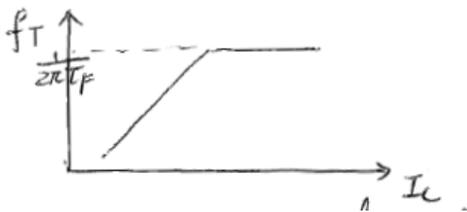

At low  $I_c$ ,  $f_T$  is dominated by depletion capacitances at Base-emitter and base collector junctions ( $C_{je}$  and  $C_{\mu}$ ). As  $I_c \uparrow$ , diffusion capacitance  $g_m \tau_F \uparrow$ , and becomes dominant.

Fundamental limit for frequency response

$$\tau_F = \frac{w_B^2}{2D_{n,p}}$$

To increase  $f_T$

- high  $I_c$  = diffusion cap. limited  $\implies$  shrink base width.
- low  $I_c$  = depletion cap. limited  $\implies$  shrink device area

Another note for MOSFET: the current gain  $\rightarrow \infty$  at  $w = 0$ .

This is because of gate oxide, DC input current = 0.  
 MOSFET not used as current amplifier at low frequency (input resistance too high)

MIT OpenCourseWare  
<http://ocw.mit.edu>

6.012 Microelectronic Devices and Circuits  
Spring 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.