

MIT OpenCourseWare
<http://ocw.mit.edu>

6.013/ESD.013J Electromagnetics and Applications, Fall 2005

Please use the following citation format:


Markus Zahn, Erich Ippen, and David Staelin, *6.013/ESD.013J Electromagnetics and Applications, Fall 2005*. (Massachusetts Institute of Technology: MIT OpenCourseWare). <http://ocw.mit.edu> (accessed MM DD, YYYY). License: Creative Commons Attribution-Noncommercial-Share Alike.

Note: Please use the actual date you accessed this material in your citation.

For more information about citing these materials or our Terms of Use, visit:
<http://ocw.mit.edu/terms>

Quiz 2 - Solutions

Problem 1

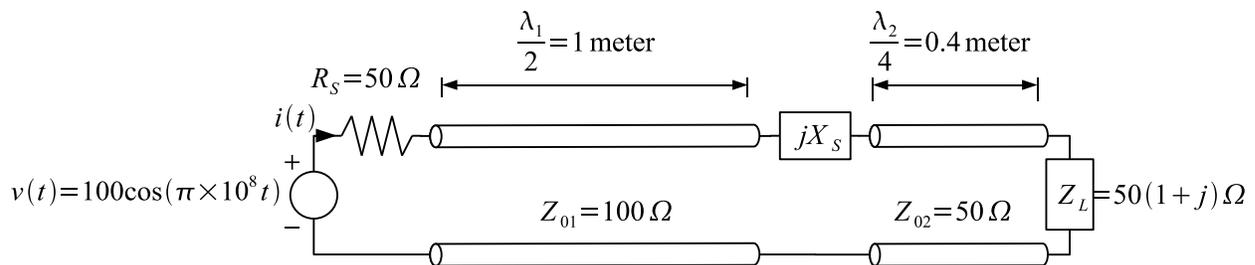

A transmission line system incorporates two transmission lines with characteristic impedances of $Z_{01} = 100 \Omega$ and $Z_{02} = 50 \Omega$ as illustrated above. A voltage source is applied at the left end, $v(t) = 100 \cos(\pi \times 10^8 t)$. At this frequency, line 1 has length of $\lambda_1/2 = 1$ meter and line 2 has length of $\lambda_2/4 = 0.4$ meter, where λ_1 and λ_2 are the wavelengths along each respective transmission line. The two transmission lines are connected by a series reactance jX_s , and the end of line 2 is loaded by impedance $Z_L = 50(1 + j) \Omega$. The voltage source is connected to line 1 through a source resistance $R_s = 50 \Omega$.

A

Question: What are the speeds c_1 and c_2 of electromagnetic waves on each line?

Solution: Using the appropriate values of $f = 50$ MHz, $\lambda_1 = 2$ m, and $\lambda_2 = 1.6$ m together with the expression $f\lambda = c$, we find that

$$c_1 = 5 \times 10^7 (2) = 10^8 \text{ m/s, and}$$

$$c_2 = 5 \times 10^7 (1.6) = 8 \times 10^7 \text{ m/s.}$$

B

Question: It is desired that X_s be chosen so that the source current $i(t) = I_0 \cos(\pi \times 10^8 t)$ is in phase with the voltage source. What is X_s ?

Solution: We have that

$$\frac{Z_L}{Z_{02}} = 1 + j,$$

$$Z_n \left(z = -\frac{\lambda_2}{4} \right) = \frac{1}{1 + j} = \frac{1 - j}{2}, \text{ and}$$

$$Z \left(z = -\frac{\lambda_2}{4} \right) = 25(1 - j).$$

However, $jX_s + 25(1 - j)$ must be real, hence $X_s = 25 \Omega$.

C

Question: For the value of X_s in part B, what is the peak amplitude I_0 of the source current $i(t)$?

Solution:

$$Z \left(z = -\frac{\lambda_2}{4} \right) = 25 \Omega \implies Z \left(z = -\frac{\lambda_2}{4} - \frac{\lambda_1}{2} \right) = 25 \Omega$$

Hence,

$$i(t) = \frac{v(t)}{75 \Omega} = \frac{4}{3} \cos(\pi \times 10^8 t) \implies I_0 = \frac{4}{3} \text{ Amperes.}$$

Problem 2

A parallel plate waveguide is to be designed so that only TEM modes can propagate in the frequency range $0 < f < 2$ GHz. The dielectric between the plates has a relative dielectric constant of $\epsilon_r = 9$ and a magnetic permeability of free space μ_0 .

A

Question: What is the maximum allowed spacing d_{\max} between the parallel plate waveguide plates?

Solution:

$$\omega_{co,n} = \frac{n\pi c}{d} = 2\pi f_{co,n} \implies f_{co,n} = \frac{nc}{2d} \text{ with } c = 10^8 \text{ m/s}$$

The lowest cut-off frequency occurs when $n = 1$, therefore

$$f_{co,1} = \frac{c}{2d} > 2 \text{ GHz} \implies d < \frac{c}{4 \times 10^9} = \frac{10^8}{4 \times 10^9} = \frac{1}{40} \text{ m.}$$

Hence $d < 2.5$ cm.


B

Question: If the plate spacing is 2.1 cm, and $f = 10$ GHz, what TE_n and TM_n modes will propagate?

Solution:

$$f_{co,n} = \frac{nc}{2d} < 10 \text{ GHz} \implies n < \frac{2d(10^{10})}{c} = \frac{2(0.021)10^{10}}{10^8} \implies n < 4.2$$

It follows then that we have the propagating modes: TE₁, TE₂, TE₃, TE₄; and TM₁, TM₂, TM₃, TM₄.

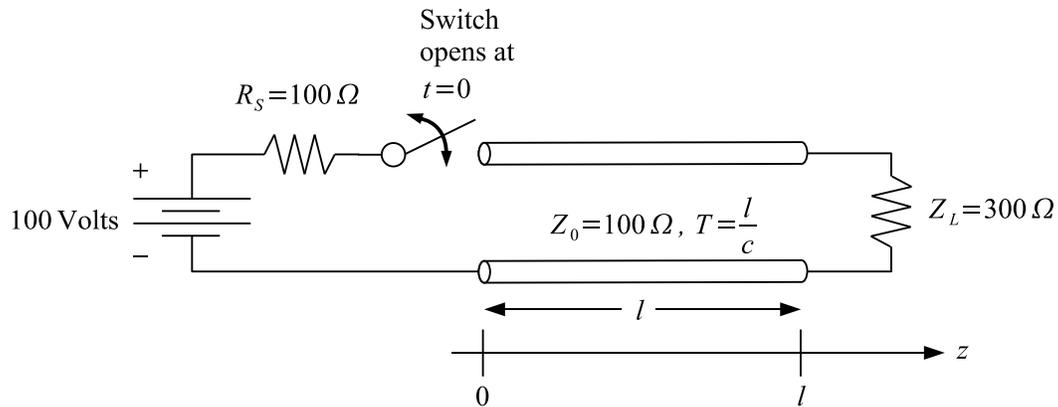Problem 3

A transmission line of length l , characteristic impedance $Z_0 = 100 \Omega$, and one-way time of flight $T = l/c$ is connected at $z = 0$ to a 100 volt DC battery through a series source resistance $R_s = 100 \Omega$ and a switch. The $z = l$ end is loaded by a 300Ω resistor.

A

Question: The switch at the $z = 0$ end has been closed for a very long time so that the system is in the DC steady state. What are the positive and negative traveling wave voltage amplitudes $V_+(z - ct)$ and $V_-(z + ct)$?

Solution:

$$v(z, t) = V_+ + V_- = 75 \text{ Volts}$$

$$Z_0 i(z, t) = V_+ - V_- = 25 \text{ Volts}$$

Solving for V_+ and V_- yields

$$V_+ = 50 \text{ Volts,}$$

$$V_- = 25 \text{ Volts.}$$


B

Question: With the system in the DC steady state, the switch is suddenly opened at time $t = 0$.

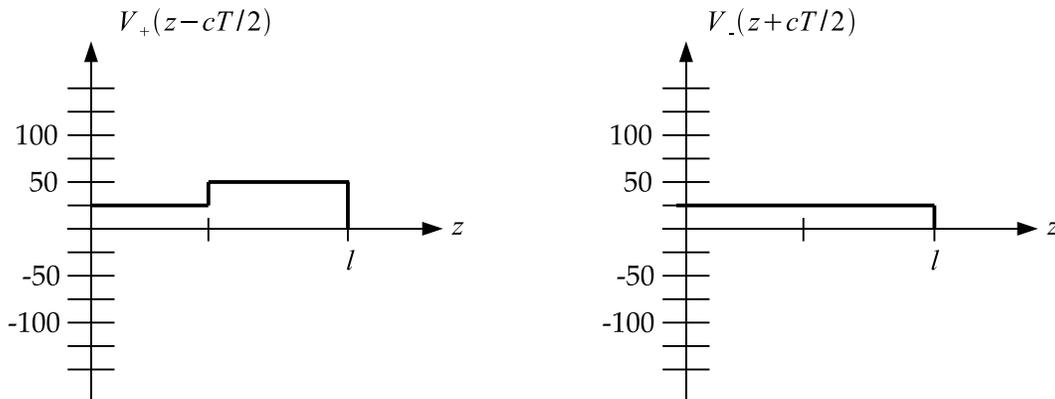I. Plot the positive and negative traveling wave voltage amplitudes, $V_+(z - ct)$ and $V_-(z + ct)$, as a function of z at time $t = T/2$.

Solution:

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{300 - 100}{300 + 100} = \frac{200}{400} = \frac{1}{2}, \Gamma_s = +1.$$



II. Plot the transmission line voltage $v(z, t)$ as a function of z at time $t = T/2$.

Solution:

