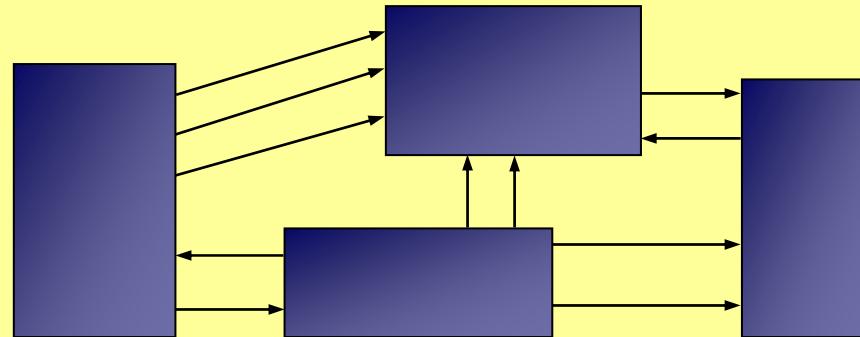


# TRANSIENT SIGNALS IN COMPUTERS


## Ideal World:

- Only 1's and 0's
- Instantaneous links


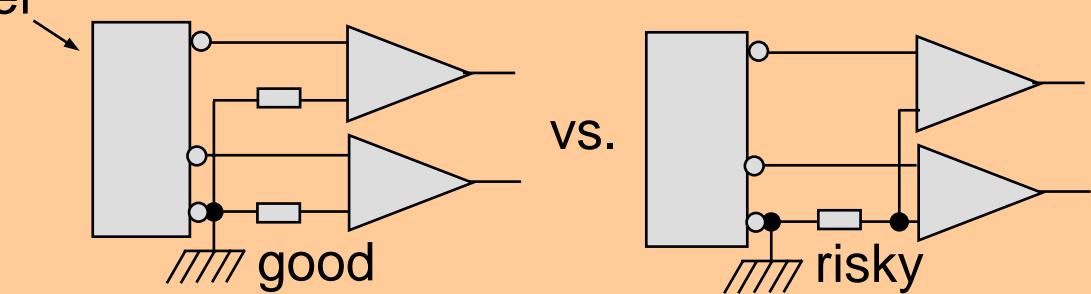
## Reality:

- Voltages exhibit propagation delay, decay, reflections
- Spurious transients can superimpose to flip bits erroneously
- RFI generated and picked up by wires can flip bits
- Ground loops matter



# TEM LINE THEVENIN EQUIVALENT


**Example: Given  $V_s(t)$ :**

$$v(z, t) = v_+(t - \frac{z}{c}) + v_-(t + \frac{z}{c})$$

$$i(z, t) = \frac{1}{Z_o} [v_+(t - \frac{z}{c}) - v_-(t + \frac{z}{c})]$$

Assume  $v_- = 0$  (no other sources)

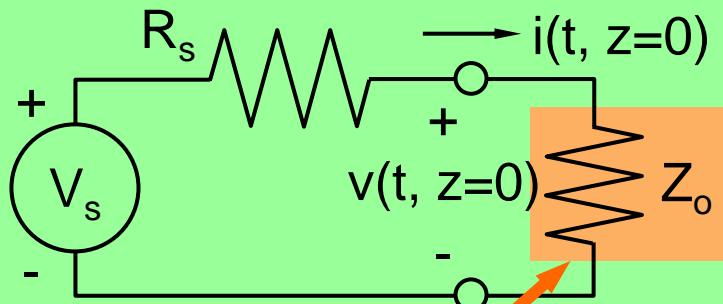Then  $v(t, z=0) = Z_o i(t, z=0)$  yields equivalent circuit



**Solution at terminals:**

$$v_+(t, z=0) = V_s(t) \frac{Z_o}{Z_o + R_s} \text{ (voltage divider equation)}$$

**Solution for all  $t, z$ :**

$$v_+(t, z) = V_s(t - \frac{z}{c}) \frac{Z_o}{Z_o + R_s} \text{ (forward propagating wave only)}$$


# TEM LINE THEVENIN EQUIVALENT

## Voltages at an Open Circuit:

$$i(t, D) = Y_o[v_+(t, D) - v_-(t, D)] = 0 \text{ (open circuit)}$$


$$\Rightarrow v_-(t, D) = v_+(t, D)$$
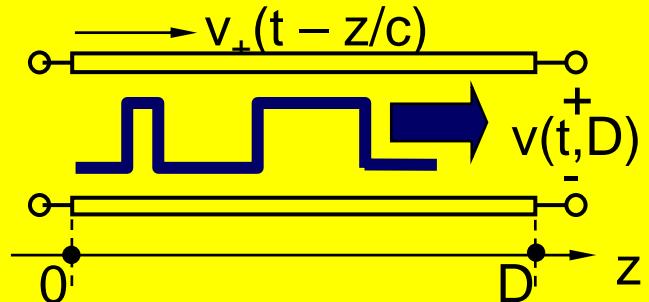
$$\Rightarrow v(t, D) = v_+(t, D) + v_-(t, D) = 2v_+(t, D)$$


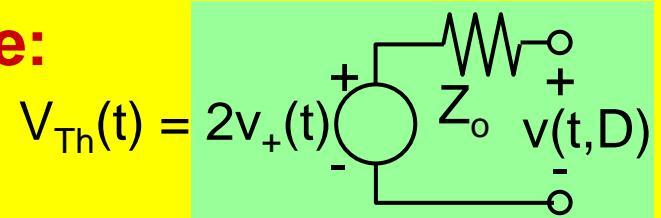
## Thevenin Equivalent for TEM source:

$$v_{\text{open circuit}}(t) = 2v_+(t) = V_{\text{Th}}(t)$$



## Example—Resistive Load:


$$\text{At } z = D: v_-(t) = v_L(t) - v_+(t)$$

$$\text{But: } v(t) = 2v_+(t) \frac{R}{R + Z_o}$$

$$\text{Thus: } v_-(t) = v_+(t) \frac{R - Z_o}{R + Z_o} = v_+(t) \Gamma$$


$$\text{Define: } \Gamma = \text{"reflection coefficient"} = v_-/v_+ \text{ at load} = \frac{R_n - 1}{R_n + 1}$$

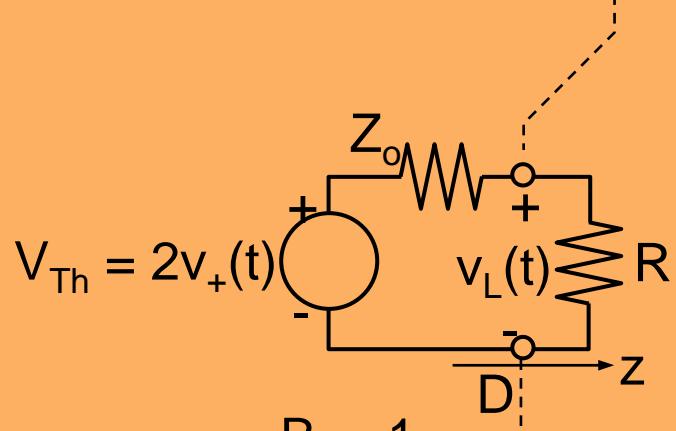( $= 0$  if  $R = Z_o$ ,  $= -1$  if  $R = 0$ , and  $= +1$  if  $R = \infty$ )



# CAPACITIVELY TERMINATED TEM LINE


## Example: Capacitive Load

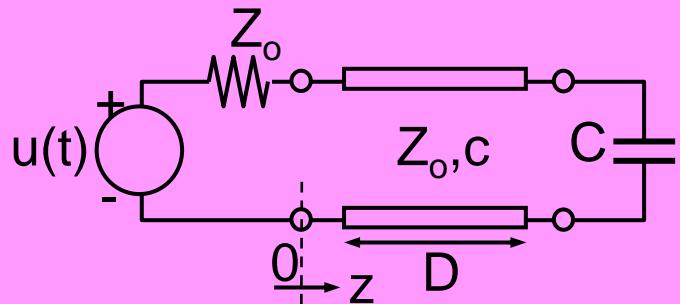


$$V_{Th} = 2v_+(t, D) = u\left(t - \frac{D}{c}\right)$$

$$i(z, t) = Y_0 [v_+\left(t - \frac{z}{c}\right) - v_-\left(t + \frac{z}{c}\right)]$$

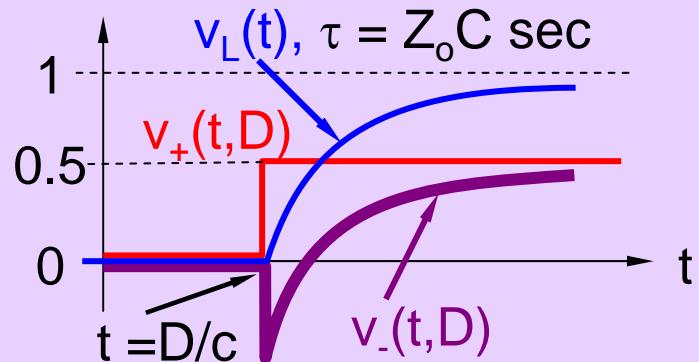$t = 0+$ , short-circuit response  
 $t \rightarrow \infty$ , open-circuit response



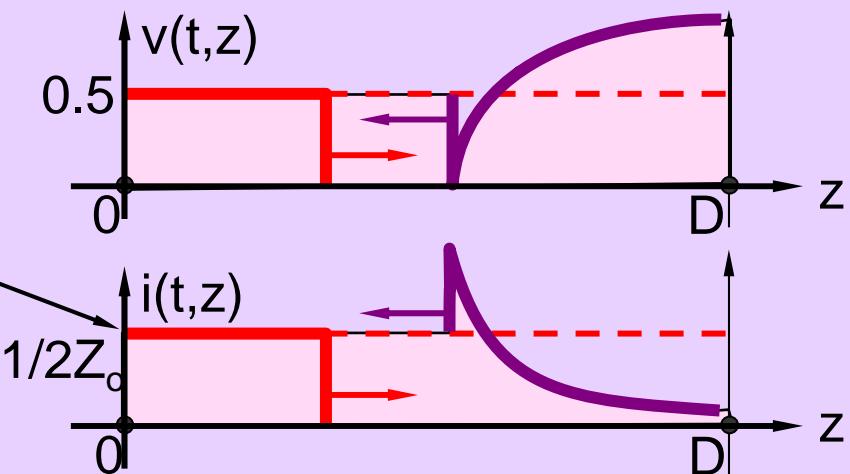
$$v_L = v_- + v_+ \text{ at the load} \Rightarrow v_-(t, D) = v_L(t, D) - v_+(t, D)$$





# DIODE-TERMINATED TEM LINE


Example -- Logic Circuit:

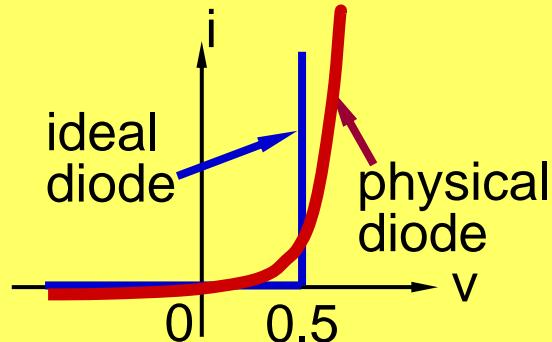

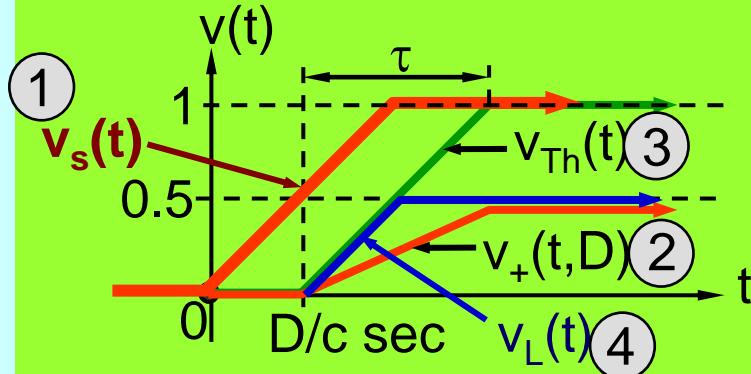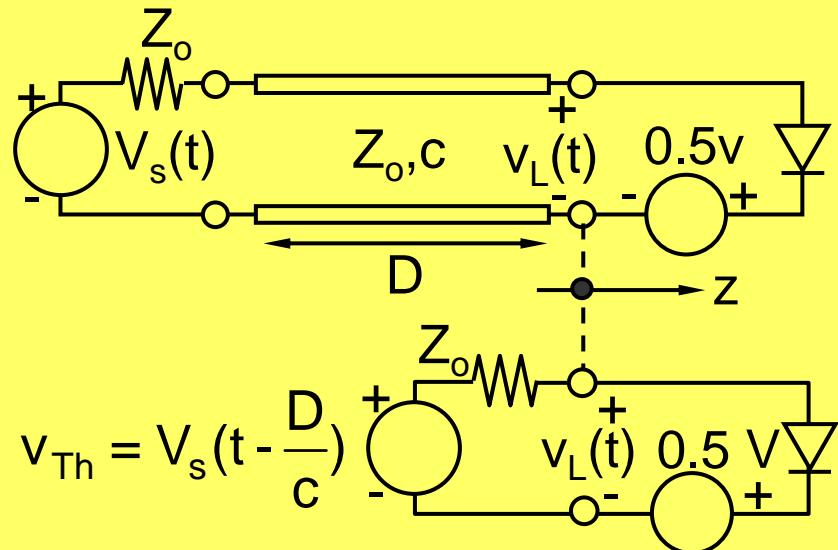Let  $v_s(t) = 1\text{-volt ramped step}$



$$v_L(t) = v_+(t, D) + v_-(t, D)$$

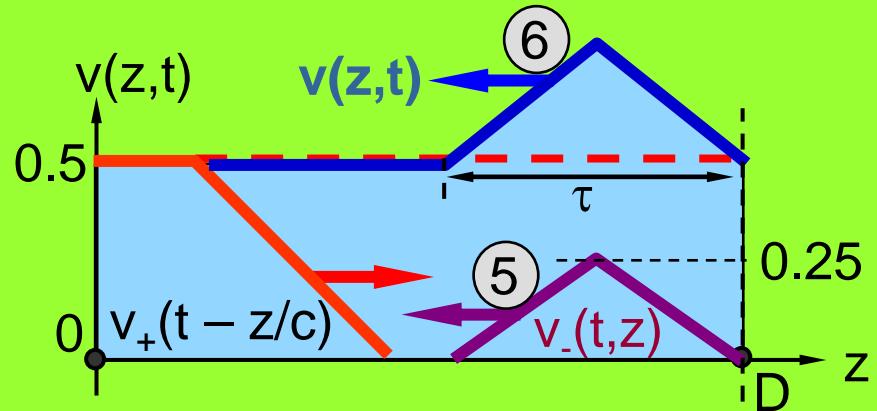

# INITIAL CONDITIONS


**Example – charged TEM line:**

$$v(z,t) = v_+(z - ct) + v_-(z + ct)$$



$$i(z,t) = \frac{1}{Z_o} [v_+(z - ct) - v_-(z + ct)]$$

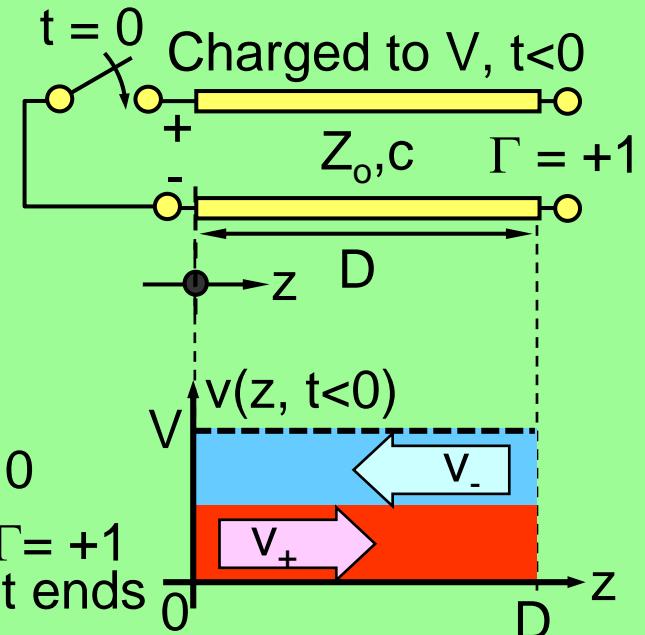**Initial voltage and currents:**

$$\begin{aligned} v_+(z,t) &= \frac{1}{2} [v(z,t) + Z_o i(z,t)] \\ v_-(z,t) &= \frac{1}{2} [v(z,t) - Z_o i(z,t)] \end{aligned} \quad \Rightarrow \quad i(t < 0) = 0$$




**Subsequent voltages and currents:**

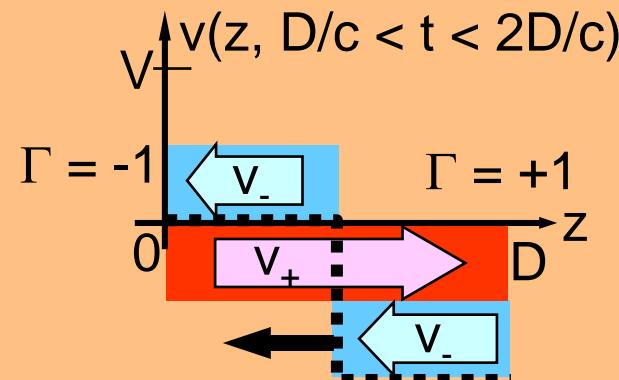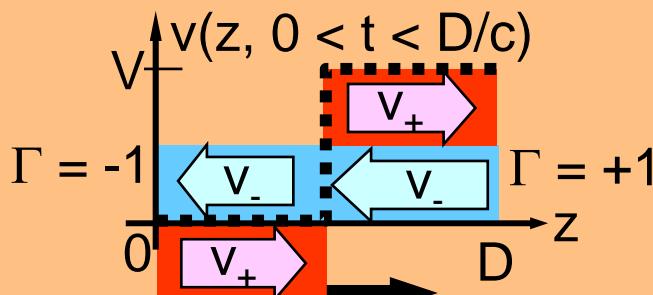

Lossless system,  
rattles forever


# INITIAL CONDITIONS

Arbitrary initial conditions:

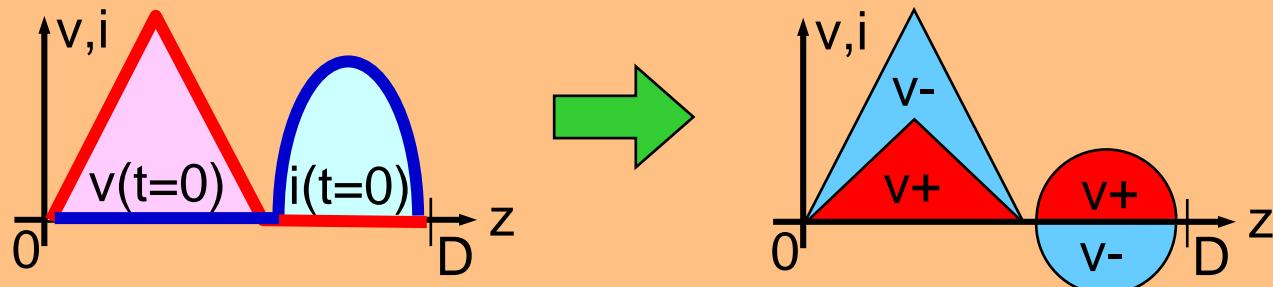


Arbitrary circuits:

Put switches anywhere

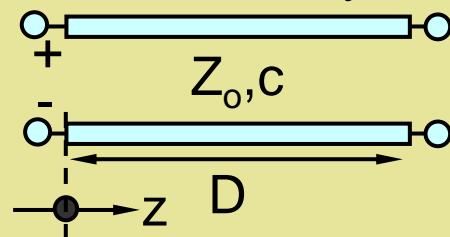

# LIGHTNING STRIKE EXAMPLE

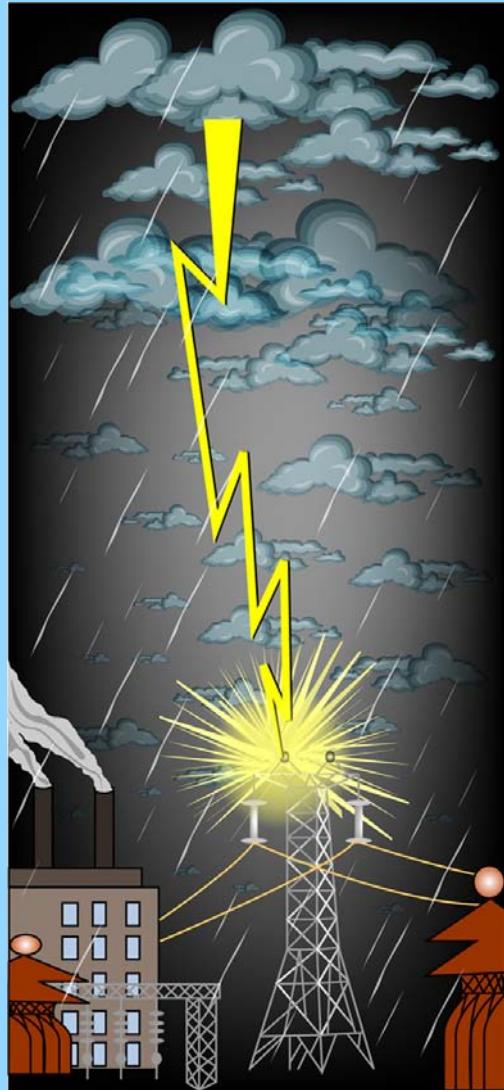

Lightning strikes the midpoint  
What happens?


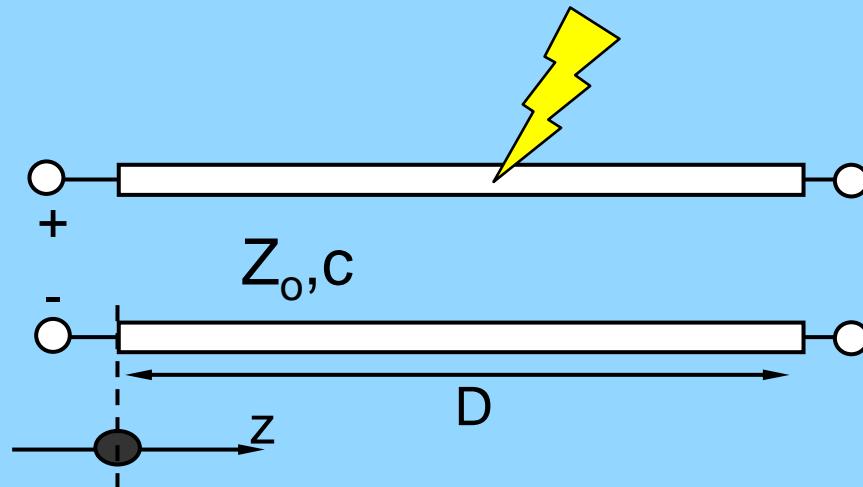


Figure by MIT OpenCourseWare.

# LIGHTNING STRIKE EXAMPLE

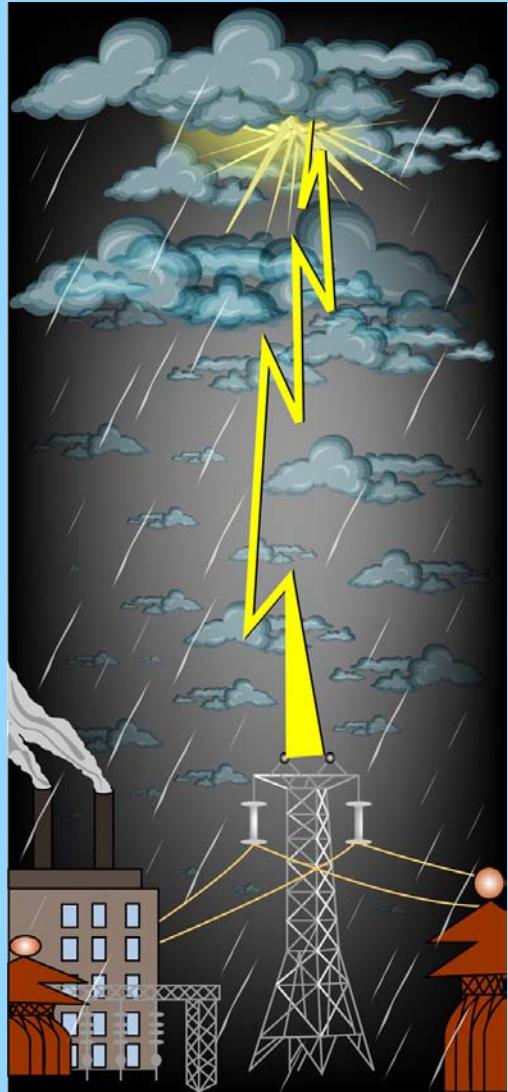

Revenge?


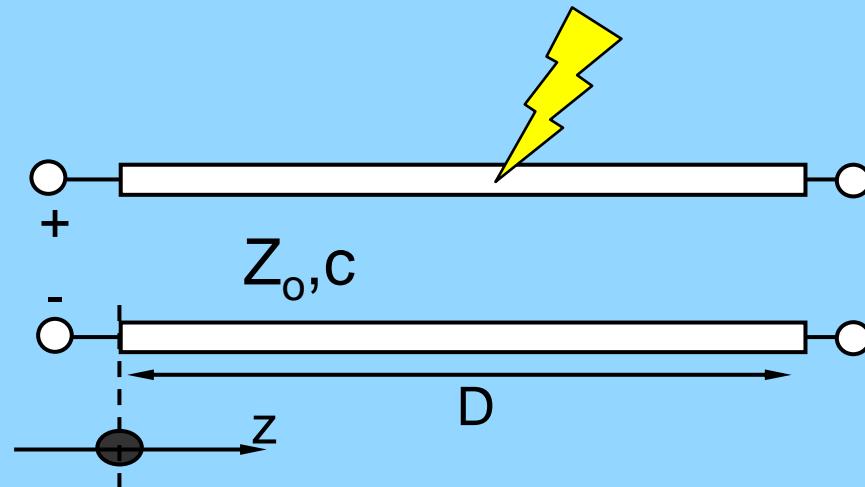


Figure by MIT OpenCourseWare.

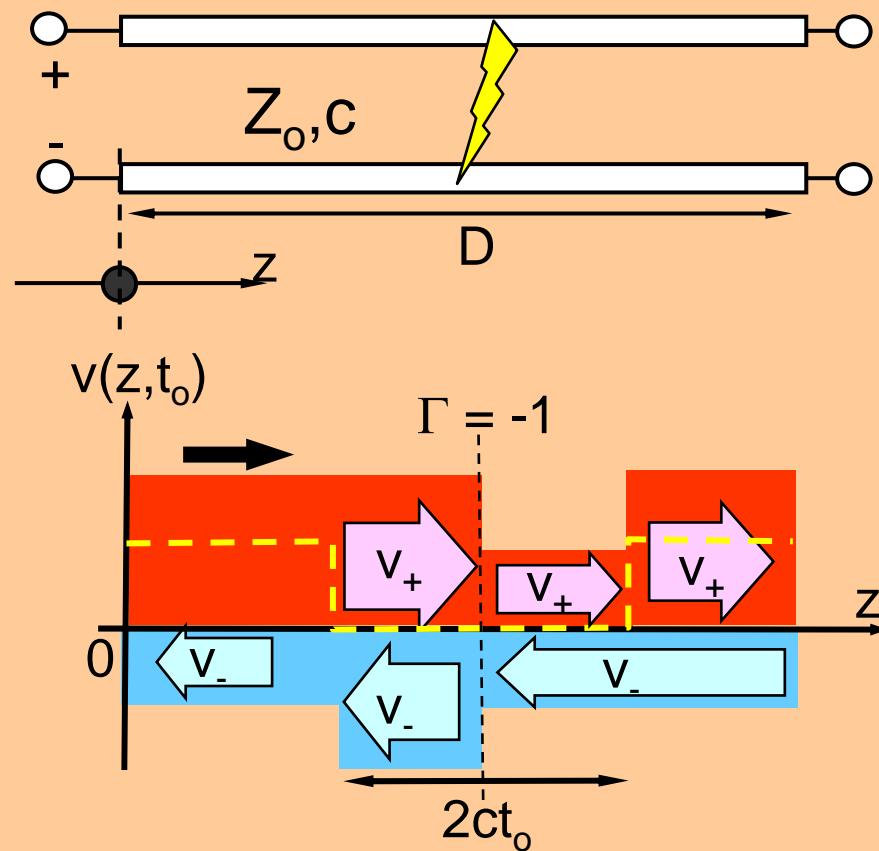
# LIGHTNING STRIKE EXAMPLE

One possibility:  
Temporary short through ionized channel



# LOSSY TRANSMISSION LINES

## Equivalent Circuit:

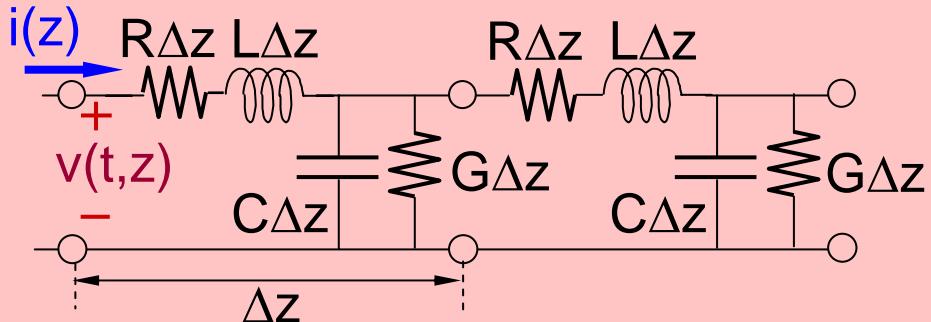

$L$  [ $\text{H m}^{-1}$ ],  $C$  [ $\text{F m}^{-1}$ ],  
 $R$  [ $\Omega \text{ m}^{-1}$ ],  $G$  [ $\text{S m}^{-1}$ ]

## Equations for $\Delta z \rightarrow 0$ :

$$\left. \begin{aligned} \frac{d\underline{V}(z)}{dz} &= -(R + j\omega L)\underline{I}(z) \\ \frac{d\underline{I}(z)}{dz} &= -(G + j\omega C)\underline{V}(z) \end{aligned} \right\} \Rightarrow \left\{ \begin{aligned} \frac{d^2\underline{V}(z)}{dz^2} &= (R + j\omega L)(G + j\omega C)\underline{V}(z) \\ \underline{V}(z) &= \underline{V}_+ e^{-jkz} + \underline{V}_- e^{+jkz} \\ k &= \sqrt{-(R + j\omega L)(G + j\omega C)} = k' - \underbrace{jk''}_{\text{decay}} \end{aligned} \right.$$

$$\left. \begin{aligned} \underline{V}(z) &= \underline{V}_+ e^{-jk'z - k''z} \\ \underline{I}(z) &= Y_o \underline{V}_+ e^{-jk'z - k''z} \end{aligned} \right\} \text{for forward wave: } Y_o = \sqrt{(G + j\omega C)/(R + j\omega L)}$$

Propagation  $e^{-jkz}$ : decay rate ( $e^{-k''z}$ ) and phase velocity ( $v_p$ ) =  $f(\omega)$   
 (Exception: “distortionless line” for which  $R/L = G/C$ )

MIT OpenCourseWare  
<http://ocw.mit.edu>

6.013 Electromagnetics and Applications  
Spring 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.