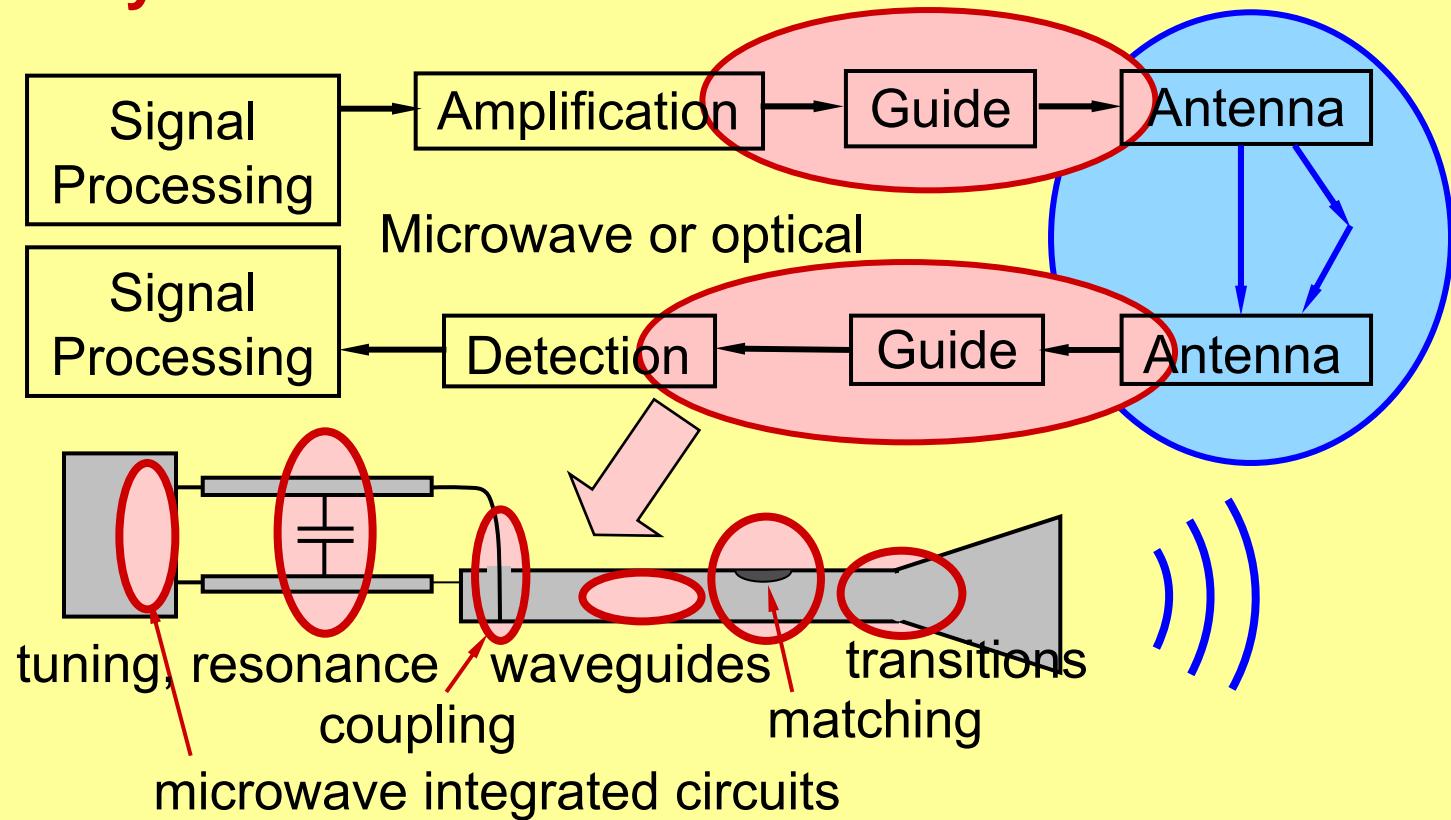


# EM GUIDANCE AND FILTERING

## Generic System Architecture:



**Systems fail at weakest link, so understand all parts**

Communications, bi-static radar—separately located systems


Radar, lidar, data recording—co-located systems

Passive sensing—uses receiver side only

# MICROWAVE CIRCUITS
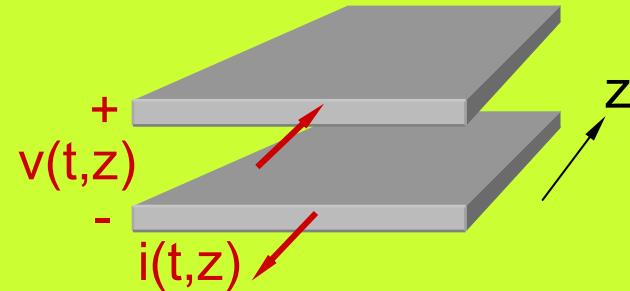
## Printed Circuits :

$$\text{"TEM"} \Rightarrow \bar{E} \bullet \hat{z} = \bar{H} \bullet \hat{z} = 0$$



## Difference Equations:

$$\underline{V}(z+\Delta z) - \underline{V}(z) = -j\omega L \Delta z \underline{I}(z)$$


$$\underline{I}(z+\Delta z) - \underline{I}(z) = -j\omega C \Delta z \underline{V}(z)$$

Limit as  $\Delta z \rightarrow 0$ :

$$\frac{d\underline{V}}{dz} = -j\omega L \underline{I}$$

$$\frac{d\underline{I}}{dz} = -j\omega C \underline{V}$$

## Equivalent TEM line circuit:

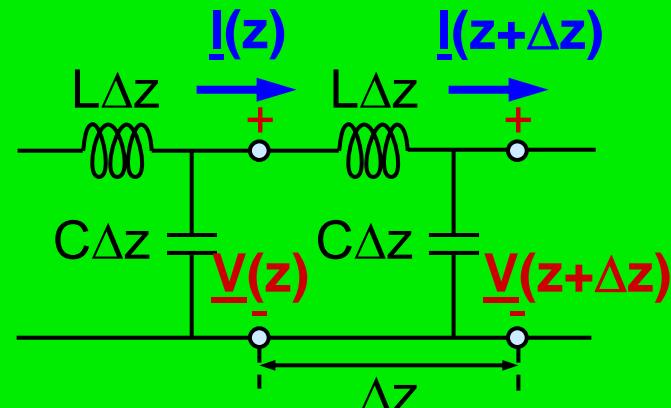

$$\Rightarrow \frac{d^2\underline{V}(z)}{dz^2} + \omega^2 LC \underline{V}(z) = 0 \quad \text{Wave Equation}$$

# TEM PHASOR EQUATIONS

**Wave Equation:**  $\left(\frac{d^2}{dz^2} + \omega^2 LC\right) \underline{V}(z) = 0$

**Voltage Solution:**  $\underline{V}(z) = \underline{V}_+ e^{-jkz} + \underline{V}_- e^{jkz}$


Test solution:  

$$[(-jk)^2 \underline{V}_+ e^{-jkz} + (jk)^2 \underline{V}_- e^{jkz}] +$$
  

$$\omega^2 LC [\underline{V}_+ e^{-jkz} + \underline{V}_- e^{jkz}] = 0$$

Passes test iff:  $k^2 = \omega^2 LC$

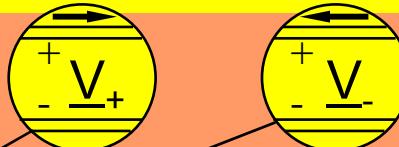**Current  $\underline{I}(z)$ :** Since:  $\frac{\partial \underline{V}(z)}{\partial z} = -j\omega L \underline{I}(z)$



Therefore: 
$$\begin{aligned} \underline{I}(z) &= \frac{1}{j\omega L} jk (\underline{V}_+ e^{-jkz} - \underline{V}_- e^{jkz}) \\ &= Y_0 (\underline{V}_+ e^{-jkz} - \underline{V}_- e^{jkz}) \end{aligned}$$

**Line admittance:**  $Y_0 = \frac{k}{\omega L} = \frac{\omega \sqrt{LC}}{\omega L} = \sqrt{\frac{C}{L}} = \frac{1}{Z_0}$

**TEM Equations:** 
$$\begin{aligned} \underline{V}(z) &= \underline{V}_+ e^{-jkz} + \underline{V}_- e^{jkz} \\ \underline{I}(z) &= Y_0 (\underline{V}_+ e^{-jkz} - \underline{V}_- e^{jkz}) \end{aligned}$$


# COMPLEX LINE IMPEDANCE $\underline{Z}(z)$

**Impedance:**

$$\underline{Z}(z) = \frac{\underline{V}(z)}{\underline{I}(z)} = R(z) + jX(z)$$

Resistance      Reactance
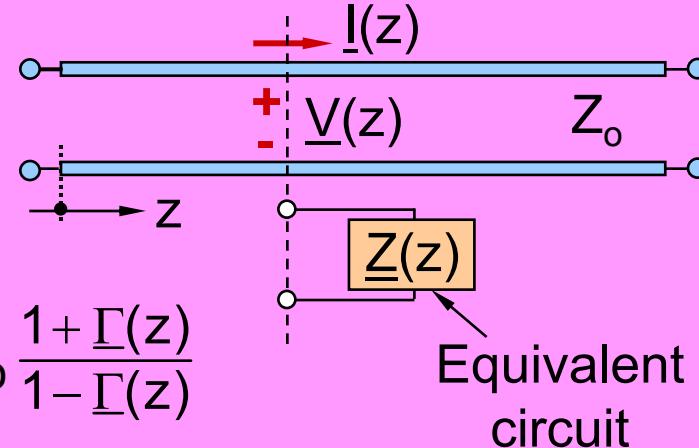
$$\underline{Z}(z) = \frac{Z_0 (\underline{V}_+ e^{-jkz} + \underline{V}_- e^{jkz})}{\underline{V}_+ e^{-jkz} - \underline{V}_- e^{jkz}} = Z_0 \frac{1 + \underline{\Gamma}(z)}{1 - \underline{\Gamma}(z)}$$




**Complex Reflection Coefficient  $\underline{\Gamma}(z)$ :**

$$\underline{\Gamma}(z) \triangleq \frac{\underline{V}_- e^{+jkz}}{\underline{V}_+ e^{-jkz}} = \underline{\Gamma}_L e^{2jkz} \quad \text{where } \underline{\Gamma}_L = \underline{\Gamma}(z=0) = \frac{\underline{V}_-}{\underline{V}_+}$$

**Examples:**  $\underline{\Gamma} = 0 \Rightarrow \underline{Z}(z) = Z_0$      $\underline{\Gamma} = 1 \Rightarrow \underline{Z} = \infty$      $\underline{\Gamma} = -1 \Rightarrow \underline{Z} = 0$

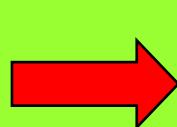**Normalized Impedance  $\underline{Z}_n(z)$ :**

Definition:  $\underline{Z}_n(z) \triangleq \frac{\underline{Z}(z)}{Z_0} = \frac{[1 + \underline{\Gamma}(z)]}{[1 - \underline{\Gamma}(z)]}$



$$\underline{\Gamma}(z) = \frac{[\underline{Z}_n(z) - 1]}{[\underline{Z}_n(z) + 1]}$$

# $Z(z)$ TRANSFORMATIONS

$\underline{Z}(z) = f(\underline{Z}_L, Z_o, k, z)$ :

Substituting:  $\Gamma_L = \frac{\underline{Z}_L - Z_o}{\underline{Z}_L + Z_o}$  into  $\underline{Z}(z) = Z_o \frac{[1 + \Gamma(z)]}{[1 - \Gamma(z)]}$ ;  $\Gamma(z) = \Gamma_L e^{2jkz}$

Yields:

$$\underline{Z}(z) = Z_o \frac{\underline{Z}_L - jZ_o \tan kz}{Z_o - j\underline{Z}_L \tan kz}$$

**Example: Open Circuit,  $Z_L = \infty$ :**

$$\underline{Z}(-\ell) = -jZ_o \cot k\ell \approx -jZ_o/k\ell \text{ for } k\ell \ll 1$$

$$= -j \frac{\sqrt{L/C}}{\omega \sqrt{LC}\ell} = \frac{1}{j\omega C\ell}$$



capacitor  $C_o$

$$= 0 \text{ when } z = -\lambda/4, -3\lambda/4, \dots$$

$$= \infty \text{ when } z = 0, -\lambda/2, \dots$$

$$\text{In general: } -j\infty < \underline{Z}(-\ell) < +j\infty$$

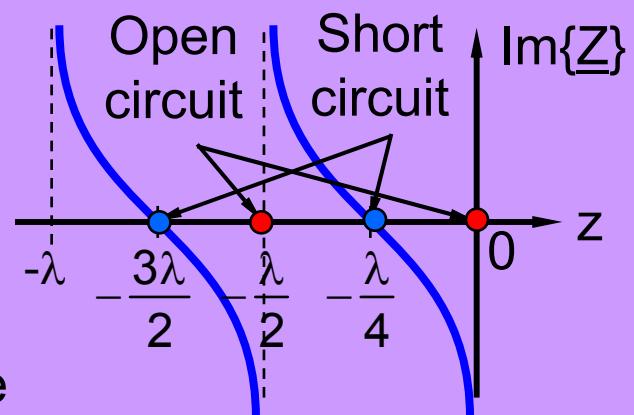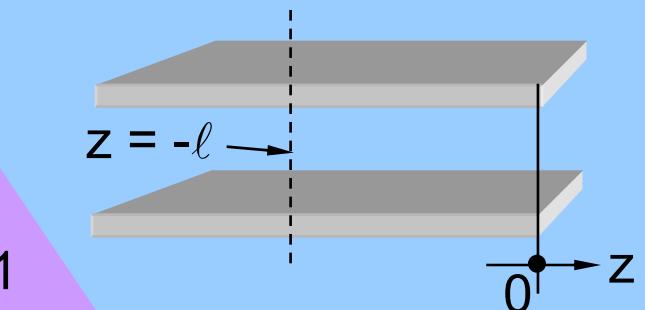
(Yields ANY capacitance or inductance  
at a SINGLE  $\omega$ )



# EXAMPLES: Z(z) TRANSFORMATIONS

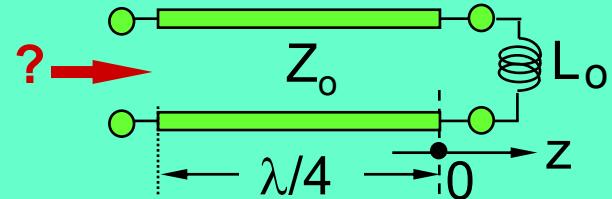**Example—Inductive Load,  $\underline{Z}_L = j\omega L_o$  for  $z = -\lambda/4$ :**

Recall:  $\underline{Z}(z) = Z_o \frac{\underline{Z}_L - jZ_o \tan kz}{\underline{Z}_o - j\underline{Z}_L \tan kz}$



Since:  $kz = -k\ell = -\frac{2\pi}{\lambda} \frac{\lambda}{4} = -\frac{\pi}{2}$ , therefore  $\tan(kz) = -\infty$

Therefore:  $\underline{Z}(-\ell) = \frac{Z_o^2}{\underline{Z}_L} = \frac{L/C}{j\omega L_o} = \frac{1}{j\omega C_o}$  ( $C_o = CL_o/L$ )


Note:  $\underline{Z}(z) = j\omega L_o$  if  $\ell = \lambda/2, \lambda, \dots$  [ $\tan(-2\pi\ell/\lambda) = 0$ ]

**Example – Source Transformation:**

$$\underline{Z}_{Th} = Z_o \frac{\underline{Z}_s + jZ_o \tan k\ell}{Z_o - j\underline{Z}_s \tan k\ell}$$

$$\begin{aligned} \underline{V}_A &= \underline{V}_s \frac{\underline{Z}_A}{\underline{Z}_s + \underline{Z}_A} \text{ where } \underline{Z}_A = -jZ_o \cot k\ell \\ &= \underline{V}_+ (e^{jk\ell} + e^{-jk\ell}) = 2\underline{V}_+ \cos k\ell \end{aligned}$$

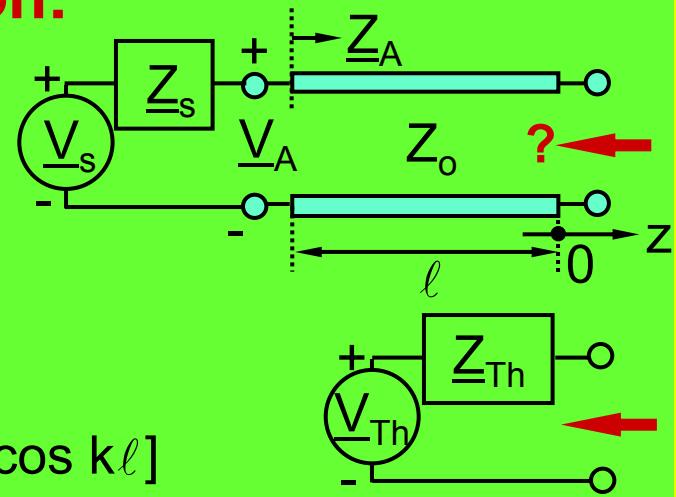Therefore:  $\underline{V}_{Th} = 2\underline{V}_+ = \underline{V}_s \underline{Z}_A / [(\underline{Z}_s + \underline{Z}_A) \cos k\ell]$



# ALTERNATE APPROACH TO FINDING $\underline{Z}(z)$

Algorithmic, rotate  $\underline{\Gamma}(z)$ :

$$\underline{Z}(z) = \underline{V}(z)/\underline{I}(z) = Z_0 \frac{\underline{V}_+ e^{-jkz} + \underline{V}_- e^{jkz}}{\underline{V}_+ e^{-jkz} - \underline{V}_- e^{jkz}}$$

$$(1) \quad \underline{Z}(z) = Z_0 \frac{1 + \underline{\Gamma}(z)}{1 - \underline{\Gamma}(z)}$$

$$(2) \quad \underline{\Gamma}(z) = \frac{\underline{V}_- e^{jkz}}{\underline{V}_+ e^{-jkz}} = \underline{\Gamma}_L e^{2jkz} = \underline{\Gamma}(z), \text{ where } \underline{\Gamma}_L = \underline{\Gamma}(z=0) = \frac{\underline{V}_-}{\underline{V}_+}$$

$$(3) \quad \underline{\Gamma}(z) = \frac{[\underline{Z}_n - 1]}{[\underline{Z}_n + 1]} \quad \underline{Z}_n(z) \triangleq \frac{\underline{Z}(z)}{Z_0}$$



$\Gamma$ -Plane Solution Method:

$$\underline{Z}_L \Leftrightarrow \underline{\Gamma}_L \Leftrightarrow \underline{\Gamma}(z) \Leftrightarrow \underline{Z}(z)$$

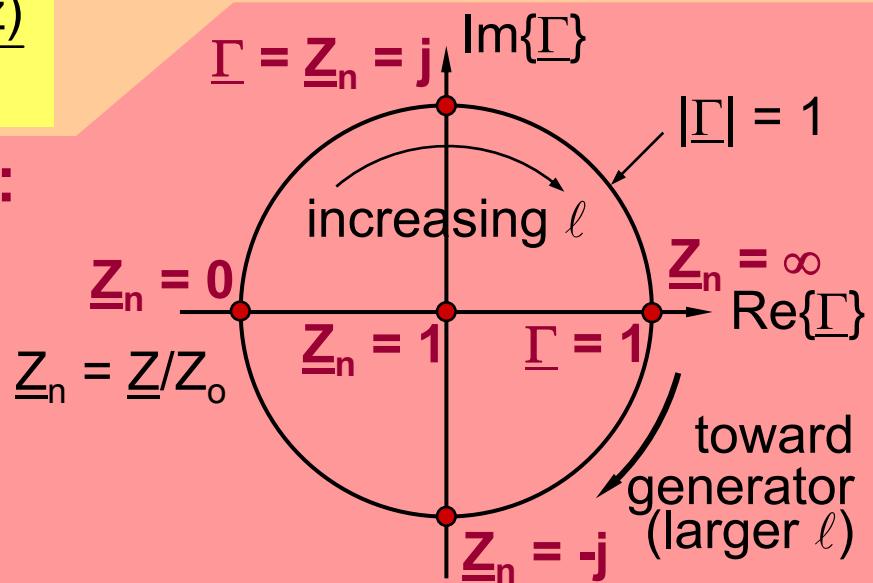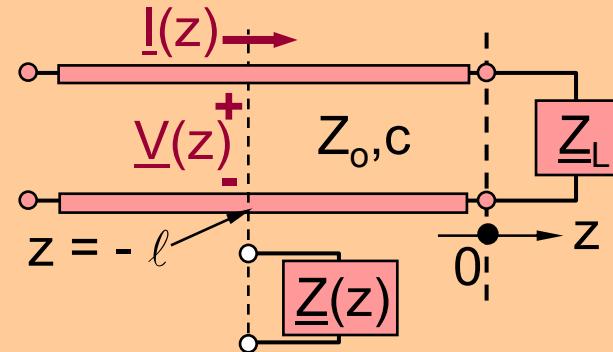(3)    (2)    (1)



$(\lambda/2 \Rightarrow \text{full rotation})$

$e^{-2jk\ell}$  goes clockwise as  $\ell \rightarrow \infty$   
 $(e^{j\phi} = \cos \phi + j \sin \phi)$



# GAMMA PLANE $\Rightarrow$ SMITH CHART

## Gamma Plane:

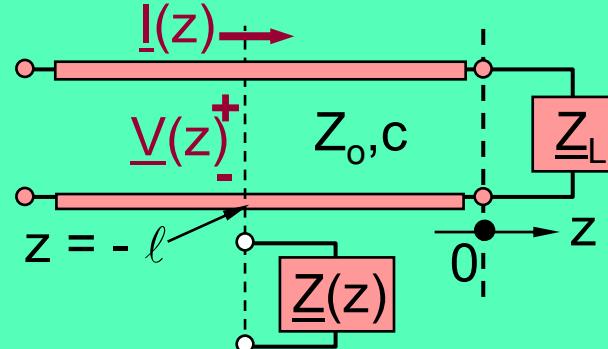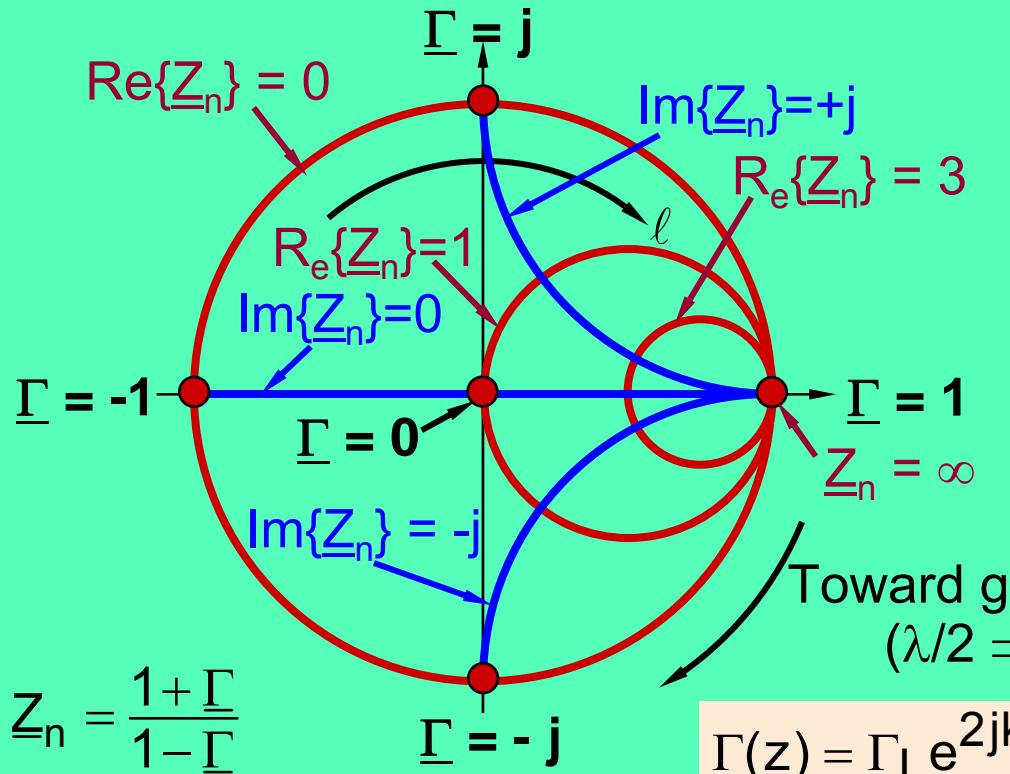

**Smith Chart = Gamma Plane +  $Z_n(z)$ :**

$$\frac{[\underline{Z}_n(z) - 1]}{[\underline{Z}_n(z) + 1]} = \underline{\Gamma}(z)$$

$$\underline{Z}_L \Leftrightarrow \underline{Z}_{L_n} \Leftrightarrow \underline{\Gamma}_L \Leftrightarrow \underline{\Gamma}(z) \Leftrightarrow \underline{Z}_n(z) \Leftrightarrow \underline{Z}(z)$$

$$\underline{Z}_n(z) \triangleq \frac{\underline{Z}(z)}{Z_0} = \frac{[1 + \underline{\Gamma}(z)]}{[1 - \underline{\Gamma}(z)]}$$

MIT OpenCourseWare  
<http://ocw.mit.edu>

6.013 Electromagnetics and Applications  
Spring 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.