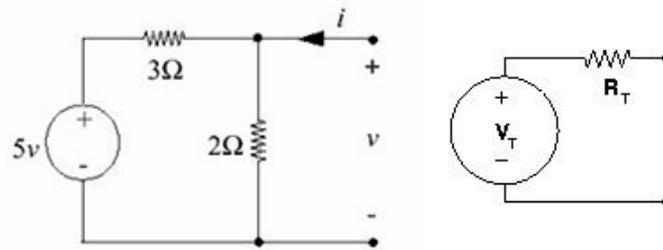


Problem Wk.9.3.1: Thevenin Equivalents



Find the Thévenin equivalent at the indicated terminals for the network shown above. Express all answers as decimal numbers correct to three places.

- V_T : Volts
- R_T : Ohms

MIT OpenCourseWare
<http://ocw.mit.edu>

6.01SC Introduction to Electrical Engineering and Computer Science
Spring 2011

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.