

Real Gain

Goals: Using a real robot head, you build the light sensor circuit you designed in [Homework 3](#), and characterize its performance, including its gain k_s .


Resources: This lab may be done with a partner (of your choice), or individually. You will need a **robot** and lab **laptop**, and in addition:



Proto board



Silver lamp

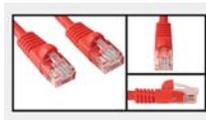

Red cable



Robot head



Robot



Two eight-pin connectors

Images (other than robot head and robot) © source unknown. All rights reserved. This content is excluded from our Creative Commons license. For more information, see <http://ocw.mit.edu/fairuse>.

Do `athrun 6.01 getFiles` to get the following file (in `Desktop/6.01/swLab09`):

- `eyeDataBrain2.py`: A brain which collects data on your light sensor circuit as a function of head angle.

1 Introduction

The main goal of this “software” lab is to measure the sensor gain k_s of the light sensor circuit you have designed for Homework 3.

If you have not yet completed your light sensor circuit design, and Tutor problem [Wk.8.4.1](#), do that first.


Once you have a circuit design, then do the following (either with a partner of your choice, or individually).

Some of the software and design labs contain the command `athrun 6.01 getFiles`. Please disregard this instruction; the same files are available on the 6.01 OCW Scholar site as a .zip file, labeled Code for [Design or Software Lab number].


2 Light Sensor Gain

To estimate k_s we will need a plot of v_s as a function of angle to the light. We'll feed the voltage v_s generated by your sensor circuit into an analog-to-digital input of the robot. Then v_s is measured by the robot as it turns 180° , while facing a fixed light source. The result is plotted in soar.

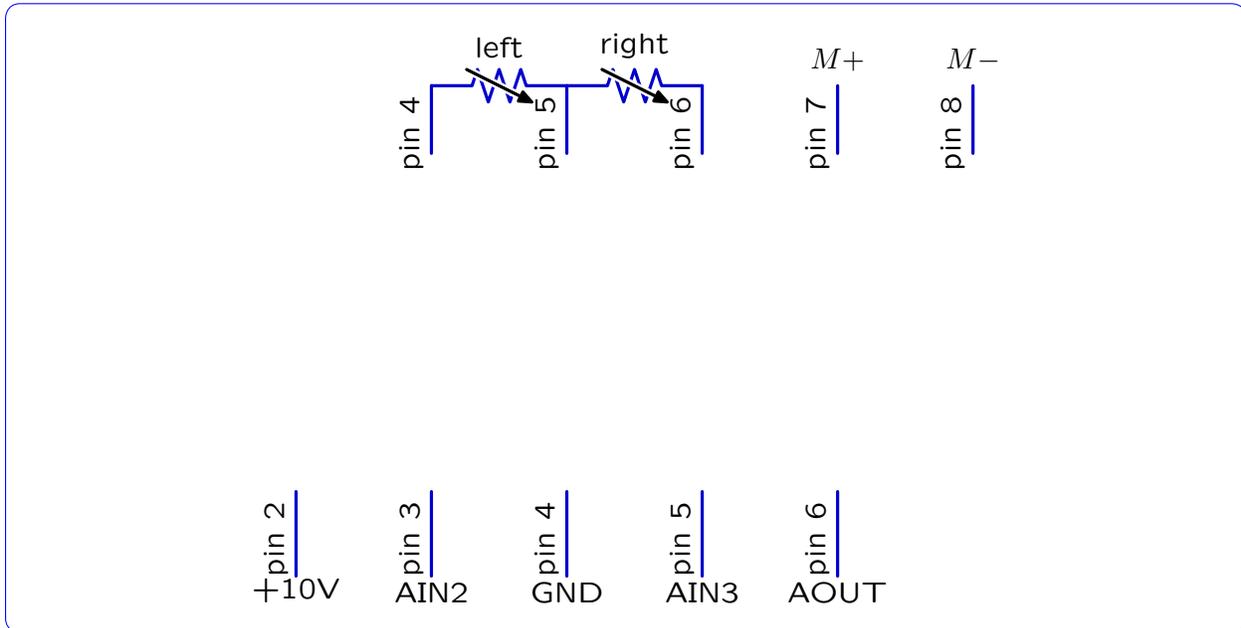- Step 1.** Draw a diagram of your light sensor circuit in the box below, showing how it is connected to the **head connector**. Also show how you use the **robot connector** to provide power supply connections. And connect the output voltage v_s of your sensor to the AIN2 analog input port of the robot. The motor pins may be left unconnected.



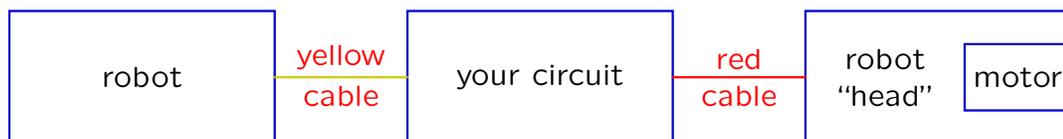- Step 2.** It is convenient to mount the head on the robot. Connect the head to your circuit, and your circuit to the robot, just as you did in Design Lab 8:



- Step 3.** Position the photoresistors so they are roughly 90° apart.
- Step 4.** Connect the output of your light sensor circuit, v_s , to analog input #2 (pin 3) on the **robot** connector. This pin connects to an **A-to-D (analog to digital) converter** within the robot; for more information on how these work, see the *Infrastructure Guide*.
- Find one of the silver lamps and hold it near the robot at approximately one meter distance.
 - Make sure the head/circuit is connected to the robot and turn the robot on.
 - Start soar and select the eyeDataBrain2.py brain.
 - Line up the robot in front of the lamp, so that the head is pointing at the lamp and the robot is about a meter from the lamp. Now manually turn the robot **clockwise** by 90° .

- Click Start in soar. This will turn the robot through 180 degrees.
- Click Stop when the robot has fully turned.

One plot should appear when you click Stop: the v_s signal as a function of rotation angle (you need to figure out what the units are).

- Step 5.** Reload the brain file in soar and repeat this procedure holding the lamp farther away, say around two meters.
- Step 6.** Now, keeping in mind what k_s means in [Homework 3](#), think about how you can estimate k_s from these plots, and give a good estimate. Does the value of k_s depend on distance?

Save your plots, labelled with the distances. Mail these results to your partner. We will discuss them at your next interview.

Checkoff 1.

Wk.9.1.1: Explain your sensor design, and how you estimated k_s , to a staff member.

MIT OpenCourseWare
<http://ocw.mit.edu>

6.01SC Introduction to Electrical Engineering and Computer Science
Spring 2011

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.