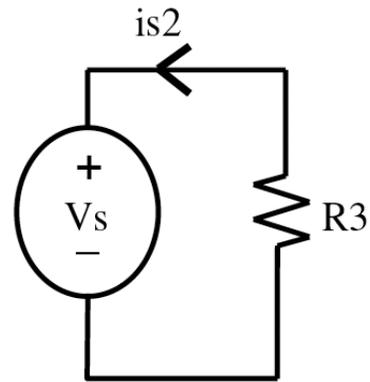
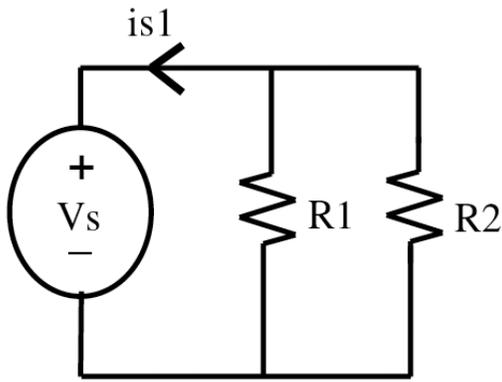


Problem Wk.7.2.1: Parallel Resistors

This problem is intended to help you build up some intuition about resistors in parallel and should be done without a calculator. The questions below refer to the following two circuits.



1. If $R_1 = R_2 = 100$ Ohms, for what value of R_3 will $i_{s1} = i_{s2}$?
 R_3 (enter floating point number): Ohms
2. If $R_1 = 100$ Ohms, and $R_2 = 10,000$ Ohms = 10K Ohms, for *approximately* what value of R_3 will $i_{s1} = i_{s2}$?
 R_3 (enter floating point number): Ohms
3. If $R_1 = 100$ Ohms, $R_2 = 1$ Ohms, for *approximately* what value of R_3 will $i_{s1} = i_{s2}$?
 R_3 (enter floating point number): Ohms

MIT OpenCourseWare
<http://ocw.mit.edu>

6.01SC Introduction to Electrical Engineering and Computer Science
Spring 2011

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.