

The following content is provided under a Creative Commons license. Your support will help MIT OpenCourseWare continue to offer high-quality educational resources for free. To make a donation or view additional materials from hundreds of MIT courses, visit MIT OpenCourseWare at ocw.mit.edu.

PROFESSOR: So today I want to start a new topic, circuits. No, that's good. That's good. Circuits are good.

AUDIENCE: Yay.

PROFESSOR: Thank you, thank you. Much better. So just to provide some perspective, I want to remind you where we are, how we got here, and where we're going. So at the beginning of the course, we promised that there were several intellectual themes that we would talk about. Probably the most important one there is designing complex systems. That's what we're really about. We would like you to be able to make very complicated systems. How do you think about parts? How do you think about connecting them? How do you think about things when you want to make something that's very complicated?

Part of that is modeling. We just finished a module on modeling. So in order to make a complex system, we'd like to be able to predict how it will behave before we completely build it. Sometimes it's impossible to build the entire system before. Sometimes it's impossible to build prototypes. Sometimes you're stuck with going with the design at launch, and figuring out how it works. In those cases in specific, it's very important to be able to model it, to have some confidence that the thing's going to work.

We're going to talk about augmenting physical systems with computation. That's the module we're about to begin. And we'll conclude by talking about how to build systems that are robust to change. So we started with the idea of, how do you make complicated systems? And we introduced this notion of primitives, combination, abstraction, and pattern in terms of software engineering. We did that because

that's the simplest possible way of getting started. It provided a very good illustration of PCAP at the low level by thinking about Python, by thinking about the primitive structures that Python gives you, how those can be combined, how you can abstract, how you can recognize patterns. But then we also built a higher level abstraction, which was the state machine idea.

There the idea was you didn't have to have state machines in order to build the brain for a robot, but it actually turns out to be easy if you do because there's a modularity there. You can figure out if each part works independent of the other parts. And then you can be pretty sure when you put it together the whole thing's going to work. So that was kind of our introduction to this notion of PCAP.

Then we went on to think about signals and systems. And that was kind of our introduction to modeling. How do you make a model of something that predicts behavior? So we transitioned from thinking about, how do you structure a design to how do you think about behavior.

Today we're going to start to think about circuits. Circuits are really going to a more primitive physical layer. How do you think about actually making a device? So the device that we'll think about is a thing to augment the capabilities -- the sensor capabilities of the robot. We'll think about making a light tracking system. And the idea is going to be that you'll build a head. The head has a neck, so you'll have to control the neck. The head has eyes. It will mount on top of the robot, and that'll let you drive the robot around looking for light. And you'll do that by designing a circuit. So that's kind of the game plan for the next three weeks.

So today, what I want to do is introduce the notion of circuits, introduce the theory for how we think about circuits. And then in the two labs this week, the idea will be to become familiar with the practice of circuits. How do you actually build something? How do you actually make something work?

So today's the theory. So the theory, the idea in circuits is to think about a physical system as the interconnection of parts and rules that connect them. In fact, the rules fall into two categories. We're going to think about the currents that go through parts

and the voltage that develops across parts. And we'll see that there's a way of thinking about the behavior of the entire circuit that integrates all of those three pieces. How does the part work? How do the currents that go through the part work? And how do the voltages that are produced across the part -- how do they work?

So I'll just start with two very simple examples. The first is the most trivial example you can think about. You can think about a flashlight as a circuit. You close the switch, current flows. Very simple idea. We will make a model of that that looks like this. We'll think about the battery being a source. In this case, a voltage source. We'll think about the light bulb being a resistor. We'll have two parts. We'll have to know the current-voltage relationships for both of the parts. And we'll have to know the ramifications for those currents and voltages when you put them together. Very, very simple.

The other simple example that I want to illustrate is this idea of a leaky tank. Here the idea that I want to get across is that the circuit idea is quite general. When we talk about circuits, we almost always talk about electronic circuits. But the theory is by no means limited to electronics.

So for example, if we think about a leaky tank, we think about a pipe spewing water into a reservoir. Maybe that's the Cambridge Reservoir. Maybe that's the water coming out of the Woburn Reservoir. Maybe that's the demand put on by the Cambridge people trying to take showers in the morning -- I don't know. So we think about flow into a tank, a reservoir, and flow out. And we can make a model for that in terms of a circuit.

In the circuit there are through variables and across variables. In an electronic circuit, the through variable is current. Here the through variable is the flow rate. So it's the flow of water in and the flow of water out, represented here by these things that look like currents. And the across variable for an electronic device is voltage. The across variable for this kind of a fluidic device, the across variable is pressure. So we think as this thing gets ahead of that thing, as there's more stuff coming in

than going out, the height goes up and the pressure builds.

Same idea. So the point is that we'll develop the theory for circuits in terms of electronics. But you should keep in the back of your mind that it's a lot more general idea than just electronics. In fact, there are two completely distinct reasons why we even bother with circuits.

One is that they're very important to physical systems. If you're designing a power network, of course you have to think about the way the power network, the power grid works as a circuit. That's obvious. In electronics, of course, if you're going to build a cell phone, you have to know how the parts interconnect electronically. That's obvious.

But probably the biggest use for circuits these days is not those applications, although those are very important. Circuits are also used as models of things. So many models for complex behaviors are in fact circuit models. So in terms of electronics, the idea is that we want to get on top of electronics. We want to understand how circuits work, so we can understand things like that.

If you look at how complex processors have got over my professional life, we start with my professional life down at about 1,000 transistors per processor. And today, we're up at about a billion. That's enormous. Even in the stone ages when we were designing things that had a thousand parts, we still had trouble thinking about those thousands parts all at once. We still need PCAP. We still needed ways of combining the activities of many things into a conceptual unit that was bigger. Here, it's just impossible if you don't have that. So that's one of the reasons we study circuits.

And the other reason is here. So here I'm showing a model for the way a nerve cell works. This model is taken from 6.021. The idea, this comes from the study of the Hodgkin-Huxley model for neural conduction, arguably the most successful mathematical theory in biophysics. Which explains the completely non-trivial relationship between how the parts from biology works and the behavior in terms of propagated action potentials works. So the idea is that we understand how this biological system works because we think about it in terms of a circuit. That's the

only successful way we have to think about that.

So what I want to do then is spend today figuring out circuits At the very most primitive level. The level that I'm going to talk about in terms of circuits is roughly analogous to the level that we talked about with Python when we were thinking about how Python provides utilities for primitives, combinations, abstractions, and patterns.

So I'm going to start at the very lowest level and think about, what are the basic primitives, the smallest units we'll ever think about in terms of circuits? And what are the rules by which we combine them? So I'll start with the very simplest ideas, the very simplest elements. We will oversimplify things and think about the very simplest kind of electronic elements as resistors that obey Ohm's Law, V equals iR . Voltage sources, things that maintain a constant voltage regardless of what you do. And current sources, things that maintain a constant current regardless of what you do. These things are, as I said, analogous to the primitive things that we looked at in Python. They're also analogous to the primitive things that we looked at in system functions.

Can somebody think of, when we were doing difference equations, what were the primitives that we started with -- when we started to study difference equations? What's the most primitive elements that we thought about?

AUDIENCE: Delay.

PROFESSOR: Delay, yeah. So we thought about things like-- so we had delay. Anything else?

AUDIENCE: Gain.

PROFESSOR: Gain. Anything else? Add. So we had exactly three primitives. And we got pretty far with those three primitives. We learned the rules for interconnection. We didn't really make a big deal out of it. We didn't formalize it, but the rules for interconnection were something like every node has to have exactly one generator. You can't connect the output of this to this, that's illegal. Every node has to have one source. And every node can source lots of inputs. That was kind of the rules of the

interconnect. The interconnects here will be a little bit more complicated. So those are the elements that we'll think about.

And the first step's going to be to think about, how do they interconnect? The simplest possible interconnections are trivial. In the case of the battery, you hook up the voltage source to the resistor. The voltage source makes the voltage across this resistor 1 Volt. If we say the resistor is 1 Ohm, then there's 1 Amp current period. Done. Easy.

Similarly, if we were to hook up the resistor to a current source, we would get something equally easy. Except now the current source would guarantee that the current through the resistor is an amp. Therefore, the voltage across the resistor, by Ohm's law, would be a Volt. So we would end up with the same solution for a completely different reason.

Here the voltage is constrained. Here the current's constrained. Just to make sure everybody's with me, figure out, what's the current i that goes through this resistor? Slightly more complicated system. Take 20 seconds, talk to your neighbor, figure out a number between (1) and (5).

OK, so what's the answer? Everybody raise your hand with a number (1) through (5). Come on, everybody vote. Come on. You can blame it on your neighbor, that's the rules. You talk to your neighbor, then you can blame dumb answers on your neighbor.

OK, about 80% correct I'd say. So how do you think about this? What's going to be the current? How would you calculate the current? What do I do first? Shout. If you shout, and especially if my head's turned away I don't know who you are.

AUDIENCE: Kirchhoff's law.

PROFESSOR: Kirchoff's law, wonderful. Which one? There's two of them.

AUDIENCE: [UNINTELLIGIBLE].

PROFESSOR: [UNINTELLIGIBLE]. What loop do you want to use?

AUDIENCE: Left.

PROFESSOR: Left side. So if we use the left side loop, we would conclude that there's a volt across the resistor. So the current would be?

AUDIENCE: 1 Amp.

PROFESSOR: An amp. Where's the current come from?

AUDIENCE: The voltage.

PROFESSOR: The voltage source just like before. So not quite. So the voltage source establishes this voltage would be 1. That makes this current be 1. That would be consistent with the current coming out of here, except we have to also think about that 1 Amp source. So the question is, what's does the 1 Amp source do? Nothing? It's just there sort of for decoration or for [UNINTELLIGIBLE] so that we can make an interesting question to ask in lecture? Maybe.

So where's the current? Where's the 1 Amp that goes through the resistor come from?

AUDIENCE: [UNINTELLIGIBLE] on the right.

PROFESSOR: It comes from the right. It comes from the current over here. So the idea is that if this current, ignore the voltage over here for the moment. If this current flowed through the resistor, then you'd have 1 Amp going through there, and you'd have 1 Volt generated by that current which just happens to be exactly the right voltage to match the voltage from the voltage source.

So if you think about this, the voltage guarantees that this is 1 Volt, but so does the current. In order to simultaneously satisfy everything, all you need to do is have all of this current go around and come down through that resistor. That will generate the volt, so there's no propensity for more current to flow out of the source because the source is 1 Volt and it's facing a circuit that's already 1 Volt. So the idea was to

try to give you something that's relatively simple that you can think through on your own, but not trivial. So the answer was 1 Amp. But the 1 Amp was not for the trivial reason. The 1 Amp is because the current from the right flows through the resistor and makes the voltage be 1. So the right answer is 1. But for the reason that you might not have originally thought.

But more importantly, I wanted to use that as a motivation for thinking about, how do we think about bigger circuits? So when the simple circuit, like two parts, it's no problem figuring out what the answer's going to be. But when the circuit has even three parts, it may require more thinking. And you may want to have a more structured way of thinking about the solution. Yes?

AUDIENCE: What would have occurred if the current provider on the right side was 2 Amps?

PROFESSOR: Great question. Had this been 2 Amps, you can't violate this voltage. So that would have been 1 Volt. So that would have been 1 Amp through the resistor. So then you're left with the problem with this guy's pushing 2 and that guy's only eating 1. But the rules for the voltage source say eat or source however much current is necessary in order to make the voltage equal to 1. So the excess amp goes through the voltage source. So the voltage source is, in fact, being supplied power rather than supplying power itself.

Had this been 2 Amps, some of the power from this source would have gone into the resistor. And some of the power from this source would have actually gone into the voltage source. So if the voltage source were, for example, a model for a rechargeable battery, that rechargeable battery would be charging. Does that make sense? So if there had been a mismatch in the conditions, you still have to satisfy all the relationships from all of the sources.

AUDIENCE: What if the voltage was larger?

PROFESSOR: The same thing would have happened. Except now the flowing current would be in the opposite direction. Let's say that if the voltage here had been 2 Volts, then the voltage would have required that there is 2 Amps flowing here. 1 Amp would come

from here, but another Amp would come from here. This voltage source will supply whatever current is necessary to make its voltage law real. Ok. In fact, what we'll do now is turn toward a discussion of more complicated systems that will let you go back and in retrospect, analyze all those cases that we just did. And you'll be able to see trivially how that has to be the right answer.

So what I want to do now is generate a formal structure for how you would solve circuits. Yes?

AUDIENCE: So did we know of anything that could generate a current without generating a voltage, like in real life?

PROFESSOR: Can anything generate a current without generating a voltage? That's a tricky question. If you think about something as generating a current, then the voltage is not necessarily determined by that part. So that's kind of illustrated here. If this guy is generating a current, this guy is not actually the element that is controlling its own voltage.

In general, if you want to speak simultaneously about the current and voltage across the device, you have to know what it was connected to. Each part-- we'll get to this in a moment in case some of you are worried about launching ahead. We will cover this. This is very good motivation for figuring out what's going to happen in the next three slides.

So each part gets to tell you one relationship between voltage and current. Generally speaking, that's not enough to solve for voltage and current. Voltage and current is like two unknowns. Each element relationship is one equation. So the current source gets to say current equals x, current equals 1 Amp. It doesn't get to tell you what the voltage is.

So being a little more physical to try to address your question more physically, there are processes that can be extremely well modeled as current generators. In fact, many electronic semiconductor parts, like transistors, work more like a current source than like anything else. So there are devices that behave as though they

were current sources, but they don't simultaneously get to tell you what is their current and what is their voltage. They only get to tell you what is their current.

So let's think about now, if you had a more complicated system, how could you systematically go about finding the solution? As was mentioned earlier, there's something called Kirchhoff's law. And in fact, there's two of them. Kirchhoff's voltage law and Kirchhoff's current law. Kirchhoff's voltage law, in its most elementary form, says that if you trace the path around any closed path in a circuit, regardless of what the path is-- every closed path-- the sum of the voltages going around that closed path is 0.

So for example in this circuit, the red path illustrates one closed path through the circuit. It goes up through the voltage source, down through this resistor, and then down through that resistor. Kirchhoff's voltage law says the sum of the voltages around that loop is 0. That's written mathematically here, minus v_1 for here, plus v_2 for here, plus v_4 for here is 0.

OK, where do the signs come from? The signs came from the reference directions that we assigned arbitrarily to the elements. Before I ever do a circuits question, I always assign a reference direction. Every voltage has a positive terminal and a negative terminal. And I must be consistent in order to apply these rules. These rules only work if I declare a reference direction and stick with it.

If midway through a problem I flip it, I'll get the wrong answer. So the minus sign has to do with the fact that as I trace this path, I enter the minus part of this guy, but the plus part of that guy and that guy. So the sign of v_1 is negated relative to the others.

A different way to think about that is here, we can think that v_1 is the sum of v_2 and v_4 . That's sometimes more intuitive because if you started here, going through this path you would end up with a voltage that is v_1 higher than where you started. Whereas starting here, you would end up with a voltage here that's v_4 higher than where you started. And then by the time you got to here, it would be v_2 plus v_4 higher than where you started.

You start one place and on one route, you end up v_1 higher. And in the other route, you get v_4 plus v_2 higher. So it must be the case that v_1 is the same as v_2 plus v_4 . Those are absolutely equivalent ways of thinking about it. So those laws are equivalent. If you think about it a path, you think about some of the paths-- no. The path coinciding with the negative direction of some of the elements and the positive direction of others.

OK, how many other paths are there? Take 20 seconds, talk to your neighbor. Figure out all of the possible paths for which KVL has to apply.

OK, so everybody raise your hand and show a number of fingers equal to the number of KVL equations less two. Oh, very good. Virtually 100% correct. Why do you all say (5)? Which is to say 7. Why do you all say 7?

So there's 3 obvious ones. I was expecting a couple of 3's. This was supposed to be-- OK, yeah, I do plot against you. I was expecting some 3's. So there's 3 obvious paths that are analogous to the first one we looked at. If I call the first path A, then there's B and C which are the excursions around here. And you can write the equations just the same. They each involve three voltages. And they each go through, some starting at the negative side and some starting at the positive side. So those are in some sense, the obvious ones. But there are others too.

So one way to think about it, what I'd like you to do is enumerate all the paths through the circuit. I should have said all the paths through the circuit that go through each element one or fewer times. I don't want you to go through the same element twice.

So here's another path that would go through elements at most one time. So up through here, over through here, which didn't go through any elements. Down through that element, across that, down through here, et cetera. And you get an equation for that. Here's another. Here's another. Here's another.

And if you try to think about a general rule, a general rule is something like, how many of those panels can you make and piece together where the loop goes

through the perimeter? You're not allowed to go through an inner place because if you went through an inner node, you'd have to go through it twice. If you wanted the path to go through an inner element, you'd have to go through that element twice.

So in fact, the answer is 7. There are 7 different paths according to Kirchhoff's voltage law, all of which the sum of the voltages around those paths has to be 0.

The problem is, of course, that those equations are not all linearly independent. So if you just had a general purpose equation solver-- and by the way, we'll write one of those in week 8 for solving circuits. If you just passed those 7 equations into a general purpose equation solver, it would tell you there's something awry with your equations because they're not linearly independent.

So you can, however, think about linearly independent in particularly simple cases. This network is a particular kind of network that we call a planar network. A planar network is one that I can draw on a sheet of paper without crossing wires.

So I can draw this network without crossing wires. I'll call it planar. And it turns out that Kirchhoff's voltage laws for the innermost loops are always independent of each other. That's kind of obvious because as you go to a -- so each loop contains at least one element that some other loop didn't have. So that's kind of the reasoning for why it works.

So if you think about this particular loop, which we included in the 7, you can think about that as being the sum of the loops this way, the A loop and the B loop. Because if you write KVL for the A loop and KVL for the B loop and add them, you end up deriving KVL for the more complicated path.

And if you think about what's going on, it's not anything terribly magical. This path is the same as the A path added to that path, where I went through this element down when I did the A path and up when I did the B path. So those parts canceled out. That was the rule that I was talking about how I don't really want to go through the same element twice when I'm applying KVL.

So the idea then is that there's a systematic way, an easy way to figure out all the

KVL loops. You just think about all the possible paths through the circuit. You do have to worry about linearly independent. In the case of planar networks, that's pretty straightforward. Planar networks, you can always figure out the linearly independent KVL equations by looking at the smallest possible loops. The loops with small area.

OK, so that's half of it. That's KVL. The other Kirchhoff's law is KCL, Kirchhoff's Current Law. There we are thinking of the flow of current. So the flow of current is analogous to the flow of incompressible fluid. Water, for example.

If you trace the amount of water that flows through a pipe that goes into a Y, then the sum of the flows out has to equal the flow in. If that weren't true, the water would be building up.

So we think about pipes as transporting the flow of water without allowing it to build up anywhere. That's precisely how we think about wires in electrical circuits. The wires allow the transport of electrons but don't allow the buildup of electrons.

OK, do electrons build up? Sure. But in our idealized world, we say they don't build up in the wires, they build up in a part. And we'll have a special part that allows the electrons to build up. So we're not excluding the possibility that they build up, we're just saying that in this formalism, we don't allow the electrons to build up in the wires. So for the purpose of the wires, current in is equal to the current out. The net current in is 0.

So we will think then, about the circuit having nodes. The nodes are the places where more than one element meets, two or more elements meet. And we will apply KCL at each node.

So for example, in this simple circuit where I would have three parts connected in what we would call parallel, they share a node at the top and they share a node at the bottom. So even though it looks like there's multiple interconnects up here, we say that's one node. And we would say that the sum of the currents into the node is equal to the sum of the currents out.

So if I lab all of the possible currents that come out of that node, I would have i_1 , i_2 , i_3 . i_1 goes through the first one, the second one and the third one. And so I would conclude from Kirchhoff's current law that the sum of i_1 , i_2 , and i_3 is 0. OK. Easy, right?

As I said, we're going to make an abstraction where the electrons don't build up in the wires. They don't even build up in the parts. They do get stored in the parts. That's a little confusing, we'll come back to that.

If they don't build up in the parts, then the current that goes in this leg has to come out that leg. If that's true, then i_1 is i_4 , i_2 is i_5 , i_3 is i_6 , and we end up with another equation down here, which turns out to be precisely the same as the one at the top. Everybody's happy with that?

So we're thinking about this just the way we would think about water flow. If there's water flow into a part, it better be coming out. If there's water flow in a pipe, the water that goes into the pipe better come out of the pipe someplace.

So here is an arbitrary network made out of four parts. How many linearly independent KCL equations are there?

So how many linearly independent KCL equations are in that network? Everyone raise your hand, some number of KCL equations.

OK, I'm seeing a bigger variety. I see (1)'s, (2)'s, and (3)'s. I don't see any (4)'s. That's probably good.

So how do you think about the number of linearly independent KCL equations? So the first thing to do is to label things. So you have to have reference directions before you can sort of think about things.

So we have four elements. We would be expecting to see four element currents. The same current that goes into an element has to come out of it. So there's element current 1, 2, 3, and 4. There are three nodes, so we might be expecting three KCL equations. Here's one node from which you would conclude that the sum

of i_1 and i_2 better be 0.

Here's a node from which you would conclude that the current in i_2 better be i_3 plus i_4 .

And here is a node from which you would conclude that i_1 plus i_3 plus i_4 is 0. So I can write one KCL equation for every node, that's not surprising. But if you look at those equations, you'll see that they're not linearly independent. In fact, if you solve this one for i_2 -- it's already solved for i_2 . Stick that answer up here, you get i_3 plus i_4 added to i_1 is 0, which is just the same as that equation. So of those three equations, only two of them are linearly independent. The answer to that problem was (2).

And there's a pattern. So think about the pattern in terms of figuring out the number of linearly independent KCL equations that are in a slightly more complicated network.

So what's the answer here, how many KCL equations are in this network? Wow. Well, I'm not getting any of the answers I would have said. What does that mean? Ah, I'm forgetting to add 2. That's my problem. OK, now I'm getting some of the answers that I would expect to get. OK, got it. I confused myself.

OK, the vast majority say (1). How do you get that? Which is 3. So again, you think of how in this circuit there are four nodes, A, B, C, D. So we can think about writing a KCL equation for each one. If we go to A, A has three currents coming out of it -- 1, 2, 3. So the sum of those has to be 0, et cetera. And if you think about those equations, they're not linearly independent either.

If you work through the math, you see that there's exactly one of those equations that you can eliminate. So you're left with three linearly independent KCL equations. And so there's a pattern emerging here. Somebody see the pattern?

1 minus. Can somebody prove the pattern?

So there's a pattern here. The pattern is take the number of nodes and the number

of independent KCL equations as one less. So the challenge is, can you prove it?
And by the theory of lectures--

AUDIENCE: Yes.

PROFESSOR: Yes. And by a corollary of the theory of lectures, the way you would prove it is?

AUDIENCE: On the next slide.

PROFESSOR: On the next slide. Exactly. So how do I prove it? Yeah?

AUDIENCE: Whenever you take minus 1, you just add all the [UNINTELLIGIBLE] together
[UNINTELLIGIBLE].

PROFESSOR: Yeah. So there's something special about the last one. Why should there be
something special about the last one.

AUDIENCE: Because the circuit's closed.

PROFESSOR: Because the circuit's closed. That's right. So the idea is to sort of generalize the way
we think about KCL. So we start with a circuit. We think about having four nodes
here. It's certainly the case that KCL holds for each node. So here's KCL for that
node. But now if you think about KCL for this node, and then add them, that looks
like a KCL equation. But it applies to a super node.

Imagine the node defined by the black box, and think about the net currents into or
out of the black node. This current i_2 , which leaves the red node, enters the green
node, but doesn't go through the surface of the black node at all. That's exactly the
current that's subtracted out when we added the red equation to the green
equation. Does that make sense? So KCL says, oh, if all the currents at a node
have to sum to 0, and if elements have the same current coming out and going in,
then if you draw a box around an element, what goes into the element is the same
as what comes out of the element. It doesn't change the net current through the
surface. So the generalization of the KCL equation, KCL says the sum of the
currents into a node is 0. The generalization says take any closed path in a circuit,
the sum of the currents going across that closed path is 0.

So if we apply that rule again, think about node 3. If we add the result of node 3 to the black node, which was the sum of 1 and 2, we get the new green curve. We get the new green equation. And what that says is the sum of the currents going across the green super node-- OK, so what's going on? i_1 is coming out of it, i_4 is coming out of it, i_5 is coming out of it. So the sum of i_1 , i_4 , and i_5 has to be 0. Well, KCL says the sum of the currents coming out of a node must be 0. The super KCL says the sum of the currents coming out of any closed region is also 0. But the interesting thing about this closed region is that it encloses all but one of the nodes. That's always true. Regardless of the system, regardless of the circuit, you can always draw a line that will isolate one node from all the others. So what that proves is that you can always write KCL for this node in terms of KCL for those nodes. Ok. So there's a generalization then that says that you can always write KCL for every node. They will always be linearly dependent. So you can always throw away one.

So in some sense now, we're done. We've just finished circuit theory. We talked about how every element has to have a law. A resistor is Ohm's Law. A voltage source says that the voltage across the terminals is always a constant. A current source says that the current through the current source is always a constant. So every element tells you one law. We know how to think about KVL. So we know the rule for how the across variables behave.

What's the aggregate behavior of all the across variables? Well, KVL has to be satisfied for every possible loop. The loops don't have to be independent. You have to worry about whether they're independent. The only simple rule we came up with-- we'll come up with another one in a moment. The only simple rule that we came up with was for planar circuits, where the innermost loops were linearly independent of each other. And you have to write KCL for all the nodes, except one. One of them never matters.

So in some sense, we're done. What we would do to solve the circuit, think about every element. For every element assign a voltage, a reference voltage. For every element, assign a current. Make sure they go in the right direction. We always

define currents to go down the potential gradient. They always go in the directions through the element from the positive to the negative. So for every element, assign a current and a voltage.

We have 6 elements, that's 12 unknowns. Now we dig and we find 12 equations. In this particular circuit, we found those 12 equations. There were three KCL equations, one for each of the inner loops. There were three KCL equations, one for each node except one. There were 5 Ohm's law equations, one for each one of the resistors. There was one source equation for the voltage source. 12 equations, 12 unknowns, we're done.

The only problem is a lot of equations. It's not a very complicated circuit. We've only got 6 elements. I tried to motivate this in terms of studying networks that had 10 to the 9 elements. This technique is not particularly great at 10 to the 9. It would probably work. But we would probably be interested in finding simpler ways. So there are simpler ways you might imagine, and we'll discuss two of them just very briefly.

The dumb way that I just talked about is what we call primitive variables, element variables. If you write all the element variables, $v_1, v_2, v_3, v_4, v_5, v_6$, all of the element currents, $i_1, i_2, i_3, i_4, i_5, i_6$, write all the equations, you can solve it. However, if you're judicious, you can figure out a smaller number of unknowns and a correspondingly smaller number of equations. One method is called the node method.

When we're thinking about the individual elements, the thing that matters is the voltage across the element. However, that's not the easy way to write the circuit equations. A much easier way is not to tell me the voltage across an element, but instead tell me the voltage associated with each of the nodes.

If I tell you the voltage associated with every node, the important thing about that way of defining the variables is that you're guaranteed that from those variables, you can tell me the voltage across every part. So for example, in this circuit, this voltage source-- so if I call this one ground, we'll always have a magic node called

ground. It is not special in the least. It's just the reference voltage. I'll come back to that. I'll say words in a minute about what the reference is.

We always get to declare one node to be ground. We get one free node. It's a node whose voltage we don't care about because it's the reference for all voltages. It's a node whose current we don't care about because we get to throw away one node when we do current equations. So we have one special mode called ground, about which we don't care too much. Except that it's the most important node in the circuit. Except for that, we don't care about it. So this guy's ground. We think about its voltage being 0. Then this voltage supply makes that node be v_0 . I don't know what that is, so I'll call it e_1 . And I don't know what that is, so I'll call it e_2 .

So if I tell you the voltage on all of those nodes, ground voltage is 0, the top voltage is v_0 , the left voltage is e_1 , the right voltage is e_2 . From those four numbers, 0 and 3 nontrivial numbers, you can find all of the component voltages.

So for example, the voltage v_6 , the voltage across R_6 is e_2 minus e_1 . The voltage v_4 , the voltage across the R_4 resistor is e_1 minus 0. So if I tell you all the node voltages, you can tell me all of the element voltages. And in general, there's fewer nodes than there are components. OK, that's great.

So instead of naming the volts across the elements, we'll name the voltages at the nodes because there's fewer of them.

Then, all we need to do in the node method is write the minimum number of KCL equations. We know we only have two unknowns, e_1 and e_2 . And it turns out-- and you can prove this, but I won't prove it today. It turns out that you need two KCL equations. Two unknowns, e_1 , e_2 , two KCL equations. And it turns out those two KCL equations are exactly the KCL equations associated with the two nodes.

So the current leaving e_1 , so KCL at e_1 -- well, there's a current that goes that way. Well, that's the voltage drop in going from e_1 to v_0 , e_1 minus v_0 , divided by R_2 . That's Ohm's law. So this term represents the current going up that leg plus the current that goes through this leg, which is e_1 minus e_2 over R_6 . Plus the current

going in that leg, which is e_1 minus 0 over R_4 . The sum of those three currents better be 0. Analogously, the sum of the currents at this node must be 0, and the equation looks virtually the same. Because v_0 is known, so it didn't add an unknown. v_0 was set by the voltage, by the voltage source. So I have two equations, two unknowns, solved. Done.

So rather than solving 12 equations and 12 unknowns, I can do it with two equations and two unknowns. That's called the node method. One of the most interesting theories about circuits is that every simplification that you can think about for voltage has an analogous simplification that you can think about in current. That's called duality. We won't do that because it's kind of complicated. But it's kind of a cute result.

If you can think of a simplification that works in voltage, then there is an analogous one, and you can prove it. In fact, you can formally derive what it must have been. This is a rule for how you can simplify things by thinking about voltages in aggregate. Rather than thinking about the element voltages, think about the node voltages.

The analogous current law is rather than thinking about the currents through the elements, the element currents, think about loop currents. OK, that's a little bizarre. So we name the loop, the current that flows in this loop, I_A , the current that flows in this loop, I_B , and the current that flows in this loop, I_C . What on earth is he doing?

Well, the element voltages are some linear combination of those loop currents. And in fact, the coefficients in the linear combination are one and minus one. So the element current I_4 , the current that flows through the R_4 resistor is the sum of I_A coming down minus I_C , which is going up. So there's a way of thinking about each element current as a sum or difference of the loop currents. Everybody get that?

So instead of thinking about the individual element currents, I think about the loop currents. And now, I need to write three KVL equations. So in the node method, I named the nodes and had to write two KCL equations. Here, I named the loop currents and I have to write three KVL equations, one for each loop. It's completely

analogous. If you write out a sentence, what did you do? I assigned a voltage to every node, and I wrote KCL of all the nodes. Then if you turn the word "current" into the word "voltage," the word "node" into the word "loop," you derive this new method.

So this says that if I write KVL at the A loop, think about spinning around this loop, as I go up through the voltage source, so I go in the negative terminal here. So that's minus v_0 . As I go down through this resistor, I have to use Ohm's law, so that's R_2 times the down current. Well, the down current is I_A down minus I_B up. So I went up through here, down through here. Now I go down through this one.

When I go down through that one, according to Ohm's law, that's R_4 times the current through that element. That current-- well, it's I_A down and it's I_C up. So this is the KVL equation for that loop. I write two more of them, and I end up with three equations and three unknowns.

Both the node method and the loop method resulted in a lot fewer equations than the primitives did. I had 12 primitive unknowns, 6 voltages and 6 currents. In the node method, I get the number of independent nodes as the number of equations and unknowns, which is less than the number of primitive variables. In the loop method, I have the number of independent loops. Which is again, smaller. So the idea then is that we have a couple of ways to think about solving circuits.

Fundamentally, all we have are the element relationships and the rules for combination. Oh, this is starting to sound like PCAP, primitives and combinations. So the primitives are, how does the element constrain the voltages and currents? We know three of those, Ohm's law, voltage source, current source. And what are the rules for combination? Well, the currents add to the node, and the voltages add around loops.

OK, just to make sure you've absorb all that, figure out the current I for this circuit.

OK, what's a good way to start? What should I do to start thinking about calculating I ? OK, bad way. Assign voltages and currents to everything. 4 elements, that's 4

voltages, 4 currents. That's 8 unknowns. Find 8 equations, solve. That'll work. Bad way. What's a better way?

OK, [UNINTELLIGIBLE PHRASE].

AUDIENCE: [UNINTELLIGIBLE PHRASE].

PROFESSOR: It was on the previous sheet. [UNINTELLIGIBLE PHRASE].

AUDIENCE: KVL [UNINTELLIGIBLE].

PROFESSOR: KVL for where?

AUDIENCE: Loops.

PROFESSOR: Which loop?

AUDIENCE: Left loop.

PROFESSOR: So do KVL on the left loop?

AUDIENCE: Yes.

PROFESSOR: OK, that's good. But you have to tell me how to assign variables. Do you want 8 primitive variables? 8 primitive variables are $v_1, i_1, v_2, i_2, v_3, i_3, v_4, i_4$. So that's what I mean by primitive variables. Or element variables is another word for it.

What's a better way than using element variables? Yeah.

AUDIENCE: Create 2 loop equations.

PROFESSOR: Create 2 loop equations, that's fantastic.

AUDIENCE: I_1 for the first loop, I_2 for the second loop.

PROFESSOR: So if you do I_1 going around here, then I_1 is actually I . And if you do I_2 going around here, what's I_2 ?

AUDIENCE: [INAUDIBLE].

PROFESSOR: So if I think about I_2 spinning around this loop, so the sum of I_1 and I_2 goes through that box. But the only current that goes through this box is?

AUDIENCE: [INAUDIBLE].

PROFESSOR: So the suggestion is that I think about-- so if I have I_1 here, but I know that's I . Then I can see immediately that since the only current that goes through here-- so if I have I_1 and I_2 . That was a very clever idea. If you have I_1 and I_2 , the only current that goes through here is I . So I_1 must've been I .

The only current that goes over here must've been this guy. So this must be minus 10. So I could redo that this way. I could say I've got 10 going that way. That make sense? So now I only have one unknown which is I . So that's a very clever way of doing it. So what I could do is showed here.

I have I going around one loop and I have 10 going around that loop. That completely specifies all the currents. So now all I need to do is write KVL for these different cases.

So if I write KVL for the left loop, then I get going up through here, that's minus 15, and going down through here, going to the right through this guy is $3I$. Going down through this guy is 2 times I plus 10. Both of these are going down, so you have to add them. So I get one equation and one unknown. And when I solve it, I get minus one. That make sense?

There's an analogous way you could have done it with one node. You could have said that the circuit has a single node and figured out KCL for that one node. KCL would be the sum of the currents here. There's a current that goes that way, that way, and that way. And again, you end up with 1 equation and 1 unknown. Yes?

AUDIENCE: [UNINTELLIGIBLE PHRASE].

PROFESSOR: Correct. If I thought about this current going this way, it would be minus 10. If I flipped the direction, then it's plus 10. So the loop current has the property that it's the only current through this element. So that has to match. It's one of two currents

that go through this element.

AUDIENCE: You said that everything that [UNINTELLIGIBLE PHRASE].

PROFESSOR: This loop is [UNINTELLIGIBLE]. Yes.

AUDIENCE: So why is the [UNINTELLIGIBLE PHRASE].

PROFESSOR: Correct. I want to have this picture now.

So if I'm doing it with loops, I have two loops. The current through this element is just I . The current through this element is just I . The current through this element is just 10. The current through this element-- well, the sum of these two currents go through that element. Does that make sense?

AUDIENCE: [INAUDIBLE]

PROFESSOR: This loop current is just a fraction of the current in the whole system. So this loop current goes through this element and contributes to this element. But so does that one. OK, if you're still confused, you should try to get it straightened out in one of the software labs or the hardware lab, or talk to me after lecture. But the idea is to decompose in the case of the node voltages. Think about the element voltages in terms of differences in the node voltages.

In the case of the loop currents, think about the element currents in terms of a sum of loop currents. OK, so the answer is minus 1 regardless of how you do it. Ok. The remaining thing I want to do today is think about abstraction.

We've talked about the primitives, which are things like resistors, voltage sources, and current sources. Means of combinations, that's KVL and KCL. Now we want to think about abstraction.

And the first abstraction that we'll talk about is, how do you think about one element that represents more than one element? This is the same thing that we did when we thought about linear systems, when we did signals and systems. We started with R's and K's and pluses, and we made single boxes that had lots of R's and pluses and

gains in them.

What was the name of the thing that was inside the box? If we combined lots of R's, gains, and pluses into a single box, what would we call the thing that's in the box?

AUDIENCE: [INAUDIBLE].

PROFESSOR: Shout again.

AUDIENCE: System function.

PROFESSOR: System function. Right? So we started with boxes that only had things like R's in them. But eventually, we got boxes that looked like much more complicated things like that. We thought about a system function which was a generalized box, that could have lots of R's, or lots of gains, or lots of pluses in it. And that was a way of abstracting complicated systems so they looked like simple systems. What we want to do here is the same thing for circuits.

We want to have a single element, a single circuit element, that represents many circuit elements. And the simplest case of that is for series in parallel combinations of resistors. It's very simple to think about how if you had two Ohm's law devices connected in series, you could replace those two with a single resistor. And the voltage-current relationships measured at the outside of the box would be the same. That's how we think about an abstraction in circuits.

When is it that you can draw a box around a piece of a circuit and think about that as one element? The very simplest cases, the series combination of two resistors, same sort of thing happens for the parallel combination. And that simple abstraction makes some things very easy.

What would be the equivalent resistance for a complicated system like that? Well, that's easy. All you need to do is think about successively reducing the pieces. Here I'm thinking about that having four resistors. I can just successively apply series and parallel in order to reduce that, make it less complicated.

So I can think about combining these two in series to get, instead of two 1 Ohm

resistors, one 2 Ohm resistor.

Then I can think about these two 2 Ohm resistors being equivalently one parallel 1 Ohm resistor. And so this whole thing looks as though it's just 2 Ohms from the outside world. That's what we mean by an abstraction. What we're trying to do and what we will do over the next two weeks, is we'll think about ways of combining circuits so that we can reduce the complexity this way.

Another convenient way of thinking about reducing the work that you need to do is to think about common patterns that result. PCAP, Primitives, Combinations, Abstractions. So the series of parallel idea was an abstraction. A pattern, here's a common pattern. If you've got two resistors in series, if the same current flows through two resistors, then there's a way of very simply calculating the voltage that falls across each. So you can think about the sum resistor, $R_1 + R_2$ since they're in series. So that allows you then to compute the current from the voltage. Then the voltage that falls across this guy is by Ohm's law, just the current times its resistor, which is like that.

And similarly with this one. So you can see that some fraction of this voltage v occurs across the v_1 terminal. And some different fraction appears across the v_2 terminal, such that the sum of the fractions is, of course, v . That's what has to happen for the two. And there's a proportional drop. The bigger R_1 , the bigger is the proportion of the voltage that falls across R_1 . So it's a simple way of thinking about how voltage drops across two resistors. There's a completely analogous way of thinking about how current splits between two resistors.

Here the result looks virtually the same, except it has kind of the unintuitive property that most of the current goes through the resistor that is the smallest. So you get a bigger current in i_1 in proportion to the R_2 . So it works very much like the voltage case, except that it has this inversion in it, that the current likes to go through the smaller resistor.

OK, so last problem. Using those kinds of ideas, think about how you could compute

the voltage v_0 and determine what's the answer.

So what's the easy way to think about this answer? What do I do first?

AUDIENCE: Superposition.

PROFESSOR: So superposition? That's one thing.

AUDIENCE: Simplify [UNINTELLIGIBLE].

PROFESSOR: Simplify. So what's a good simplification? Collapse?

AUDIENCE: You can put the two [UNINTELLIGIBLE] in series and treat them as one.

PROFESSOR: So you can treat this as a series combination, and you can replace the series of 1 and 3 with a?

AUDIENCE: [UNINTELLIGIBLE PHRASE].

AUDIENCE: 4..

PROFESSOR: 4. So this can be replaced by four [UNINTELLIGIBLE] resistor. Now what?

AUDIENCE: You can do the same on the parallel one.

PROFESSOR: So you can replace the parallel of the 6 and a 12 with a?

AUDIENCE: 4.

PROFESSOR: Amazing -- with a 4. So there's a 4 there and there's a 4 there. And the answer is?

AUDIENCE: It's half.

PROFESSOR: Half of whatever it was by voltage [UNINTELLIGIBLE] relationship. So you think about this becoming that. You think about the parallel becoming that. You get a simple divide by 2 voltage divider. So the answer is 7 and 1/2, which was the middle answer. And so what we did today was basically a whirlwind tour of the theory of circuits. And the goal for the rest of the week is to go to the lab and do the same sort of thing with practical where you build a circuit, and try to use some of these

ideas to understand what it does.

MIT OpenCourseWare
<http://ocw.mit.edu>

6.01SC Introduction to Electrical Engineering and Computer Science
Spring 2011

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.