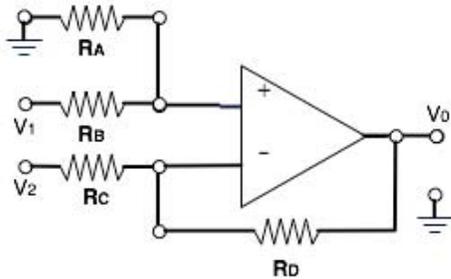


Problem Wk.10.3.6: Subtraction action (Optional)

Your answers below should be numbers.

1. In the following circuit:



Find values for R_A , R_B , and R_D , so that $V_0 = (2 V_1 - 3 V_2)$? Note that we have specified R_C .

$R_A =$ KOhms

$R_B =$ KOhms (Hint... use 2K)

$R_C = 1$ KOhms

$R_D =$ KOhms

MIT OpenCourseWare
<http://ocw.mit.edu>

6.01SC Introduction to Electrical Engineering and Computer Science
Spring 2011

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.