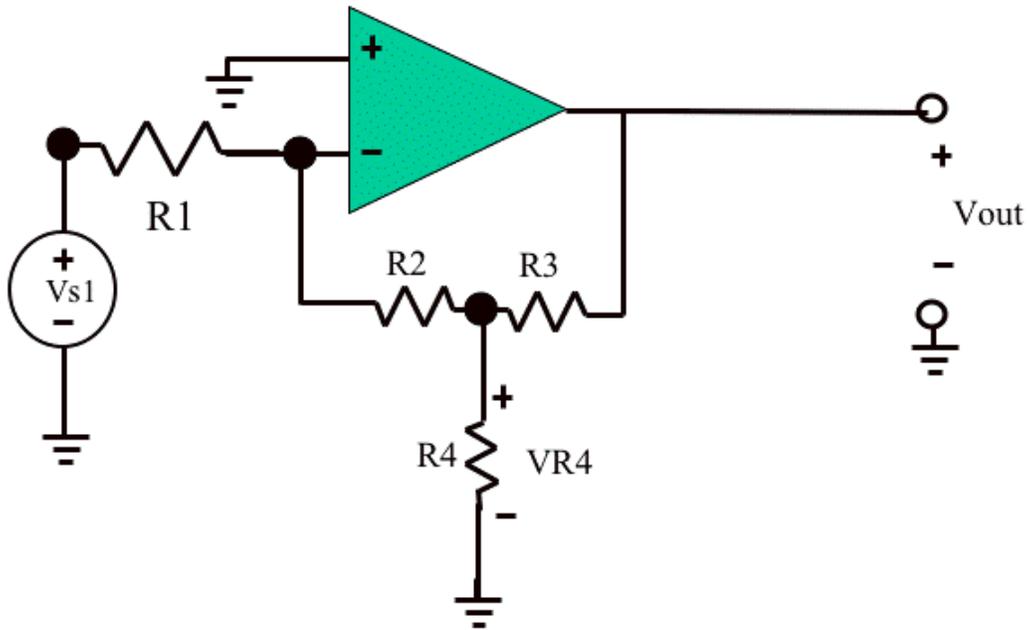


Problem Wk.10.3.8: Op Amp (Optional)



Express all answers as decimal numbers correct to three places.

1. Suppose $V_{s1} = 2.5V$, $R_1 = R_2 = R_3 = R_4 = 10K$ ohms, what is V_{R4} ?
Volts
2. What is the V_{out} given the values above? Volts

MIT OpenCourseWare
<http://ocw.mit.edu>

6.01SC Introduction to Electrical Engineering and Computer Science
Spring 2011

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.