

Massachusetts Institute of Technology
Department of Electrical Engineering and Computer Science
 6.061 Introduction to Power Systems

Problem Set 4

Issued February 21, 2011

Due March 2, 2011

Reading: Chapters 3 and 4 in the text.

Problem 1: From the text, do Chapter 3, problems 3 and 4 (parts a through d for 6.061, whole problem for 6.690). Note that, in Problem 3, the short is at the left hand end of the line and the terminating resistor is at the right.

Problem 2: A lossy transmission line problem is shown in Figure 1. Assume that the magnitude of voltage at the sending and receiving ends is the same: $|V_s| = |V_r| = 10\text{kV}$, RMS, and that the resistance R is one ohm and the reactance X_L is 10 ohms. The parallel capacitive reactance is $X_C = 60\Omega$. The phase shift from sending to receiving end is δ .

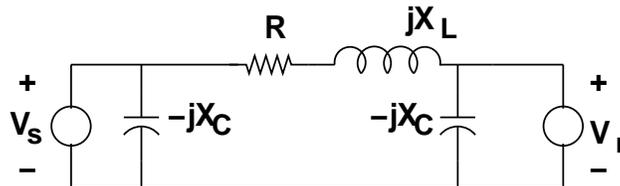


Figure 1: Compensated Transmission Line

1. Construct and sketch the sending end and receiving end power circle (P vs. Q with $0 < \delta < \pi/2$). Use the convention that complex power flow is from the source to the line at the sending end and from the line to the source at the receiving end.
2. (for 6.960) What is the phase shift δ across the line when 7,500 kW is the real power flow at the receiving end? What is real power at the sending end? What are reactive flows at each end for that case?

Problem 3: Shown in Figure 2 is a three-phase voltage source. The three phase voltages are:

$$\begin{aligned} v_a &= \sqrt{2} \cdot 120 (\cos \omega t) \\ v_b &= \sqrt{2} \cdot 120 \left(\cos \omega t - \frac{2\pi}{3} \right) \\ v_c &= \sqrt{2} \cdot 120 \left(\cos \omega t + \frac{2\pi}{3} \right) \end{aligned}$$

and note that the center point of this source is grounded. This represents the very commonly used '120/208' volt system in which line to neutral voltage is 120 volts, RMS and line to line voltage is 208 volts, RMS. It can be loaded line to neutral, line to line or three phase to drive motors.

For each of the six loads shown in Figure 3, find currents drawn from the three sources.

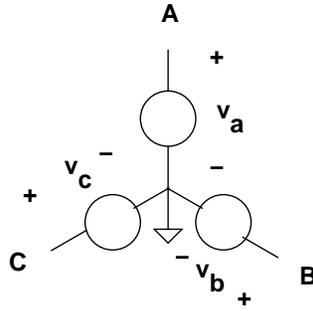


Figure 2: Three-Phase Voltage Source

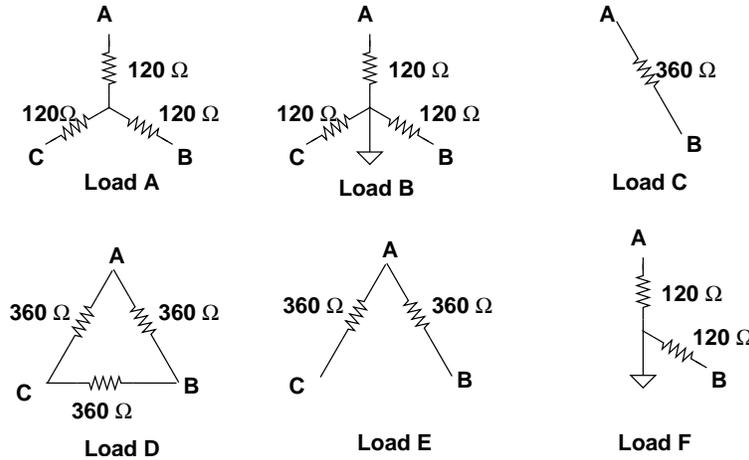


Figure 3: Resistive loads for Problem 3

Problem 4: The situation is as shown in Figure 4. A three phase *current* source is feeding a three-phase resistive load. The currents are actually square waves, as shown in Figure 5. Assume the amplitude of the currents is 100 A and that each of the load resistances in Figure 4 is 10Ω . The ground resistance is $R_g = 50\Omega$. Estimate and draw a dimensioned sketch of each of the four voltages: v_a, v_b, v_c, v_g .

Problem 5: For 6.690 A three-phase *ungrounded* voltage source is shown in Figure 6 It is connected to an unbalanced wye connected load consisting of two 1Ω resistors and one 2Ω resistor, as shown. Assume the voltage source is a balanced three phase 120/208 volt source as shown in Figure 2 above.

1. Find the three lead currents and draw a phasor diagram.
2. What is the voltage between the neutral of the wye connected resistors and then neutral of the voltage source?

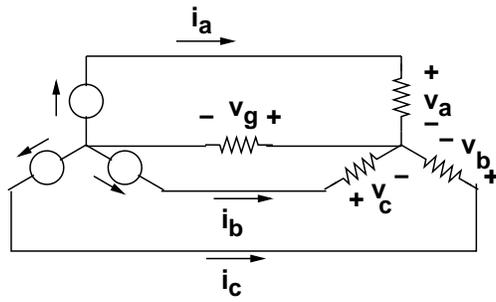


Figure 4: Current Source Feeding Resistive Load

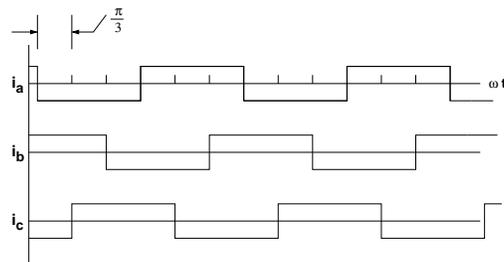


Figure 5: Currents

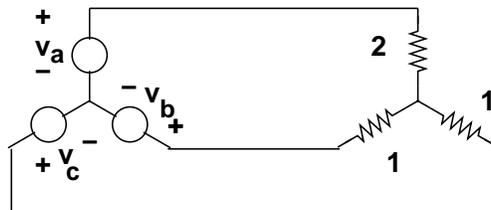


Figure 6: Voltage Source and Load

MIT OpenCourseWare
<http://ocw.mit.edu>

6.061 / 6.690 Introduction to Electric Power Systems
Spring 2011

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.