

Massachusetts Institute of Technology
Department of Electrical Engineering and Computer Science
 6.061/6.690 Introduction to Power Systems

Problem Set 10 Solutions

April 22, 2011

Chapter 9, Problems 2, 3 and 4 The equivalent circuit for this machine is shown in Figure 1. The new element is a resistance that represents core loss:

$$R_c = \frac{V_{\ell-\ell}^2}{P_{\text{core}}}$$

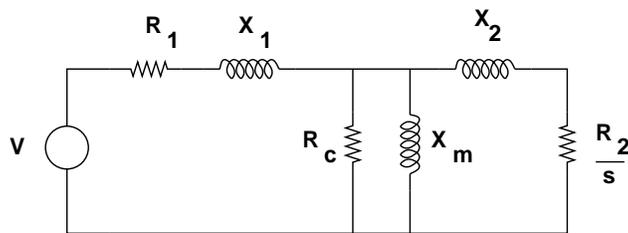


Figure 1: Induction Motor Equivalent Circuit

The script that is appended carries out the analysis. First, line-neutral voltage is:

$$V = \frac{V_{\ell-\ell}}{\sqrt{3}}$$

Then, straightforward circuit analysis yields:

$$\begin{aligned} Z_c &= R_c || jX_m \\ Z_r &= \frac{R_2}{s} + jX_2 \\ Z_{ag} &= Z_c || Z_r \\ Z_t &= Z_{ag} + R_1 + jX_1 \\ I_1 &= \frac{V}{Z_t} \\ I_2 &= I_1 \frac{Z_c}{Z_c + Z_r} \\ T_e &= 3 \frac{p}{\omega} |I_2|^2 \frac{R_2}{s} \end{aligned}$$

To get a torque-speed curve this calculation must be done many times for a range of points in slip. It is my experience that a logarithmically spaced set of points in slip works better

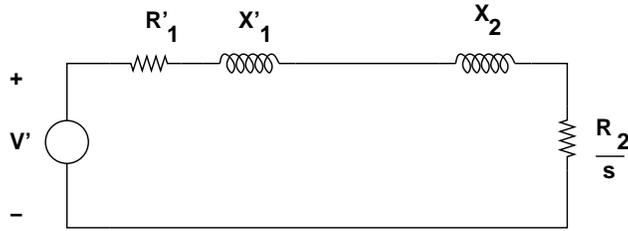


Figure 2: Induction Motor Equivalent Circuit

since it can yield a lot of points for small values of slip and fewer points for high slip where things are not very interesting. Generally we would want to plot things against speed:

$$RPM = 60 \frac{f}{p} (1 - s)$$

Current vs. Speed and Torque vs. Speed are displayed in Figures 3 and 4 respectively.

The lazy way of getting peak torque is to use MATLAB's `max()` function. But if you want to use the formula in the book, we first construct the simplified equivalent circuit, shown in Figure 2

The revised elements in this circuit are:

$$\begin{aligned} V' &= |V \frac{X_m}{R_1 + j * X_1 + j X_m}| \\ R'_1 + j X'_1 &= R_1 + j * X_1 || j X_m \\ R'_1 &= \frac{R_1 X_1 X_m}{R_1^2 + (X_1 + X_m)^2} \\ X'_1 &= \frac{X_m R_1^2 + X_1 X_m (X_1 + X_m)}{R_1^2 + (X_1 + X_m)^2} \end{aligned}$$

Then peak torque is, from the un-numbered expression on page 296 of the book:

$$T_{\max} = \frac{3 p}{2 \omega} \frac{|V'|^2}{R'_1 + \sqrt{(R'_1)^2 + (X'_1 + X_2)^2}}$$

Note that I have left off the impact of the core resistance in the expressions above, due to sloth. However, numerically I did calculate the equivalent circuit elements with the core effect included. The results produced by the script are pretty close together, vindicating my laziness.

Max Torque = 246.343

Classical Calc = 246.623

Classical with complete params = 246.345

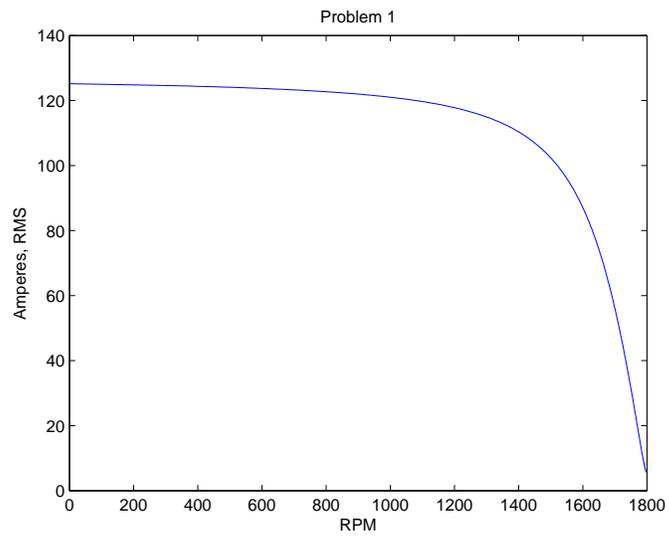


Figure 3: Induction Motor Current vs. Speed

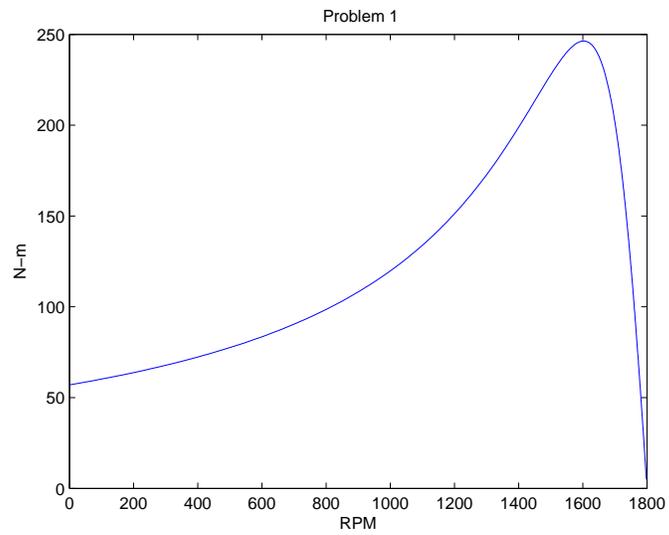


Figure 4: Induction Motor Torque vs. Speed

Script for Problem 1:

```
% Problem Set 10, Problem 1

% parameters
Vl1 = 480;
p = 2;
f = 60;
r1 = .2;
r2 = .24;
x1 = 1;
x2 = 1.2;
xm = 50;
Pc = 400;
Pf = 75;

rc = Vl1^2/Pc;           % core resistance
V = Vl1/sqrt(3);       % line-neutral voltage
om = 2*pi*f;

Vp = V*xm/abs(r1+j*(xm+x1)); % for max torque calc
rp = (r1*x1*xm^2)/(r1^2+(x1+xm)^2);
xp = (xm*r1^2+x1*xm*(x1+xm))/(r1^2+(x1+xm)^2);

zc = j*xm*rc/(j*xm+rc); % core branch impedance

s = logspace(-3,0,500); % slip

zr = j*x2 + r2 ./ s;    % rotor impedance
zag = zr .* zc ./ (zr+zc); % air gap impedance

zt = r1+j*x1 + zag;    % terminal impedance

It = V ./ zt;          % terminal current
I2 = It .* zc ./ (zc + zr); % secondary current

Te = 3*(p/om) * r2 .* abs(I2) .^2 ./ s; % torque

omm = (om/p) .* (1 - s); % mechanical speed
rpm = (30/pi) .* omm;    % in RPM

Tp1 = max(Te);          % first cut at max torque

figure(1)
plot(rpm, Te)
```

```

title(' Problem 1')
ylabel('N-m')
xlabel('RPM')

% alternate to max torque 1:
Tp2 = (1.5*p/om) *abs(Vp)^2/(rp+sqrt(rp^2 + (xp+x2)^2));

fprintf('Max Torque = %g\n', Tp1)
fprintf('Classical Calc = %g\n', Tp2)

% third attempt at max torque
zs = (r1+j*x1)*zc/(r1+j*x1+zc);
rpa = real(zs);
xpa = imag(zs);
vpa =abs(V*zc/(r1+j*x1+zc));

Tp3 = (1.5*p/om) *abs(vpa)^2/(rpa+sqrt(rpa^2 + (xpa+x2)^2));
fprintf('Classical with complete params = %g\n', Tp3)

% plot of terminal current:
figure(2)
plot(rpm, abs(It))
title('Problem 1')
ylabel('Amperes, RMS')

```

Problem 2 This problem has several parts and starts out very much like Problem 1. In fact the machine is the same motor as in Problem 1, re-wound for a different terminal voltage. All of the calculations for this problem and the next one are carried out in the attached script.

1. Torque vs. speed is plotted in Figure 5
2. Current vs. speed is plotted in Figure 6.
3. Breakdown torque is calculated using the `max()` function in Matlab:

Part 3: Max Torque = 242.723

4. When running light, the motor is delivering only friction and windage, assumed to be, somewhat improbably, constant. To find that point we employ a two-step strategy.
 - First, find two adjacent points in slip for which the net shaft power (that is power minus friction and windage) are, respectively, negative and then positive. This means the actual operating point is somewhere between the two points.
 - Use linear interpolation (See Figure 7 to estimate the point in slip where the motor is delivering the right power. the better estimate for slip is:

$$s_z = s_1 + (s_2 - s_1) \frac{-P_1}{P_2 - P_1}$$

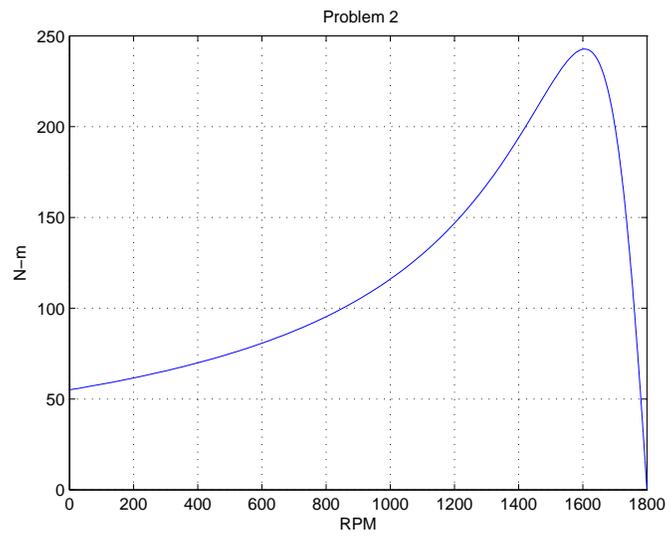


Figure 5: Induction Motor Torque vs. Speed

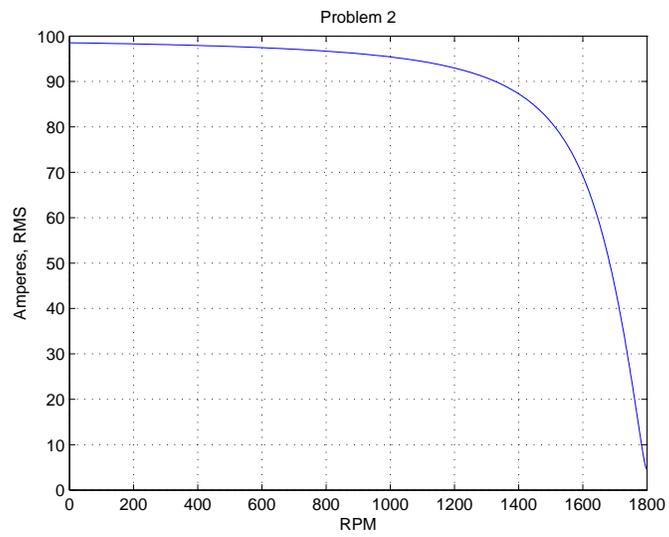


Figure 6: Induction Motor Current vs. Speed

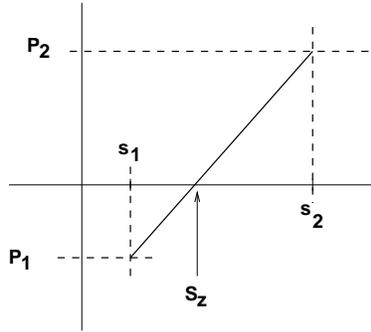


Figure 7: Linear Interpolation

Note this is not a perfect estimate, but it appears to give a fairly close estimate of the correct value of slip.

Using that interpolated value of slip, motor operation is re-evaluated at the one point and we find:

Part 4: Running Light: Speed = 1799.85 RPM
 Real Power = 476.681 Reactive Power = 4697.06
 Current = 4.54297 A

5. Locked rotor (or 'blocked rotor') is easy since we know the speed. The equivalent circuit is evaluated and the magnitude of impedance dictates the voltage that needs to be used. The rest is straightforward. Note that this test actually produces relatively little torque:

Part 5: Locked Rotor Test
 Current = 22.4 A Voltage = 78.756 V
 Real Power = 994.037 W Reactive Power = 5198.21 VAR
 Torque = 2.99466 N-m

6. We actually have all we need for the calculation of efficiency and power factor: all that is required is to identify which values of slip correspond with the lower and upper bounds of power. Then we can calculate efficiency (Power out/power in) and power factor (power in/apparent power) over that range of slips and do a cross-plot. This is shown in Figure 8.
7. This last part corresponds to volts-per-Hz control of the machine. With only a few curves to plot we can calculate them one by one and then plot them on a static plot window using 'hold'. There are a couple of things to recognize are important:
 - Voltage varies with speed, so it is important to schedule the right voltage
 - Reactances are functions of frequency, so we simply multiply the reactances X_1 , X_2 and X_m by the ratio of frequency to base frequency (60 Hz).

The torque-speed curves are shown in Figure 9

The script that was used to generate all of this stuff was also used for Problem 3 and will appear after that problem.

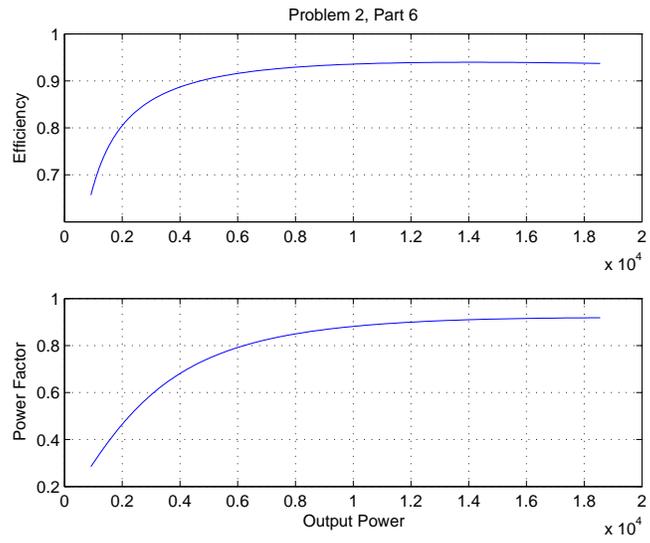


Figure 8: Efficiency and Power Factor vs. Load

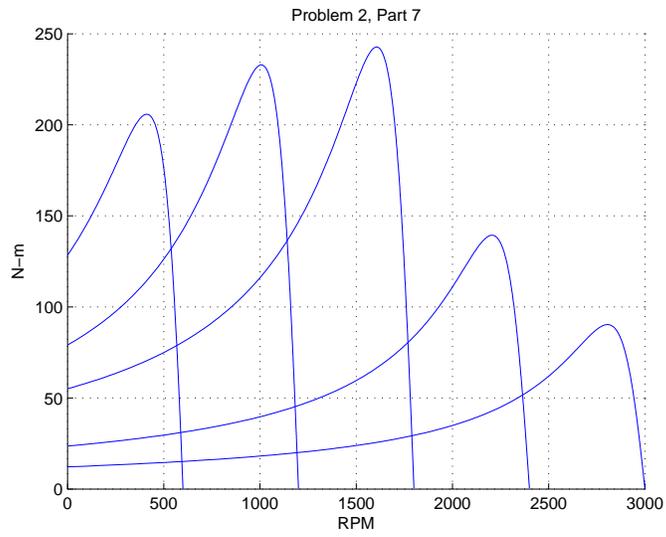


Figure 9: Torque vs. Speed, Volts/Hz Control

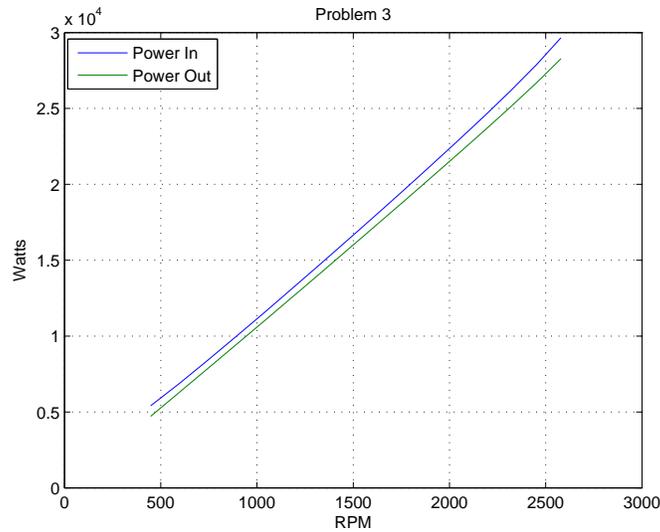


Figure 10: Volts per Hz. Input and Output Power

Problem 3: Volts/Hz Operation The procedure for this problem is very similar to what was used in the Problem 2 to find the 'running light' point and, of course, the last part of that problem. It is all in the script. For each of several points in frequency a torque vs. speed curve is run, then the actual point in slip is identified by:

- finding two points that straddle the required torque,
- linear interpolation is used to find the slip appropriate for that speed,
- The model is run again for the single point, and real and reactive power in and power out are identified

And then efficiency and power factor are calculated. The results are shown in Figures 10 and 11.

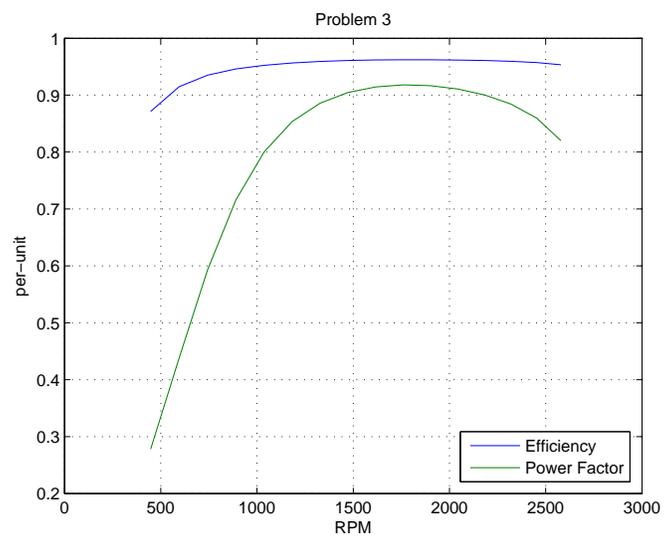


Figure 11: Volts per Hz. Efficiency and Power Factor vs. Speed

Script for Problems 2 and 3:

```
% Problem Set 10, Problems 2 and 3

% parameters
Vl1 = 600;
p = 2;
f = 60;
r1 = .3;
r2 = .375;
x1 = 1.6;
x2 = 1.9;
xm = 75;
Pc = 400;
Pf = 75;
Pmin = 933;
Pmax = 18650;

rc = Vl1^2/Pc; % core resistance
V = Vl1/sqrt(3); % line-neutral voltage
om = 2*pi*f; % frequency in radians/second
zc = j*xm*rc/(j*xm+rc); % core branch impedance
s = logspace(-4,0,500); % slip range
zr = j*x2 + r2 ./ s; % rotor impedance
zag = zr .* zc ./ (zr+zc); % air gap impedance
zt = r1+j*x1 + zag; % terminal impedance
It = V ./ zt; % terminal current
I2 = It .* zc ./ (zc + zr); % secondary current
Te = 3*(p/om) * r2 .* abs(I2) .^2 ./ s; % torque
Pm = (om/p) .* Te .* (1-s) - Pf; % shaft power produced
Pin = real(3 .* V .* conj(It)); % input power
Qin = imag(3 .* V .* conj(It)); % input reactive power
omm = (om/p) .* (1 - s); % mechanical speed
rpm = (30/pi) .* omm; % in RPM
Tp1 = max(Te);

figure(1)
plot(rpm, Te)
title(' Problem 2')
ylabel('N-m')
xlabel('RPM')
grid on

% plot of terminal current:
figure(2)
```

```

plot(rpm, abs(It))
title('Problem 2')
ylabel('Amperes, RMS')
xlabel('RPM')
grid on

fprintf('Part 3: Max Torque = %g\n', Tp1)

figure(3)
plot(rpm, Pm)
title('Problem 2')
ylabel('Output Power, Watts')
xlabel('RPM')
grid on

% running light: it makes only friction and windage, Pf
% search over s to find light operating point
for k = 1:length(s)-1
    if Pm(k) < 0 & Pm(k+1) >0,
        kz = k;
        break;
    end
end
% now do linear interpolation
sz = s(kz) - (s(kz+1)-s(kz)) * Pm(kz)/(Pm(kz+1)-Pm(kz));
zr1 = j*x2 + r2 / sz;           % rotor impedance
zag1 = zr1 *zc / (zr1+zc);     % air gap impedance
ztl = r1+j*x1 + zag1;         % terminal impedance

It1 = V / ztl;                % terminal current
I2l = It1 * zc / (zc + zr1);   % secondary current

Pem = 3 * (r2/sz) * abs(I2l) .^2 - Pf; % net shaft power

Pl = real(3*V*conj(It1));
Ql = imag(3*V*conj(It1));
Nl = (60*f/p)*(1-sz);

fprintf('Part 4: Running Light: Speed = %g RPM\n', Nl)
fprintf('Real Power = %g   Reactive Power = %g\n', Pl, Ql)
fprintf('Current = %g A\n', abs(It1))

% blocked rotor test

```

```

I1rm = 22.4; % test current magnitude
zr1 = j*x2+r2;
zag1 = zr1 * zc / (zr1 + zc);
ztl = r1 + j*x1 + zag1;
Vlr = abs(I1rm * ztl);
Ilr = Vlr / ztl; % actual test current
I2lr = Ilr * zc/(zc+zr1); % rotor current
Plr = real(3*Vlr*conj(Ilr));
Qlr = imag(3*Vlr*conj(Ilr));
Tlr = 3*(p/om)*r2*abs(Ilr)^2;

fprintf('Part 5: Locked Rotor Test\n')
fprintf('Current = %g A Voltage = %g V\n', abs(Ilr), Vlr)
fprintf('Real Power = %g W Reactive Power = %g VAR\n', Plr, Qlr)
fprintf('Torque = %g N-m\n', Tlr)

% part 6: over some range of operation
% minimum
for k = 1:length(s)-1
    if Pm(k) < Pmin & Pm(k+1) >Pmin,
        kmin = k;
        break;
    end
end
for k = 1:length(s)-1
    if Pm(k) < Pmax & Pm(k+1) >Pmax,
        kmax = k;
        break;
    end
end

P_out = Pm(kmin:kmax);
P_in = Pin(kmin:kmax);
Q_in = Qin(kmin:kmax);
VA_in = sqrt(P_in.^2 + Q_in.^2);
Eff = P_out ./ P_in;
PFACT = P_in ./ VA_in;

figure(4)
subplot 211
plot(P_out, Eff)
title('Problem 2, Part 6')
ylabel('Efficiency')
grid on
subplot 212

```

```

plot(P_out, PFACT)
ylabel('Power Factor')
xlabel('Output Power')
grid on

% part 7: Adjustable voltage
F = [20 40 60 80 100];
vr = [2/6 4/6 1 1 1];
f0 = 60;

figure(5)
clf
hold on
for k = 1:length(F)
    f = F(k);
    om = 2*pi*f; % frequency in radians/second
    zc = j*(f/f0)*xm*rc/(j*(f/f0)*xm+rc); % core branch impedance
    s = logspace(-4,0,500); % slip range
    zr = j*(f/f0)*x2 + r2 ./ s; % rotor impedance
    zag = zr .*zc ./ (zr+zc); % air gap impedance
    zt = r1+j*(f/f0)*x1 + zag; % terminal impedance
    It = vr(k)*V ./ zt; % terminal current
    I2 = It .* zc ./ (zc + zr); % secondary current
    Te = 3*(p/om) * r2 .* abs(I2) .^2 ./ s;% torque
    N = (60*f/p) .* (1-s);

    plot(N, Te)
end
hold off
title('Problem 2, Part 7')
ylabel('N-m')
xlabel('RPM')
grid on

% Problem 3: continuation of adjustable voltage
T_l = 100; % constant load characteristic
F = 15:5:150; % this frequency range
V_ph = zeros(size(F));
P_in = zeros(size(F)); % scratch space
P_out = zeros(size(F));
PFact = zeros(size(F));
Efficiency = zeros(size(F));
Nr = zeros(size(F));
for k = 1:length(F) % set volts/Hz
    if f<60

```

```

        V_ph(k) = V*F(k)/60;
    else
        V_ph(k) = V;
    end
end

% now do the calculation: should be familiar by now

for k = 1:length(F)
    f = F(k);
    Vt = V_ph(k);
    om = 2*pi*f; % frequency in radians/second
    zc = j*(f/f0)*xm*rc/(j*(f/f0)*xm+rc); % core branch impedance
    s = logspace(-4,0,500); % slip range
    zr = j*(f/f0)*x2 + r2 ./ s; % rotor impedance
    zag = zr .*zc ./ (zr+zc); % air gap impedance
    zt = r1+j*(f/f0)*x1 + zag; % terminal impedance
    It = Vt ./ zt; % terminal current
    I2 = It .* zc ./ (zc + zr); % secondary current
    T_em = 3 * (p/om) .*r2 .* abs(I2) .^2 ./ s; % shaft torque
    % now we find the slip for the load torque
    if max(T_em) < T_l % all done
        kmax = k-1;
        break;
    else
        for kk = 1:length(s)-1
            if T_em(kk) < T_l && T_em(kk+1) > T_l,
                kr = kk;
                break;
            end
        end
        % improve our guess by linear interpolation
        sr = s(kr) + (s(kr+1)-s(kr)) * (T_l - T_em(kr))/(T_em(kr+1)-T_em(kr));
        % now do the calculation at this point

        zrr = j*(f/f0)*x2 + r2 / sr; % rotor impedance
        zagr = zrr *zc / (zrr+zc); % air gap impedance
        ztr = r1+j*(f/f0)*x1 + zagr; % terminal impedance
        Itr = Vt / ztr; % terminal current
        I2r = Itr * zc / (zc + zrr); % secondary current
        P_out(k) = 3 * (r2/sr) * abs(I2r) .^2; % - Pf*(f/f0)^3; % net shaft power
        P_in(k) = real(3*Vt*conj(Itr)); % real power in
        Q_in(k) = imag(3*Vt*conj(Itr)); % real power out
        Nr(k) = (60*f/p)*(1-sr); % rotational speed
        VA = sqrt(P_in(k)^2 + Q_in(k)^2);
    end
end

```

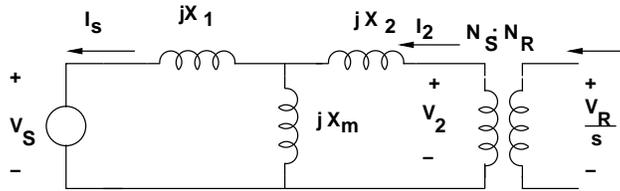


Figure 12: Doubly Fed Induction Machine Equivalent Circuit

```

Efficiency(k) = P_out(k)/P_in(k);
PFact(k) = P_in(k)/VA;
end
end

% now need to clip all of these to match actual capacity
Nrp = Nr(1:kmax);
P_inp = P_in(1:kmax);
P_outp = P_out(1:kmax);
PFactp = PFact(1:kmax);
Effp = Efficiency(1:kmax);

figure(6)
plot(Nrp, P_inp, Nrp, P_outp);
title('Problem 3')
ylabel('Watts')
xlabel('RPM')
legend('Power In', 'Power Out')
grid on

figure(7)
plot(Nrp, Effp, Nrp, PFactp)
title('Problem 3')
ylabel('per-unit')
xlabel('RPM')
legend('Efficiency', 'Power Factor')
grid on

```

Problem 4: DFM as Wind Generator If we take the liberty of ignoring resistances, the DFM can be represented as shown in 12

Noting the sign convention here, we know that power input to the rotor is related to power output from the stator by:

$$P_R = sP_S$$

Then, since mechanical power into the machine must be equal to the difference between these:

$$P_M = P_S - P_R$$

We can find power out of the stator of the machine

$$P_S = \frac{P_M}{1-s}$$

If, as stated in the problem description, the system side of the bidirectional converter is interacting with the power system at unity power factor, meaning zero reactive power, all reactive power to the system must be supplied by the stator, so that, using pf as power factor:

$$Q_S = P_M \left(\frac{1}{pf^2} - 1 \right)$$

Real and reactive power are:

$$P_S + jQ_S = 3VI^*$$

which means that terminal current (in this case *out* of the stator is:

$$I_S = \frac{P_S + jQ_S}{3V}$$

Keeping within the system frequency part of the equivalent circuit, we can find voltage across the magnetizing branch:

$$V_m = V + jX_1 I_S$$

The resulting current through the magnetizing branch is:

$$I_m = \frac{V_m}{jX_m}$$

and since $I_2 = I_S + I_m$,

$$V_2 = V_m + jX_2 I_2$$

Real and reactive power into the rotor, apparent from the stator frame, are:

$$P_2 + jQ_2 = 2V_2 I_2^*$$

And then real and reactive power at the terminals of the rotor (slip rings) are:

$$\begin{aligned} P_R &= sP_2 \\ Q_R &= |s|Q_2 \end{aligned}$$

Alternatively, rotor voltage and current can be seen to be modified by the stator to rotor transformer ratio and, in the case of voltage, slip:

$$\begin{aligned} V_R &= \frac{N_R}{N_S} sV_2 \\ I_R &= \frac{N_S}{N_R} I_2 \end{aligned}$$

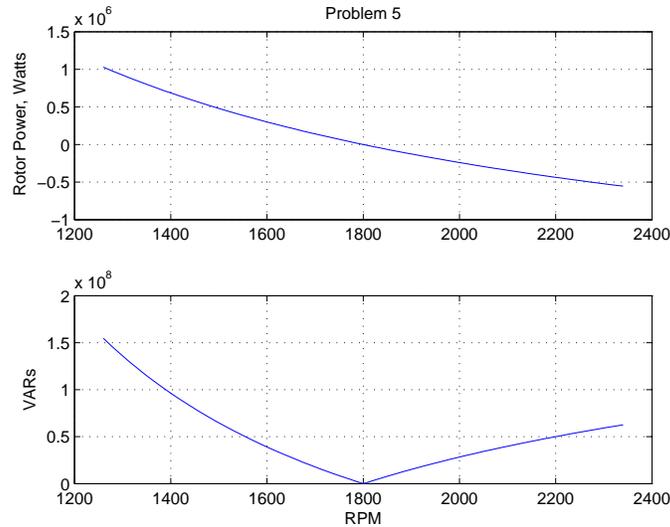


Figure 13: Real and Reactive Power into Slip Rings of DFM

There is one subtlety here: for negative values of slip, where rotor power is negative (that is real power is coming out of the rotor), the phase sequence on the rotor reverses, so that the reactive component of current changes sign (with respect to positive slip). This gives an extra sign change to reactive power, which is why it is multiplied by $|s|$.

The calculations described here are carried out in the attached script and result in:

Problem 4

+30 percent slip

Rotor Real Power = 1.02857e+06 W Reactive = 1.54624e+08 VARs

-30 percent slip

Rotor Real Power = -553846 W Reactive = 6.26373e+07 VARs

Problem 5: More DFM as Wind Turbine There is relatively little new in this, beyond what was done in Problem 4, aside from finding rotor speed, which is:

$$N_m = \frac{60f}{p} (1 - s)$$

The calculations described above are carried out for a collection of points in slip and then cross-plotted against speed in RPM, and the results are shown in Figure 13

Matlab Code for Problems 4 and 5

```

% Problem Set 10, Problems 4 and 5
% data

f = 60;                % system frequency
p = 2;                % pole pairs
om = 2*pi*f;          % radians per second
Pm = 2.4e6;           % turbine power
pf = 0.8;             % power factor
Vs = 690/sqrt(3);     % stator voltage
N = 3;

X1 = om*(.0035+.00175); % machine reactances
X2 = om*(.0315+.01575)/N^2; % referred to the stator
Xm = om*.0104/N;

s = .3:(-.01):-0.3;   % this is the range of speeds
Ps = Pm ./ (1-s);     % stator OUTPUT power
Q0 = Pm *(1/pf^2 - 1); % reactive power

Qs = Q0 .* ones(size(Ps)); % so they match

Is = (Ps - j .* Qs) ./ (3*Vs); % terminal current

Vm = Vs + j*X1 .* Is; % magnetizing branch voltage
Im = Vm ./ (j*Xm);
I2 = Is + Im;         % rotor side current
V2 = Vm + j*X2 .* I2; % rotor voltage

P2 = 3 .* real(V2 .* conj(I2));
Q2 = 3 .* imag(V2 .* conj(I2));

Pr = s .* P2;
Qr = abs(s) .* Q2;

% alternate calc

Ir = I2 ./ N;
Vr = V2 .* N .* s;

Pra = 3 .* real(Vr .* conj(Ir));
Qra = 3 .* imag(Vr .* conj(Ir));

% Problem 4

Pr1 = Pr(1);

```

```

Pr2 = Pr(length(Pr));

Qr1 = Qr(1);
Qr2 = Qr(length(Pr));

% check
Pr1a = Pra(1);
Pr2a = Pra(length(Pr));

Qr1a = Qra(1);
Qr2a = Qra(length(Pr));

fprintf('Problem 4\n')
fprintf('+30 percent slip\n')
fprintf('Rotor Real Power = %g W   Reactive = %g VARs\n', Pr1, Qr1)
fprintf('-30 percent slip\n')
fprintf('Rotor Real Power = %g W   Reactive = %g VARs\n', Pr2, Qr2)
fprintf('Check:\n')
fprintf('+30 percent slip\n')
fprintf('Rotor Real Power = %g W   Reactive = %g VARs\n', Pr1a, Qr1a)
fprintf('-30 percent slip\n')
fprintf('Rotor Real Power = %g W   Reactive = %g VARs\n', Pr2a, Qr2a)

% Problem 5
RPM = (60*f/p) .* (1-s);

figure(1)
subplot 211
plot(RPM, Pr)
title('Problem 5')
ylabel('Rotor Power, Watts')
grid on
subplot 212
plot(RPM, Qr)
ylabel('VARs')
xlabel('RPM')
grid on

```

MIT OpenCourseWare
<http://ocw.mit.edu>

6.061 / 6.690 Introduction to Electric Power Systems
Spring 2011

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.