

Massachusetts Institute of Technology
Department of Electrical Engineering and Computer Science
6.111 – Introductory Digital Systems Laboratory

Problem Set 3 Solutions


Issued: September 30, 2002

Problem 1

(a)

Q_A	Q_B	X	D_A	D_B	Z
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	0	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1

(b)

 

(c)

-- This is a sample solution to Problem set 3

```

library ieee;
use ieee.std_logic_1164.all;
use work.std_arith.all;
entity cd_fsm is port(
  clk      : in std_logic;
  reset    : in std_logic;
  X        : in std_logic;
  Z        : out std_logic;
  stateout : out std_logic_vector(1 downto 0));
end cd_fsm;

```

```

architecture state_machine of cd_fsm is
  type StateType is (ZeroZero, ZeroOne, OneZero, OneOne);
  signal present_state, next_state : StateType;

```

```

begin --state_machine
  with present_state select
    stateout <=
      "00" when ZeroZero,
      "11" when OneOne,
      "01" when ZeroOne,
      "10" when OneZero,
      "10" when others;

```

-- combinational process, Z changes even when state does not change

```

state_comb:process(present_state, X)
begin
  case present_state is
    when ZeroZero =>
      next_state <= ZeroZero;
      Z <= X;
    when ZeroOne =>
      if X = '1' then
        next_state <= OneZero;
      else
        next_state <= ZeroZero;
      end if;
      Z <= '1';
    when OneZero =>
      if X = '1' then
        next_state <= OneOne;
      else
        next_state <= ZeroOne;
      end if;
      Z <= X;
    when OneOne =>
      next_state <= OneOne;
      Z <= '1';
  end case;
end process;

```


```

when others =>
  next_state <= OneZero;
  Z <= '0';
end case;
--present_state;
end process;
--state_comb;

state_clocked:process(clk, reset) begin -- state transitions
  if (reset = '1') then
    present_state <= ZeroOne;
  elsif rising_edge(clk) then
    present_state <= next_state;
  end if;
end process state_clocked;
end state_machine;

```

(d)

 

Problem 2

(a)

Q_C	Q_B	Q_A	U/D	D_C	D_B	D_A
0	0	0	0	1	1	1
0	0	0	1	0	0	1
0	0	1	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	0	1	1
0	1	1	0	0	1	0
0	1	1	1	1	0	0
1	0	0	0	0	1	1
1	0	0	1	1	0	1
1	0	1	0	1	0	0
1	0	1	1	1	1	0
1	1	0	0	1	0	1
1	1	0	1	1	1	1
1	1	1	0	1	1	0
1	1	1	1	0	0	0

On reset, D_C , D_B , D_A should be set to 0.


(b)

QcQb	00	01	11	10
QaU	1	0	1	0
01	0	0	1	1
11	0	1	0	1
10	0	0	1	1

QcQb	00	01	11	10
QaU	1	1	1	1
01	1	1	1	1
11	0	0	0	0
10	0	0	0	0

QcQb	00	01	11	10
QaU	1	0	0	1
01	0	1	1	0
11	1	0	0	1
10	0	1	1	0

(c)

 **Problem 3**

(a)

Inputs should be connected as follows:

A = 1

B = C = D = 0

 $/LD = Q_A \text{ nand } Q_D$ $/CLR = 1$

(b)

Inputs should be connected as follows:

$$A = 0$$

$$B = \text{not } Q_B$$

$$C = Q_C \text{ or } (Q_B \text{ and not } Q_D)$$

$$D = (\text{not } Q_D \text{ and } Q_C \text{ and } Q_B) \text{ or}$$

$$(Q_D \text{ and not } Q_B) \text{ or}$$

$$(Q_D \text{ and not } Q_C)$$

$$/LD = 0$$

$$/CLR = 1$$

(c)

Inputs should be connected as follows:

$$A = Q_B \text{ and not } Q_A$$

$$B = (\text{not } Q_D \text{ and not } Q_C) \text{ or } (Q_D \text{ and } Q_C)$$

$$C = (\text{not } Q_D \text{ and } Q_B \text{ and } Q_A) \text{ or } (Q_D \text{ and } Q_B \text{ and not } Q_A)$$

$$D = Q_C$$

$$/LD = 0$$

$$/CLR = 1$$