

Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science  
6.111 Introductory Digital Systems Laboratory

Lecture # 2

Now some basics (This IS about digital logic...)

The values here (x and y) represent something like voltage (is it +5 volts (1) or zero (0)? Or is a light ON or OFF?

(That is, anything that can take on one of two values)

Slice

**AND:**

x	y	x • y
0	0	0
0	1	0
1	0	0
1	1	1

**OR:**

x	y	x + y
0	0	0
0	1	1
1	0	1
1	1	1

**NOT:**

x	$\bar{x}$
0	1
1	0

Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science  
6.111 Introductory Digital Systems Laboratory

**Identities:**

Boolean Algebra

Elementary:

$$A * 0 = 0$$

$$A * 1 = A$$

$$A * A = A$$

$$A * \bar{A} = 0$$

$$A + 1 = 1$$

$$A + 0 = A$$

$$A + A = A$$

$$A + \bar{A} = 1$$

Commutative:

$$A * B = B * A$$

$$A + B = B + A$$

Distributive:

$$A * (B + C) = A * B + A * C$$

$$A + (B * C) = (A + B) * (A + C)$$

Absorption:

$$A * (A + B) = A$$

$$A + (A * B) = A$$

DeMorgan's:

$$A * (\bar{A} + B) = A * B$$

$$A + (\bar{A} * B) = A + B$$

Consensus:

$$(A + B) * (\bar{A} + C) * (B + C) \\ = (A + B) * (\bar{A} + C)$$

$$A * B + \bar{A} * C + B * C \\ = A * B + \bar{A} * C$$

Massachusetts Institute of Technology  
 Department of Electrical Engineering and Computer Science  
 6.111 Introductory Digital Systems Laboratory

**DeMorgan's Theorem:**

$$\overline{A \bullet B \bullet \dots} = \overline{A} + \overline{B} + \dots$$

$$\overline{A + B + \dots} = \overline{A} \bullet \overline{B} \bullet \dots$$

**Duality:**

$$F(A, B, 0, 1, *, +) = \overline{F}(\overline{A}, \overline{B}, 1, 0, +, *)$$

$$F_d(A, B, 1, 0, +, *) = \overline{F_d}(\overline{A}, \overline{B}, 0, 1, *, +)$$

**Proof of DeMorgan's Theorem:**

$x$	$y$	$x + y$	$\overline{(x + y)}$	$\overline{x}$	$\overline{y}$	$\overline{x} \bullet \overline{y}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

$x$	$y$	$x \bullet y$	$\overline{(x \bullet y)}$	$\overline{x}$	$\overline{y}$	$\overline{x} + \overline{y}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science  
6.111 Introductory Digital Systems Laboratory

Massachusetts Stoplight Example

F=1 implies stoplight is working correctly

F=0 implies stoplight is busted

Slide 3

Truth Table:

r	y	g	F	F =
0	0	0	0	
0	0	1	1	$\bar{r} \cdot \bar{y} \cdot g +$
0	1	0	1	$\bar{r} \cdot y \cdot \bar{g} +$
0	1	1	0	
1	0	0	1	$r \cdot \bar{y} \cdot \bar{g} +$
1	0	1	0	
1	1	0	1	$r \cdot y \cdot \bar{g}$
1	1	1	0	

Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science  
6.111 Introductory Digital Systems Laboratory

Obsolete Stoplight Example: Reduction using Boolean Algebra

$$F = R * /Y * /G + /R * Y * /G + /R * /Y * G + R * Y * /G$$

Step 1: Since  $Y + /Y = 1$ , [Slide 3](#)

$$R*/Y*/G + R*Y*/G = R*(Y + /Y) * /G = R * /G$$

$$F = R * /G + /R * Y * /G + /R * /Y * G$$

Step 2: Use Absorption:  $R + /R * Y = R + Y$

$$R*/G + /R * Y * /G = (R + /R * Y) * /G = (R + Y) * /G$$

$$F = (R + Y) * /G + /R * /Y * G = R * /G + Y * /G + /R * /Y * G$$

Using Demorgan:

$$/F = ((/R * /Y) + G) * (/G + (R * Y)) = /R*/Y*/G + G * (R + Y)$$

Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science  
6.111 Introductory Digital Systems Laboratory

Truth Table:

r	y	g	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Or look at the zeros:

$$\overline{F} = \overline{r} \cdot \overline{y} \cdot \overline{g} + \overline{r} \cdot y \cdot g + r \cdot \overline{y} \cdot g + r \cdot y \cdot \overline{g}$$

Slide 3

Which, by Demorgan (Duality) is:

$$F = (\overline{r} + \overline{y} + \overline{g}) \cdot (\overline{r} + y + g) \cdot (r + \overline{y} + g) \cdot (r + y + g)$$

Massachusetts Institute of Technology  
 Department of Electrical Engineering and Computer Science  
 6.111 Introductory Digital Systems Laboratory

**Common Logic Functions and Gate Symbols**

**AND**



x	y	f
0	0	0
0	1	0
1	0	0
1	1	1

**OR**



x	y	f
0	0	0
0	1	1
1	0	1
1	1	1

**NAND**  
(Not AND)




x	y	f
0	0	1
0	1	1
1	0	1
1	1	0


**NOR**  
(Not OR)




x	y	f
0	0	1
0	1	0
1	0	0
1	1	0

**Karnaugh Maps are:**

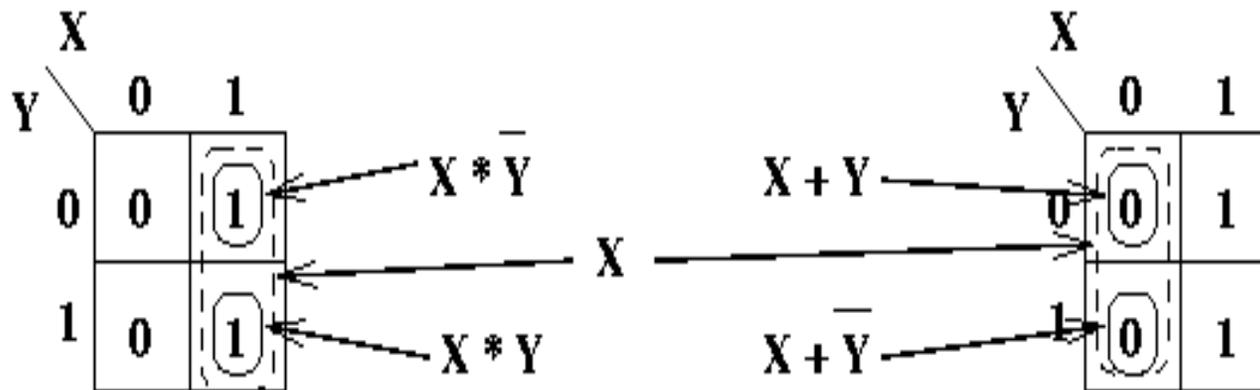1. A simple re-mapping of truth tables
2. A graphical means of reducing logic functions




$$X = X * Y + X * \bar{Y}$$


$$\bar{X} = (\bar{X} * Y) * (\bar{X} * \bar{Y})$$

Massachusetts Institute of Technology  
 Department of Electrical Engineering and Computer Science  
 6.111 Introductory Digital Systems Laboratory

Logic Function Implementation: Gates

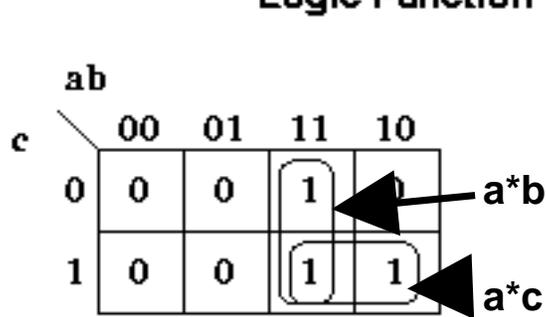


$$F = a * b + a * c$$

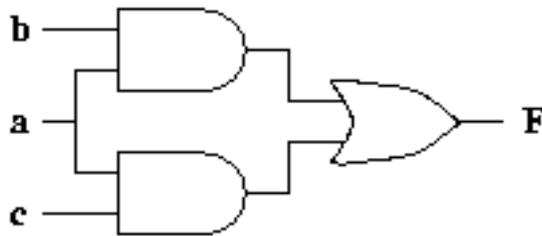


MSP: OR of ANDs  
 Circle 1's

$$F = a*b + a*c = a*(b+c)$$

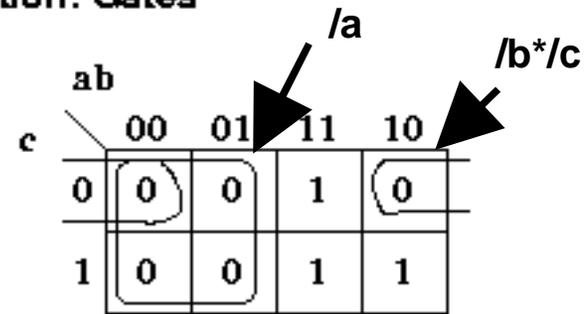

$$F = a * (b + c)$$

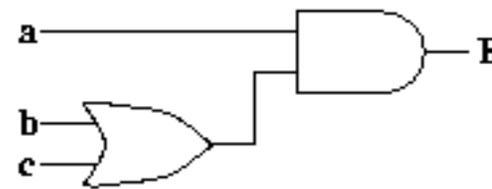

MPS: AND of ORs  
 Circle 0's

$$/F = /( /a + /(b+c)) = /( /a + (/b * /c))$$

$$F = /a + /b * /c$$

Massachusetts Institute of Technology  
 Department of Electrical Engineering and Computer Science  
 6.111 Introductory Digital Systems Laboratory

**K- maps are useful for 3-6 variables (HARD for > 4!)  
 Adjacent cells have one bit change, like a Gray Code**

**Karnaugh Maps**

**Truth Table**

A	B	C	Cell
0	0	0	0
0	0	1	1
0	1	0	2
0	1	1	3
1	0	0	4
1	0	1	5
1	1	0	6
1	1	1	7

		A	
		0	1
BC	00	0	4
	01	1	5
	11	3	7
	10	2	6

		AB			
		00	01	11	10
C	0	0	2	6	4
	1	1	3	7	5

Massachusetts Institute of Technology  
 Department of Electrical Engineering and Computer Science  
 6.111 Introductory Digital Systems Laboratory

		<b>ab</b>			
	<b>cd</b>	<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>
<b>00</b>		<b>0</b>	<b>4</b>	<b>C</b>	<b>8</b>
<b>01</b>		<b>1</b>	<b>5</b>	<b>D</b>	<b>9</b>
<b>11</b>		<b>3</b>	<b>7</b>	<b>F</b>	<b>B</b>
<b>10</b>		<b>2</b>	<b>6</b>	<b>E</b>	<b>A</b>

**4- Input K map**

		<b>ab</b>						<b>a</b>
	<b>cd</b>	<b>00</b>	<b>01</b>	<b>11</b>	<b>10</b>			
—	<b>00</b>							
	<b>01</b>							
<b>c</b> —	<b>11</b>							
—	<b>10</b>							
								<b>b</b>


**Inputs group like this**

Massachusetts Institute of Technology  
 Department of Electrical Engineering and Computer Science  
 6.111 Introductory Digital Systems Laboratory

**Massachusetts Stoplight Check Function**


		ry			
		00	01	11	10
g	0	0	1	1	1
	1	1	0	0	0
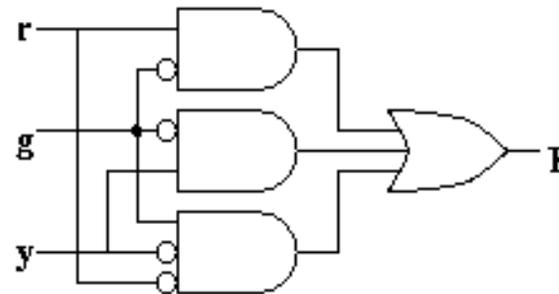
$$\text{MSP} = r \cdot /g + y \cdot /g + /r \cdot /y \cdot g$$




		ry			
		00	01	11	10
g	0	0	1	1	1
	1	1	0	0	0
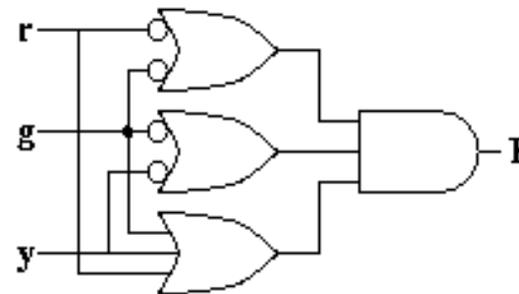
$$\text{MPS} = (/r + /g) \cdot (/y + /g) \cdot (r + y + g)$$




Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science  
6.111 Introductory Digital Systems Laboratory

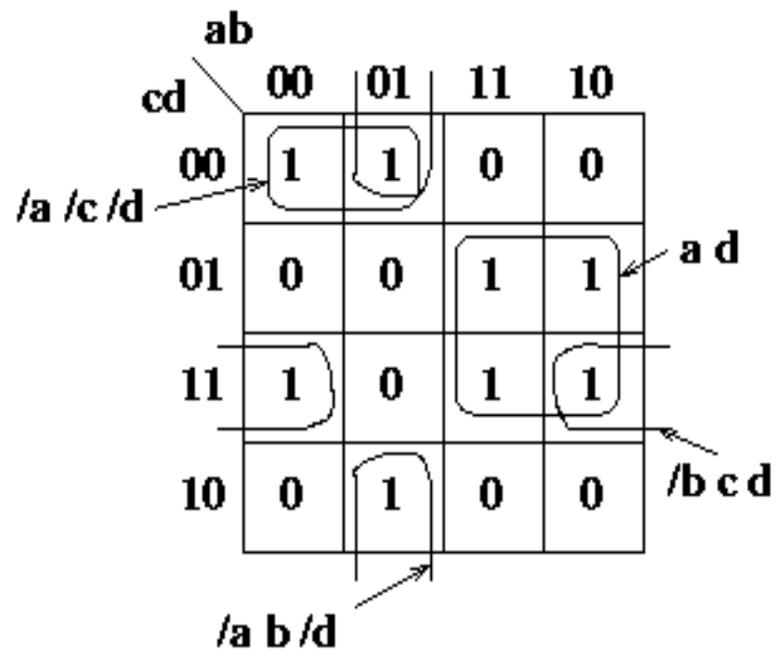**The simplest groups are the largest: this is how we can use K-maps to simplify logical expressions**



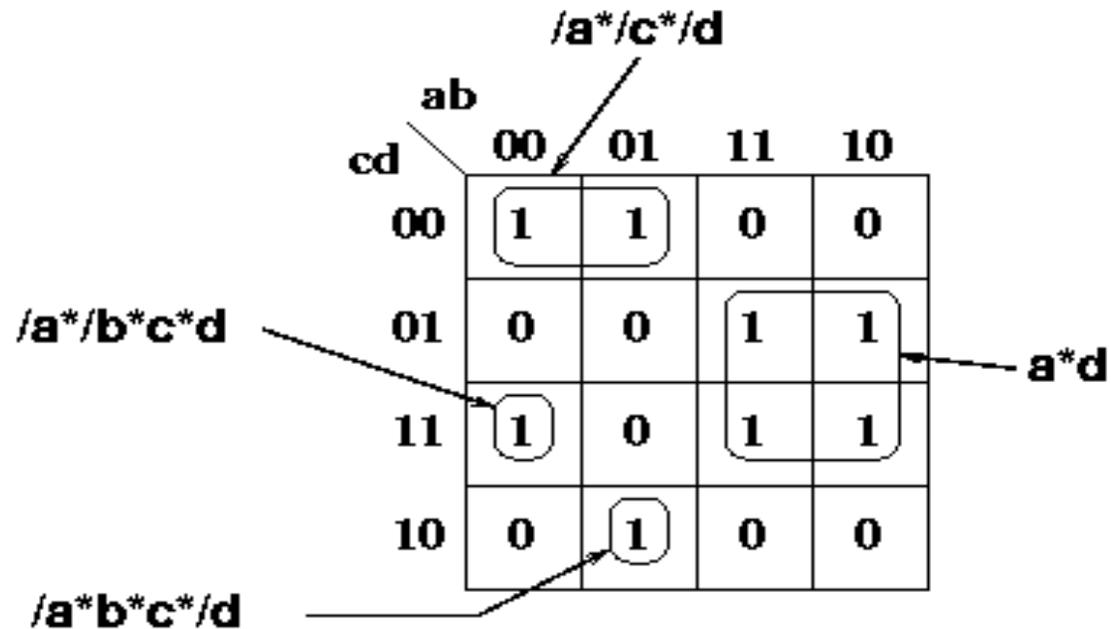**Simplest Groupings are the largest**  
**This one is more complex than need be!**



Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science  
6.111 Introductory Digital Systems Laboratory

**Groupings may not be unique!**

		ab			
		00	01	11	10
cd	00	1	1	0	0
	01	0	1	1	0
	11	0	0	1	1
	10	1	0	0	1

		ab			
		00	01	11	10
cd	00	1	1	0	0
	01	0	1	1	0
	11	0	0	1	1
	10	1	0	0	1

Massachusetts Institute of Technology  
 Department of Electrical Engineering and Computer Science  
 6.111 Introductory Digital Systems Laboratory

Or MSP may be unique and MPS not, or vice versa

	ab			
cd	0	1	1	0
	1	0	1	1
	0	0	1	1
	0	1	1	0

$$F = b/d + a d + /b /c d$$

	ab			
cd	0	1	1	0
	1	0	1	1
	0	0	1	1
	0	1	1	0

$$F = (b + d) * (a + /b + /d) * (a + /c + /d)$$

	ab			
cd	0	1	1	0
	1	0	1	1
	0	0	1	1
	0	1	1	0

$$F = (b + d) * (a + /b + /d) * (a + b + /c)$$

Massachusetts Institute of Technology  
 Department of Electrical Engineering and Computer Science  
 6.111 Introductory Digital Systems Laboratory

**"Don't Cares" can simplify things: (impossible inputs, for example)**

		a b			
		00	01	11	10
c d	00	1	0	0	1
	01	0	X	1	X
	11	1	1	X	0
	10	1	0	0	1

		a b			
		00	01	11	10
c d	00	1	0	0	1
	01	0	X	1	X
	11	1	1	X	0
	10	1	0	0	1

$$MSP = \overline{b} \overline{d} + b d + \overline{a} c d \quad MPS = (\overline{b} + d) * (\overline{a} + \overline{c} + \overline{d}) * (a + c + \overline{d})$$

Here  $abcd = 0101, 1111$  and  $1001$  are "don't care"s

Note that MSP may not equal MPS (and doesn't here)

Massachusetts Institute of Technology  
 Department of Electrical Engineering and Computer Science  
 6.111 Introductory Digital Systems Laboratory


Now, there are some functions you can't do very much with:

Like this one: a "parity" function

		ab			
		00	01	11	10
c	0	0	1	0	1
	1	1	0	1	0


$$\begin{aligned}
 F &= \bar{a} \bar{b} \bar{c} + \bar{a} \bar{b} c + \bar{a} b \bar{c} + a \bar{b} \bar{c} + a \bar{b} c + a b \bar{c} + a b c \\
 &= (\bar{a} \bar{b} + a \bar{b}) \bar{c} + (\bar{a} \bar{b} + a \bar{b}) c \\
 &= (a \oplus b) \bar{c} + \overline{(a \oplus b)} c \\
 &= (a \oplus b) \oplus c
 \end{aligned}$$

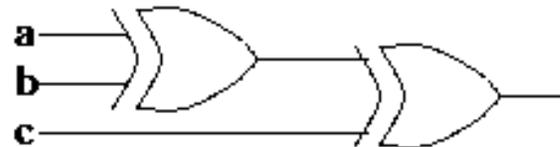It can be implemented with this (new) function, the "exclusive OR"




Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science  
6.111 Introductory Digital Systems Laboratory

**Exclusive OR**       $F = X \oplus Y$

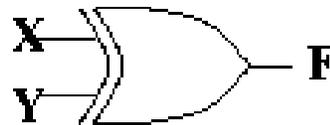

<b>X</b>	<b>Y</b>	<b>F</b>
<b>0</b>	<b>0</b>	<b>0</b>
<b>0</b>	<b>1</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>0</b>

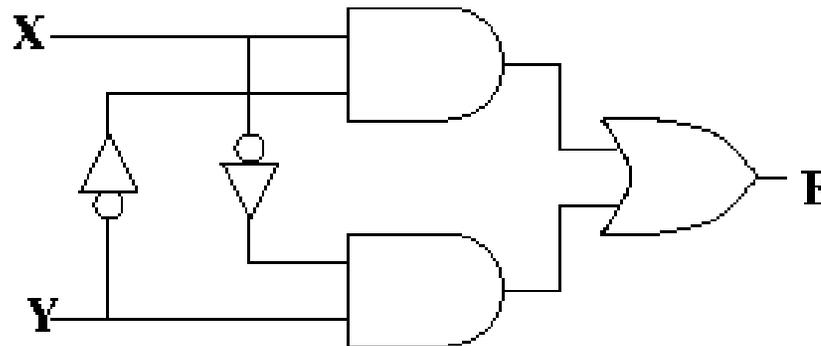

Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science  
6.111 Introductory Digital Systems Laboratory

**if file foo.txt contains:**

```
a = (x + z) * (/x + y) * (z + y);  
b = a ^ c;  
d = x * a;
```

Slide 3

**then if you do:**



```
reduce -b < foo.txt > foo_out.txt
```

**you get in foo.out:**



```
a = x * y + /x * z;  
/a = x * /y + /x * /z;  
b = a * /c + /a * c;  
/b = /a * /c + a * c;  
d = x * a;  
/d = /a + /x;
```

Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science  
6.111 Introductory Digital Systems Laboratory

**Massachusetts Stoplight Check:**

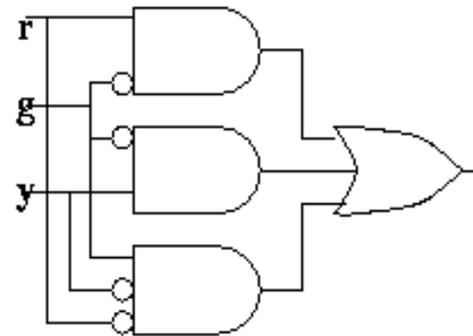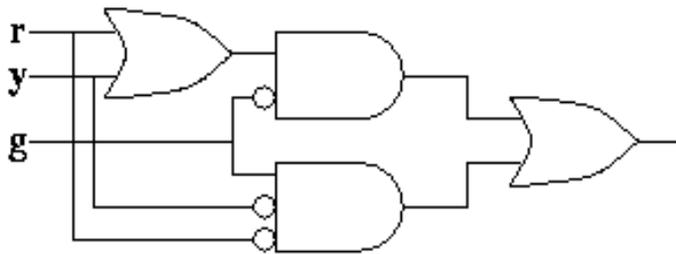


**Done with real gates: NAND's**

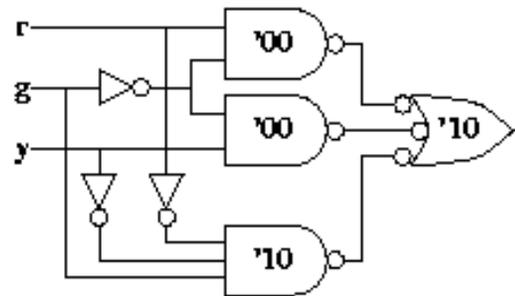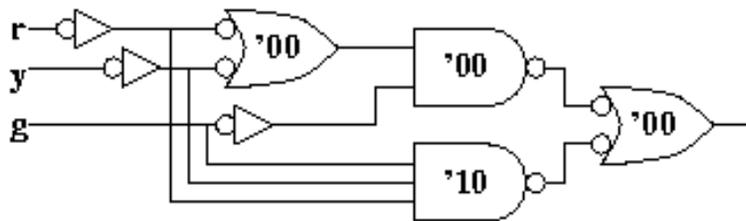


Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science  
6.111 Introductory Digital Systems Laboratory

Here it is with **NOR** gates

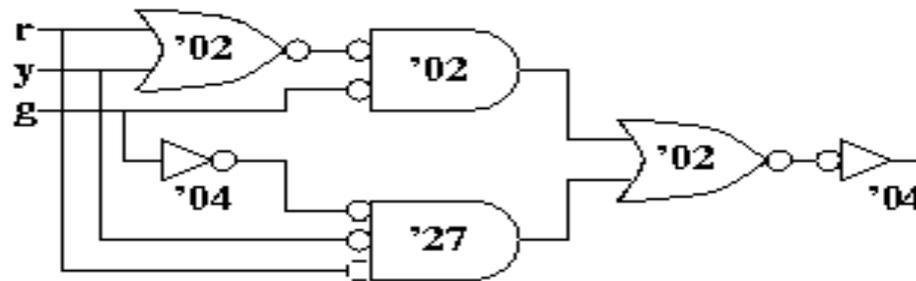
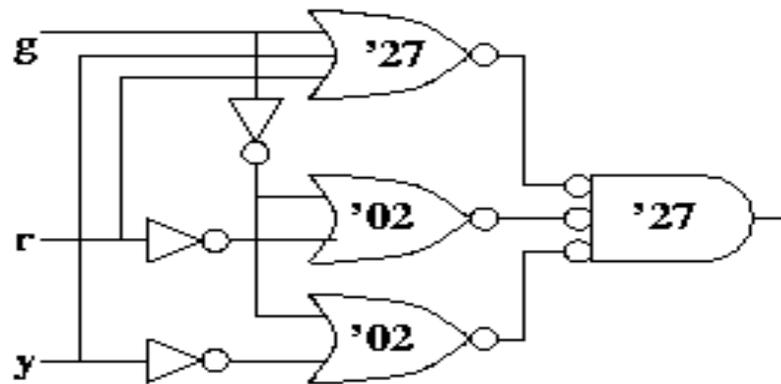
$$\mathbf{MPS = (r + y + g) * (/g + /r) * (/g + /y)}$$




Massachusetts Institute of Technology  
 Department of Electrical Engineering and Computer Science  
 6.111 Introductory Digital Systems Laboratory

**TTL logic requires current at its input.  
 This leads to loading limits.**

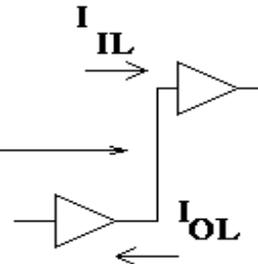**Here is the sign convention**

**Logical LOW dominates for MOST  
 gates.**





	Current (mA)		
	74LS	74S	74
<b>Output Capability <math>I_{OL}</math></b>	8	20	16
<b>Input Required <math>I_{IL}</math></b>	-0.4	-2	-1.6
<b>Equivalent LS Inputs</b>	1	5	4
<b>Output Can Drive LS Inputs</b>	20	50	40
<b>74 LS Can Drive</b>	20	4	5

**These are typical numbers, but there are many exceptions.  
 i.e. Read the data sheets to be sure.**

Voltage Levels For TTL:	Input	Output
<b>High</b>	> 2.0	> 2.7
<b>Low</b>	< 0.8	< 0.4


**Totem Pole Output  
(Common for TTL)**

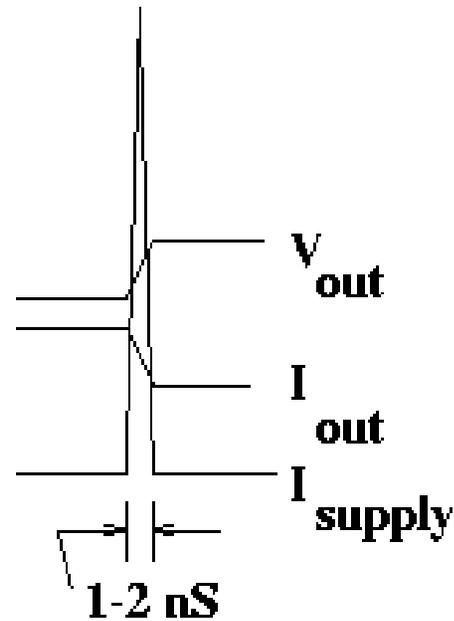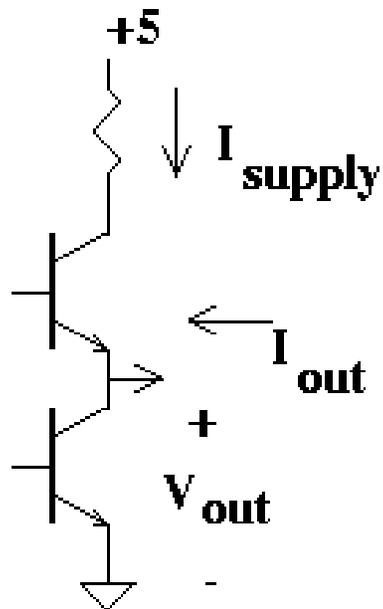


**TTL Totem Pole Outputs  
can draw LARGE current  
spikes on switching**

Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science  
6.111 Introductory Digital Systems Laboratory

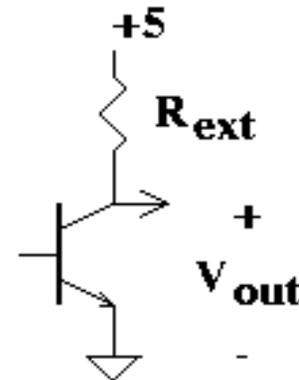**Some outputs are open collector: need a pull-up resistor. Speed is affected by  $R_{ext}$  and by external and junction capacitance**



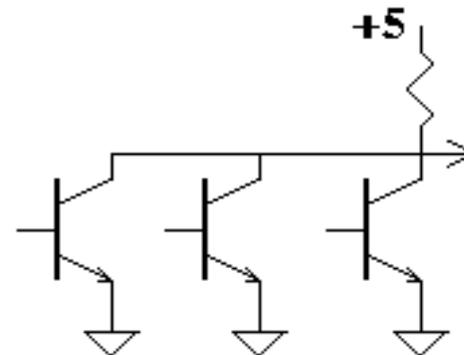**Open collector gates can be wired together like this to make 'wired AND's.**



**This is a 'bus' that can be driven by more than one input source**

**You can't do this with Totem Pole outputs!**


Massachusetts Institute of Technology  
 Department of Electrical Engineering and Computer Science  
 6.111 Introductory Digital Systems Laboratory

**Static Hazards: Consider this function:**

$$F = A * \bar{C} + B * C$$


		AB			
		00	01	11	10
C	0	0	0	1	1
	1	0	1	1	0

**Implemented with MSI gates:**

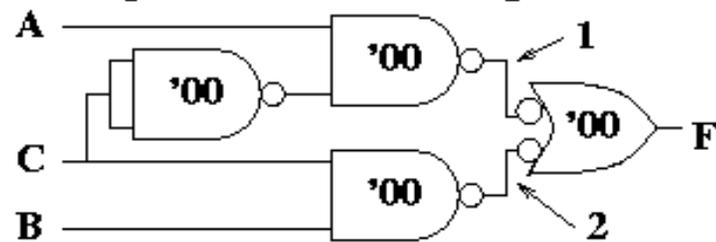

**Consider this transient:**

$$A = B = 1$$

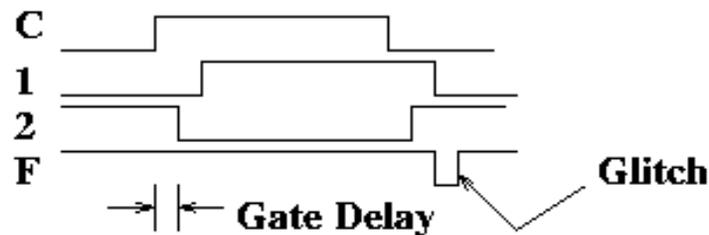

**The 'glitch is the result of timing differences in parallel data paths.**

Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science  
6.111 Introductory Digital Systems Laboratory

**The 'glitch is the result of timing differences in parallel data paths. It is associated with the function jumping between 'patches' or product terms on the K-map. To fix it, cover it up with another patch!**

		AB			
		00	01	11	10
C	0	0	0	1	1
	1	0	1	1	0

$$F = A * \bar{C} + B * C + A * B$$

