

Massachusetts Institute of Technology
Department of Electrical Engineering and Computer Science
6.111 - Introductory Digital Systems Laboratory

Problem Set 1 Solutions

Issued: February 8, 2006

Boolean Algebra Practice Problems (*not graded*)


- 1) $a + 0 = a$
- 2) $\bar{a} \cdot 0 = 0$
- 3) $a + \bar{a} = 1$
- 4) $a + a = a$
- 5) $a + ab = a(1 + b) = a$
- 6) $a + \bar{a}b = (a + \bar{a})(a + b) = a + b$
- 7) $a(\bar{a} + b) = a\bar{a} + ab = ab$
- 8) $ab + \bar{a}b = b(a + \bar{a}) = b$
- 9) $(\bar{a} + \bar{b})(\bar{a} + b) = \bar{a}\bar{a} + \bar{a}b + \bar{b}\bar{a} + \bar{b}b = \bar{a} + \bar{a}b + \bar{a}\bar{b} = \bar{a}(1 + b + \bar{b}) = \bar{a}$
- 10) $a(a + b + c + \dots) = aa + ab + ac + \dots = a + ab + ac + \dots = a$
- 11) $f(a, b, ab) = a + b + ab = a + b$
- 12) $f(a, b, \bar{a} \cdot \bar{b}) = a + b + \bar{a}\bar{b} = a + b + \bar{a} = 1$
- 13) $f[a, b, (\bar{a}b)] = a + b + \overline{(\bar{a}b)} = a + b + \bar{a} + \bar{b} = 1$
- 14) $y + y\bar{y} = y$
- 15) $xy + x\bar{y} = x(y + \bar{y}) = x$
- 16) $\bar{x} + y\bar{x} = \bar{x}(1 + y) = \bar{x}$
- 17) $(w + \bar{x} + y + \bar{z})y = y$
- 18) $(x + \bar{y})(x + y) = x$
- 19) $w + [w + (wx)] = w$
- 20) $x[x + (xy)] = x$
- 21) $\overline{(\bar{x} + \bar{x})} = x$
- 22) $\overline{(x + \bar{x})} = 0$
- 23) $w + (\bar{w}xyz) = w(1 + \bar{w}xyz) = w$
- 24) $\bar{w} \cdot \overline{(wxyz)} = \bar{w}(\bar{w} + \bar{x} + \bar{y} + \bar{z}) = \bar{w}$
- 25) $xz + \bar{x}y + zy = xz + \bar{x}y$
- 26) $(x + z)(\bar{x} + y)(z + y) = (x + z)(\bar{x} + y)$
- 27) $\bar{x} + \bar{y} + xy\bar{z} = \bar{x} + \bar{y} + \bar{z}$

Problem 1: Karnaugh Maps and Minimal Expressions


i) Truth Tables

abcd 1)	wxyz 2)
0000 0	0000 1
0001 1	0001 1
0010 0	0010 0
<u>0011 0</u>	<u>0011 1</u>
0100 0	0100 0
0101 1	0101 0
0110 0	0110 0
<u>0111 0</u>	<u>0111 1</u>
1000 0	1000 0
1001 0	1001 0
1010 0	1010 0
<u>1011 0</u>	<u>1011 0</u>
1100 0	1100 1
1101 0	1101 1
1110 1	1110 0
1111 0	1111 1

ii) Karnaugh Maps

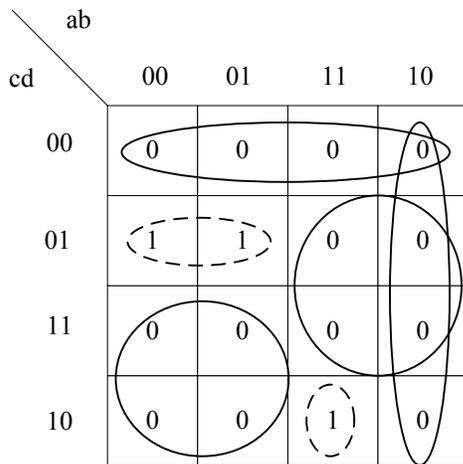

(1)

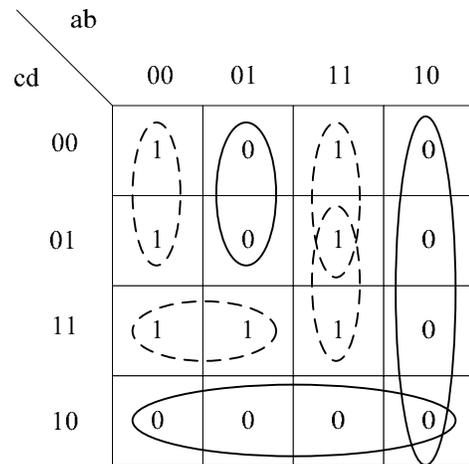

(2)

iii) Minimum Sum of Products

$$(1) \bar{a} \cdot \bar{c} \cdot d + a \cdot b \cdot c \cdot \bar{d}$$


$$(2) \bar{a} \cdot \bar{b} \cdot \bar{c} + a \cdot b \cdot \bar{c} + a \cdot b \cdot d + \bar{a} \cdot c \cdot d$$

iv) Minimum Product of Sums

$$(1) (c + d)(\bar{a} + b)(\bar{a} + \bar{d})(a + \bar{c})$$

$$(2) (\bar{c} + d)(\bar{a} + b)(a + \bar{b} + c)$$

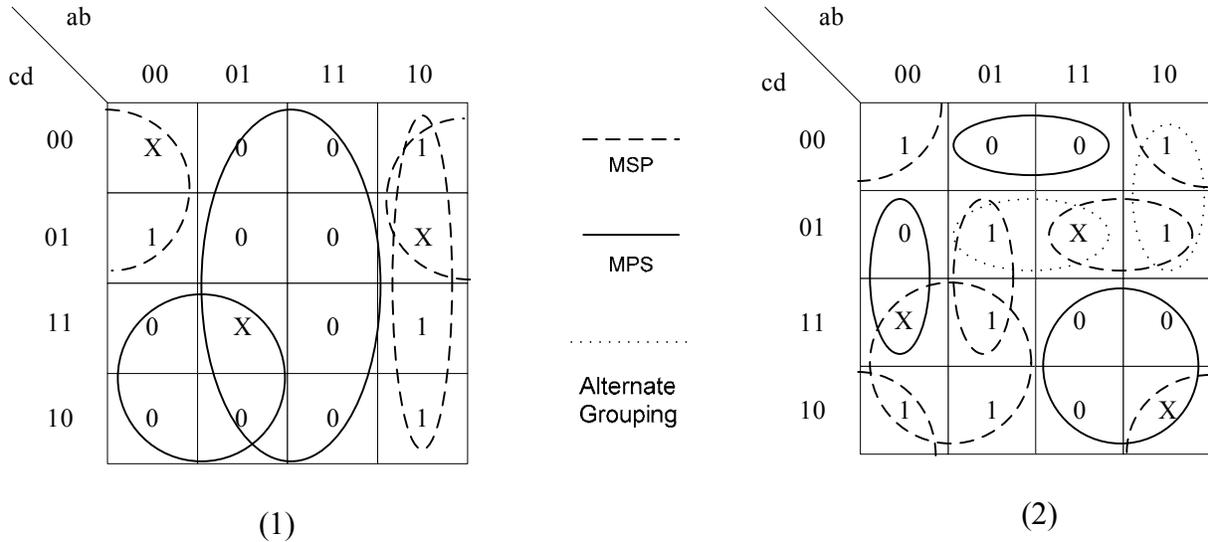Problem 2: Karnaugh Maps with “Don’t Cares”



(1)

- i. $\bar{b} \cdot \bar{c} + a \cdot \bar{b}$
- ii. $\bar{b} \cdot (\bar{c} + a)$
- iii. Both solutions are unique.
- iv. Yes, MSP = MPS

(2)


- i. $\bar{b} \cdot \bar{d} + c \cdot \bar{a} + \bar{a} \cdot b \cdot d + a \cdot \bar{c} \cdot d$
- ii. $(\bar{b} + c + d)(\bar{a} + \bar{c})(a + b + \bar{d})$
- iii. The MPS solution is unique, the MSP is not.
 In the MSP: $\bar{a} \cdot b \cdot d$ can be replaced with $\bar{c} \cdot b \cdot d$.
 $a \cdot \bar{c} \cdot d$ can be replaced with $a \cdot \bar{c} \cdot \bar{b}$.
- iv. No, MSP \neq MPS.

Problem 3: DeMorgan’s Theorem


- 1) $\overline{(a \cdot b \cdot c \cdot d)} = a + \bar{b} + c + d$
- 2) $\overline{(a + \bar{b} + c + \bar{d})} = a \cdot b \cdot \bar{c} \cdot d$
- 3) $(a \cdot \bar{d}) \cdot (\bar{b} \cdot c) \cdot (c \cdot \bar{d}) = a \cdot \bar{b} \cdot c \cdot \bar{d}$

Problem 4: Transistor/Gate Level Synthesis

- 1) Transistor implementation

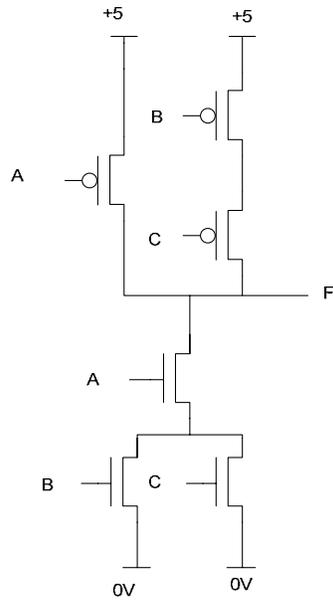

2) NAND gate implementation

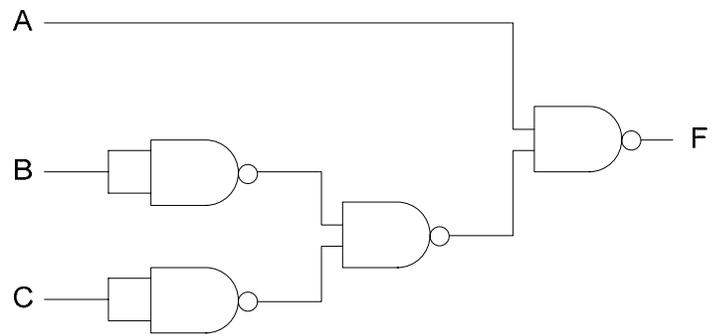

Problem 5: Setup and Hold times for D Flip-Flop

- 1) The setup time is twice the delay of the inverter, the hold time is zero.
- 2) The new memory element is a negative edge triggered flip-flop.
- 3) The setup time is $2t_{inv}$, the hold time is zero, and the clock to Q delay is $2t_{inv}$.