

L10: Analog Building Blocks (OpAmps, A/D, D/A)




Acknowledgement:

Materials in this lecture are courtesy of the following sources and are used with permission.

Dave Wentzloff

MIT Introduction to Operational Amplifiers


DC Model

 

- Typically very high input resistance $\sim 300\text{K}\Omega$
- High DC gain ($\sim 10^5$)
- Output resistance $\sim 75\Omega$


$$V_{out} = a(f) \cdot V_{in}$$

LM741 Pinout

 

Reprinted with permission of National Semiconductor Corporation.

 
Reprinted with permission of National Semiconductor Corporation.



The Inside of a 741 OpAmp




 
Reprinted with permission of National Semiconductor Corporation.




**Gain Is Sensitive to Operating Condition
(e.g., Device, Temperature, Power supply voltage, etc.)**

Reprinted with permission of National Semiconductor Corporation.

Simple Model for an OpAmp

  


Linear Mode

 


If $-V_{CC} < v_{out} < V_{CC}$

Negative Saturation

 

$v_{id} < -\varepsilon$


Positive Saturation

 

$v_{id} > \varepsilon$

Small input range for “Open” loop Configuration

The Power of (Negative) Feedback

 


$$\frac{v_{in} + v_{id}}{R_1} + \frac{v_{out} + v_{id}}{R_2} = 0 \quad v_{id} = \frac{v_{out}}{a} \quad \frac{v_{in}}{R_1} = -\frac{v_{out}}{a} \left[\frac{1}{R_1} + \frac{a}{R_2} + \frac{1}{R_2} \right]$$

$$\frac{v_{out}}{v_{in}} = -\frac{R_2 a}{(1+a)R_1 + R_2} \approx -\frac{R_2}{R_1} \text{ (if } a \gg 1)$$


- Overall (closed loop) gain does not depend on open loop gain
- Trade gain for robustness
- Easier analysis approach: “virtual short circuit approach”
 - $v_+ = v_- = 0$ if OpAmp is linear

Voltage Follower (buffer)

 


$$v_{out} \approx v_{in}$$

Differential Input

 


$$v_{out} \approx \frac{R_2}{R_1} (v_{in2} - v_{in1})$$

Non-inverting

 

$$v_{out} \approx \frac{R_1 + R_2}{R_1} v_{in}$$

Integrator

 

$$v_{out} \approx -\frac{1}{RC} \int_{-\infty}^t v_{in} dt$$

Use With Open Loop


Analog Comparator:

Is $V_+ > V_-$?




The Output is a DIGITAL signal

Analog Comparator: Analog to TTL


LM 311 Needs Pull-Up

 

LM311 is a single supply
comparator

   
A/D Conversion**D/A Conversion**

 - Quantization noise exists even with *ideal* A/D and D/A converters




Non-idealities in Data Conversion

 
Offset – a constant voltage offset that appears at the output when the digital input is 0



 
Gain error – deviation of slope from ideal value of 1




 Integral Nonlinearity – maximum deviation from the ideal analog output voltage



 Differential nonlinearity – the largest increment in analog output for a 1-bit change




 

$$V_{\text{out}} = \frac{1}{6} V_{\text{ref}} [B_7 + \frac{1}{2}B_6 + \frac{1}{4}B_5 + \dots + \frac{1}{128}B_0]$$

- Note that the driving point impedance (resistance) is the same for each cell.
- R-2R Ladder achieves large current division ratios with only two resistor values

DAC (AD 558) Specs

 

Input Logic Coding

Digital Input Code			Output Voltage	
Binary	Hexadecimal	Decimal	2.56 V Range	10.000 V Range
0000 0000	00	0	0	0
0000 0001	01	1	0.010 V	0.039 V
0000 0010	02	2	0.020 V	0.078 V
0000 1111	0F	15	0.150 V	0.586 V
0001 0000	10	16	0.160 V	0.625 V
0111 1111	7F	127	1.270 V	4.961 V
1000 0000	80	128	1.280 V	5.000 V
1100 0000	C0	192	1.920 V	7.500 V
1111 1111	FF	255	2.55 V	9.961 V

Image courtesy of Analog Devices. Used with permission.

- 8-bit DAC
- Single Supply Operation: 5V to 15V
- Integrates required references (bandgap voltage reference)
- Uses a R-2R resistor ladder
- Settling time 1µs
- Programmable output range from 0V to 2.56V or 0V to 10V
- Simple Latch based interface

Chip Architecture and Interface

 



Table I. AD558 Control Logic Truth Table

Input Data	\overline{CE}	\overline{CS}	DAC Data	Latch Condition
0	0	0	0	"Transparent"
1	0	0	1	"Transparent"
0	g	0	0	Latching
1	g	0	1	Latching
0	0	g	0	Latching
1	0	g	1	Latching
X	1	X	Previous Data	Latched
X	X	1	Previous Data	Latched

NOTES

X = Does not matter.

 g = Logic Threshold at Positive-Going Transition.



t_w = STORAGE PULSE WIDTH = 200ns MIN

t_{DH} = DATA HOLD TIME = 10ns MIN

t_{DS} = DATA SETUP TIME = 200ns MIN

$t_{SETTLING}$ = DAC OUTPUT SETTLING TIME TO $\pm 1/2$ LSB

**Outputs are noisy
when input bits settle,
so it is best to have inputs
stable before latching
the input data**


 


Figure 6. AD558 Control Logic Function

Image courtesy of Analog Devices. Used with permission.

Setting the Voltage Range

 

Very similar to a
non-inverting amp


Strap output for
different voltage
ranges

Input Logic Coding


Digital Input Code			Output Voltage	
Binary	Hexadecimal	Decimal	2.56 V Range	10.000 V Range
0000 0000	00	0	0	0
0000 0001	01	1	0.010 V	0.039 V
0000 0010	02	2	0.020 V	0.078 V
0000 1111	0F	15	0.150 V	0.586 V
0001 0000	10	16	0.160 V	0.625 V
0111 1111	7F	127	1.270 V	4.961 V
1000 0000	80	128	1.280 V	5.000 V
1100 0000	C0	192	1.920 V	7.500 V
1111 1111	FF	255	2.55 V	9.961 V

Image courtesy of Analog Devices. Used with permission.

Convert data to
Offset binary

 

 MIT Another Approach: Binary-Weighted DAC MIT



- Switch binary-weighted currents
- MSB to LSB current ratio is 2^N

- Analog Devices AD9768 uses two banks of ratioed currents
- Additional current division performed by $750\ \Omega$ resistor between the two banks


 
 




Image courtesy of Analog Devices. Used with permission.

 - Glitching is caused when switching times in a D/A are not synchronized
- Example: Output changes from 011 to 100 – MSB switch is delayed
- Filtering reduces glitch but increases the D/A settling time
- One solution is a thermometer code D/A – requires $2^N - 1$ switches but no ratioed currents




Successive-Approximation A/D

  - D/A converters are typically compact and easier to design. Why not A/D convert using a D/A converter and a comparator?
- D to A generates analog voltage which is compared to the input voltage
- If D to A voltage > input voltage then set that bit; otherwise, reset that bit
- This type of A to D takes a fixed amount of time proportional to the bit length




 Example: 3-bit A/D conversion, $2 \text{ LSB} < V_{in} < 3 \text{ LSB}$




- Serial conversion takes a time equal to $N(t_{D/A} + t_{comp})$

Successive-Approximation A/D (AD670)

 


Unipolar (BPO = 0)

 

2a. 0 V to 2.55 V (10 mV/LSB)


Bipolar (BPO = 1)

 

3a. ±1.28 V Range

Image courtesy of Analog Devices. Used with permission.

 Single Write, Single Read Operation (see data sheet for other modes)



t_w (write/start pulse width) = 300ns (min)

t_{DC} (delay to start conversion) = 700ns (max)


t_c (conversion time) = 10 μ s (max)

t_{TD} (Bus Access Time) = 250 (max)

t_{DT} (Output Float Delay) = 150 (max)

- Control bits **CE** and **CS** can be wired to ground if A/D is the only chip driving the bus
- Suggestion: tie **CE** and **CS** pins together and hardwire BPO and Format

Simple A/D Interface FSM

 

Status should be synchronized: why?

Courtesy of James Oey and
Cemal Akcaba

 


Figure by MIT OpenCourseWare.

```
module AD670 (clk, reset, sample, dataavail,  
r_wbar, cs_bar, status, state);  
  
// System Clk  
input clk;  
// Global Reset signal, assume it is synchronized  
input reset;  
  
// User Interface  
input sample;  
output dataavail;  
  
// A-D Interface  
input status;  
reg status_d1, status_d2;  
output r_wbar, cs_bar;  
output [3:0] state;  
  
// internal state  
reg [3:0] state;  
reg [3:0] nextstate;  
reg r_wbar_int, r_wbar;  
reg cs_bar_int, cs_bar;  
reg dataavail;
```

1/5

```
// State declarations.  
parameter IDLE = 0;  
parameter CONV0 = 1;  
parameter CONV1 = 2;  
parameter CONV2 = 3;  
parameter WAITSTATUSHIGH = 4;  
parameter WAITSTATUSLOW = 5;  
parameter READDELAY0 = 6;  
parameter READDELAY1 = 7;  
parameter READCYCLE = 8;  
  
always @ (posedge clk or negedge reset)  
begin  
    if (!reset) state <= IDLE;  
    else state <= nextstate;  
  
    status_d1 <= status;  
    status_d2 <= status_d1;  
  
    r_wbar <= r_wbar_int;  
    cs_bar <= cs_bar_int;  
end
```

2/5

```
always @ (state or status_d2 or sample) begin
    // defaults
    r_wbar_int = 1; cs_bar_int = 1; dataavail = 0;

    case (state)

        IDLE: begin
            if(sample) nextstate = CONV0;
            else nextstate = IDLE;
        end

        CONV0:
        begin
            r_wbar_int = 0;
            cs_bar_int = 0;
            nextstate = CONV1;
        end

        CONV1:
        begin
            r_wbar_int = 0;
            cs_bar_int = 0;
            nextstate = CONV2;
        end
    endcase
end
```

3/5

```
CONV2:
begin
    r_wbar_int = 0;
    cs_bar_int = 0;
    nextstate = WAITSTATUSHIGH;
end

WAITSTATUSHIGH:
begin
    cs_bar_int = 0;
    if (status_d2) nextstate = WAITSTATUSLOW;
    else nextstate = WAITSTATUSHIGH;
end

WAITSTATUSLOW:
begin
    cs_bar_int = 0;
    if (!status_d2) nextstate = READDELAY0;
    else nextstate = WAITSTATUSLOW;
end
```

4/5


```
READDELAY0:  
begin  
    cs_bar_int = 0;  
    nextstate = READDELAY1;  
end  
  
READDELAY1:  
begin  
    cs_bar_int = 0;  
    nextstate = READCYCLE;  
end  
  
READCYCLE:  
begin  
    cs_bar_int = 0;  
    dataavail = 1;  
    nextstate = IDLE;  
end  
  
    default: nextstate = IDLE;  
endcase // case(state)  
end // always @ (state or status_d2 or sample)  
endmodule // adcInterface
```

5/5

Simulation

On reset, present state goes to 0

 
r_w_b must stay low for at least 3 cycles (@ 100ns period)



Sample pulse initiates
data conversion



Notice a one cycle delay since A/D
control signal delayed through a register

Flash A/D Converter

 

- Brute-force A/D conversion
- Simultaneously compare the analog value with every possible reference value
- Fastest method of A/D conversion
- Size scales exponentially with precision
(requires 2^N comparators)

Can be implemented as OpAmp in open loop

  


TIMING SPECIFICATIONS

	Symbol	Min	Typ	Max	Units
Maximum Conversion Rate					MHz
Clock Period	t_c	20	35		ns
Clock High	t_{CH}	50			ns
Clock Low	t_{CL}	25			ns
Output Delay	t_{OD}	25	18	30	ns
Pipeline Delay (Latency)				2.5	Clock Cycles
Sampling Delay	t_{DS}		4		ns
Aperture Jitter			30		ps


Image courtesy of Analog Devices. Used with permission.

High Performance Converters: Use Pipelining and Parallelism!

 Pipelining (used in video rate, RF basestations, etc.)



Parallelism (use many slower A/D's in parallel to build very high speed A/D converters)

 

[ISSCC 2003],
Poulton et. al.

**20Gsamp/sec,
8-bit ADC
from Agilent Labs**

Figure by MIT OpenCourseWare. Adapted from Poulten, Ken, et al. "A 20 GS/s 8b ADC with a 1MB Memory in 0.18um CMOS." IEEE International Solid-State Circuits Conference Paper 18.1, 2003.

New Trend: Eliminate OpAmps! (Use Comparators, more digital...)

- Op amps must achieve high open-loop gain and fast settling time under feedback.
- High gain becomes increasingly difficult to achieve due to low device gain.
- Solution: Comparator based analog Design
- Dramatic power savings possible



Courtesy of Prof. Harry Lee, ISSCC 2006. Used with permission.

- Analog blocks are integral components of any system. Need data converters (analog to digital and digital to analog), analog processing (OpAmps circuits, switched capacitors filters, etc.), power converters (e.g., DC-DC conversion), etc.
- We looked at example interfaces for A/D and D/A converters
 - Make sure you register critical signals (enables, R/W, etc.)
- **Analog design incorporate digital principles**
 - Glitch free operation using coding
 - Parallelism and Pipelining!
 - More advanced concepts such as calibration