

# L8/9: Arithmetic Structures



## Acknowledgements:

Materials in this lecture are courtesy of the following sources and are used with permission.

- Rex Min
- Kevin Atkinson
- Prof. Randy Katz (Unified Microelectronics Corporation Distinguished Professor in Electrical Engineering and Computer Science at the University of California, Berkeley) and Prof. Gaetano Borriello (University of Washington Department of Computer Science & Engineering) from Chapter 2 of R. Katz, G. Borriello. *Contemporary Logic Design*. 2nd ed. Prentice-Hall/Pearson Education, 2005.
- J. Rabaey, A. Chandrakasan, B. Nikolic, *Digital Integrated Circuits: A Design Perspective* Prentice Hall/Pearson, 2003.



## How to represent negative numbers?


- Three common schemes: sign-magnitude, ones complement, twos complement
- Sign-magnitude: MSB = 0 for positive, 1 for negative
  - Range:  $-(2^{N-1} - 1)$  to  $+(2^{N-1} - 1)$
  - Two representations for zero: 0000... & 1000...
  - Simple multiplication but complicated addition/subtraction
- Ones complement: if N is positive then its negative is  $\bar{N}$ 
  - Example: 0111 = 7, 1000 = -7
  - Range:  $-(2^{N-1} - 1)$  to  $+(2^{N-1} - 1)$
  - Two representations for zero: 0000... & 1111...
  - Subtraction implemented as addition and negation

Twos complement = bitwise complement + 1

$$0111 \rightarrow 1000 + 1 = 1001 = -7$$

$$1001 \rightarrow 0110 + 1 = 0111 = 7$$

 - Asymmetric range:  $-2^{N-1}$  to  $+2^{N-1}-1$
- Only one representation for zero
- Simple addition and subtraction
- Most common representation





4	0100	-4	1100	4	0100	-4	1100
<u>+ 3</u>	<u>0011</u>	<u>+ (-3)</u>	<u>1101</u>	<u>- 3</u>	<u>1101</u>	<u>+ 3</u>	<u>0011</u>
7	0111	-7	11001	1	10001	-1	1111

[Katz05]

  
# Overflow Conditions

Add two positive numbers to get a negative number or two negative numbers to get a positive number



If carry in to sign equals carry out then can ignore carry out, otherwise have overflow

# Binary Full Adder

 


$$\begin{aligned} S &= A \oplus B \oplus C_i \\ &= A\bar{B}\bar{C}_i + \bar{A}BC_i + \bar{A}\bar{B}C_i + ABC_i \end{aligned}$$

$$C_o = AB + C_i(A+B)$$

A	B	Cl	S	CO
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Cl	AB				
	00	01	11	10	
S	0	0	1	0	1
	1	1	0	1	0

Cl	AB				
	00	01	11	10	
CO	0	0	0	1	0
	1	0	1	1	1

 


Worst case propagation delay linear with the number of bits


$$t_{\text{adder}} = (N-1)t_{\text{carry}} + t_{\text{sum}}$$

- Under two's complement, subtracting B is the same as adding the bitwise complement of B then adding 1

 **Combination addition/subtraction system:**



# Comparator (one approach)

 


$$\begin{aligned}
 A < B &= N \\
 A = B &= Z \\
 A \leq B &= Z + N
 \end{aligned}$$

# Alternate Adder Logic Formulation

How to Speed up the Critical (Carry) Path?  
(How to Build a Fast Adder?)

<i>A</i>	<i>B</i>	<i>C<sub>i</sub></i>	<i>S</i>	<i>C<sub>o</sub></i>	<i>Carry status</i>
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

 

$$\text{Generate } (G) = AB$$


$$\text{Propagate } (P) = A \oplus B$$

$$C_o(G, P) = G + PC_i$$

$$S(G, P) = P \oplus C_i$$


Note: can also use  $P = A + B$  for  $C_o$

# Carry Bypass Adder

 

**Key Idea:** if  $(P_0 P_1 P_2 P_3)$  then  $C_{o,3} = C_{i,0}$

# 16-bit Carry Bypass Adder

 

**Assume the following for delay each gate:**


P, G from A, B: 1 delay unit

P, G,  $C_i$  to  $C_o$  or Sum for a FA: 1 delay unit

2:1 mux delay: 1 delay unit

**What is the worst case propagation delay for the 16-bit adder?**

# Critical Path Analysis

 

For the second stage, is the critical path:

$BP2 = 0$  or  $BP2 = 1$ ?

**Message: Timing Analysis is Very Tricky –  
Must Carefully Consider Data Dependencies For  
False Paths**

Re-express the carry logic as follows:

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 \quad C_1 = G_1 + P_1 \quad G_0 + P_1 \quad P_0 \quad C_0$$

$$C_3 = G_2 + P_2 \quad C_2 = G_2 + P_2 \quad G_1 + P_2 \quad P_1 \quad G_0 + P_2 \quad P_1 \quad P_0 \quad C_0$$


$$C_4 = G_3 + P_3 \quad C_3 = G_3 + P_3 \quad G_2 + P_3 \quad P_2 \quad G_1 + P_3 \quad P_2 \quad P_1 \quad G_0 + P_3 \quad P_2 \quad P_1 \quad P_0 \quad C_0$$

...

- Each of the carry equations can be implemented in a two-level logic network
- Variables are the adder inputs and carry in to stage 0




Ripple effect has been eliminated!

# Carry Lookahead Logic

 

Adder with propagate and generate outputs

   Later stages have increasingly complex logic



$G_{j:i}$  and  $P_{j:i}$  denote the **Generate** and **Propagate** functions, respectively, for a group of bits from positions  $i$  to  $j$ . We call them **Block Generate** and **Block Propagate**.  $G_{j:i}$  equals 1 if the group generates a carry **independent** of the incoming carry.  $P_{j:i}$  equals 1 if an incoming carry propagates **through the entire group**. For example,  $G_{3:2}$  is equal to 1 if a carry is generated at bit position 3, or if a carry out is generated at bit position 2 and propagates through position 3.  $G_{3:2} = G_3 + P_3 G_2$ .  $P_{3:2}$  is true if an incoming carry propagates through both bit positions 2 and 3.  $P_{3:2} = P_3 P_2$

$$C_2 = (G_1 + P_1 G_0) + (P_1 P_0) C_0 = G_{1:0} + P_{1:0} C_0$$

$$C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

$$= (G_3 + P_3 G_2) + (P_3 P_2) C_{0,1} = G_{3:2} + P_{3:2} C_2$$

$$= G_{3:2} + P_{3:2}(G_{1:0} + P_{1:0} C_0) = G_{3:0} + P_{3:0} C_0$$

The carry out of a 4-bit block can thus be computed using only the block generate and propagate signals **for each 2-bit section**, plus the carry in to bit 0. The same formulation will be used to generate the carry out signals for a 16-bit adder using the block generate and propagate from 4-bit sections.

$$(g, p) \bullet (g', p') = (g + pg', pp')$$

**The above dot operator obeys the associative property, but it is not commutative**



$$(G_{3:2}, P_{3:2}) = (G_3, P_3) \bullet (G_2, P_2)$$

$$(C_{0,3}, 0) = ((G_3, P_3) \bullet (G_2, P_2) \bullet (G_1, P_1) \bullet (G_0, P_0)) \bullet (C_{i,0}, 0)$$


$$\begin{aligned} (G_{3:0}, P_{3:0}) &= [(G_3, P_3) \bullet (G_2, P_2)] \bullet [(G_1, P_1) \bullet (G_0, P_0)] \\ &= (G_{3:2}, P_{3:2}) \bullet (G_{1:0}, P_{1:0}) \end{aligned}$$

$$(C_{0,k}, 0) = ((G_k, P_k) \bullet (G_{k-1}, P_{k-1}) \bullet \dots \bullet (G_0, P_0)) \bullet (C_{i,0}, 0)$$


# Logarithmic Look-Ahead Adder

   $t_p: O(N)$  $t_p: O(\log_2 N)$


# 16-bit Kogge-Stone Tree Adder

 

# Adder Performance

 


# Addition of M, N-bit Numbers

 

# 16-bit Carry Lookahead Schematic

181 configured for A+B:

$M = 0, S_{3:0} = 1001$

 


# Binary Multiplication


$$\begin{array}{r}
 \times \\
 \begin{array}{cccc} x_3 & x_2 & x_1 & x_0 \end{array} \text{ Multiplicand} \\
 \begin{array}{cccc} y_3 & y_2 & y_1 & y_0 \end{array} \text{ Multiplier} \\
 \hline
 \begin{array}{cccc} x_3y_0 & x_2y_0 & x_1y_0 & x_0y_0 \end{array} \\
 \begin{array}{cccc} x_3y_1 & x_2y_1 & x_1y_1 & x_0y_1 \end{array} \\
 \begin{array}{cccc} x_3y_2 & x_2y_2 & x_1y_2 & x_0y_2 \end{array} \\
 + \quad \begin{array}{cccc} x_3y_3 & x_2y_3 & x_1y_3 & x_0y_3 \end{array} \\
 \hline
 z_7 \quad z_6 \quad z_5 \quad z_4 \quad z_3 \quad z_2 \quad z_1 \quad z_0
 \end{array}$$

Result

 
➤ Partial product computation  
is simple (single and gate)



# A Serial (Magnitude) Multiplier

 

# Timing Diagram

 


```
module serialmult(shift, clk,
                   x, y, xy);
  input shift, clk;
  input [3:0] x, y;
  output [7:0] xy;
  reg [7:0] xReg;
  reg [3:0] yReg;
  reg [7:0] xBus, acc_out,
  xy_int;
  wire[7:0] add_out;
  assign add_out = xBus +
  acc_out;
  assign xy = xy_int;

  always @ (yReg[0] or xReg)
  begin
    if (yReg[0] == 1'b0) xBus =
    8'b0;
    else xBus = xReg;
  end


  always @ (posedge clk)
  begin
    if (shift == 1'b0)
      begin
        xReg <= {4'b0, x};
        yReg <= y;
        acc_out <= 8'b0;
        xy_int <= add_out;
      end
    else
      begin
        xReg <= {xReg[6:0], 1'b0};
        yReg <= {y[3], yReg[3:1]};
        acc_out <= add_out;
        xy_int <= xy;
      end // if shift
  end // always
endmodule
```

# Simulation

 
 
# Twos Complement Multiplication

$$\begin{array}{r}
 & \begin{array}{cccc} x_3 & x_2 & x_1 & x_0 \end{array} \text{ Multiplicand} \\
 \times & \begin{array}{cccc} y_3 & y_2 & y_1 & y_0 \end{array} \text{ Multiplier} \\
 \hline
 & \begin{array}{cccc} \overline{x_3y_0} & x_2y_0 & x_1y_0 & x_0y_0 \end{array} \\
 & \begin{array}{cccc} \overline{x_3y_1} & x_2y_1 & x_1y_1 & x_0y_1 \end{array} \\
 & \begin{array}{cccc} \overline{x_3y_2} & x_2y_2 & x_1y_2 & x_0y_2 \end{array} \\
 & \begin{array}{cccc} x_3y_3 & \overline{x_2y_3} & \overline{x_1y_3} & \overline{x_0y_3} \end{array} \\
 + 1 & \hline
 z_7 & z_6 & z_5 & z_4 & z_3 & z_2 & z_1 & z_0
 \end{array}$$



- Performance of arithmetic blocks dictate the performance of a digital system
- Architectural and logic transformations can enable significant speed up (e.g., adder delay from  $O(N)$  to  $O(\log_2(N))$ )
- Similar concepts and formulation can be applied at the system level
- **Timing analysis is tricky:** watch out for false paths!
- Area-Delay trade-offs (serial vs. parallel implementations)