

# MASSACHUSETTS INSTITUTE OF TECHNOLOGY

Department of Electrical Engineering

## 6.331 Advanced Circuit Techniques

Laboratory 2  
Power Converters

Issued : March 15, 2002  
Due : Friday, April 5, 2002

---

Design, build, and demonstrate a switching power supply that meets the following specs. (You may choose to build either the boost or flyback topology.)

### Specifications

- Output voltage: for the boost 20 V, for the flyback  $-10$  V
- Steady state error: Zero (use an integrator in the loop).
- Output voltage ripple:  $\leq 200$  mVpp (peak-to-peak)
- Input voltage range:  $8\text{ V} \leq V_{in} \leq 16\text{ V}$
- Input ripple current (calculated):  $\leq 10$  mA rms
- Output power: 5 watts
- Small signal bandwidth:  $\geq 5$  kHz
- Small signal step overshoot:  $\leq 10\%$

### Lab Hints

Build your converter in stages rather than attempting to construct and test the entire loop in one smoke-producing flip of the switch.

#### 1. Build the switching section

- use ceramic capacitors for the main filtering caps in your converter. use electrolytics only for damping legs.
- drive the switch with a function generator ( $D = 0.5$  or whatever)
- start with a small input voltage ( $V_{in} = 0.5$  V or so)
- if the waveforms look ok, gradually increase  $V_{in}$
- use the function generator's symmetry control to vary  $D$ , and convince yourself that the converter is operating correctly.

#### 2. Build the controller section

- test the controller section using "fake" inputs

- use lab kit supplies to power controller circuitry (not  $V_{in}$  supply)
- verify proper operation before attempting to close the loop

3. Consider start-up details before closing the loop.

- soft-start
- current-limit
- duty-cycle limit

4. Pray, sacrifice a token 3904, then power up the closed-loop system