

MIT OpenCourseWare  
<http://ocw.mit.edu>

6.334 Power Electronics  
Spring 2007

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.

**MASSACHUSETTS INSTITUTE OF TECHNOLOGY**  
**Department of Electrical Engineering and Computer Science**

6.334 Power Electronics

Issued: April 31, 2007

Problem Set 10

Due: May 7, 2007

---

Reading: KSV Chapter 4

---

**Problem 10.1**

Consider a continuous conduction mode buck converter to be operated under peak current mode control. The converter parameters are  $f_{sw} = 500$  kHz,  $L = 16$   $\mu$ H,  $C = 800$   $\mu$ F, and  $V_{out,ref} = 24$  V. What is the smallest magnitude of compensating ramp that will yield stable dynamics for the ripple instability over an input voltage range of  $36$  V  $< V_{in} < 75$  V?

*Note: Models for computing the ripple dynamics will be discussed in class. They can also be found in: H. Hsu, A. Brown, L. Rensink, and R.D. Middlebrook, "Modeling and Analysis of Switching dc-to-dc Converters in Constant-Frequency Current-Programmed Mode," 1979 IEEE Power Electronics Specialists Conference, pp. 284-301, and in R.W. Erickson, Fundamentals of Power Electronics, Boston: Kluwer, 1997, Chapter 11 (Current Programmed Control).*

**Problem 10.2** KSV Prob. 4.6

**Problem 10.3** KSV Prob. 4.7

**Problem 10.4** KSV Prob. 4.8