

MITOPENCOURSEWARE

MASSACUSETTS INSTITUTE OF TECHNOLOGY

6.976

High-Speed Communication Circuits and Systems

Lecture 29

Lowpass and Bandpass Delta-Sigma Modulation

Richard Schreier



Copyright © 2003 Richard Schreier

Outline

1 $\Delta\Sigma$ Basics

1st-Order Modulator

2 Advanced $\Delta\Sigma$

High-Order $\Delta\Sigma$ Modulators

Multi-bit and Multi-Stage Modulation


3 Bandpass $\Delta\Sigma$ Modulation

4 Example Bandpass ADC

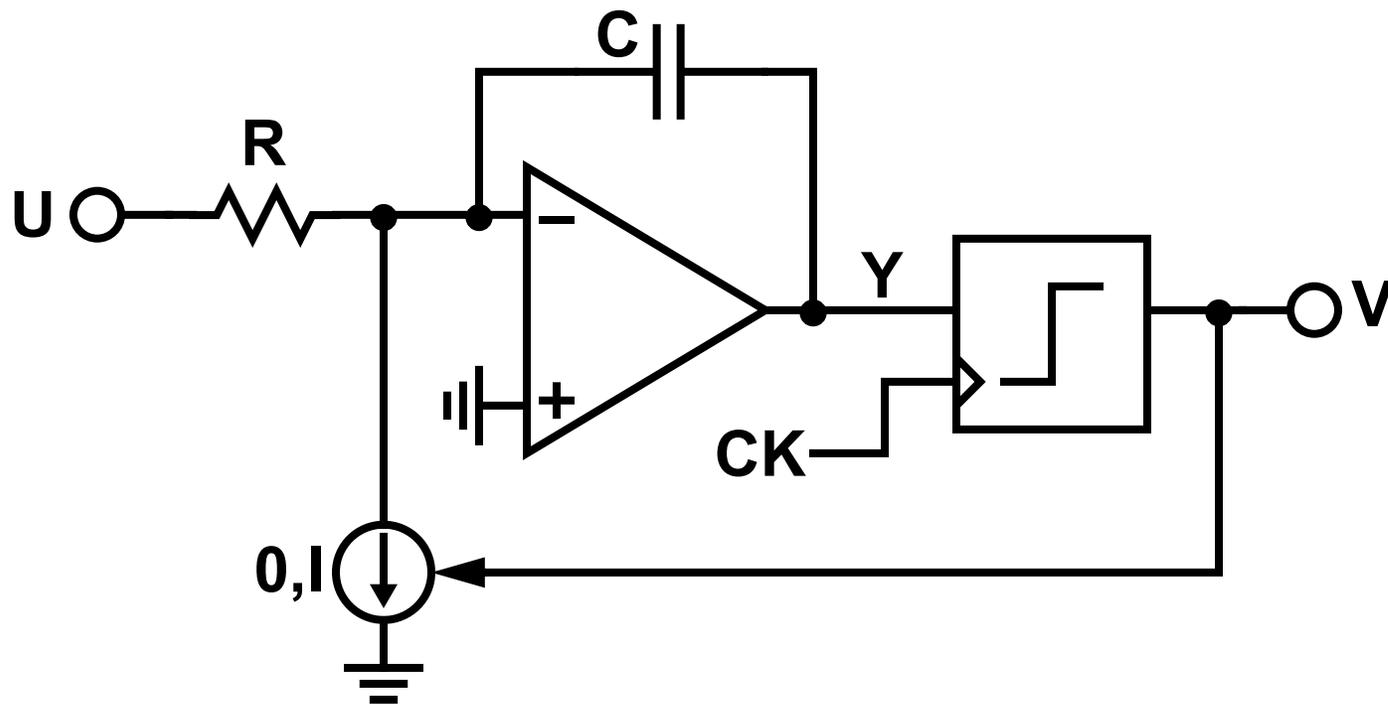1. $\Delta\Sigma$ Basics

CTMOD1: A 1st-Order Continuous-Time $\Delta\Sigma$ Modulator

- The input signal, U , is converted into a sequence of bits, $V \in (0,1)$.



Properties of CTMOD1

DC Inputs

- **Integrator ensures that input current is exactly balanced by the (average) feedback current**
“Infinite resolution”
- **Signals which alias to DC are rejected**
“Inherent anti-aliasing”

Non-ideal Effects in CTMOD1


- **Component shifts**
 - $R \rightarrow R + \Delta R$ or $I \rightarrow I + \Delta I$ merely changes full-scale.
 - $C \rightarrow C + \Delta C$ scales the output of the integrator, but does not affect the comparator's decisions.
- **Op-amp offset, input bias current, DAC imbalance**
 - All translate into a DC offset, which is unimportant in many communications applications.
- **Comparator offset & hysteresis**
 - Overcome by integrator.
- **Finite op-amp gain**
 - Creates "dead-bands."

Non-ideal Effects (cont'd)

- **DAC jitter**
Adds “noise.”
- **Resistor nonlinearity (e.g. due to self-heating)**
Introduces distortion.
- **DAC nonlinearity**
Introduces distortion and intermodulation of shaped quantization noise.
- **Capacitor nonlinearity**
Irrelevant.
- **Op-amp nonlinearity**
Same effects as DAC nonlinearity, but less severe.


CTMOD1 Model

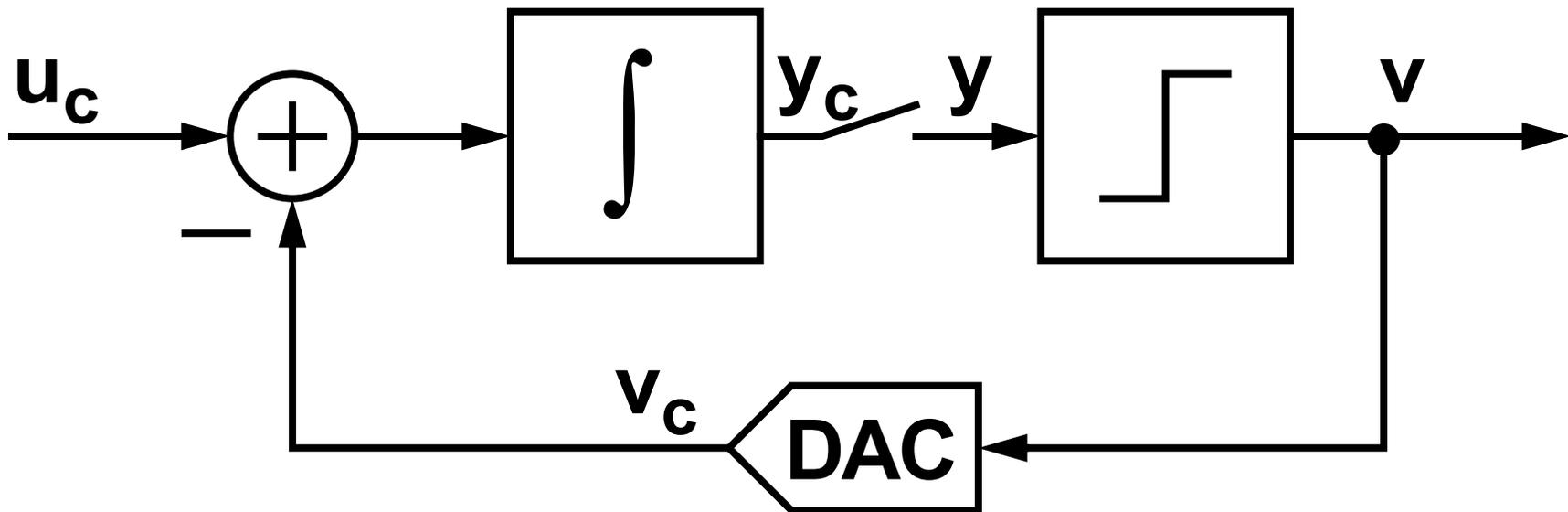- **Normalize $R=1\Omega$, $C=1F$, $I=1A$, $F_s=1Hz$**
Full-scale range is $[0,1]V$.
- **Assume comparator and DAC are delay-free**




Waveforms/Timing


$$u = 0.2$$

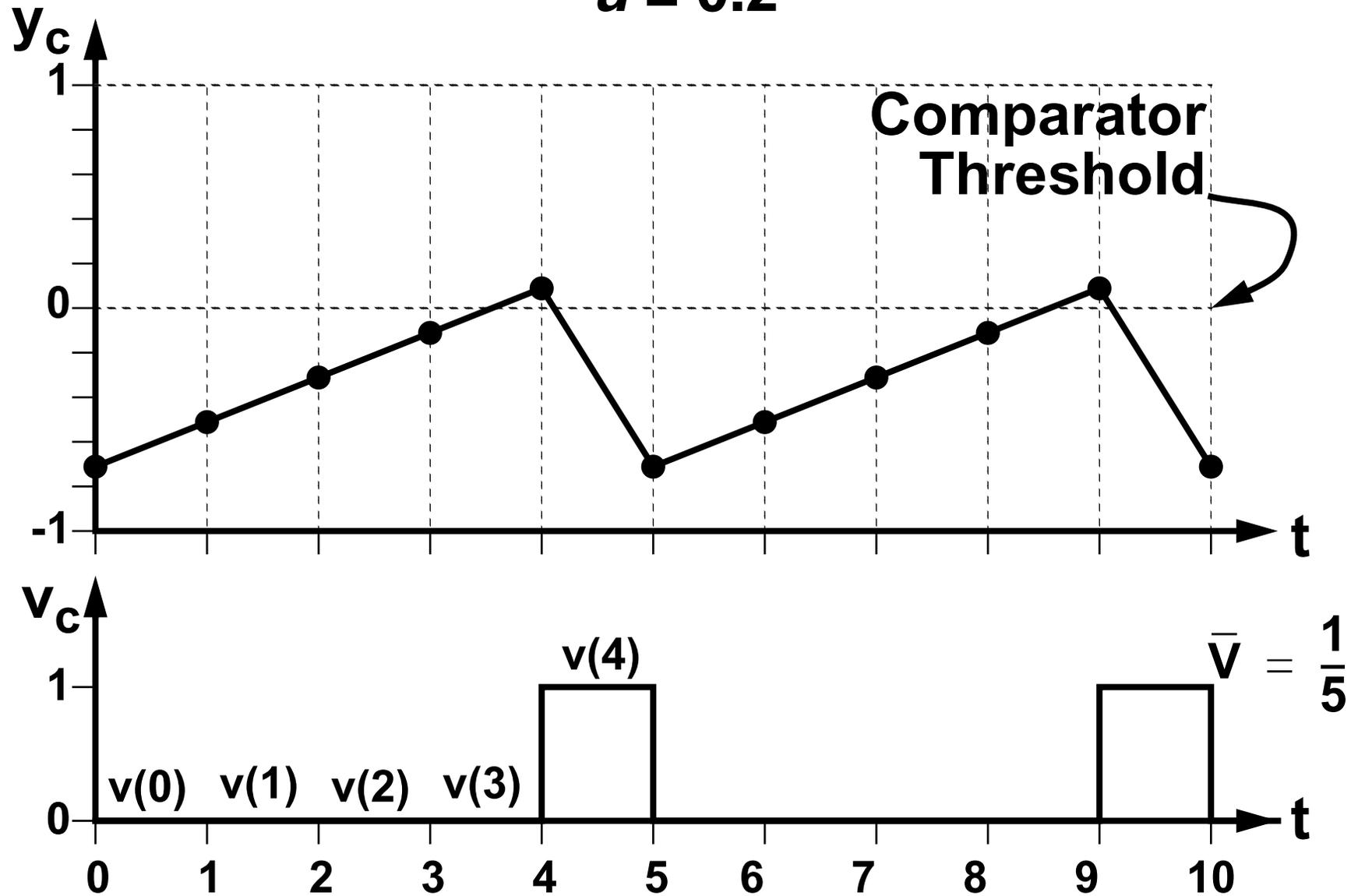


CTMOD1 @ 5% 1's density

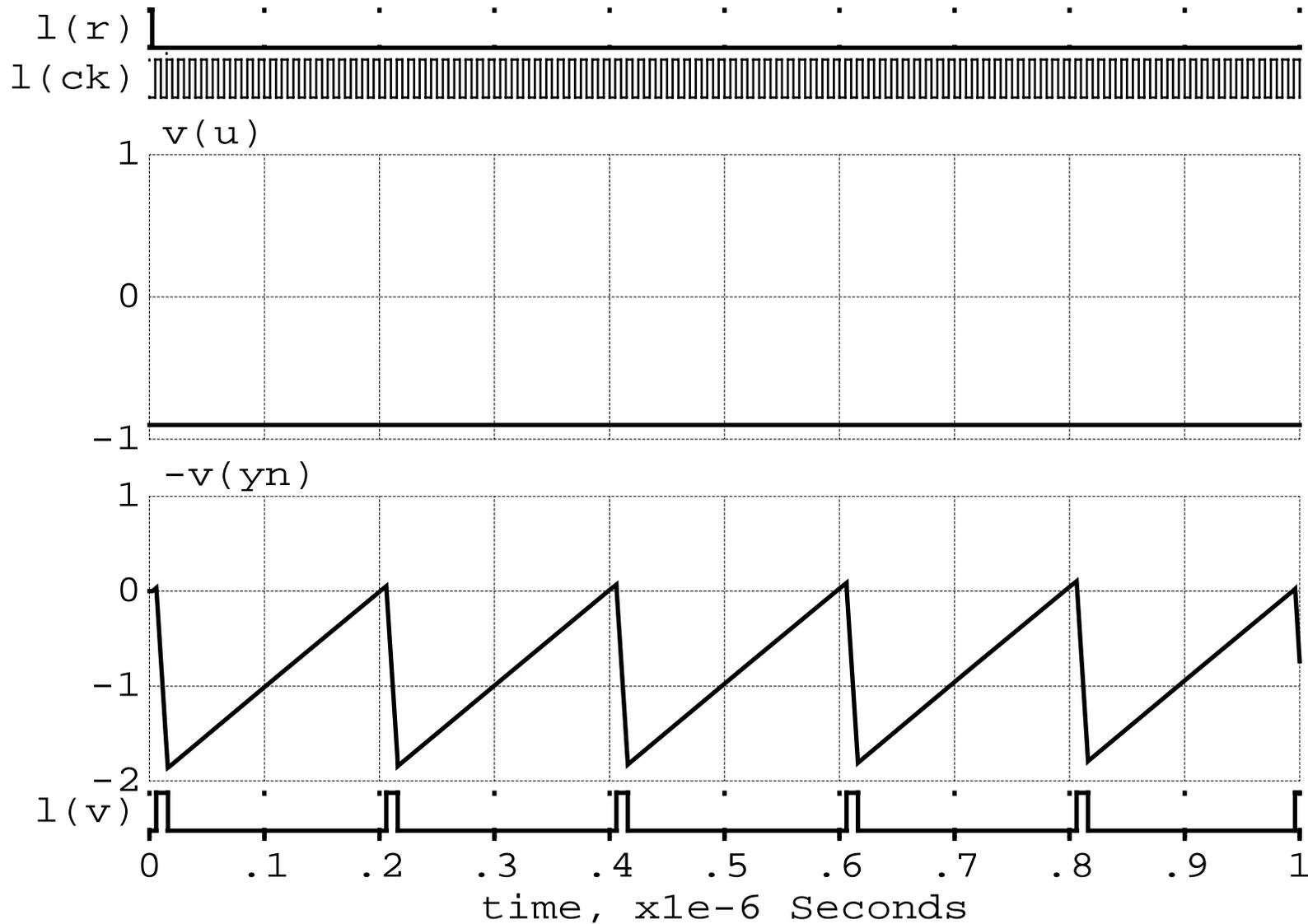


CTMOD1 @ 10% 1's density

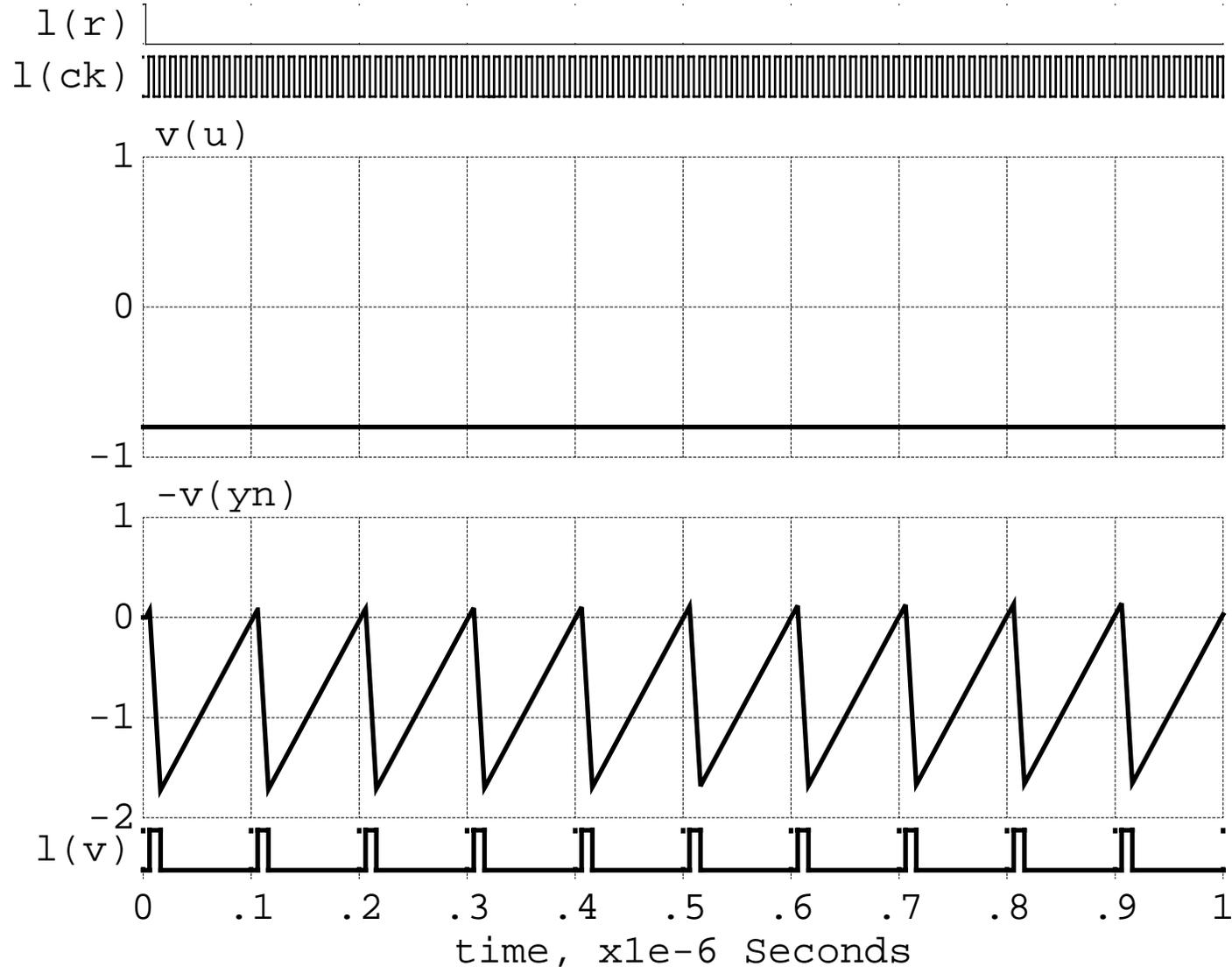

CTMOD1 @ 51% 1's density

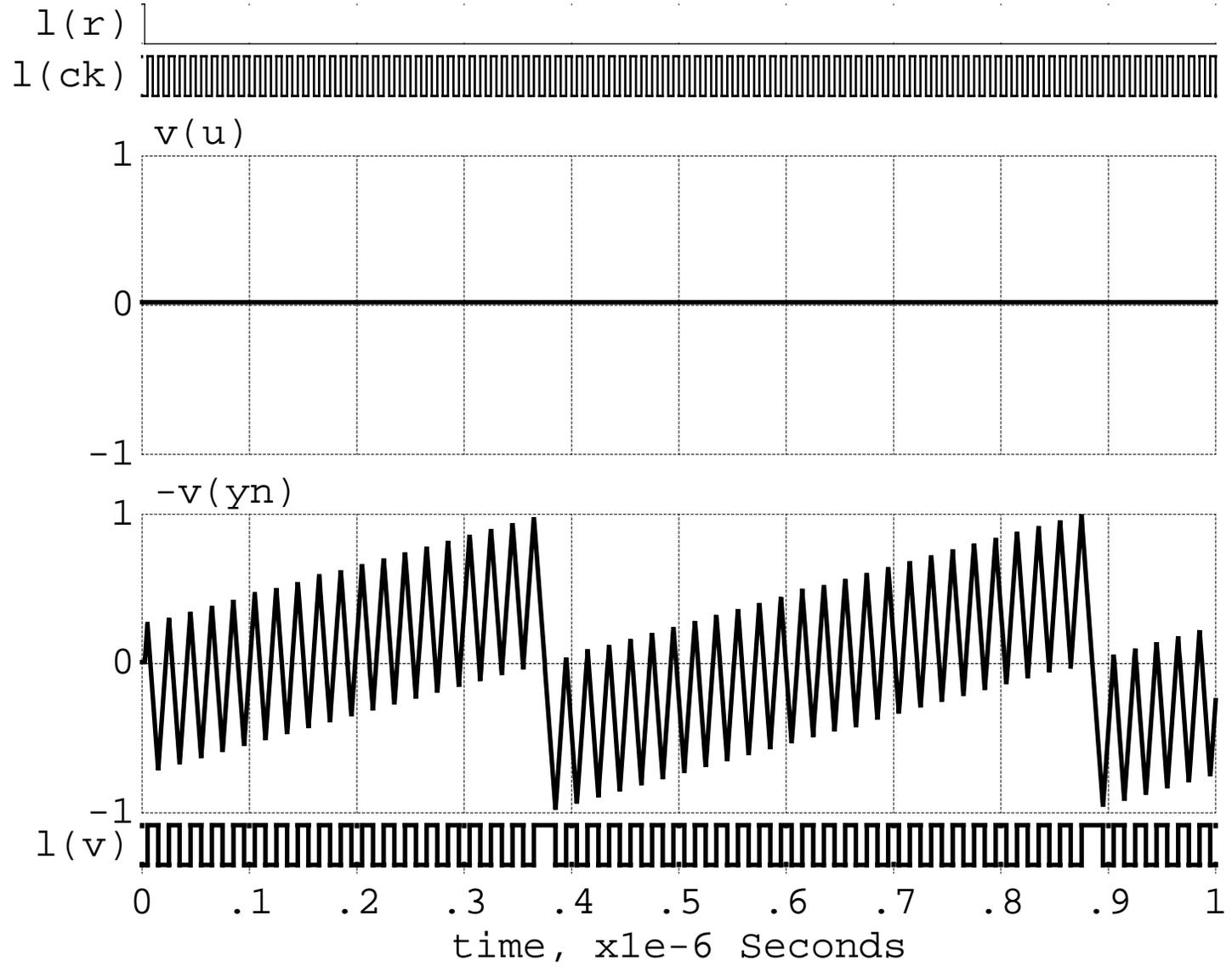

CTMOD1 @ $1/\pi$ 1's density

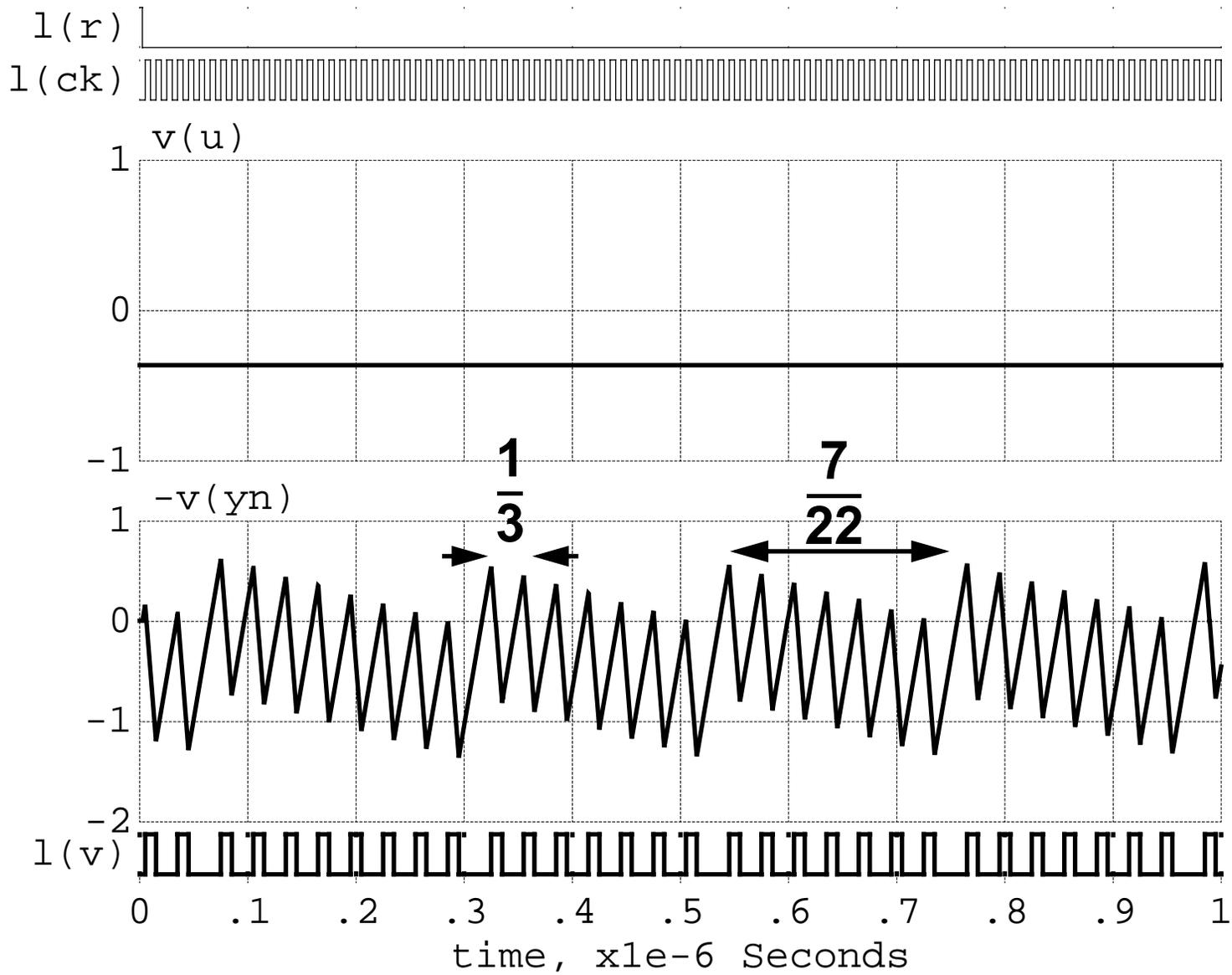

Analysis of CTMOD1

From the diagram:

$$\mathbf{y}_c(\mathbf{n}) = \mathbf{y}_c(\mathbf{n} - 1) + \int_{\mathbf{n}-1}^{\mathbf{n}} (\mathbf{u}_c(\tau) - \mathbf{v}_c(\tau)) d\tau$$

1) Sample y_c at integer time and identify $y(n) = y_c(n)$.

2) Observe that $\int_{\mathbf{n}-1}^{\mathbf{n}} \mathbf{v}_c(\tau) d\tau = \mathbf{v}(\mathbf{n} - 1)$

3) Define $\mathbf{u}(\mathbf{n}) = \int_{\mathbf{n}-1}^{\mathbf{n}} \mathbf{u}_c(\tau) d\tau$


THEN

$$\mathbf{y}(\mathbf{n}) = \mathbf{y}(\mathbf{n} - 1) + \mathbf{u}(\mathbf{n}) - \mathbf{v}(\mathbf{n} - 1)$$

Also, from the diagram

$$\mathbf{v}(\mathbf{n}) = \mathbf{Q}(\mathbf{y}(\mathbf{n}))$$

CTMOD1 Equivalent

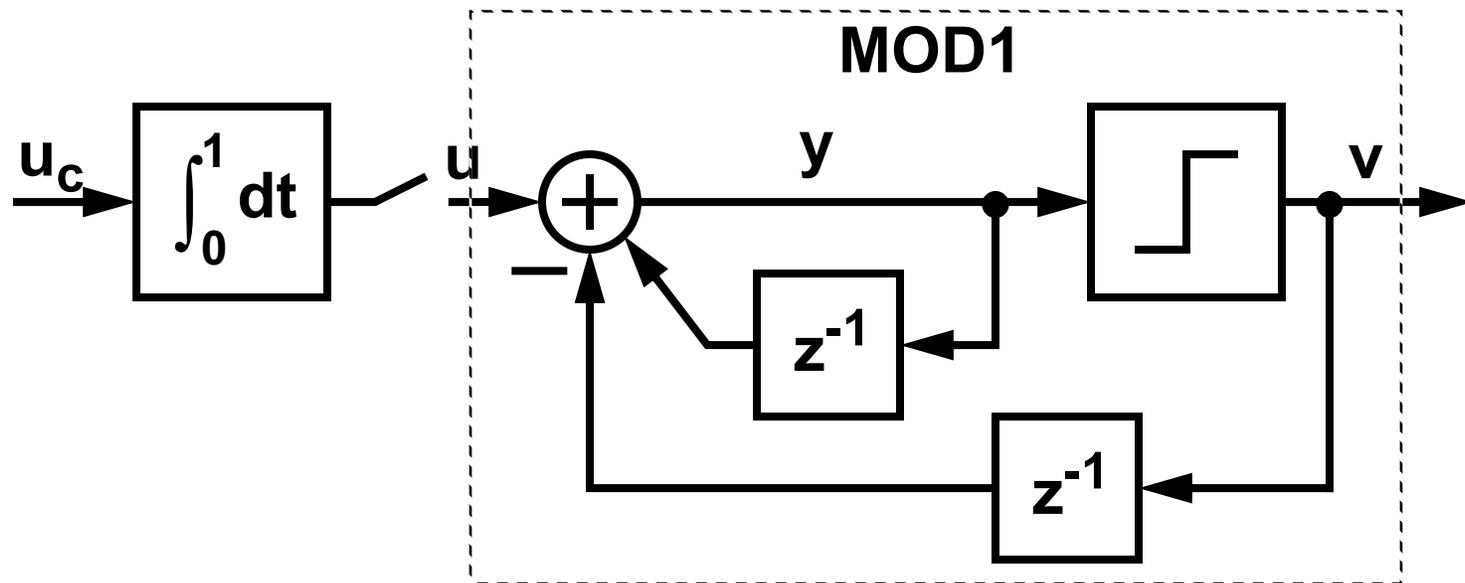


- **CTMOD1 is the same as a discrete-time first-order modulator (MOD1) preceded by a sinc filter!**

CTMOD1 NTF and STF


- The NTF is the same as MOD1:

$$\text{NTF}(z) = 1 - z^{-1}$$

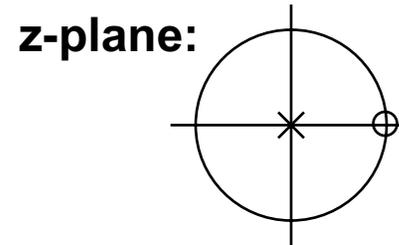


- MOD1's STF is 1, so the overall STF is just the TF of the prefilter:

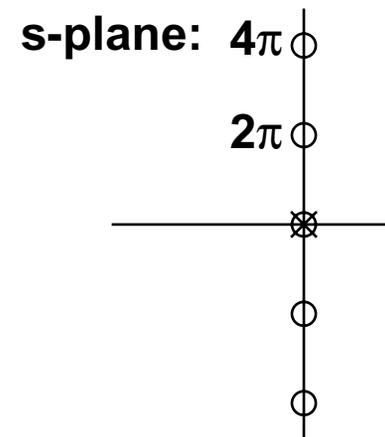
$$\begin{aligned}\text{STF}(s) &= \int_0^{\infty} e^{-st} g_p(t) dt \\ &= \int_0^1 e^{-st} dt = \frac{(1 - e^{-s})}{s} \\ &= \frac{(1 - z^{-1})}{s}, \text{ where } \mathbf{z} = \mathbf{e}^s\end{aligned}$$



Frequency Responses

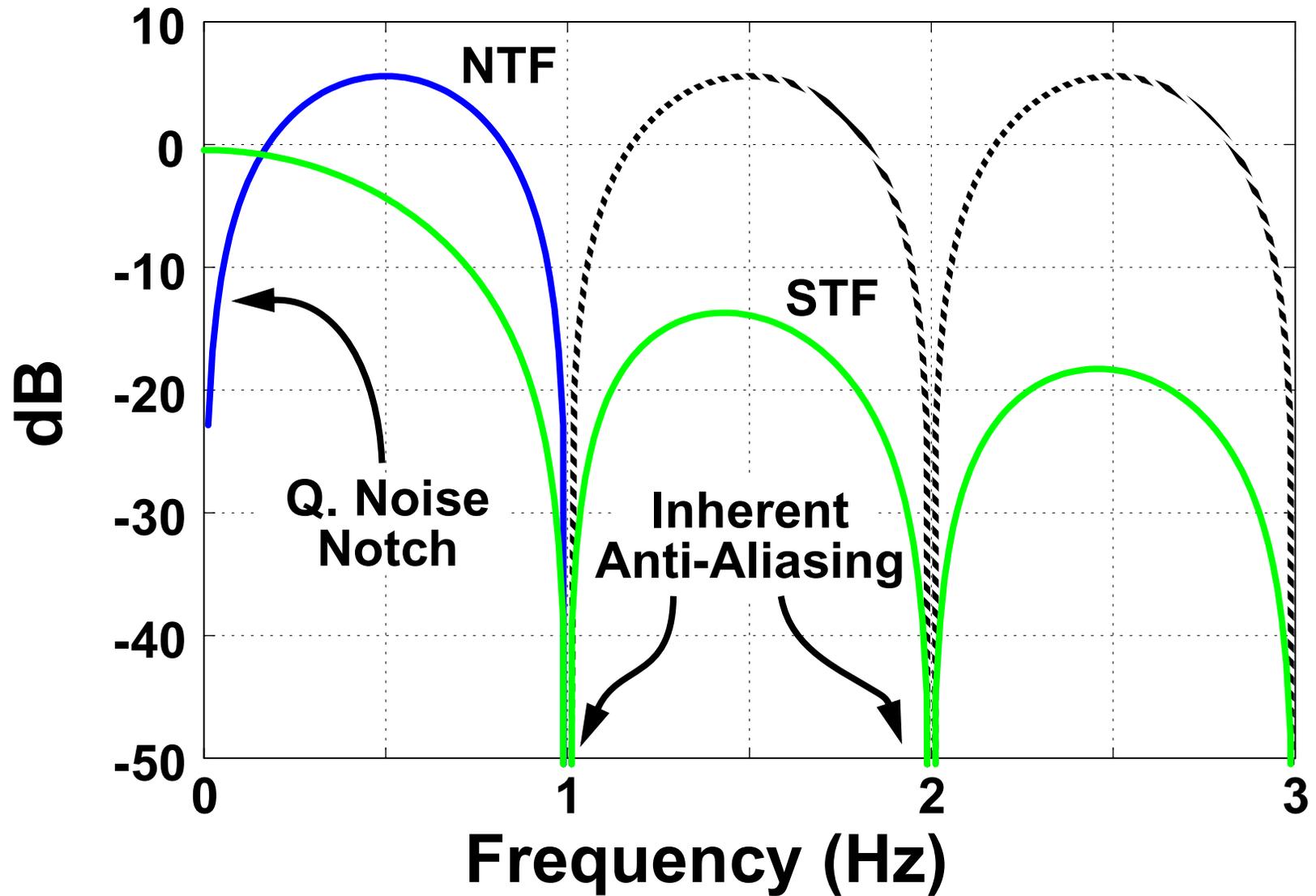

CTMOD1 Spectra

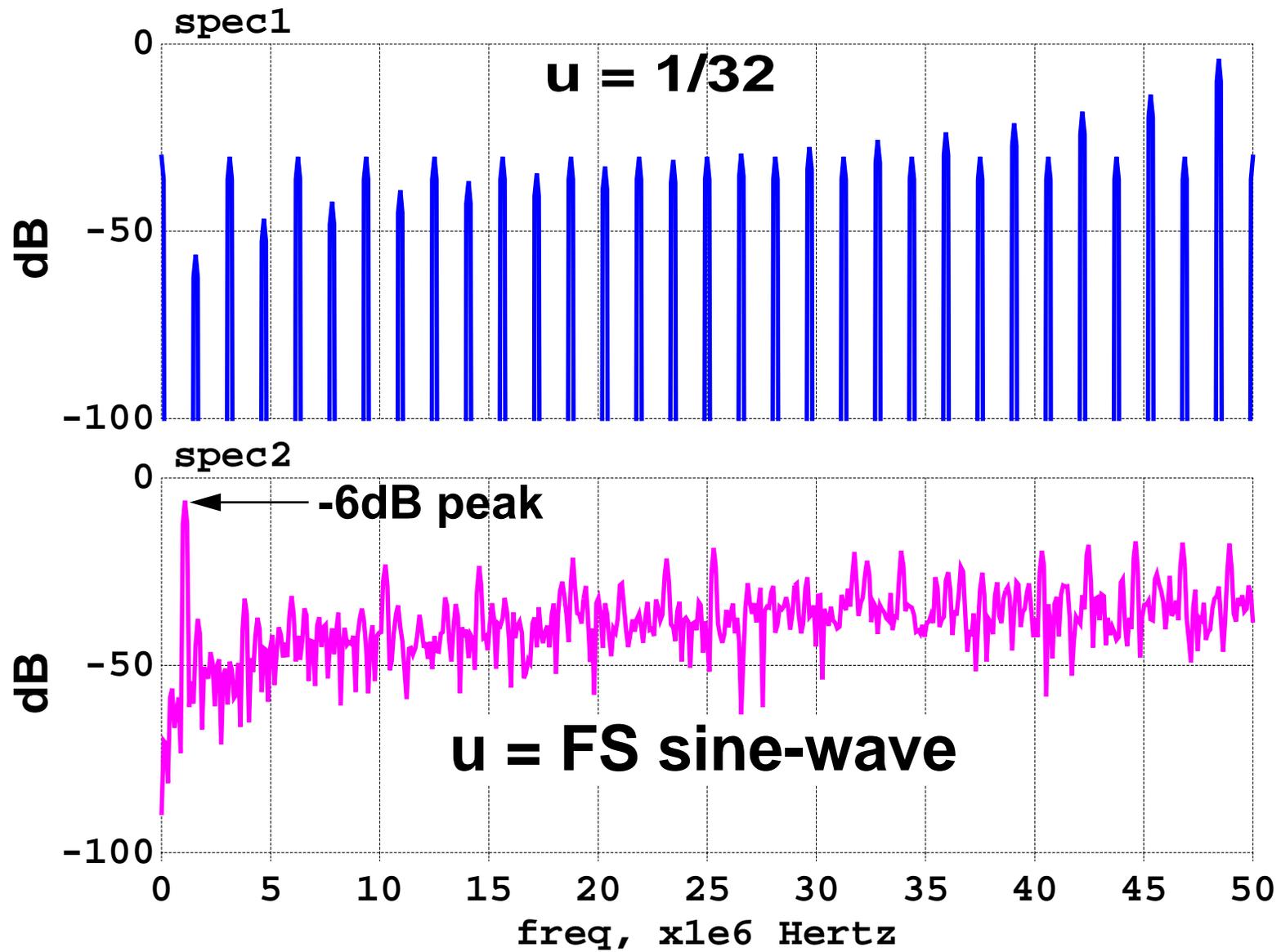

Properties of MOD1

- **Single-bit quantization yields “inherent linearity.”**
The DAC defines two points and two points can always be joined with a line. (Not so simple in continuous-time.)
- $0 \leq u \leq 1 \Rightarrow |y| \leq 1$
MOD1 is stable for inputs all the way up to full-scale.
The quantizer in MOD1 does not “overload.”
- **Assuming the quantization error is white with power σ_e^2 , the in-band noise power is**
$$N_0^2 \cong \frac{\pi^2 \sigma_e^2}{3(\text{OSR})^3} \cdot \sim 12\text{-bit performance at OSR}=256.$$


Doubling OSR reduces noise power by a factor of 8.
“1.5 bits increase in SNR per octave increase in OSR”

MOD1 Properties (cont'd)


- **DC input $u = \frac{a}{b}$ results in period- b behavior.**
The spectrum of the error is not white! Spectrum consists of a finite set of harmonics of f_s/b .
- **Irrational DC inputs result in aperiodic behavior.**
Nonetheless, the spectrum of the error is still discrete!
Spectrum consists of an infinite number of tones with frequencies that are irrational fractions of f_s .
- **Finite op-amp gain shifts NTF zero inside the unit circle and allows a range of u values to produce the same limit cycle.**
Worst case is around $u = 0, 1, \frac{1}{2}$ etc.; yields “dead bands.”
- **The behavior of MOD1 is erratic.**

2. Advanced $\Delta\Sigma$

A Single-Loop $\Delta\Sigma$ Modulator

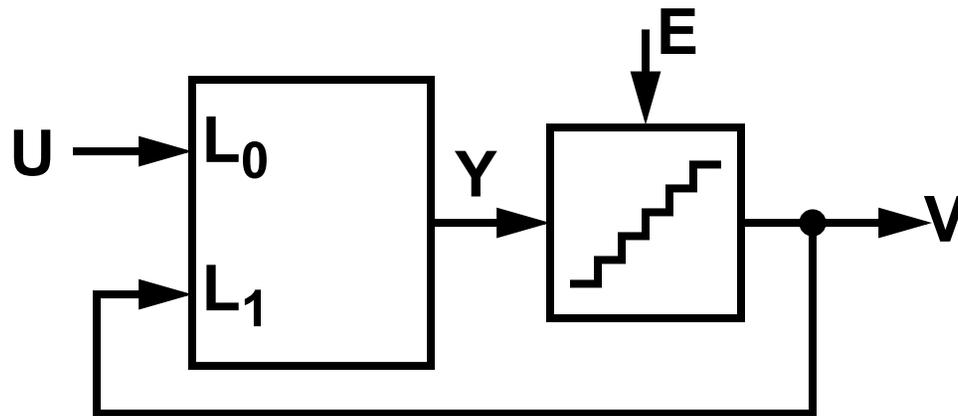
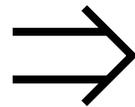
$$\begin{aligned} Y &= L_0 U + L_1 V \\ V &= Y + E \end{aligned}$$



$$\begin{aligned} V &= GU + HE, \text{ where} \\ H &= \frac{1}{1 - L_1} \quad \& \quad G = L_0 H \end{aligned}$$

Inverse Relations:


$$L_1 = 1 - 1/H, \quad L_0 = G/H$$

- The zeros in H come from the poles in L_1


A 5th-Order Lowpass NTF

Zeros optimized for OSR=32


- Pole/Zero diagram:

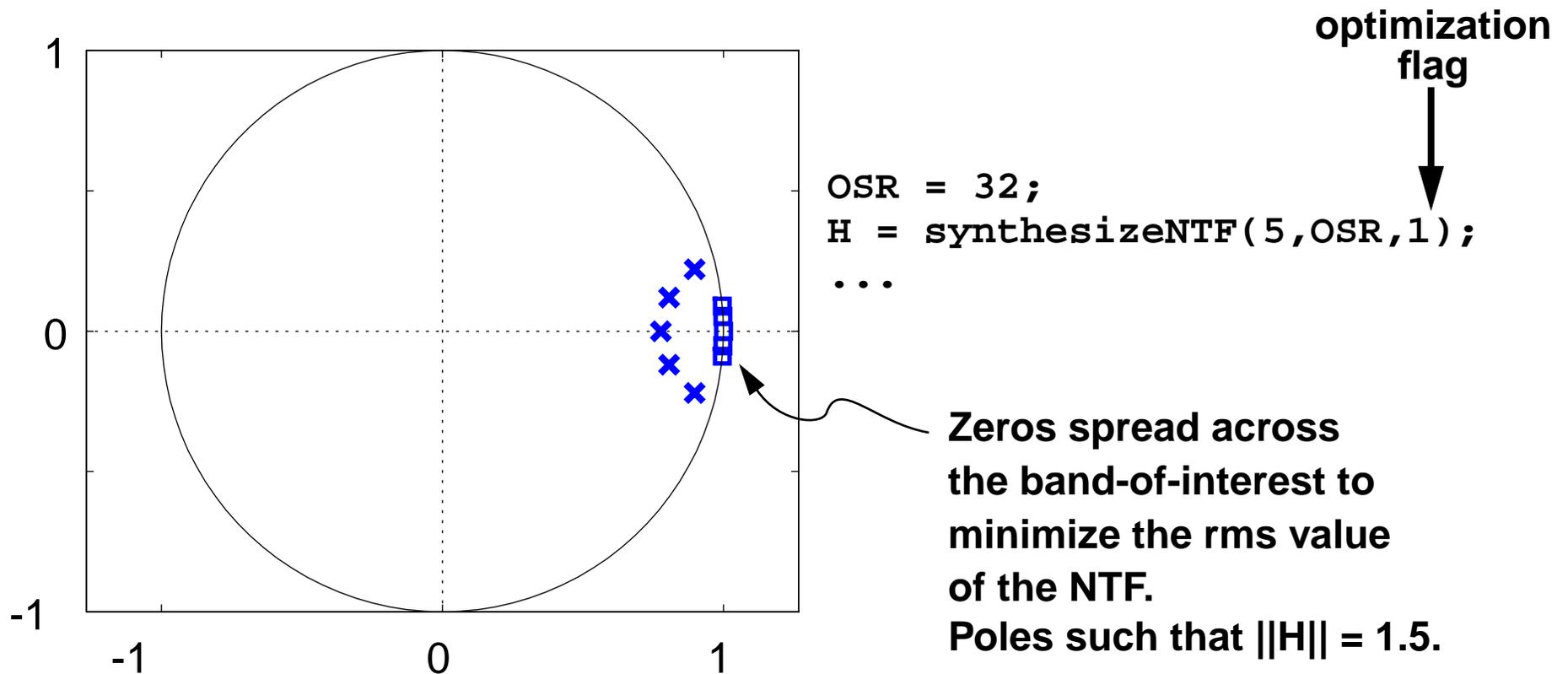

Example: 5th-Order Modulator

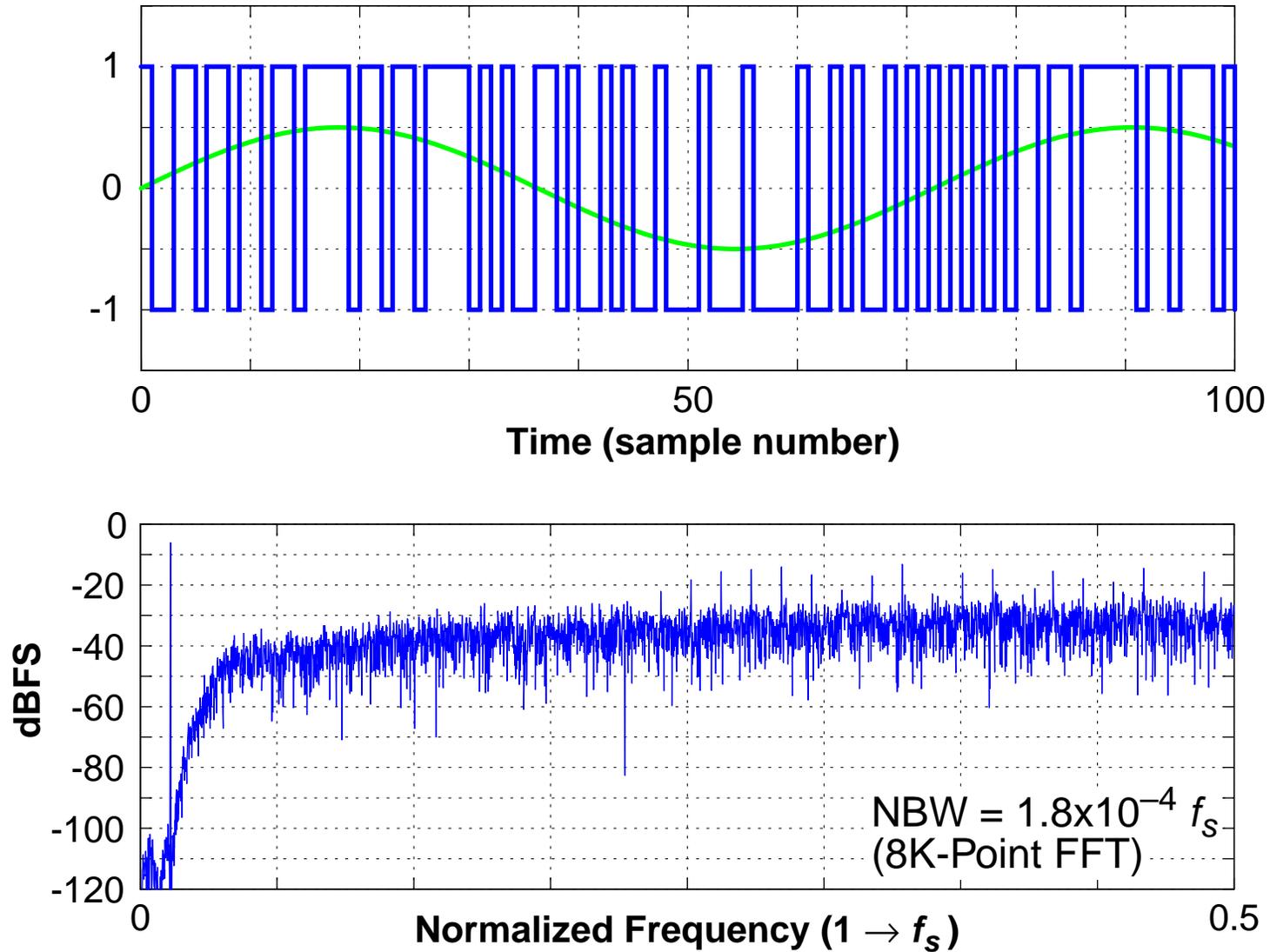

SQNR Limits for Binary Modulators

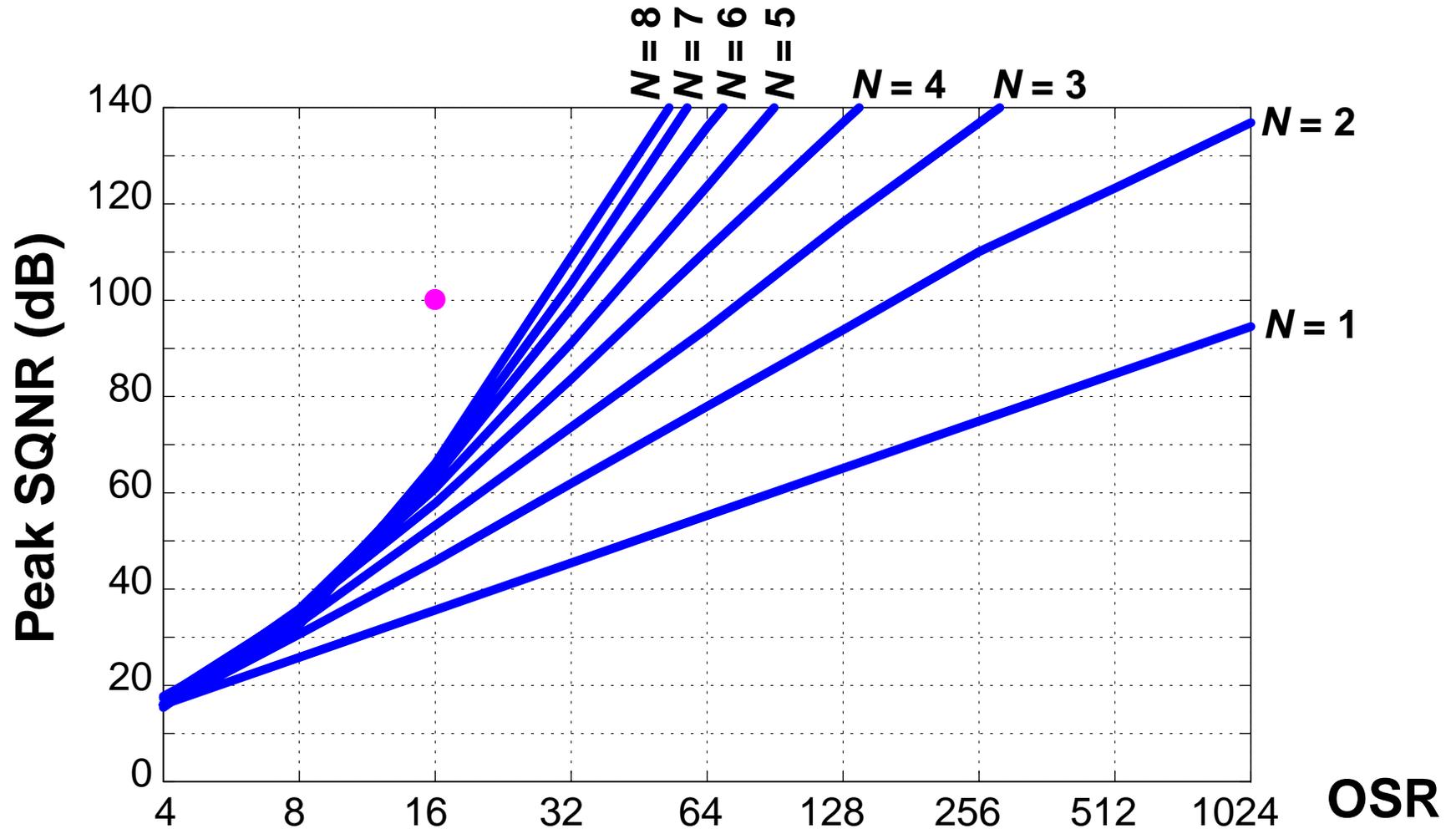


Multi-Bit Quantization

Toolbox Conventions

- Single-bit quantizer output interpreted as ± 1 instead of 0,1.


Quantizer step size, Δ , is 2; input range is $[-1,+1]$.

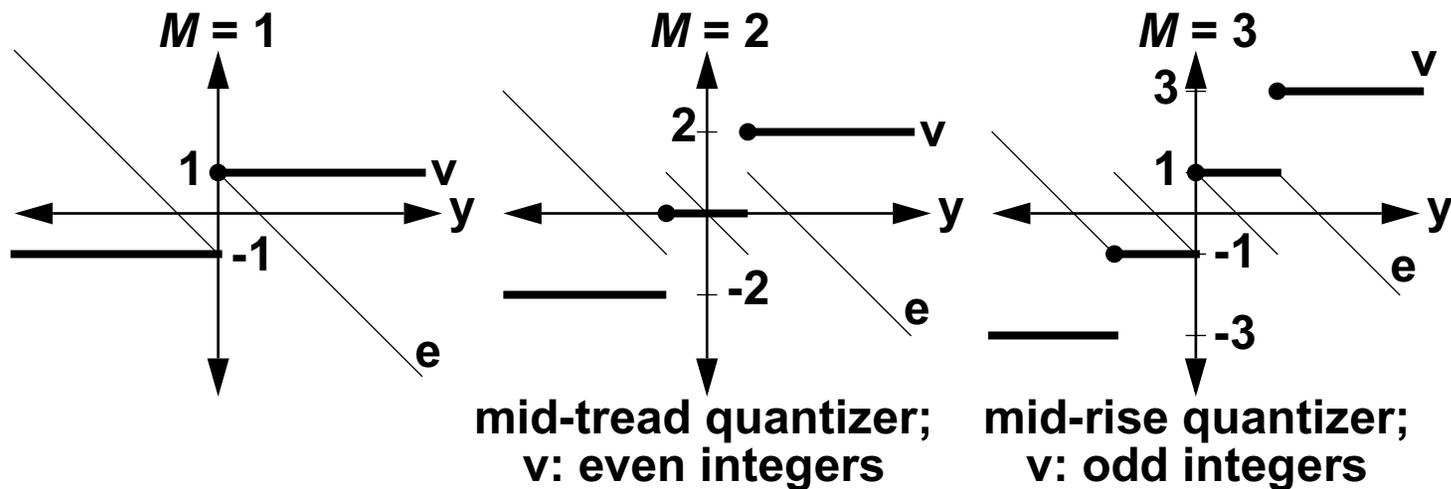- Convention for multi-bit quantization is:




$\Delta = 2$; # of Q. levels is $nlev = M+1$, from $-M$ to $+M$;
no-overload range ($|e| \leq 1$) is $-nlev$ to $+nlev$.

SQNR Limits for 3-bit Modulators

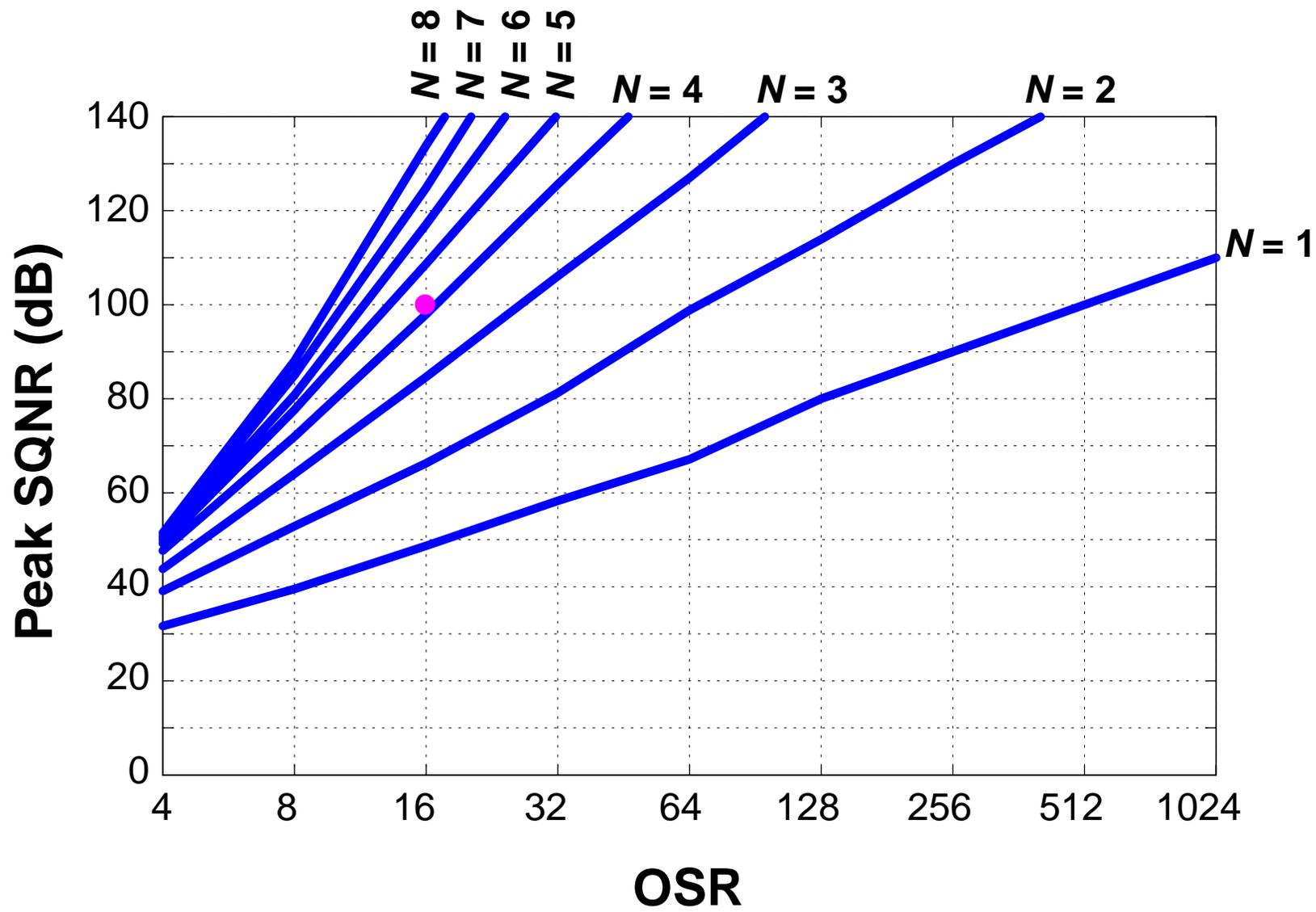

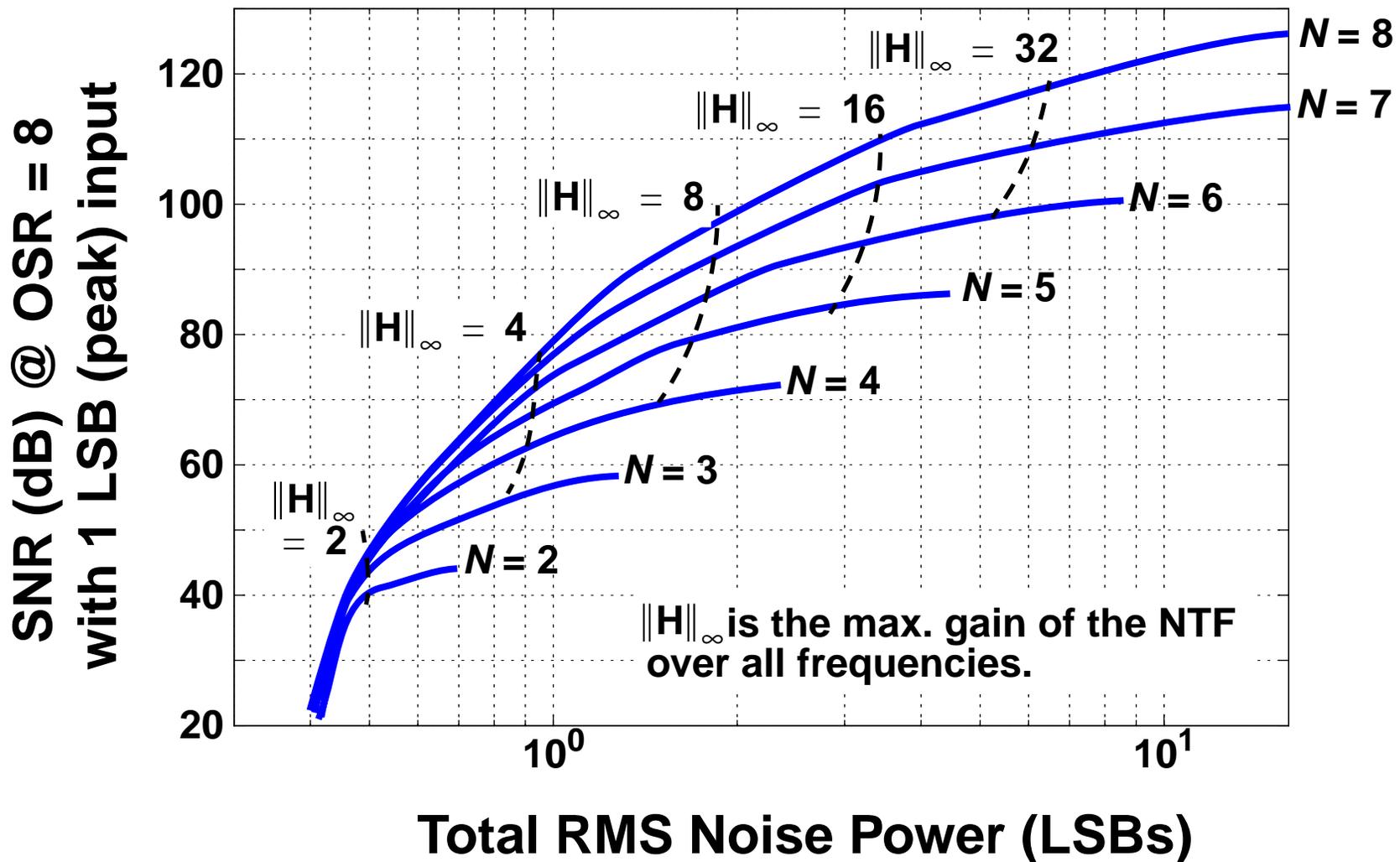Theoretical SNR Limits for Multi-Bit Modulators




Multi-Bit Quantization

Pros and Cons

- **Multi-bit quantization overcomes stability-induced restrictions on the NTF**
Dramatic improvements are possible!
- **Multi-bit quantization loses the inherent linearity property of a binary DAC**
DAC levels are not evenly spaced and so cannot be joined with a straight line.
DAC errors are effectively added to the input, and thus are not shaped.
Can be overcome with calibration, digital correction or mismatch-shaping.

Digital Correction



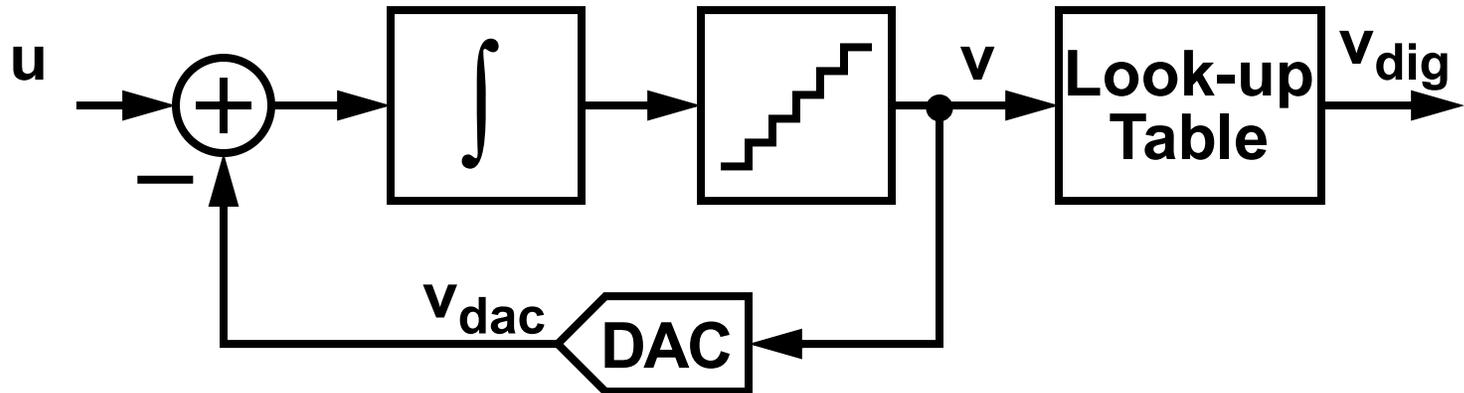


- **Lookup table contains the digital equivalent of each DAC level**
In practice, the look-up table only needs to store the differences between the actual and ideal DAC levels.
- **Thus $v_{dig} = v_{dac}$, so DAC errors are now shaped by the loop!**


Mismatch-Shaping

- Shapes mismatch-induced noise by ensuring that each element in a unit-element DAC is driven by a shaped sequence

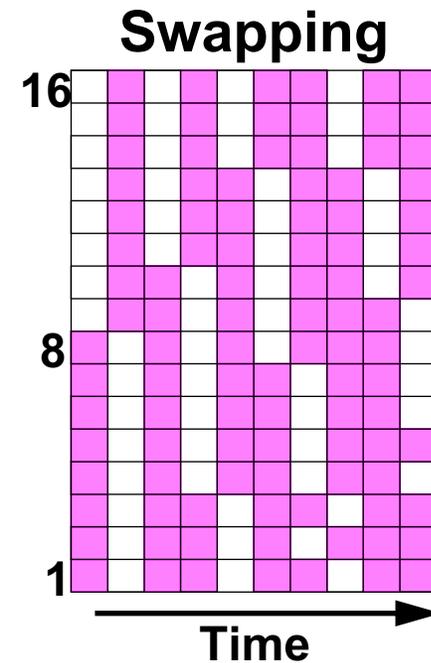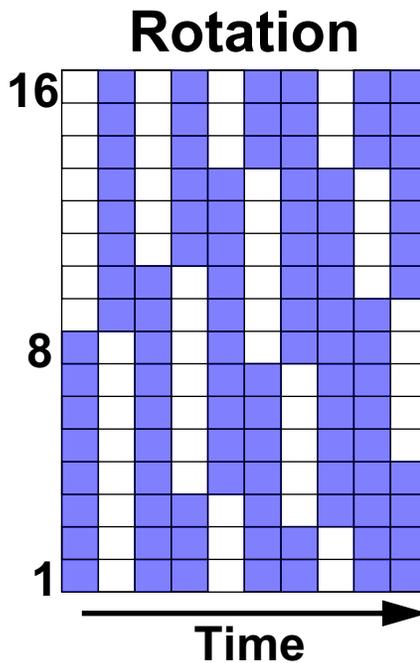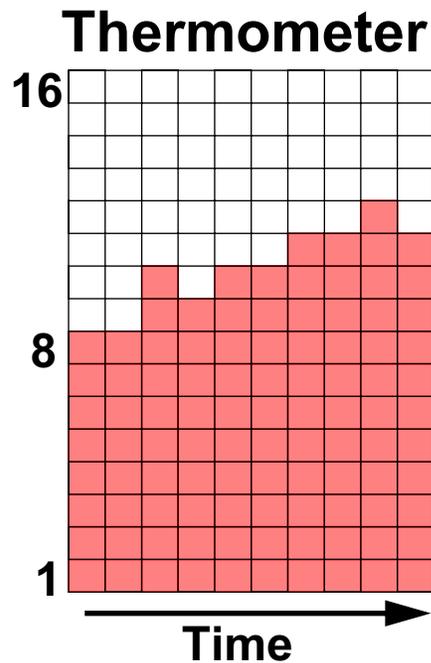Two popular forms of mismatch-shaping are *element-rotation* and *element-swapping*.




Multi-Stage Modulation

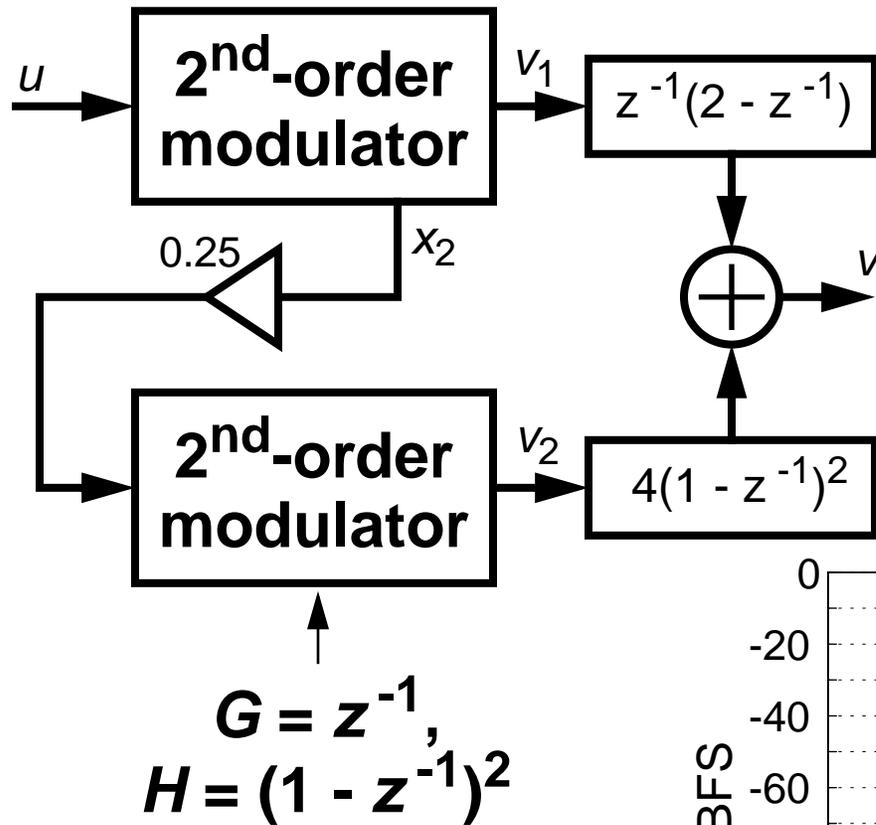

```


mod = mod2;
ABCD = mod.ABCD;
[v1 x] = simulateDSM(input,ABCD);
v2 = simulateDSM(x(2,:)/4,ABCD);
v = filter([0 2 -1],1,v1) + ...
    4*filter([1 -2 1],1,v2);
    
```

Composite NTF is $4H^2$

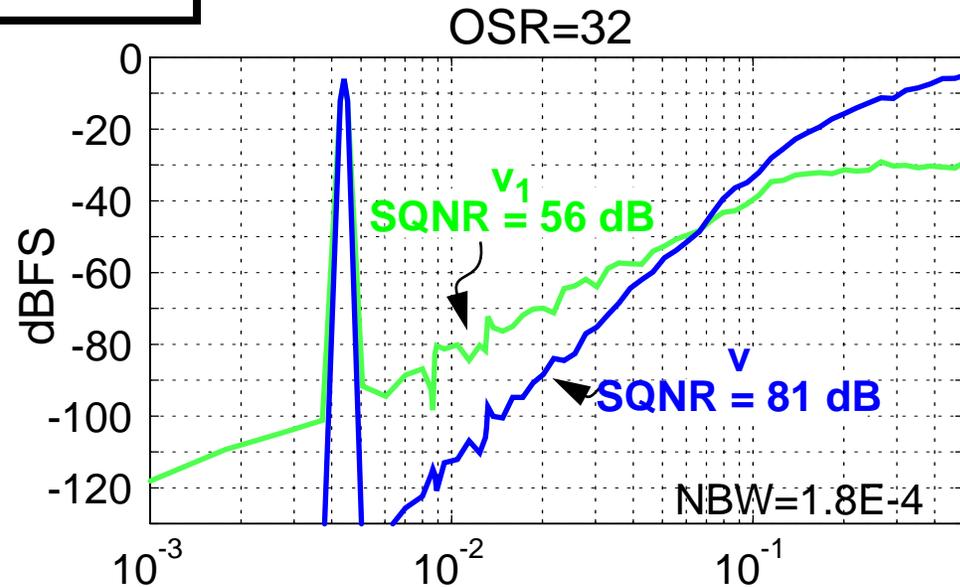

$\Delta\Sigma$ Toolbox Summary
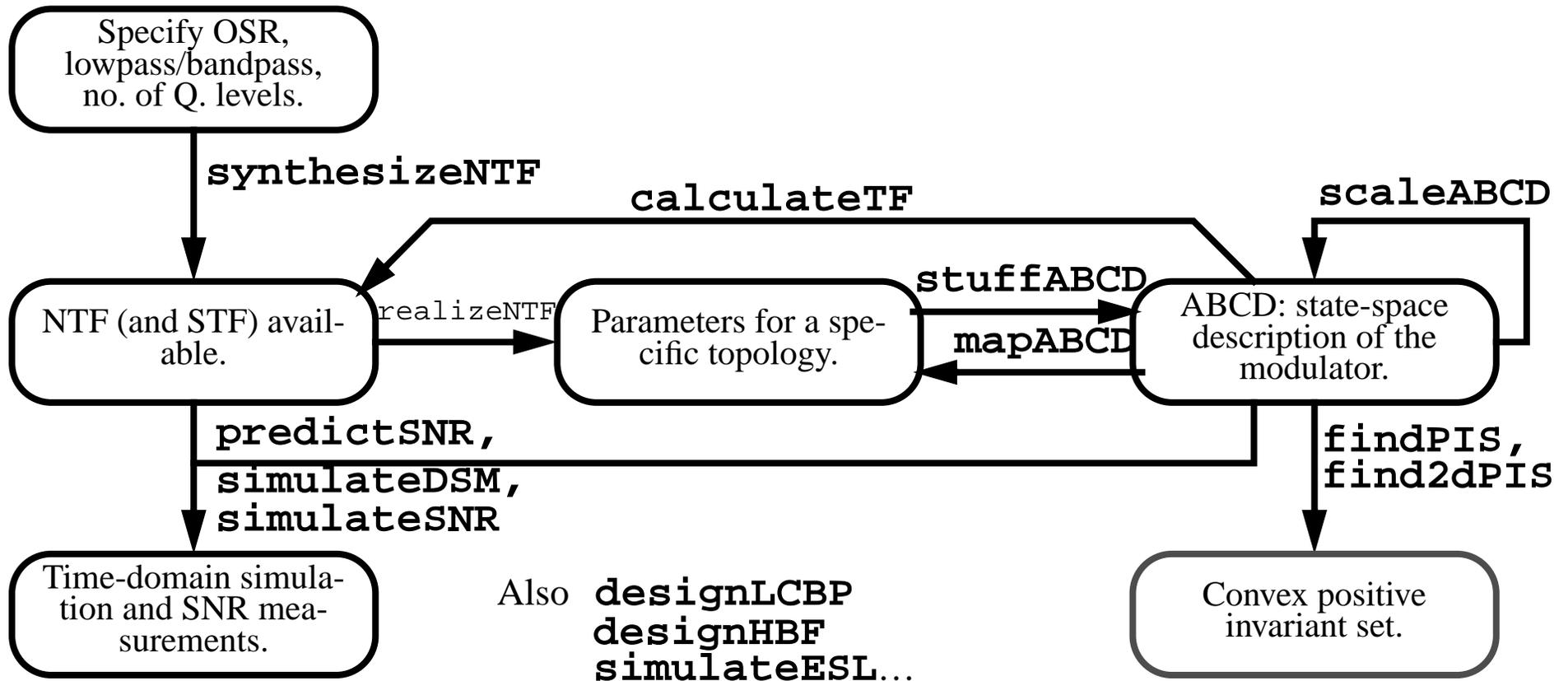
<http://www.mathworks.com/matlabcentral/fileexchange/>
 Click on Control Systems, then delsig




3. Bandpass $\Delta\Sigma$

A Bandpass $\Delta\Sigma$ ADC

- Like a lowpass $\Delta\Sigma$ ADC, a bandpass $\Delta\Sigma$ ADC converts its analog input into a bit-stream

The output bit-stream is essentially equal to the input in the band of interest.

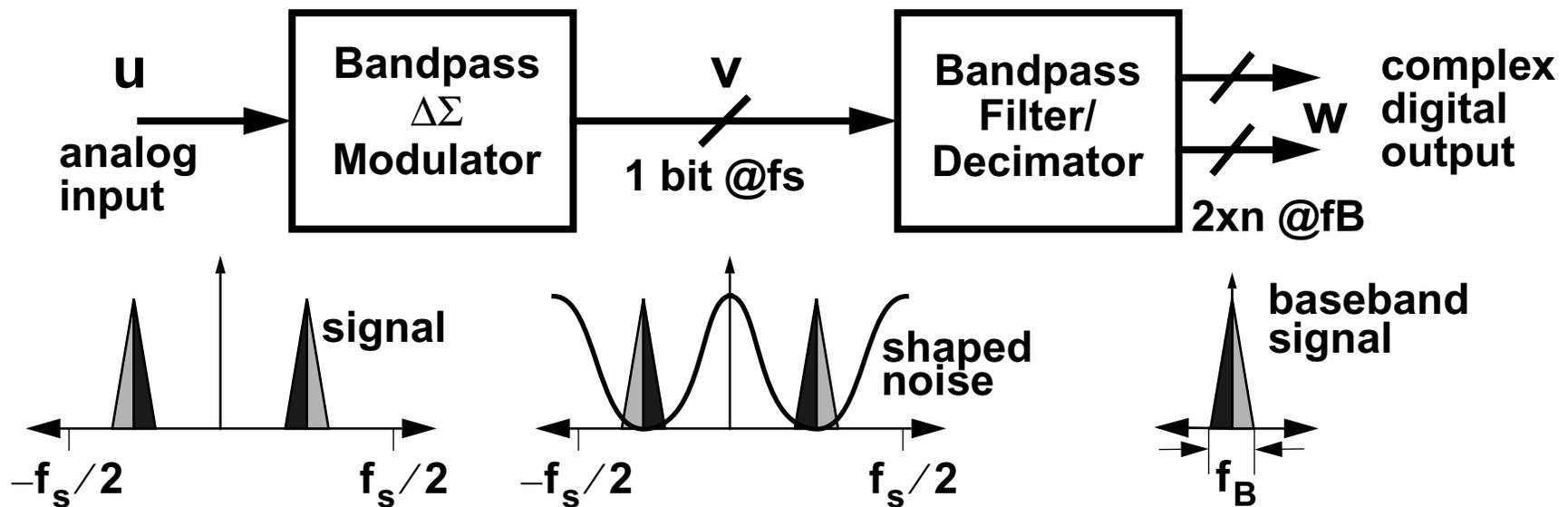
- A digital filter removes out-of-band noise and mixes the signal to baseband



BP $\Delta\Sigma$ Perspective #1

It is just Filtering and Feedback

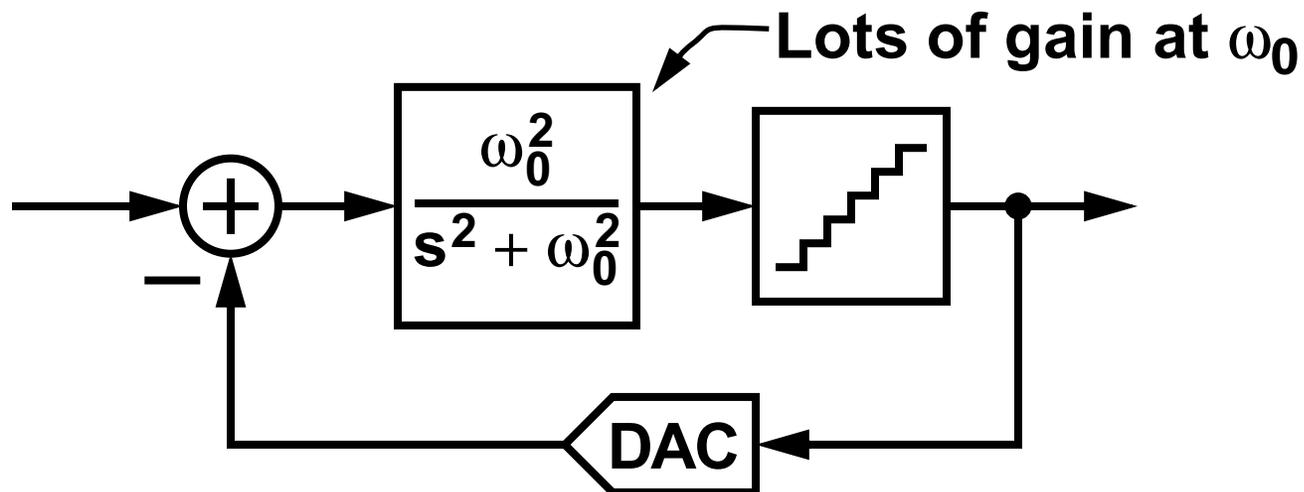- Putting the poles of the loop filter at ω_0 forces H to have zeros at ω_0
- Example system diagram:



BP $\Delta\Sigma$ Perspective #2

**It is just the result of an
“ N -Path Transformation”**


- **$z \rightarrow -z^2$ (a “pseudo 2-path transformation”) applied to $H(z) = 1 - z^{-1}$ yields $H'(z) = 1 + z^{-2}$**
- **This transformation can be applied to any system that processes DT signals, including SC filters, digital filters, $\Delta\Sigma$ modulators and even mismatch-shaping logic**

By replacing the state storage elements (registers), or by interleaving two copies of the original system and negating alternate inputs and outputs

BP $\Delta\Sigma$ Perspective #3

It is something New and Valuable

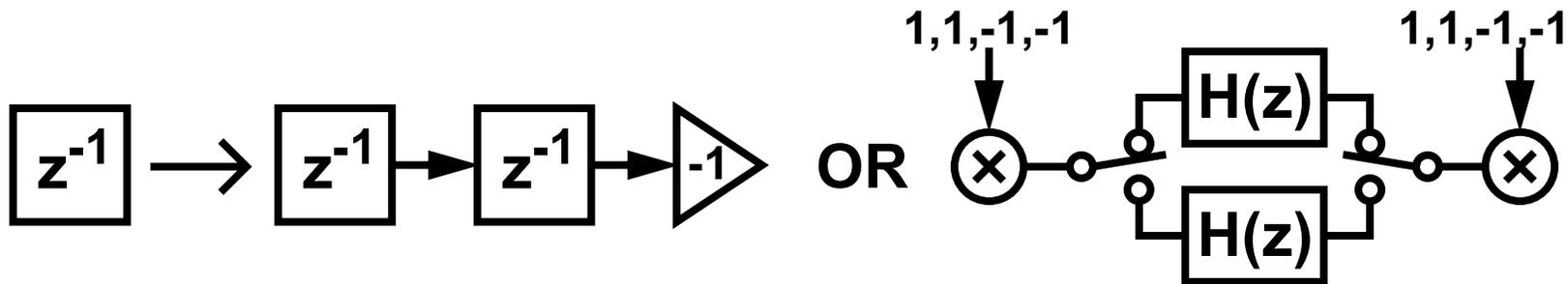
- **BP $\Delta\Sigma$ offers a way to make a “tuned” ADC**
Possibly the only way.
Ideally-suited to narrowband systems, i.e. radios.
- **BP $\Delta\Sigma$ keeps the signal away from 1/f noise as well as low-frequency distortion products**
Like regular narrowband bandpass systems, second-harmonic distortion is not problematic.



A 6th-Order Bandpass NTF


- Pole/Zero diagram:
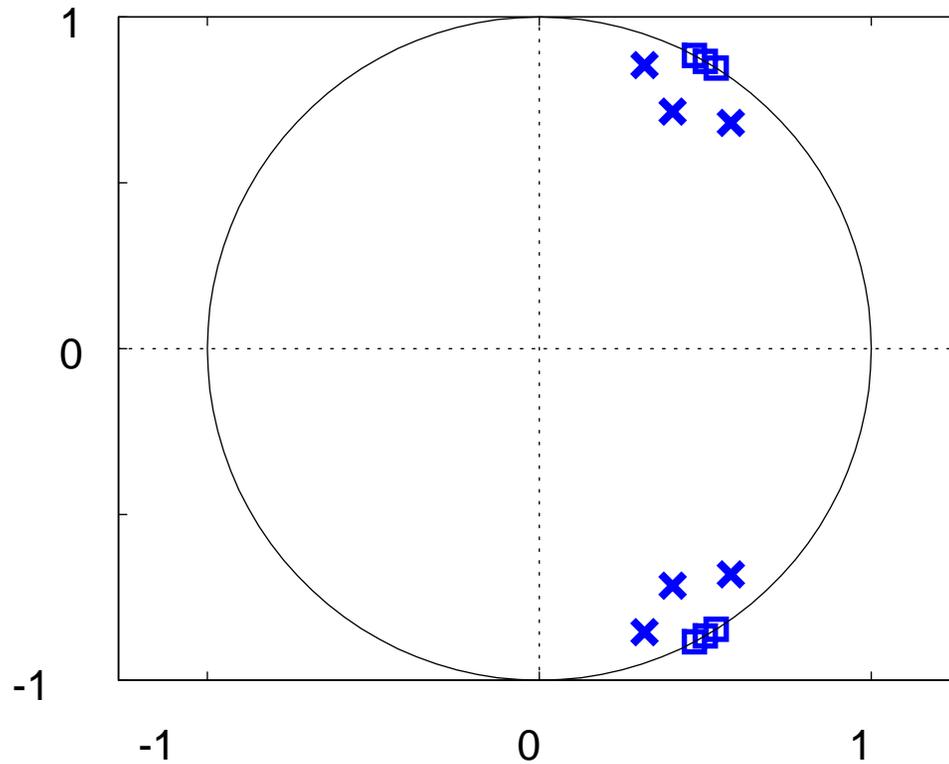
```
OSR = 64;  
f0 = 1/6;  
H=synthesizeNTF(6,OSR,1,[],f0);...
```




Example Waveform

8th-Order $f_s/8$ Bandpass Modulator

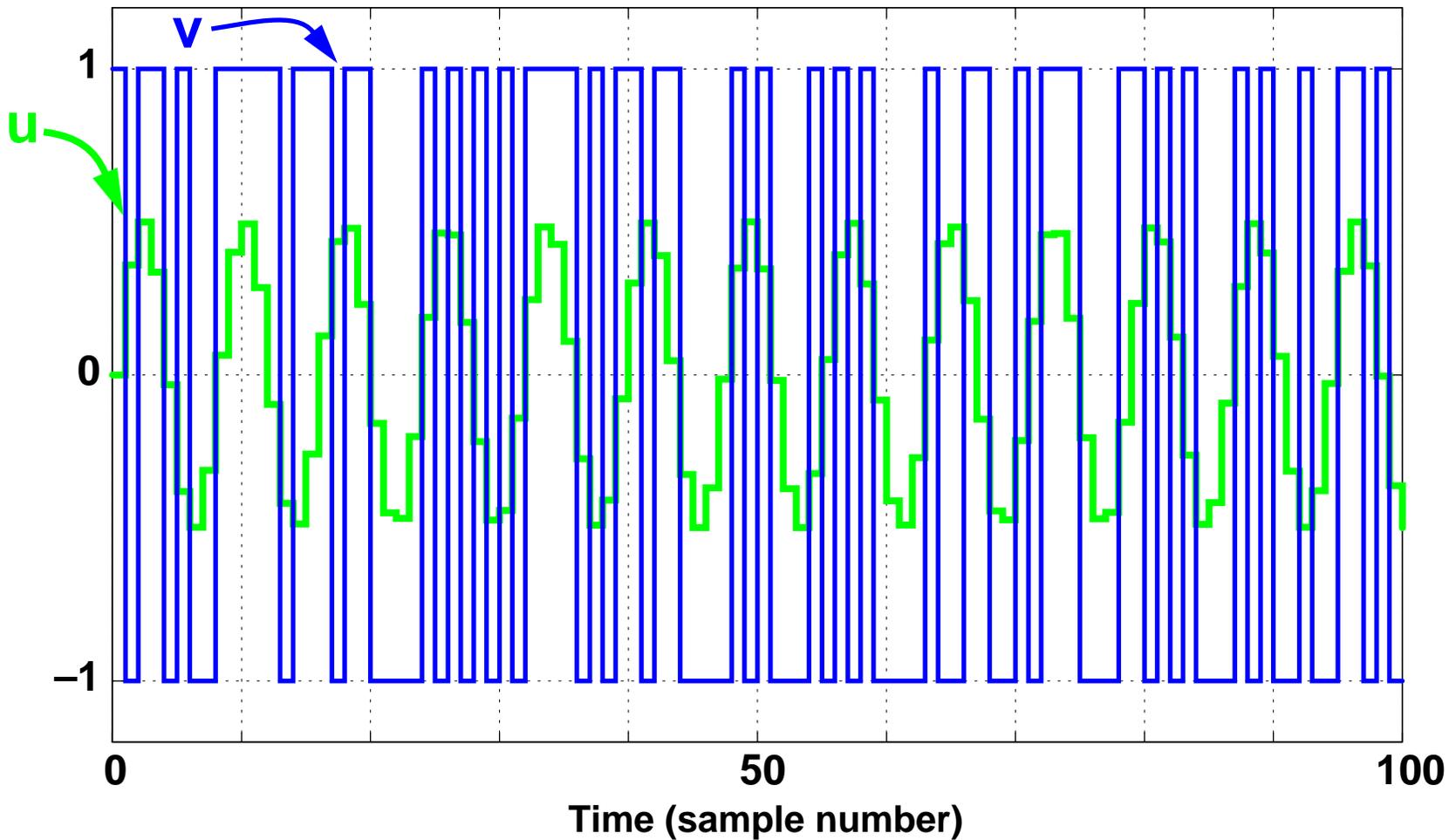


Example Spectrum

8th-Order $f_s/8$ Bandpass Modulator

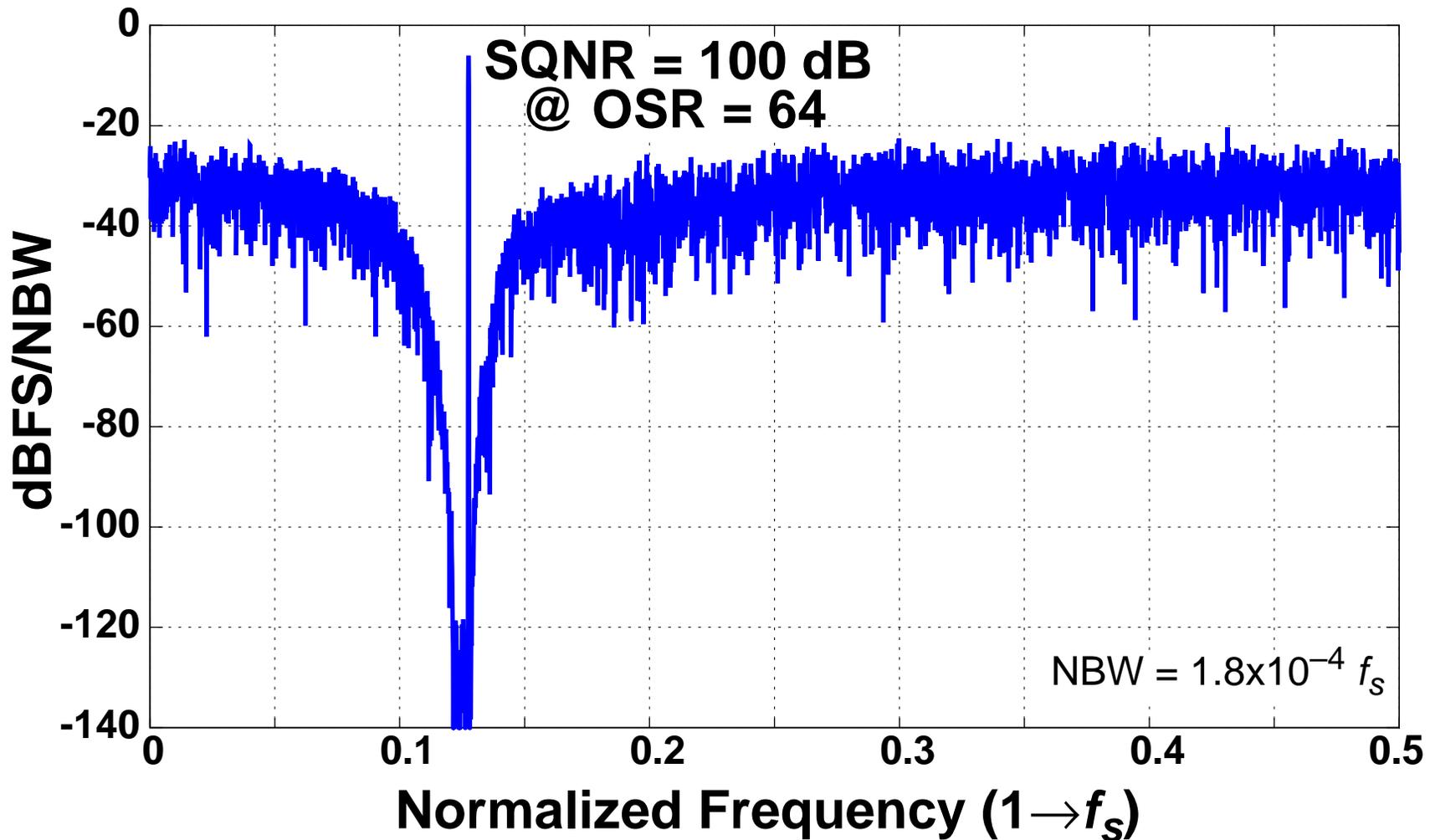


Bandpass Modulator Structure

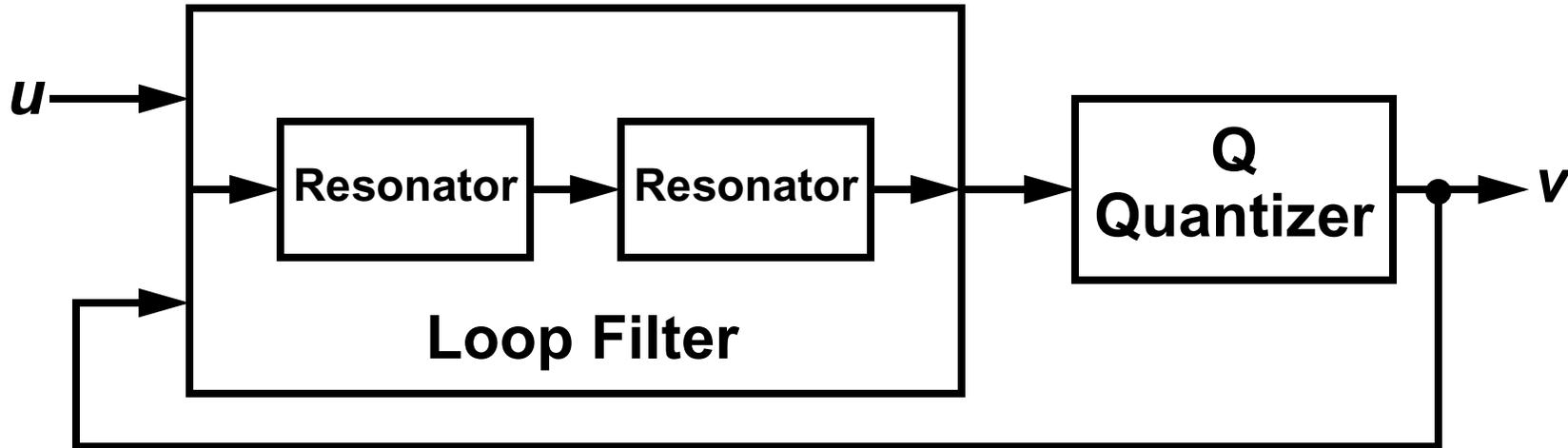

- **The loop filter consists of a cascade of resonators**
 - The resonance frequencies determine the poles of the loop filter and hence the zeros of the NTF.**
- **Multibit and multistage variants are also possible**

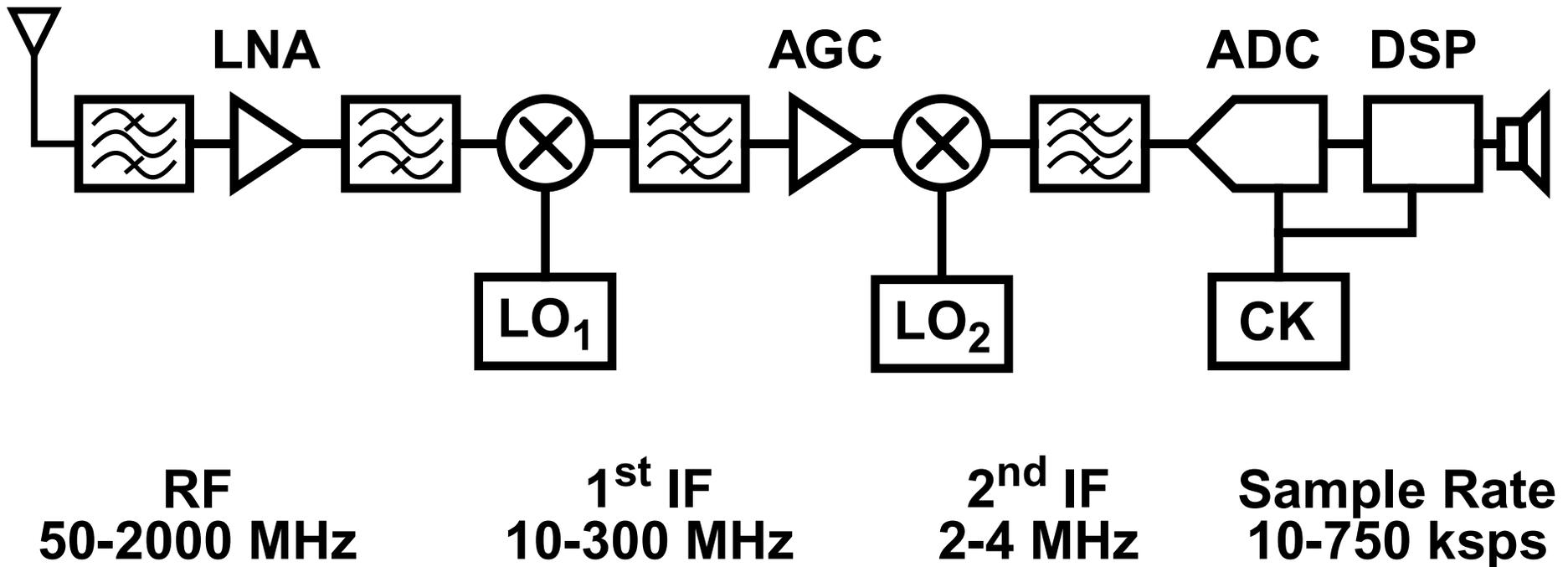
4. Design Example

A Dual-Conversion Superheterodyne Receiver




- A bandpass ADC fits naturally into this narrowband system
Perfect I/Q, high dynamic range. Low power?

System Partitioning

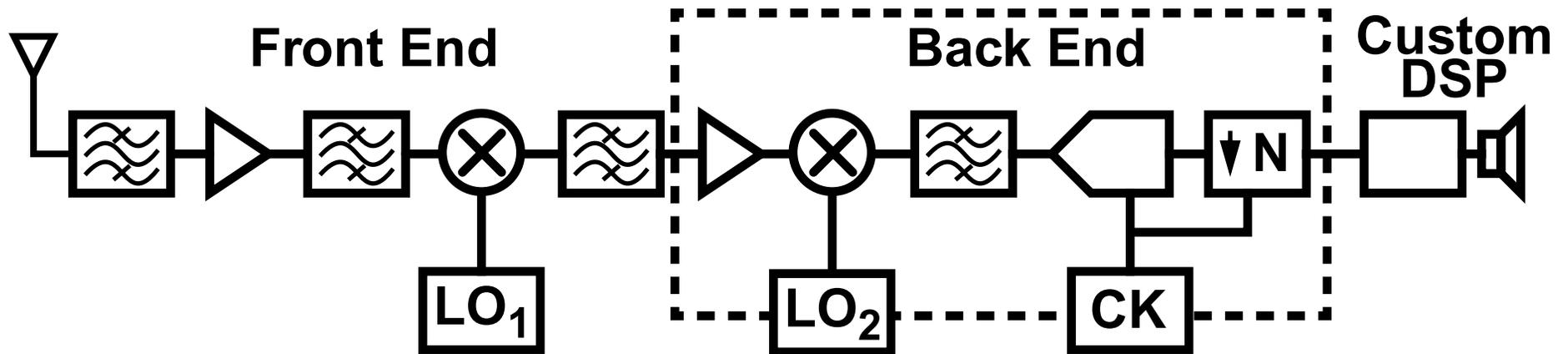

- **Goal: a general-purpose, high-performance, low-power back-end**

Traditional Implementation

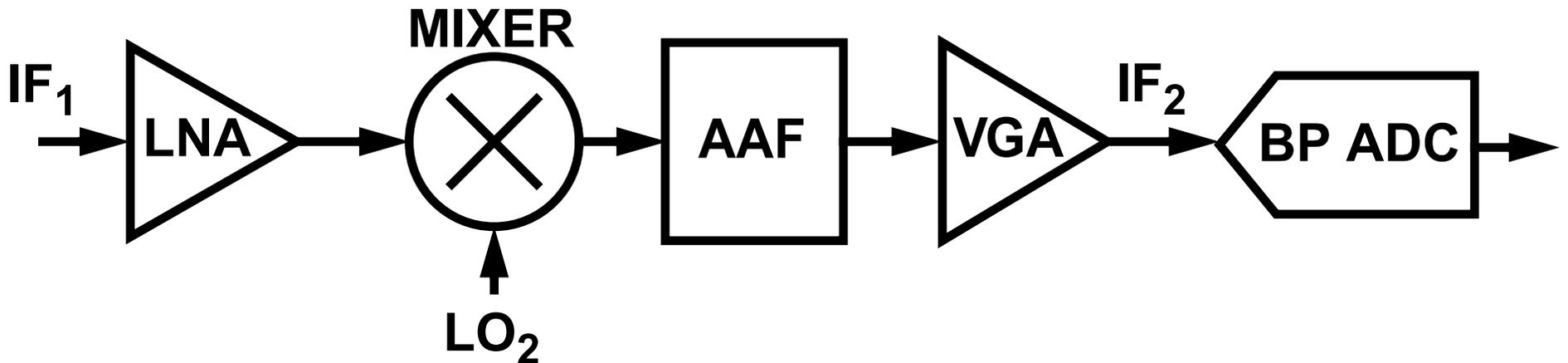

Numerous high-dynamic range blocks




Noise and power budgets are very tight



Large VGA range needed

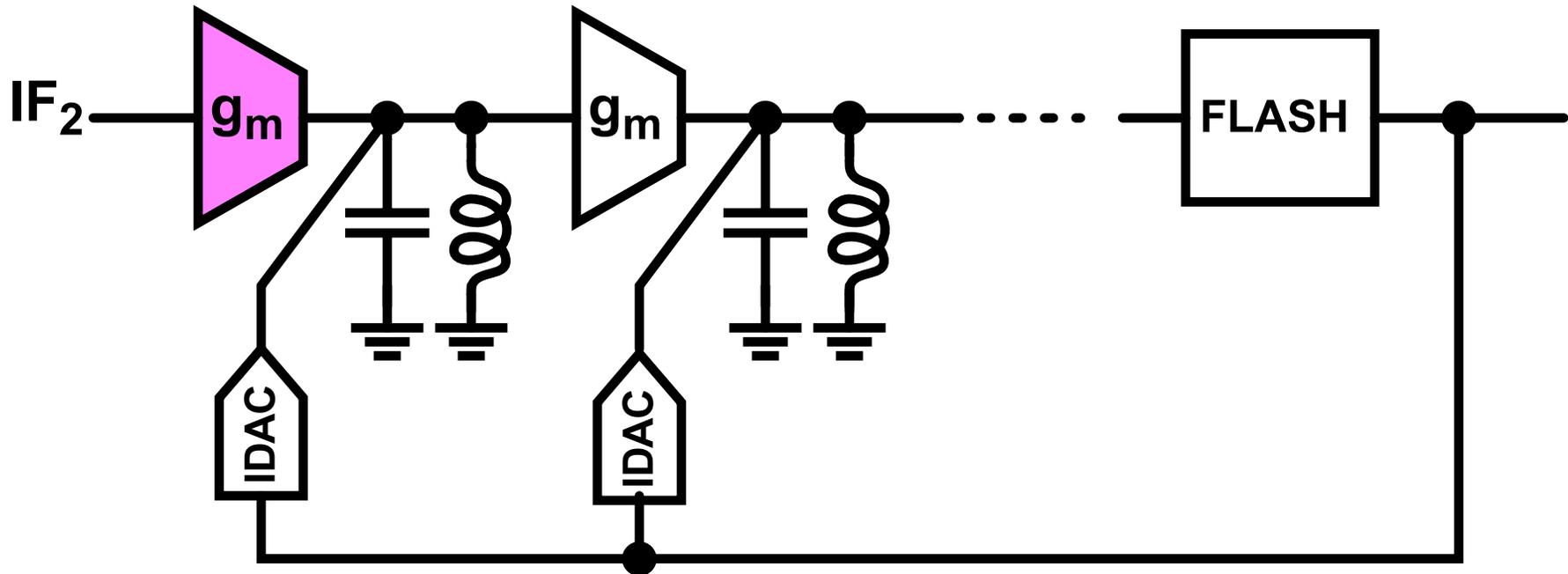Eliminating the AAF with a Continuous-Time BP $\Sigma\Delta$ ADC




Anti-alias filtering is inherent




But still need a **low-noise, linear V-I converter**

Eliminating the Input g_m

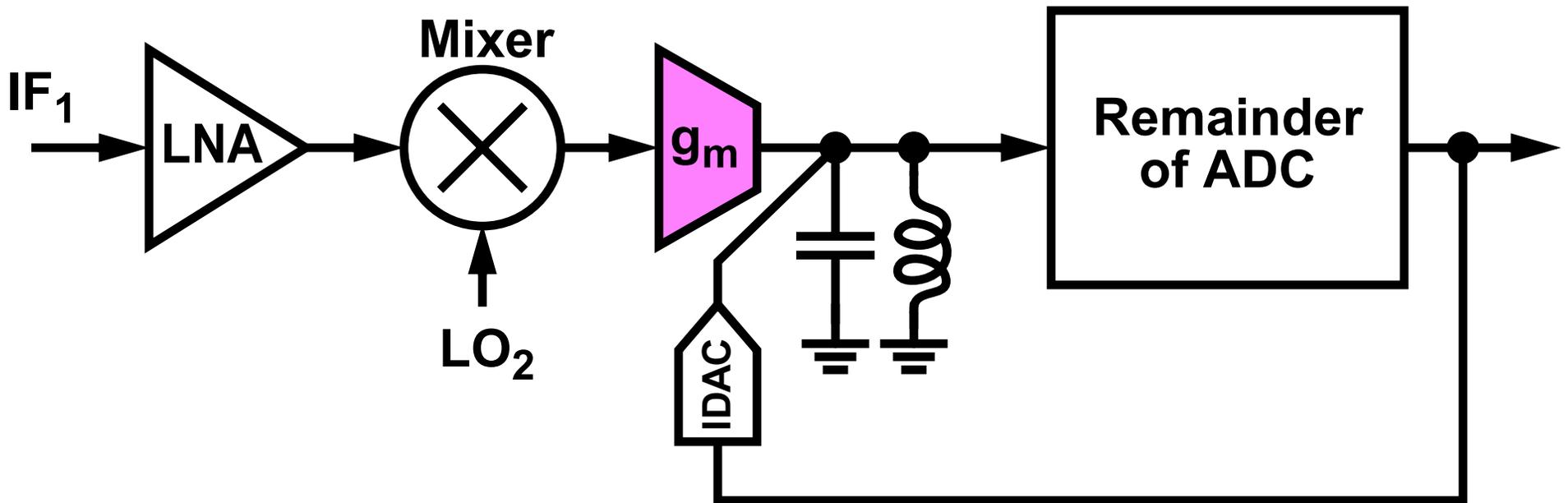


The output of the mixer is available in current form, so ...

Merge ADC with Mixer!

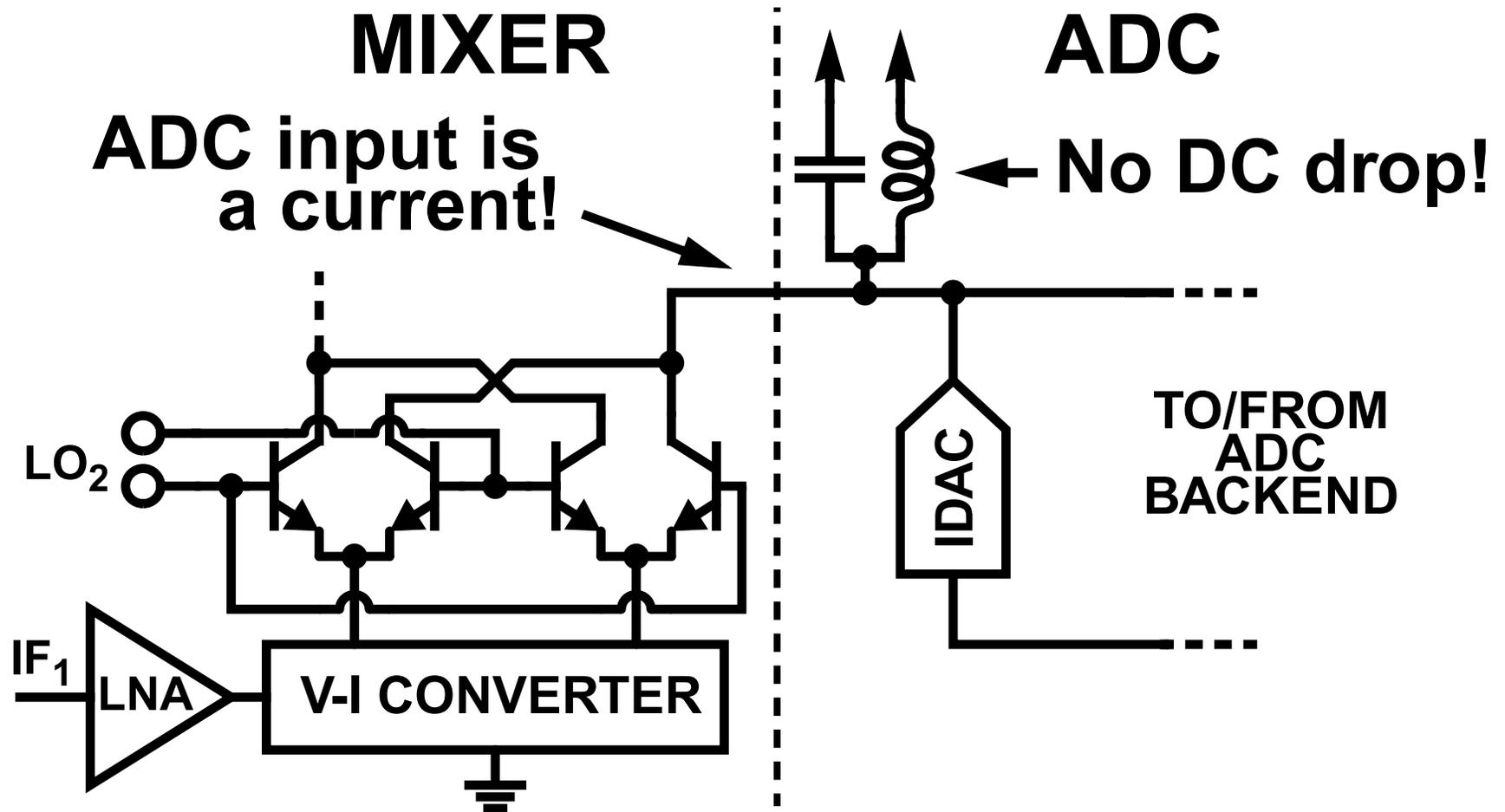

- **Eliminates redundant I-V & V-I conversion**
- **Gives mixer and IDAC more headroom**

Merge ADC with Mixer!

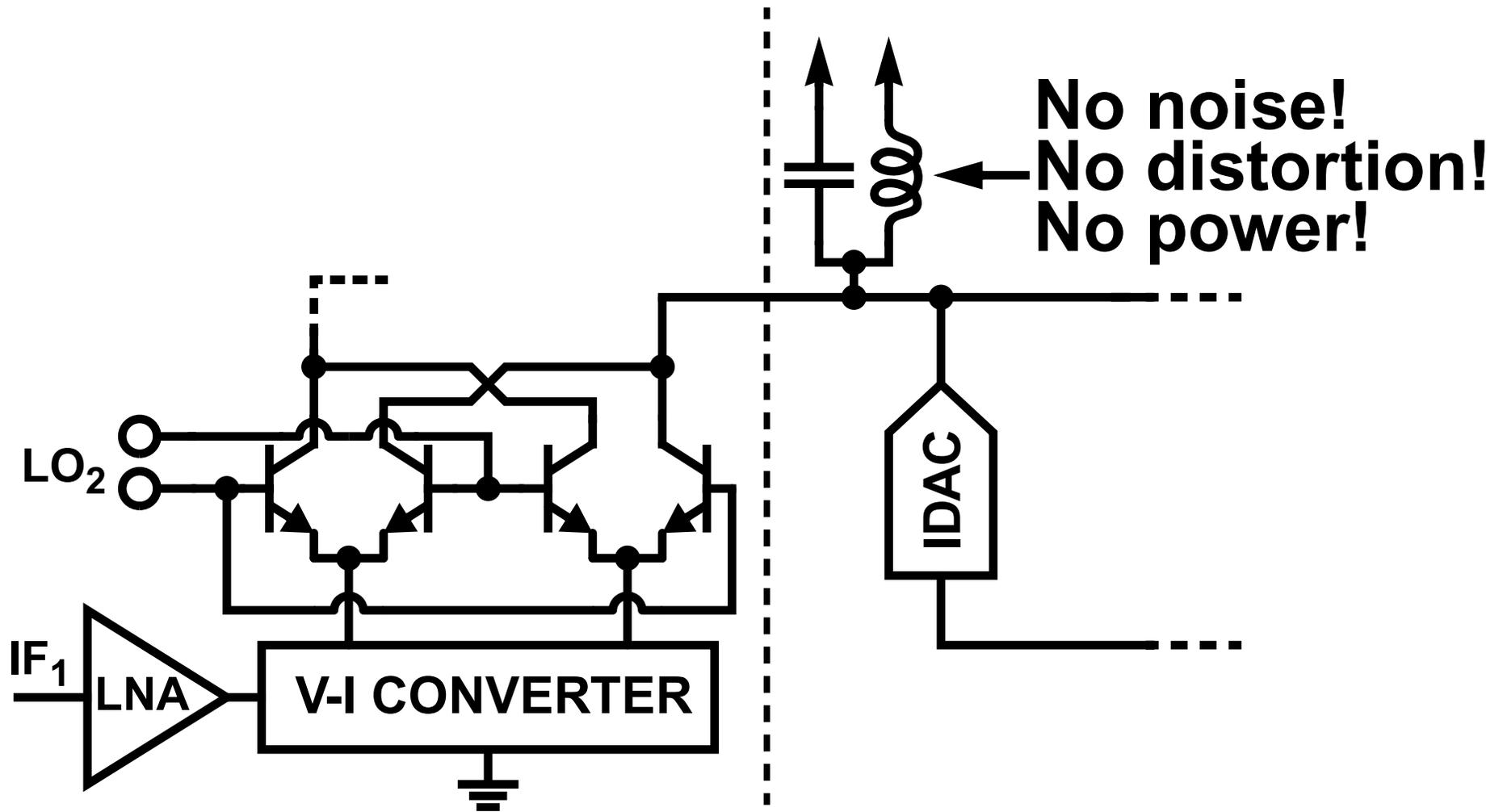

LC tank effectively adds gain, without adding noise, adding distortion or consuming power


Z_{eff}

- **Near resonance, $|Z_L| = |Z_C|$
 $|Z_{L,C}| \approx 300\Omega$ in this design**
- **At resonance, $|Z| \approx Q \cdot |Z_{L,C}|$
About $6k\Omega$ for $Q = 20 \Rightarrow g_m Z \approx 60$.**
- **More generally, the effective tank impedance is found by integrating the input-referred noise over the band of interest:**

$$\int \left(\frac{v_n}{g_m Z(\omega)} \right)^2 d\omega = \left(\frac{v_n}{g_m} \right)^2 \int Y(\omega)^2 d\omega = \left(\frac{v_n}{g_m Z_{eff}} \right)^2$$

$$\Rightarrow Z_{eff} = (Y_{rms})^{-1}$$

Z vs. Frequency

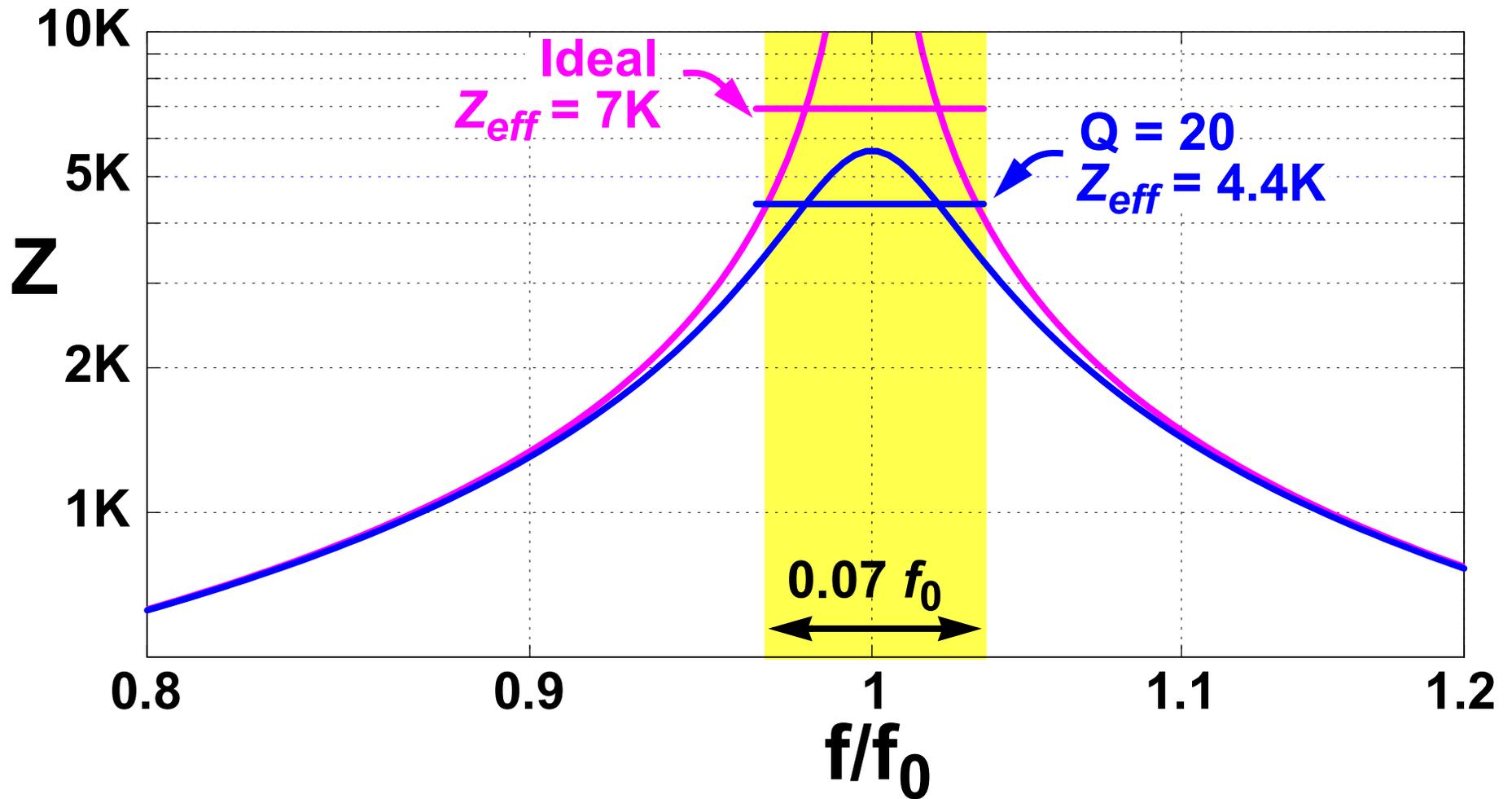


- $Q = 20$ reduces Z_{eff} by about 4 dB


Tuning the LC Tank

- $\Delta f_0/f_0 = 2\% \Rightarrow 3 \text{ dB reduction in } Z_{eff}$
Inductor accuracy is 10%, so tuning is required

Make an oscillator:

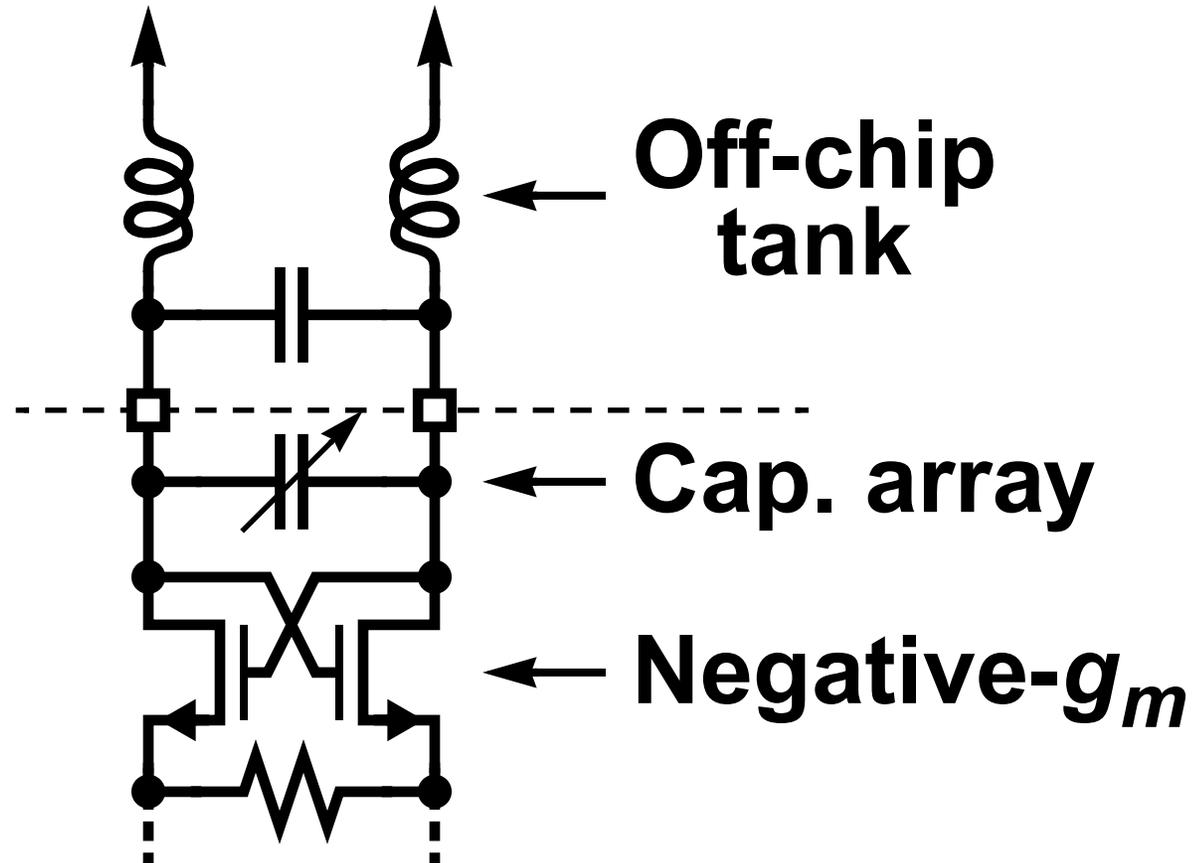


Remainder of ADC?

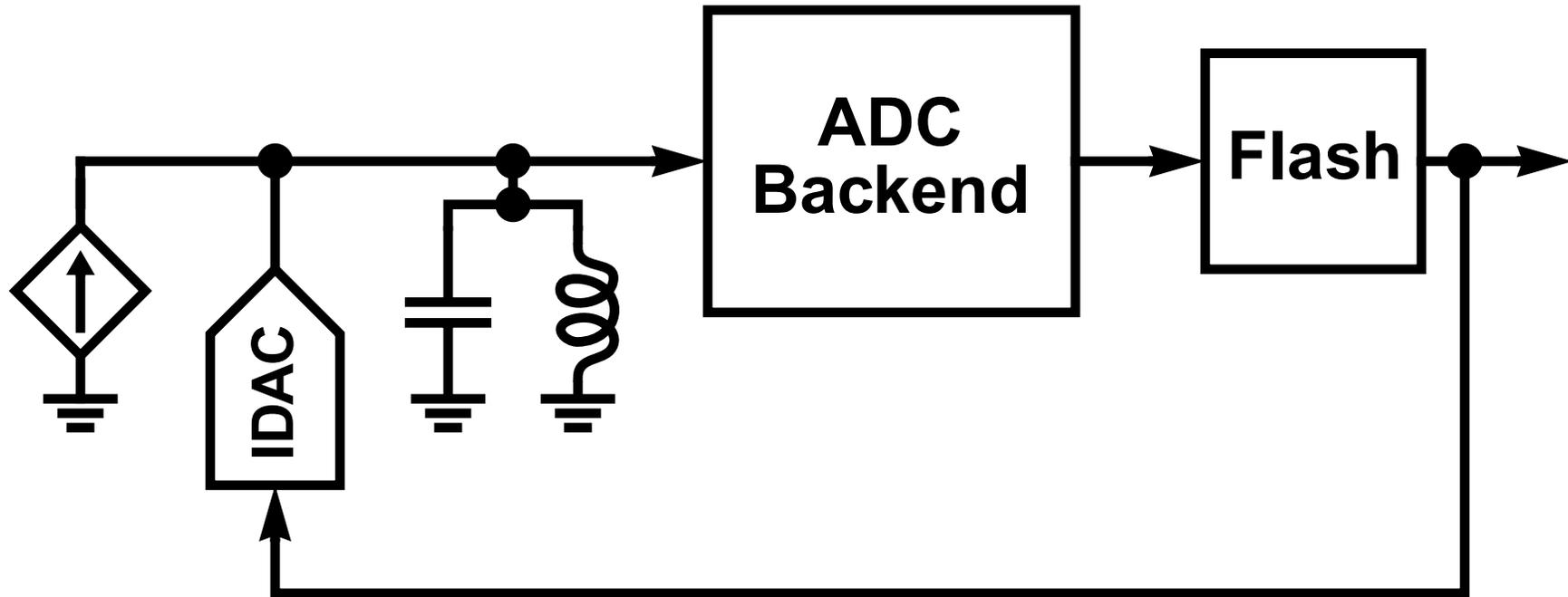


- Add resonator stages until the quantization noise of the flash is low enough

Second Resonator?

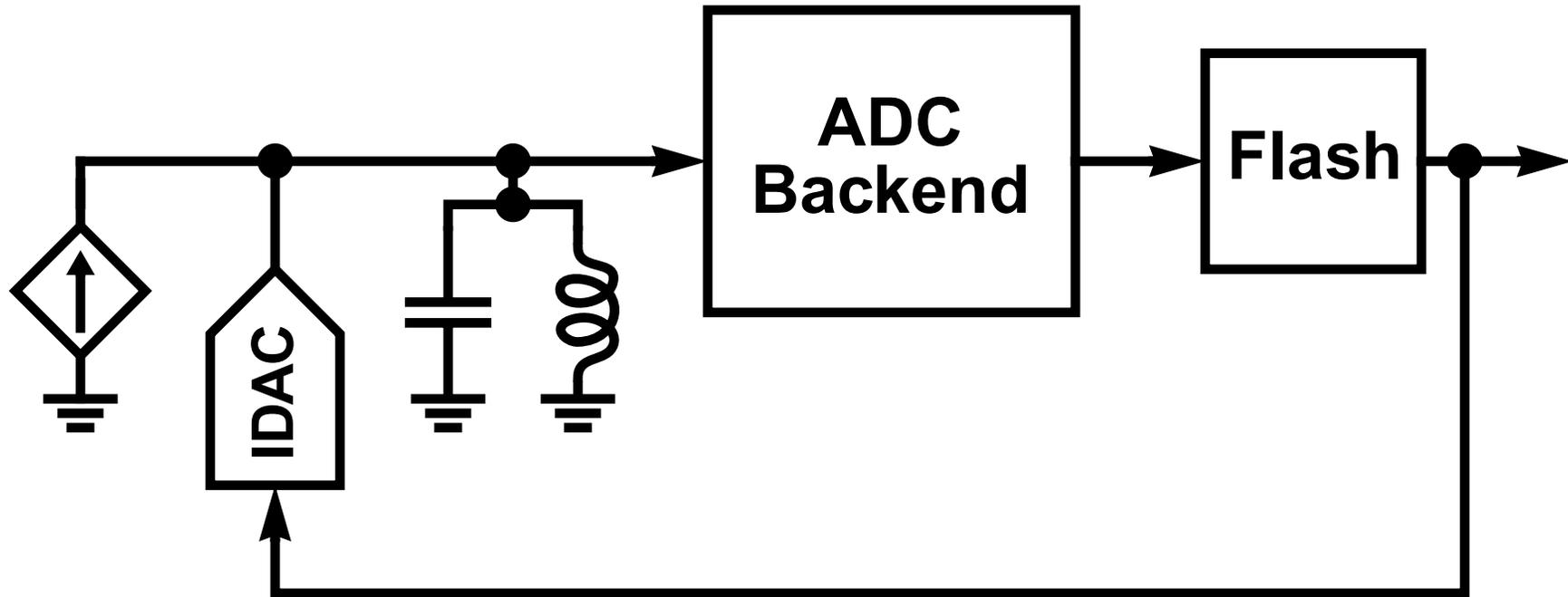


- **LC: Needs more external components plus associated pins**
- **Active-RC: 2 mA for $50 \text{ nV}/\sqrt{\text{Hz}}$ input-referred noise**
- **Switched-Cap: est. $>10 \text{ mA}$ for same noise**

Third Resonator?

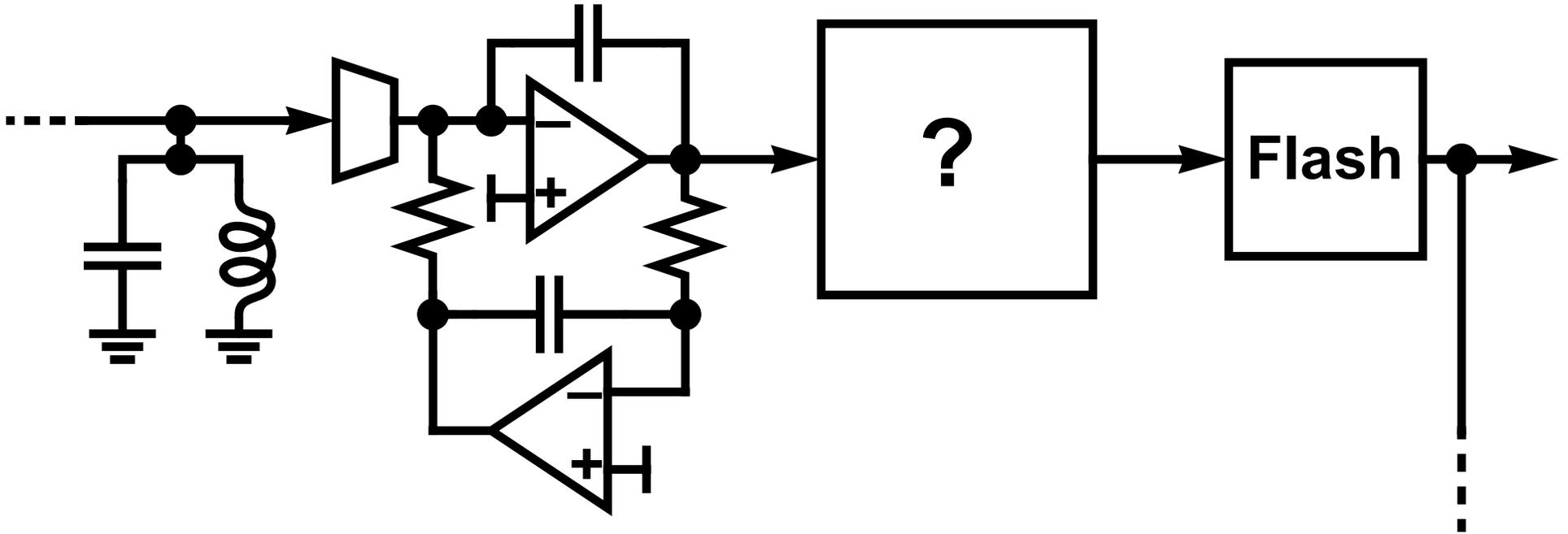


- **Active-RC:** $Q \approx 10 \Rightarrow$ Need 4th resonator
- **Switched-Cap:** Q is high & drift is low;
<1 mA for $300 \text{ nV}/\sqrt{\text{Hz}}$ i.r.n.

Complete ADC

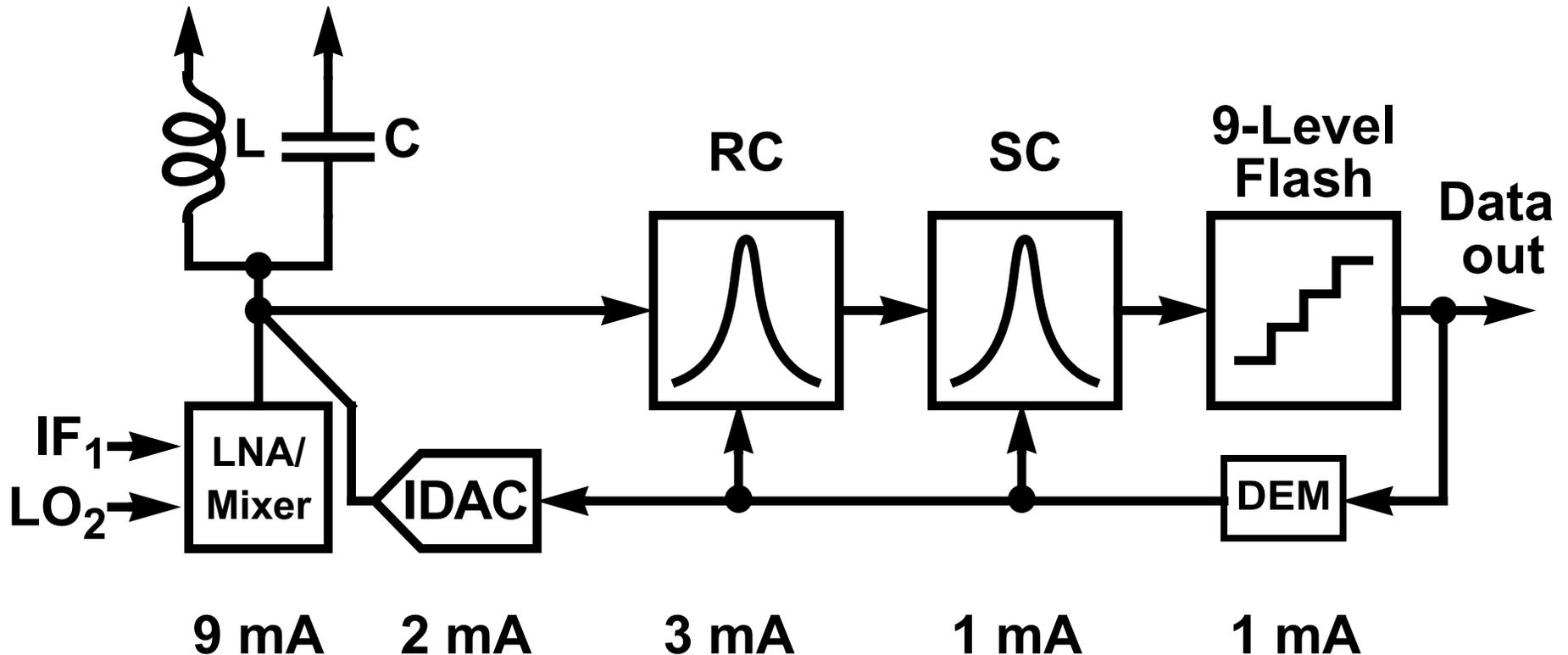


- **Eliminates high-power VGA & AAF**
2/3 of the total power used by LNA, Mixer & IDAC
- **Uses cts-time and discrete-time elements, plus multi-bit quantization and mismatch-shaping**

ADC in More Detail

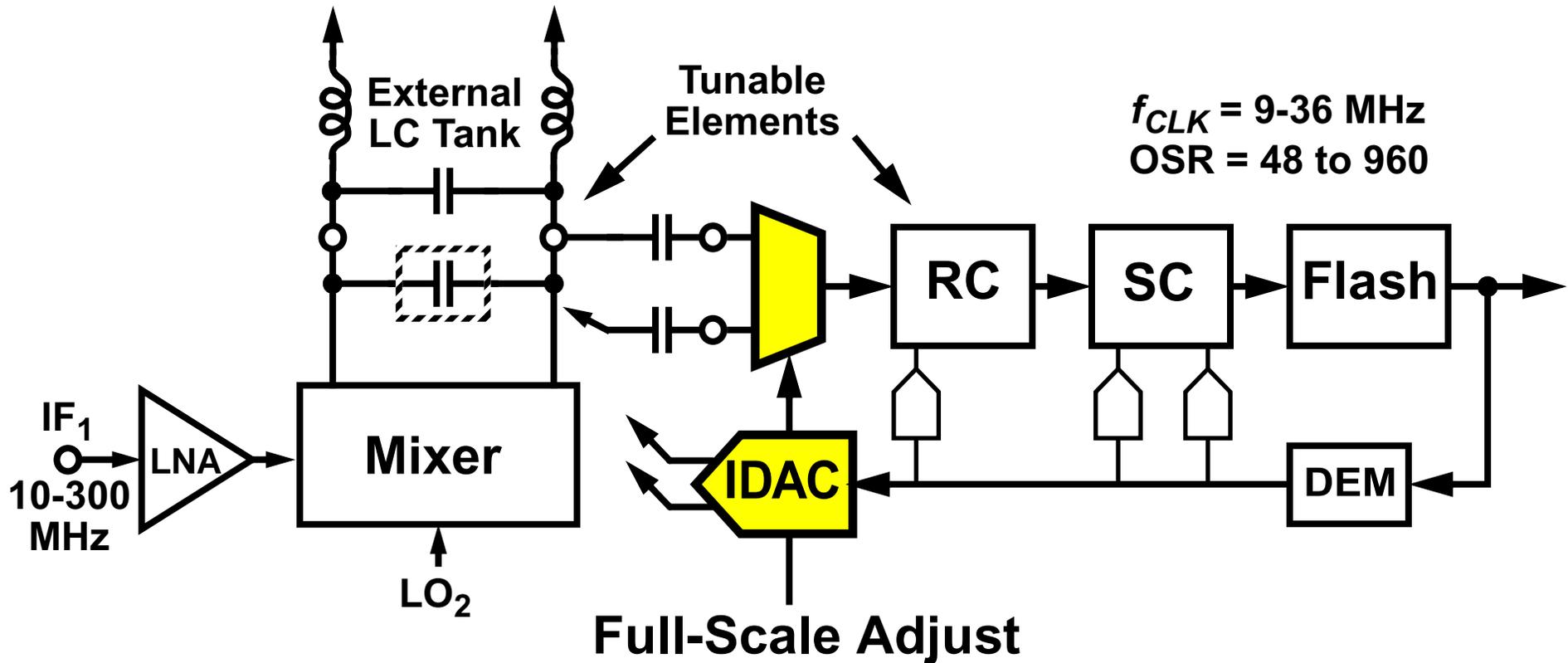


- **Can save power under small-signal conditions by reducing IDAC's full-scale**
By a factor of 4, in this ADC


Noise vs. Full-Scale

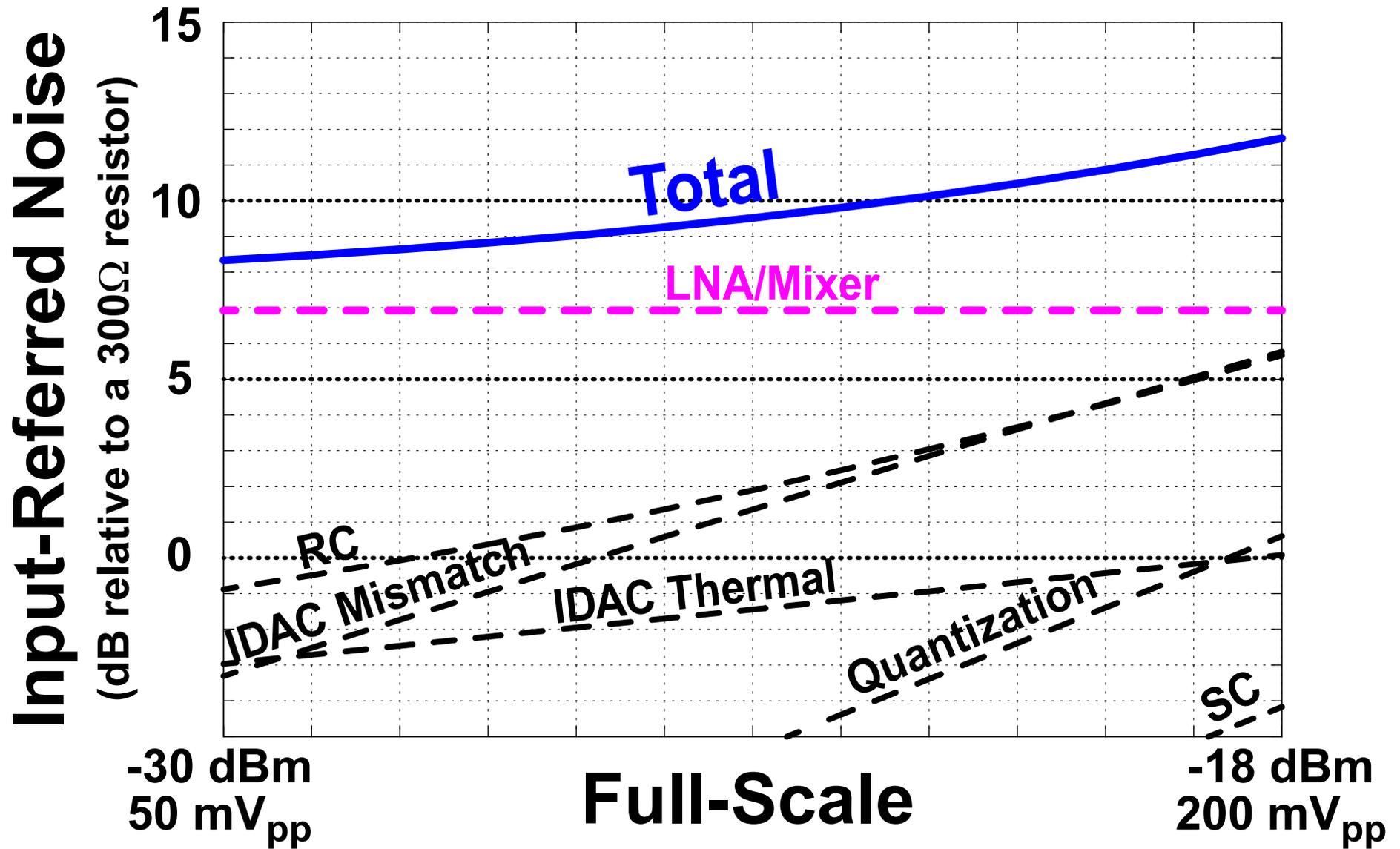


Measured STF & NTF

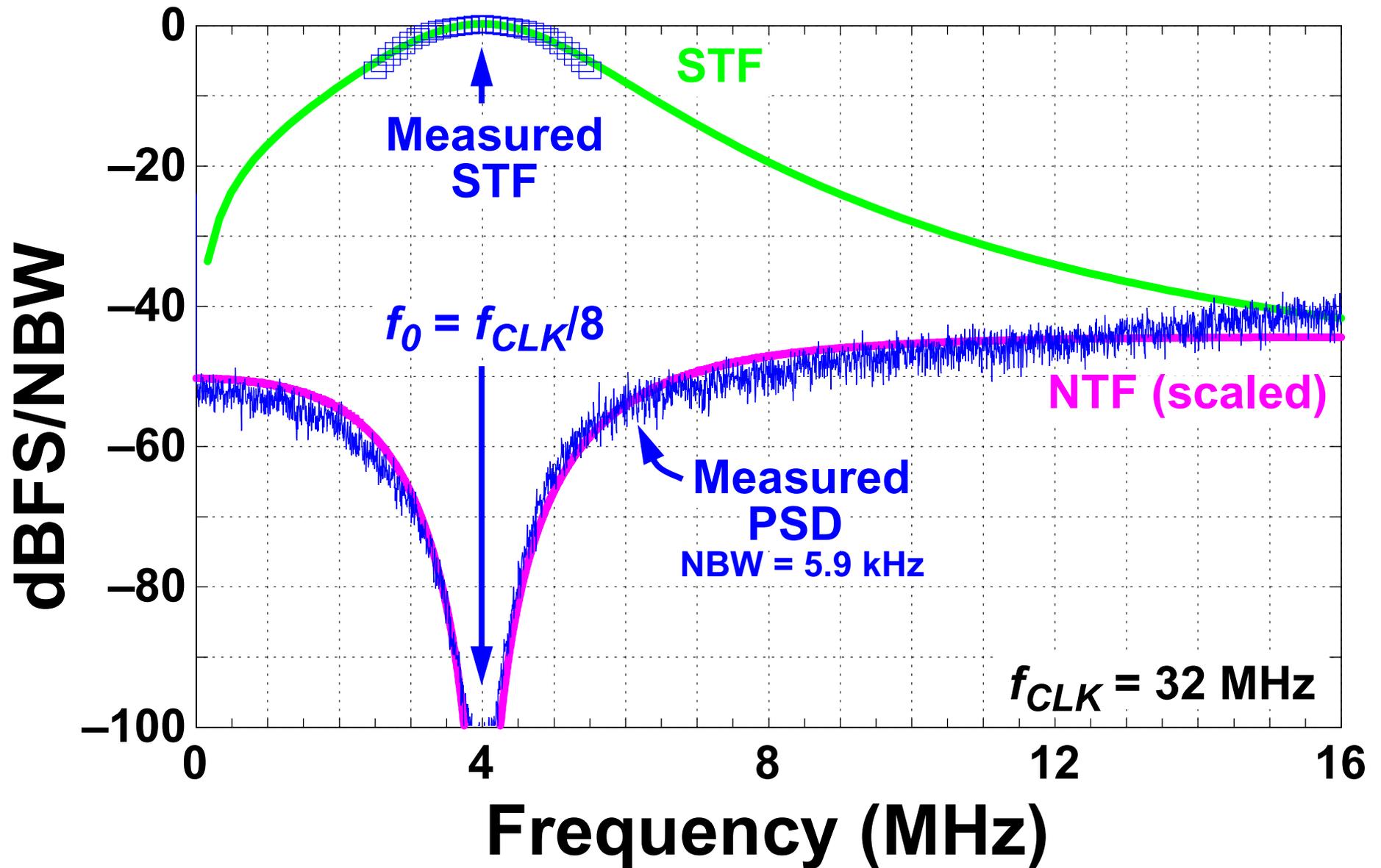


In-Band Spectrum (OSR=48)

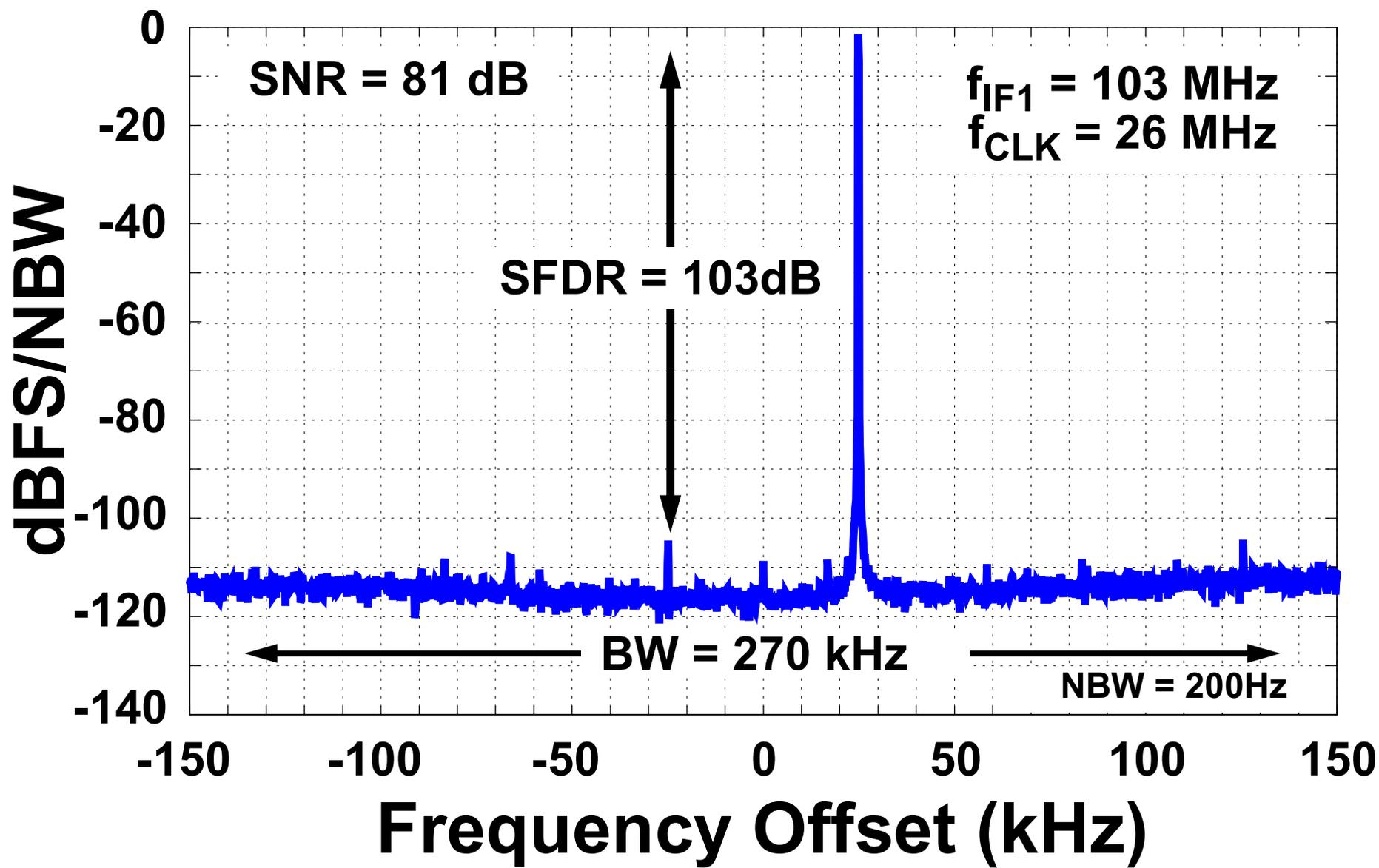

In-Band Spectrum (OSR=900)

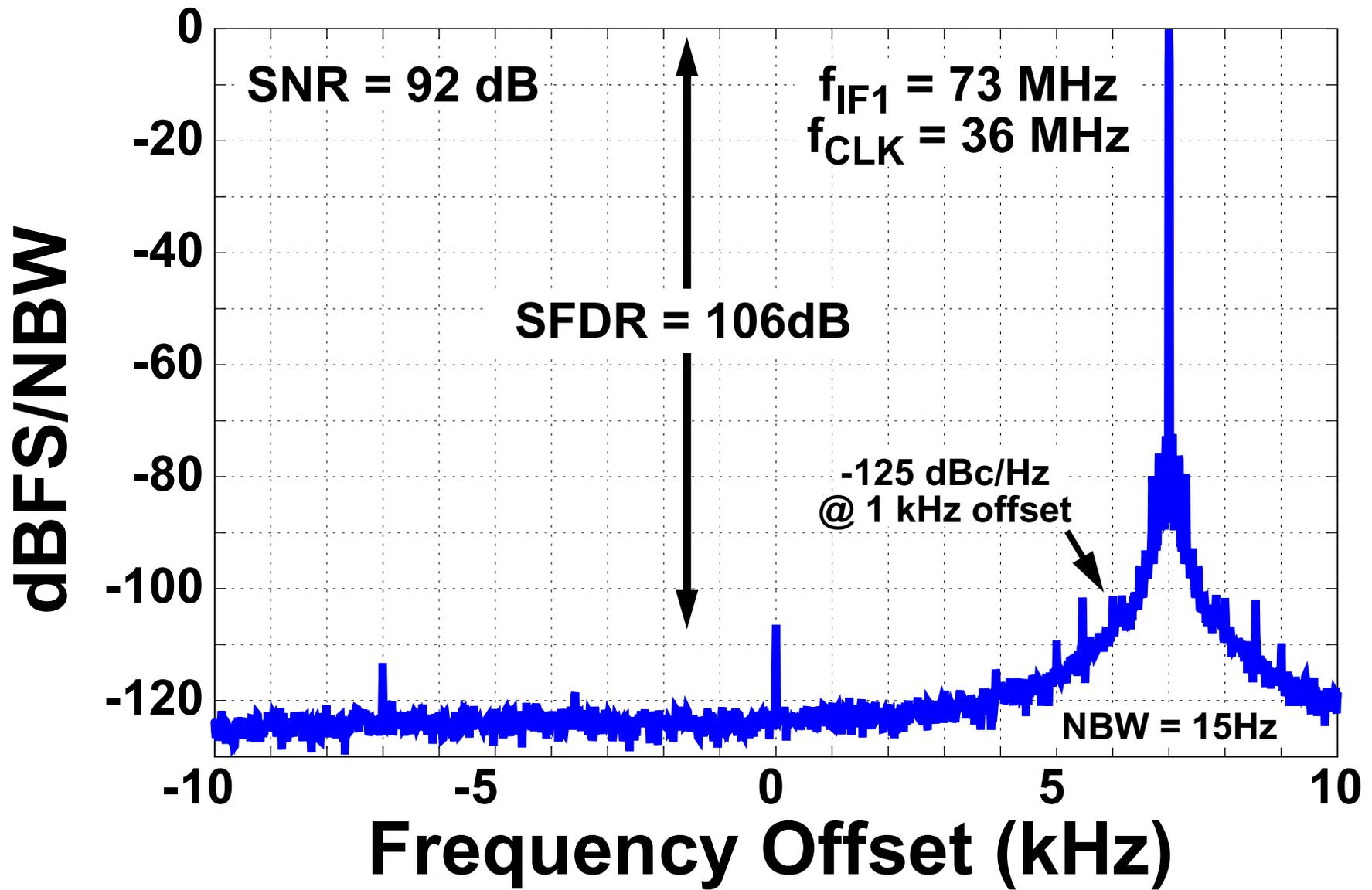

SNR vs. Input Power

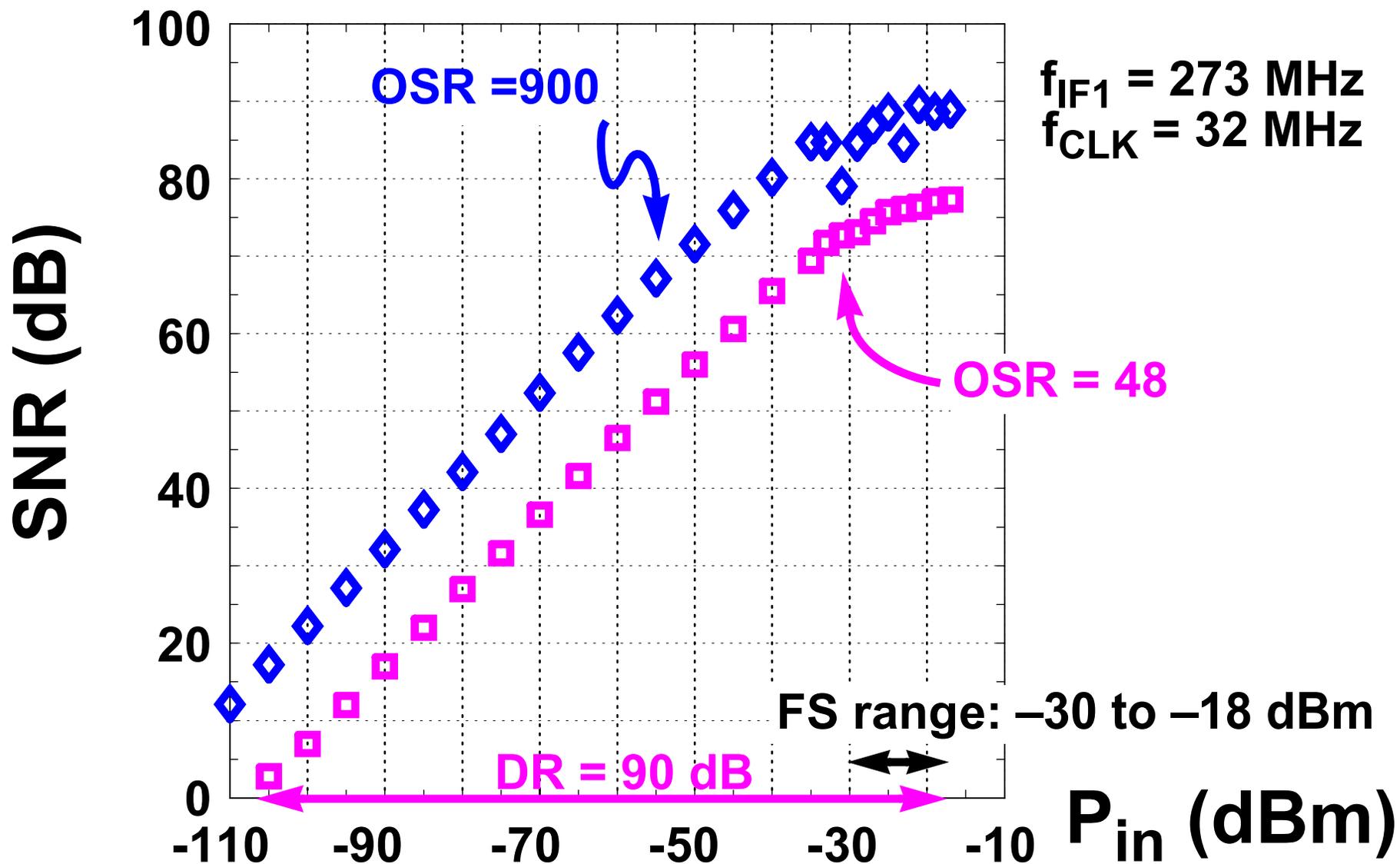

Architectural Highlights



Merging a mixer with a continuous-time bandpass ADC containing an LC tank yields a flexible, high-performance, low-power receiver backend.



Performing a component-count/performance/power trade-off in each resonator section results in a multi-bit, hybrid continuous-time/discrete-time architecture.



A variable full-scale saves power *and* reduces noise.


Performance Summary

Bandwidth	5 - 375	kHz
Input Frequency	10-300	MHz
Clock Frequency	9 - 36	MHz
Full-Scale Range	12	dB
Die Area	5	mm²

@ $f_{IF} = 73\text{MHz}$, $BW = 333\text{kHz}$, $f_{CLK} = 32\text{MHz}$, $VDD = 3\text{V}$:

Dynamic Range	90	dB
Current Consumption	16.5	mA
Noise Figure @ min FS	9	dB
IIP3	0	dBm

Bandpass $\Delta\Sigma$ ADCs

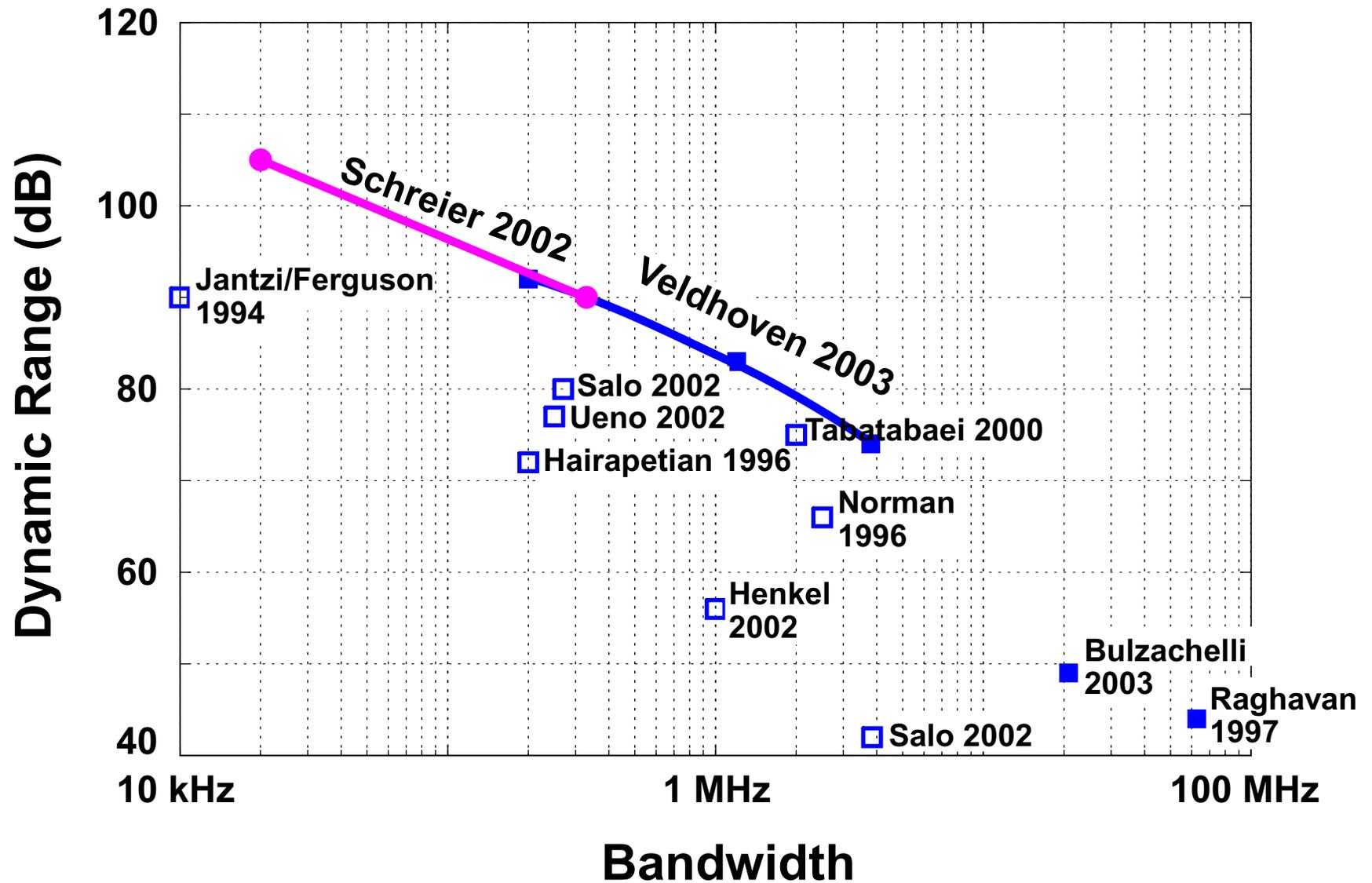

Summary

- **$\Delta\Sigma$ is fun**
All kinds of exotic behavior: limit-cycles, dead-bands sub-harmonic locking and even chaotic dynamics!
- **$\Delta\Sigma$ is a rich field**
ADCs and DACs; Single-bit and Multi-bit; Single-stage and Multi-stage; Lowpass and Bandpass; Discrete-time and Continuous-time...
- **A bandpass $\Delta\Sigma$ ADC converts an IF signal into digital form and can do so with high dynamic range and low power consumption**
With wideband or tunable modulators, conversion of RF to digital may soon be feasible.
ADC = “Antenna to Digital Converter”