

MITOPENCOURSEWARE
MASSACHUSETTS INSTITUTE OF TECHNOLOGY

6.976

High Speed Communication Circuits and Systems

Lecture 14


High Speed Frequency Dividers

Michael Perrott

Massachusetts Institute of Technology


Copyright © 2003 by Michael H. Perrott

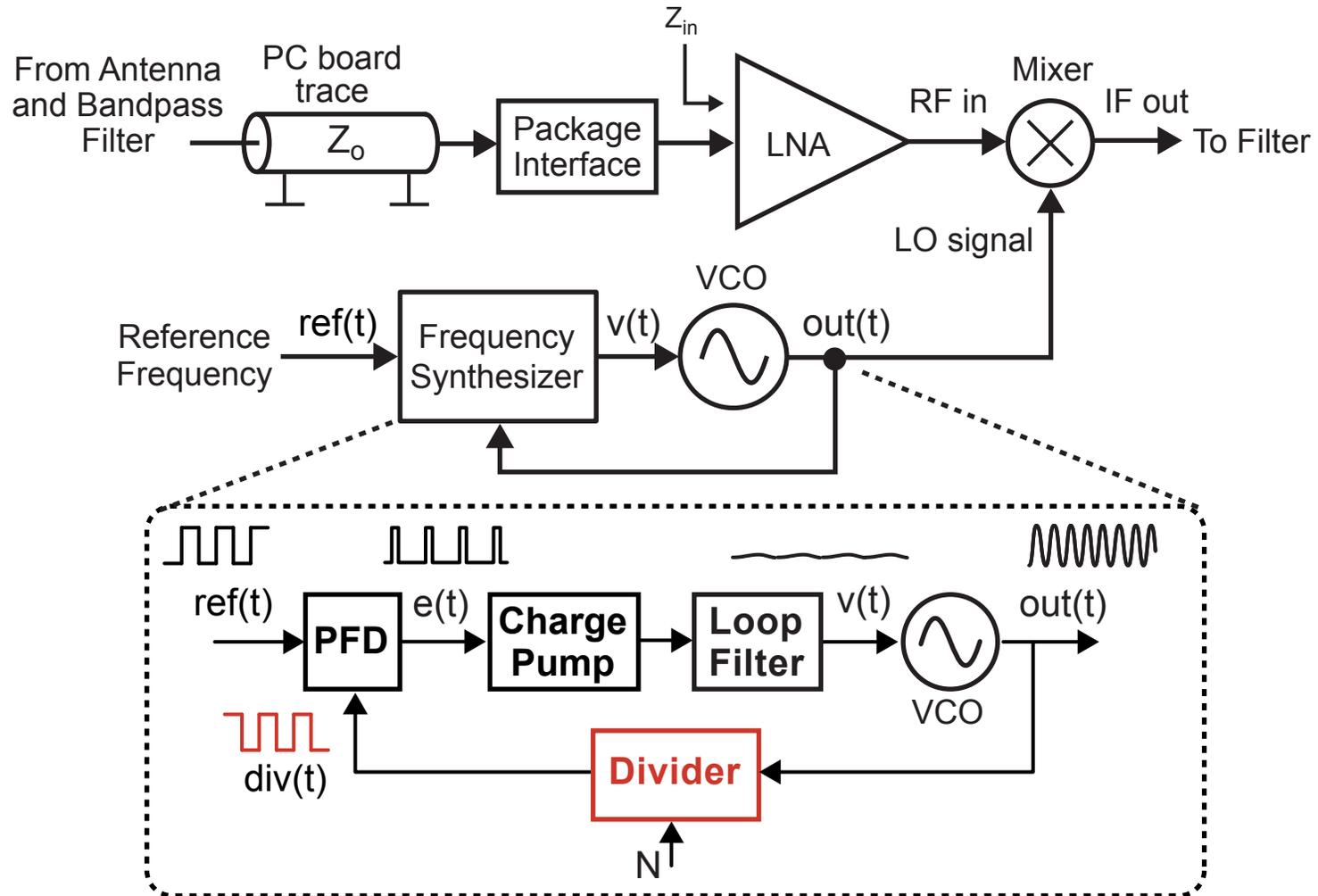High Speed Frequency Dividers in Wireless Systems





- Design Issues: high speed, low power

Divide-by-2 Circuit (Johnson Counter)

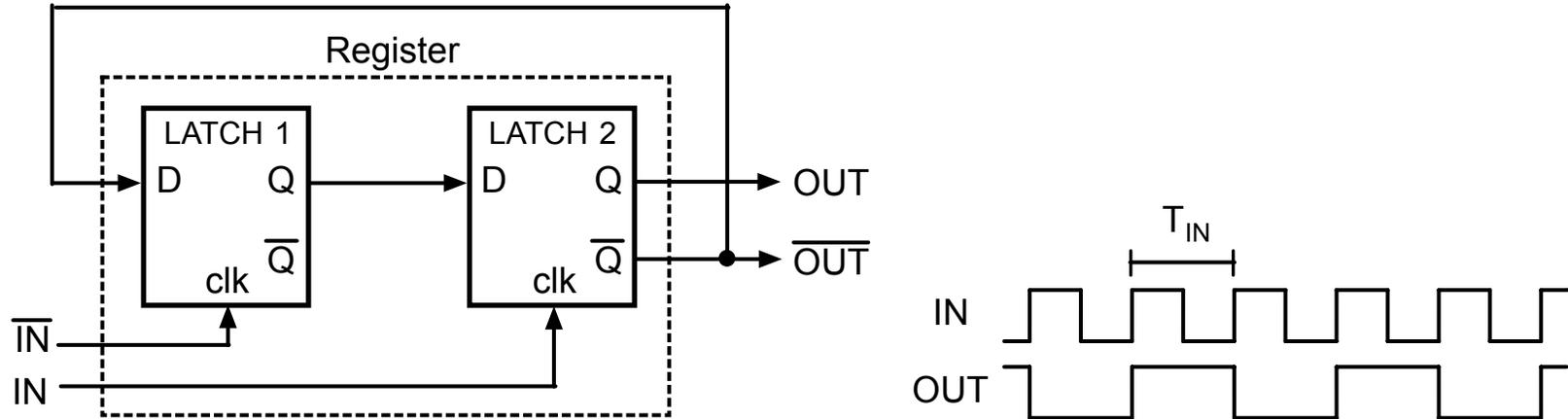

- Achieves frequency division by clocking two latches (i.e., a register) in negative feedback
- Latches may be implemented in various ways according to speed/power requirements

Divide-by-2 Using a TSPC register

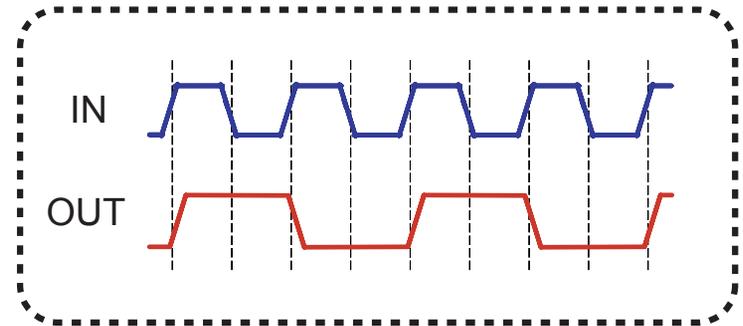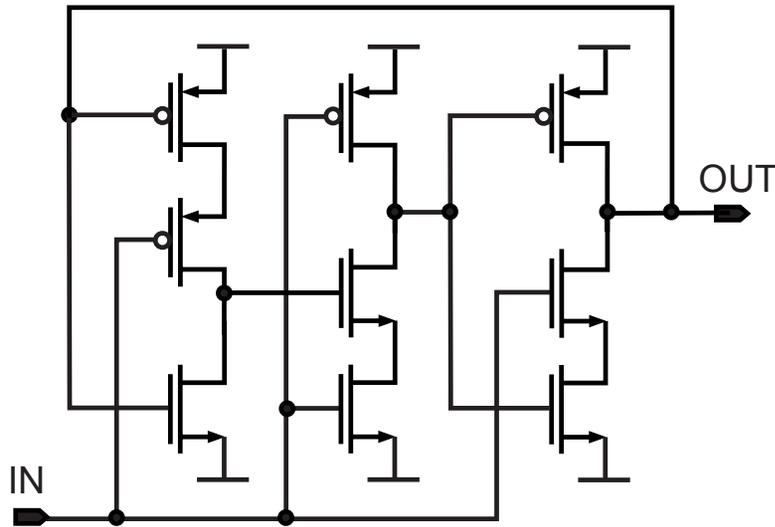



■ Advantages

- Reasonably fast, compact size
- No static power dissipation, differential clock not required

■ Disadvantages


- Slowed down by stacked PMOS, signals goes through three gates per cycle
- Requires full swing input clock signal

Divide-by-2 Using Razavi's Topology

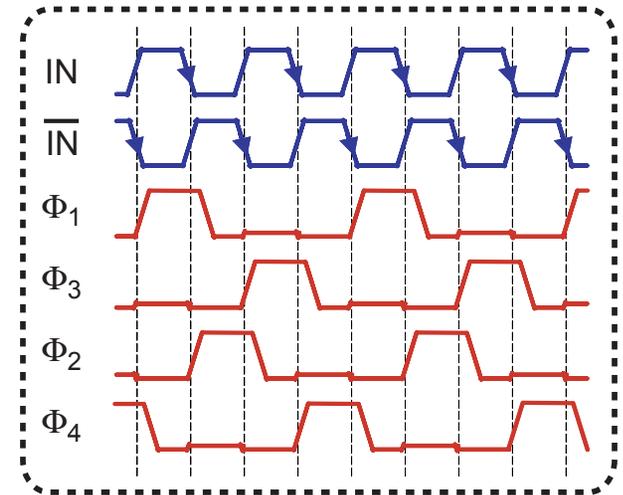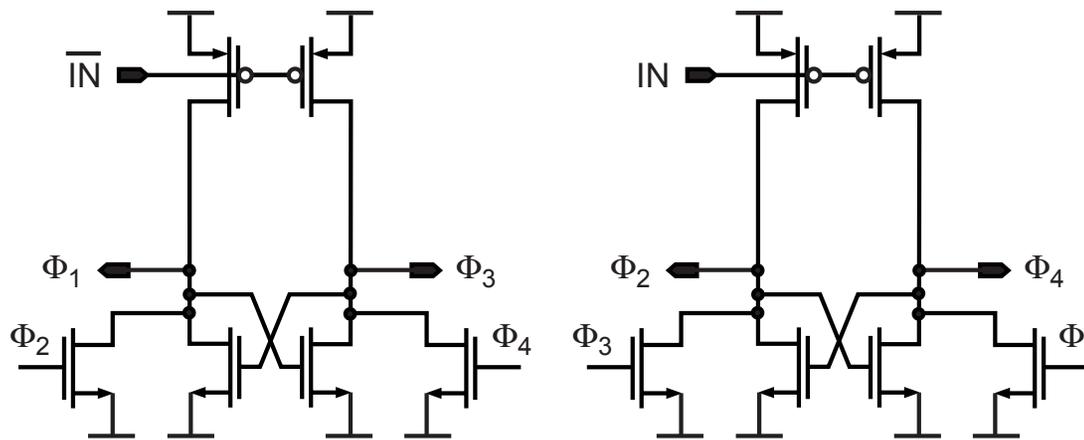

- **Faster topology than TSPC approach**
- **See B. Razavi et. al., “Design of High Speed, Low Power Frequency Dividers and Phase-Locked Loops in Deep Submicron CMOS”, JSSC, Feb 1995, pp 101-109**

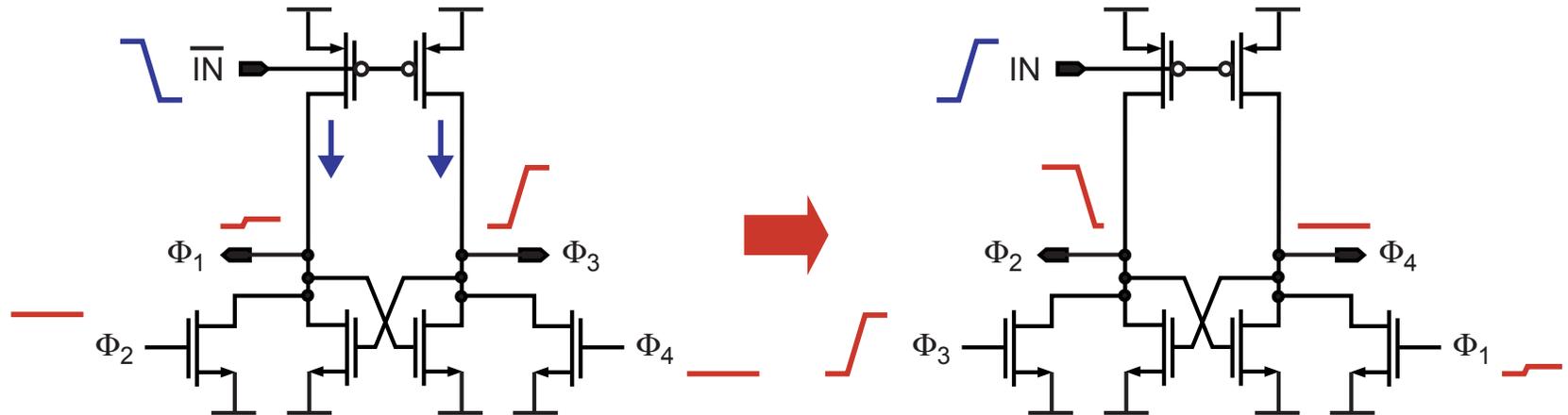Explanation of Razavi Divider Operation (Part 1)




■ Left latch:

- Clock drives current from PMOS devices of a given latch onto the NMOS cross-coupled pair
- Latch output voltage rises asymmetrically according to voltage setting on gates of outside NMOS devices

■ Right latch:

- Outside NMOS devices discharge the latch output voltage as the left latch output voltage rises

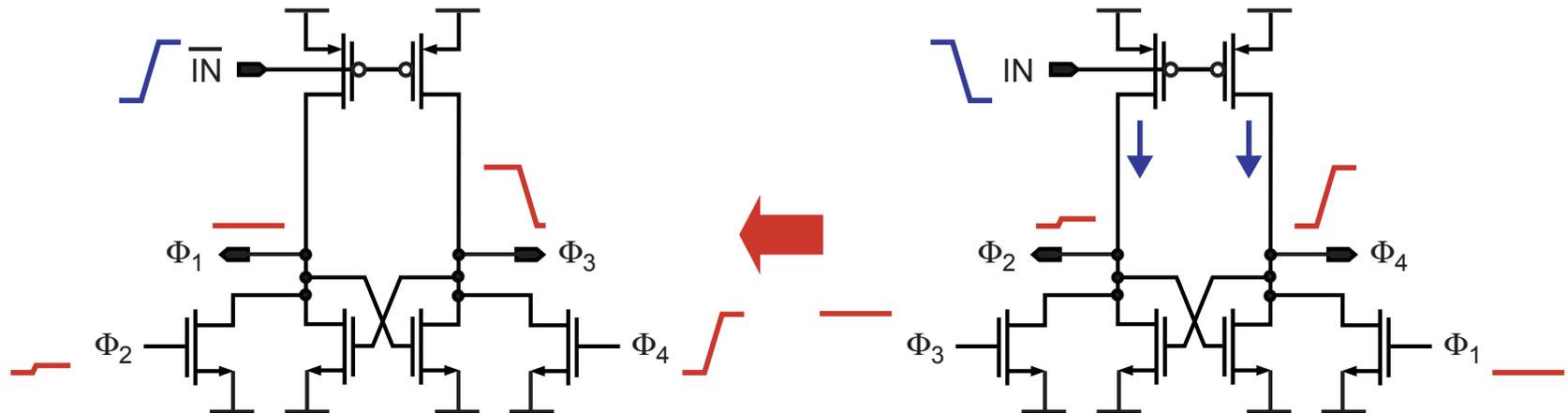Explanation of Razavi Divider Operation (Part 2)




■ Right latch:

- Clock drives current from PMOS devices of a given latch onto the NMOS cross-coupled pair
- Latch output voltage rises asymmetrically according to voltage setting on gates of outside NMOS devices

■ Left latch:



- Outside NMOS devices discharge the latch output voltage as the left latch output voltage rises

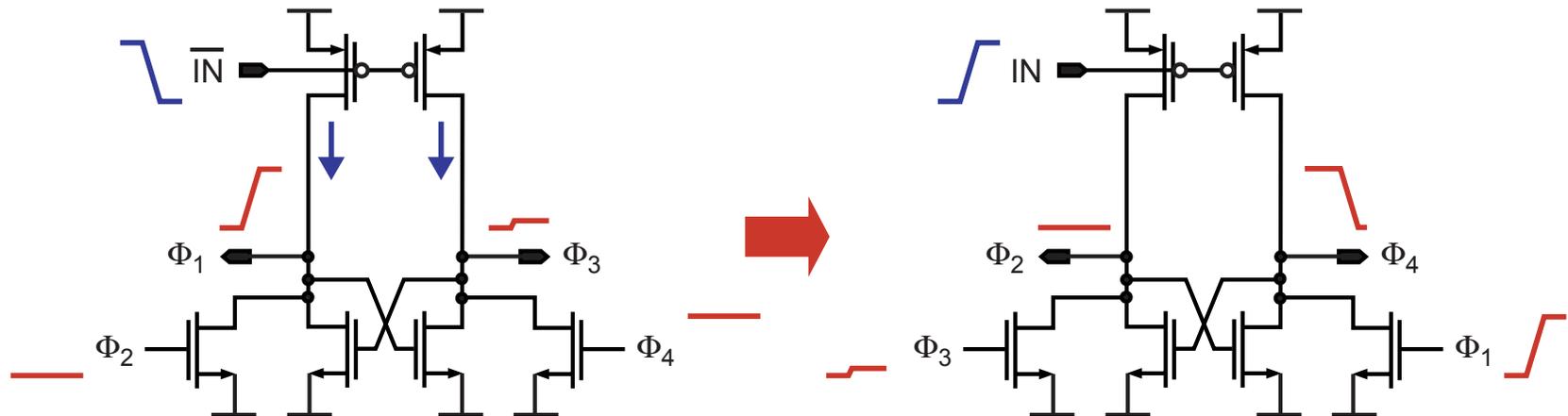Explanation of Razavi Divider Operation (Part 3)



- **Process starts over again with current being driven into left latch**
 - Voltage polarity at the output of the latch has now flipped

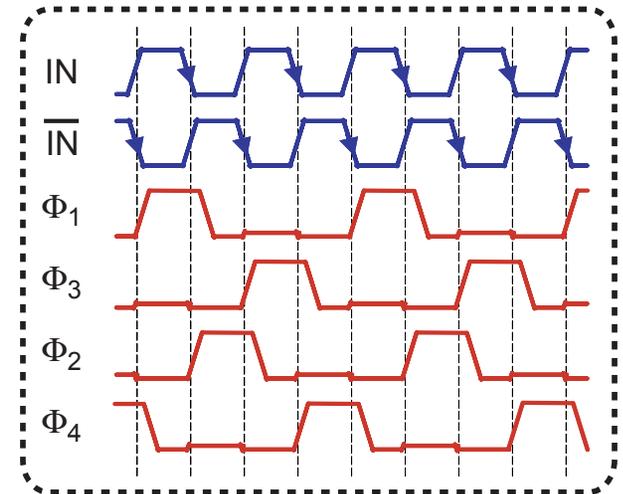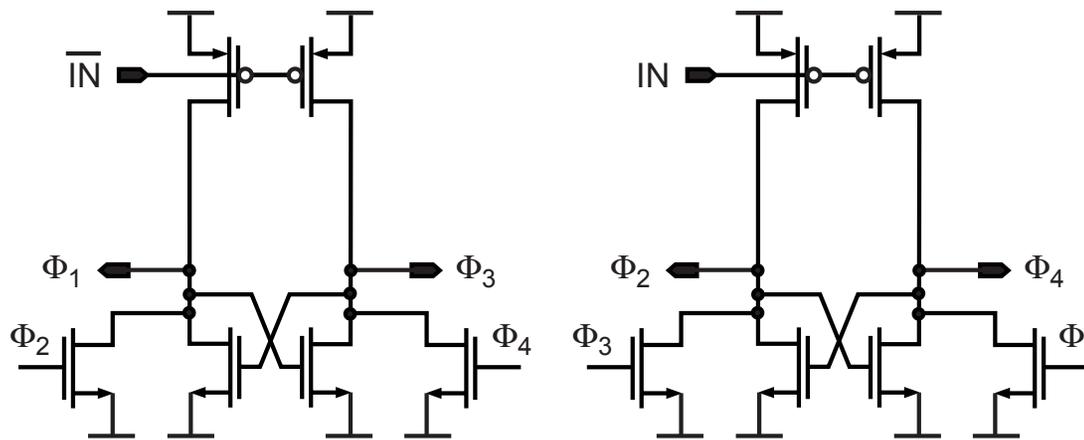Advantages and Disadvantages of Razavi Topology



Advantages

- Fast – no stacked PMOS, signal goes through only two gates per cycle


Disadvantages

- Static power
- Full swing, differential input clock signal required

- Note: quarter period duty cycle can be turned into fifty percent duty cycle with OR gates after the divider


- See my thesis at <http://www-mtl.mit.edu/~perrott>

Divide-by-2 Using Wang Topology

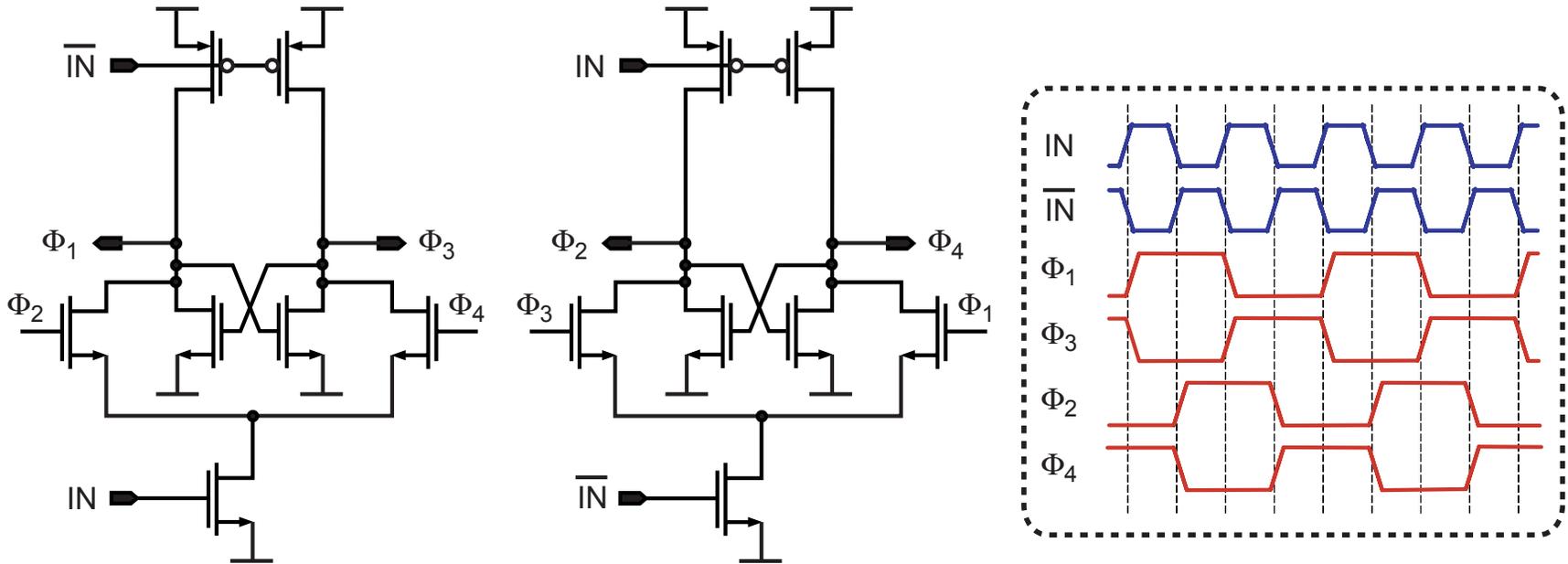

- **Claims to be faster than Razavi topology**
 - Chief difference is addition of NMOS clock devices and different scaling of upper PMOS devices
- **See HongMo Wang, “A 1.8 V 3 mW 16.8 GHz Frequency Divider in 0.25 μ m CMOS”, ISSCC 2000, pp 196-197**

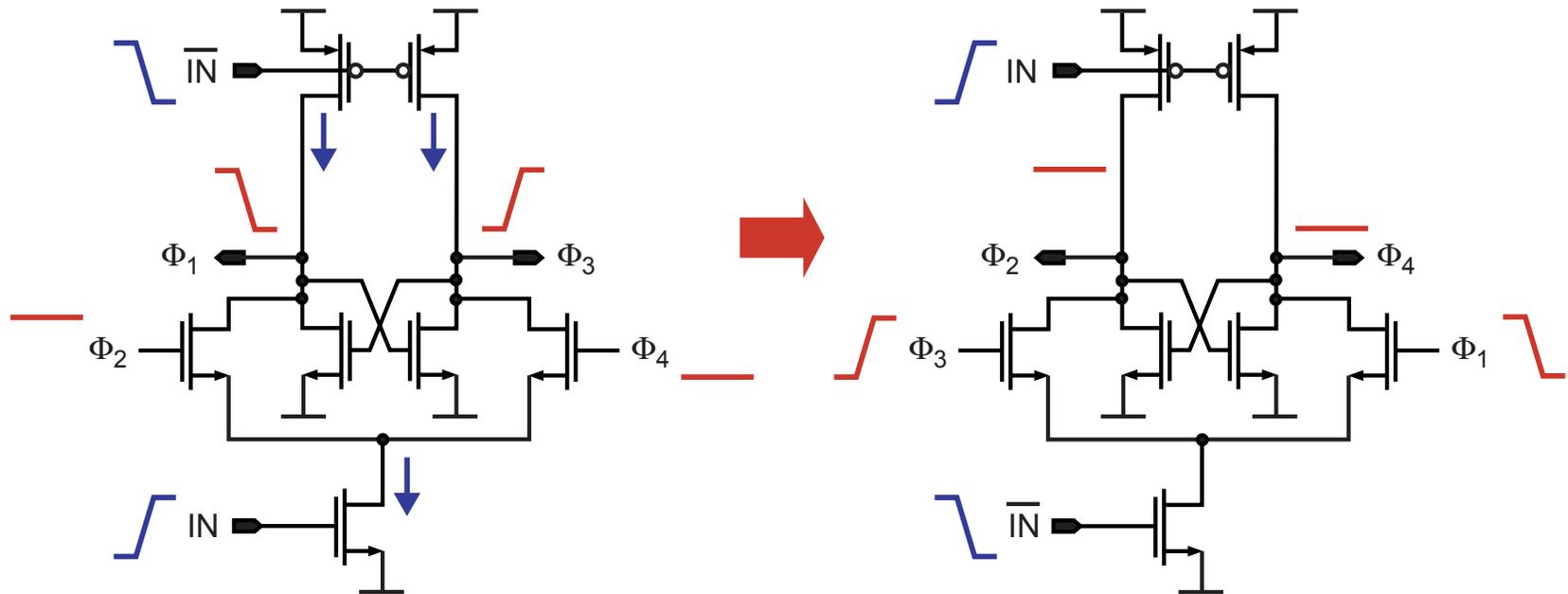Explanation of Wang Topology Operation (Part 1)




■ Left latch

- Current driven into latch and output voltage responds similar to Razavi architecture

■ Right latch


- Different than Razavi architecture in that latch output voltage is *not* discharged due to presence of extra NMOS

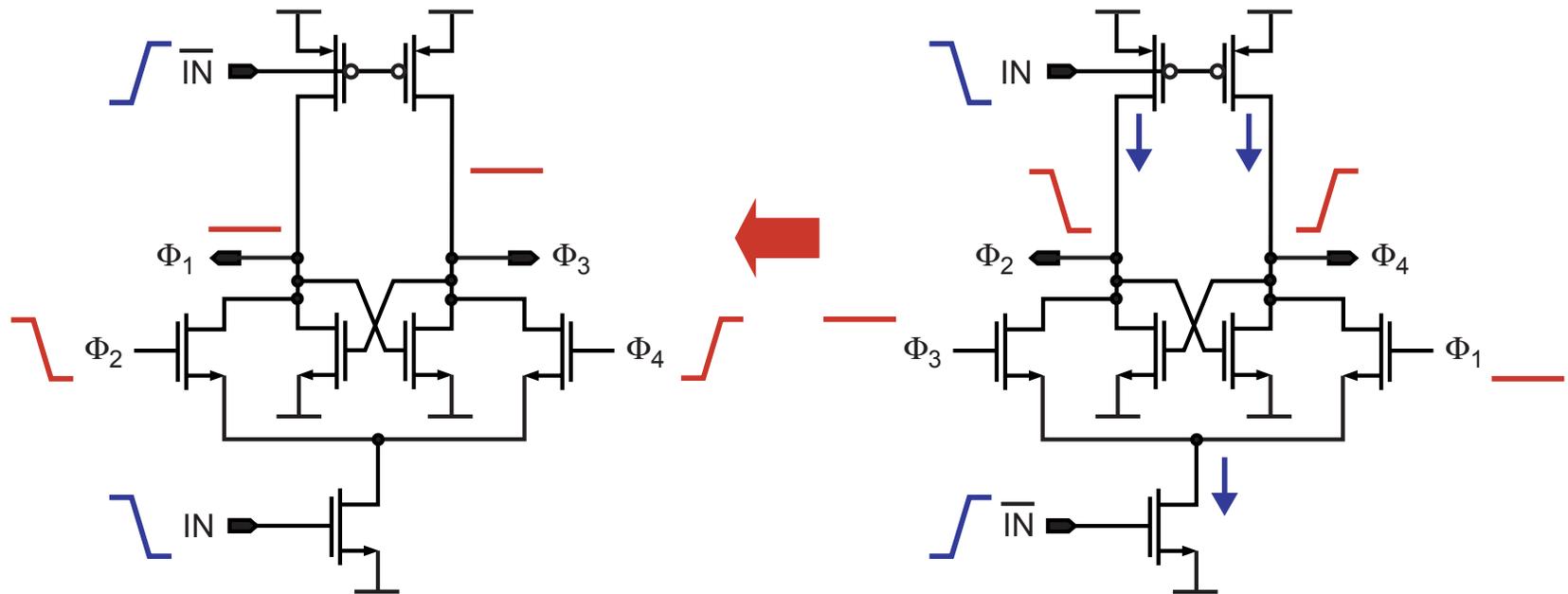Explanation of Wang Topology Operation (Part 2)



- Same process repeats on the right side
 - The left side maintains its voltages due to presence of NMOS device

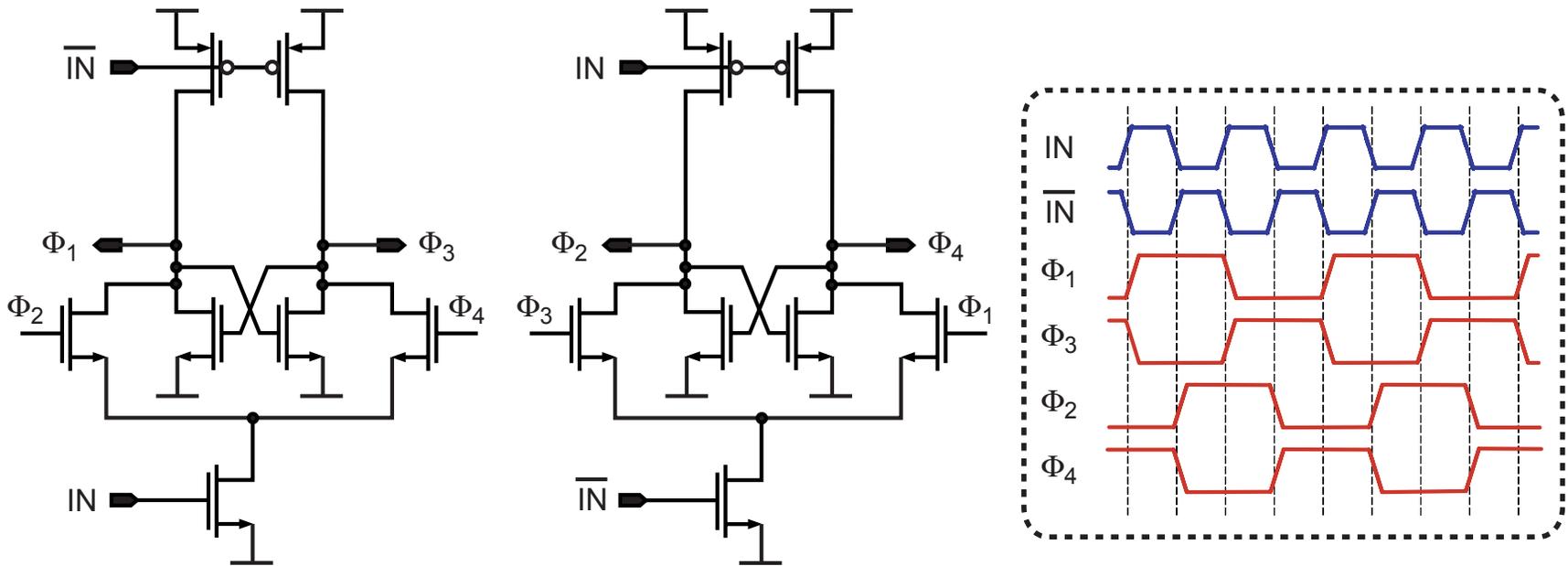Advantages and Disadvantages of Wang Topology




■ Advantages

- Fast – no stacked PMOS, signal goes through only two gates per cycle

■ Disadvantages


- Static power
- Full swing, differential input clock signal required

Divide-by-2 Using SCL Latches

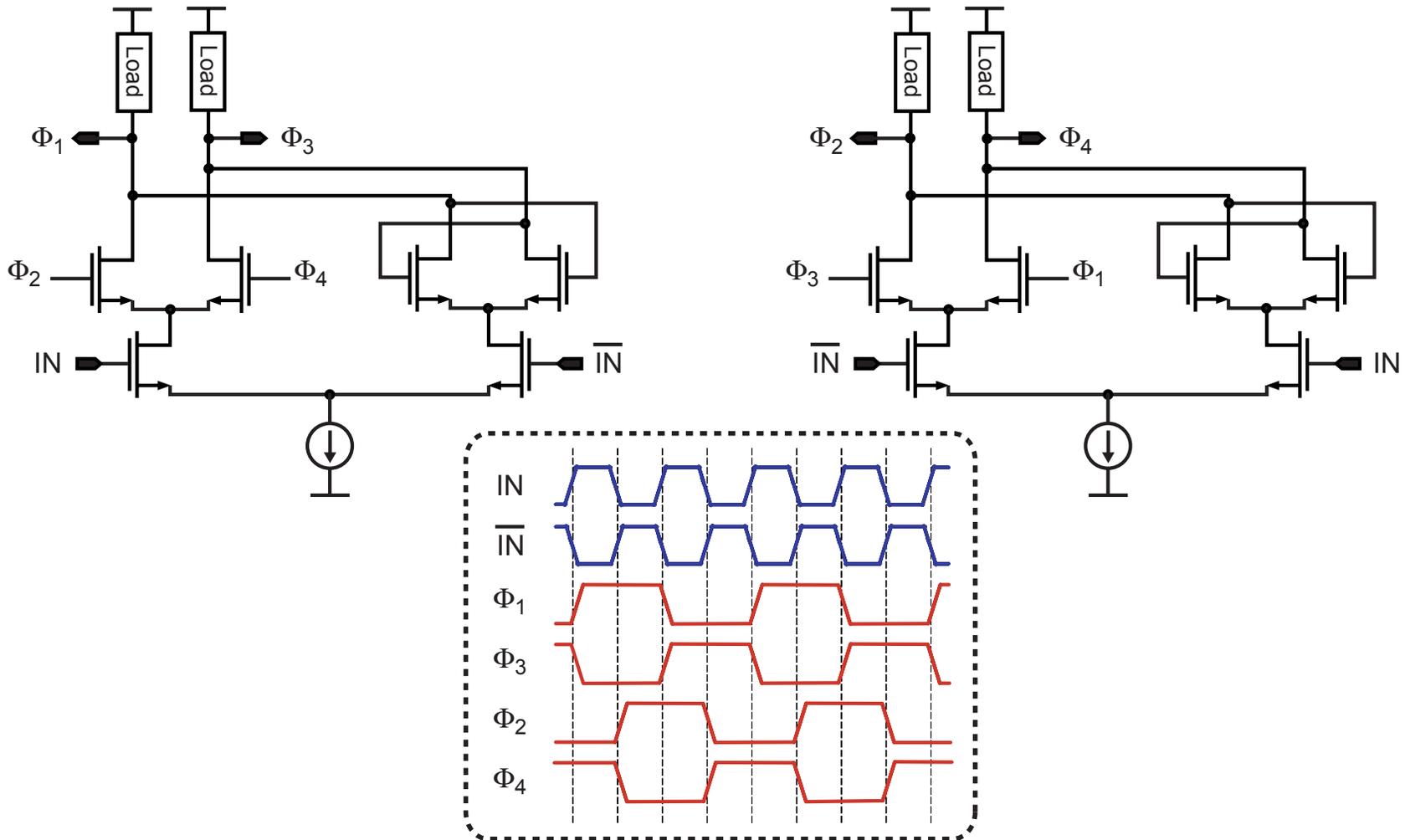

- Fastest structure uses resistors for load

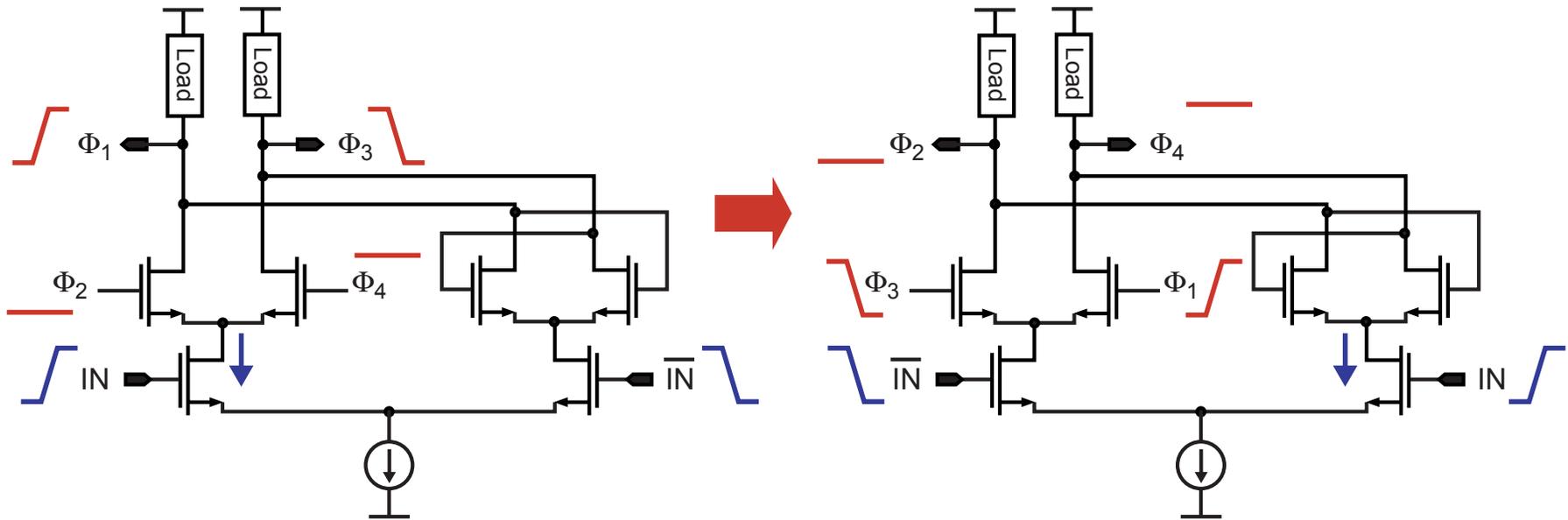Explanation of SCL Topology Operation (Part 1)




■ Left latch

- Current directed into differential amp portion of latch
 - Latch output follows input from right latch

■ Right latch

- Current directed into cross-coupled pair portion of latch
 - Latch output is held

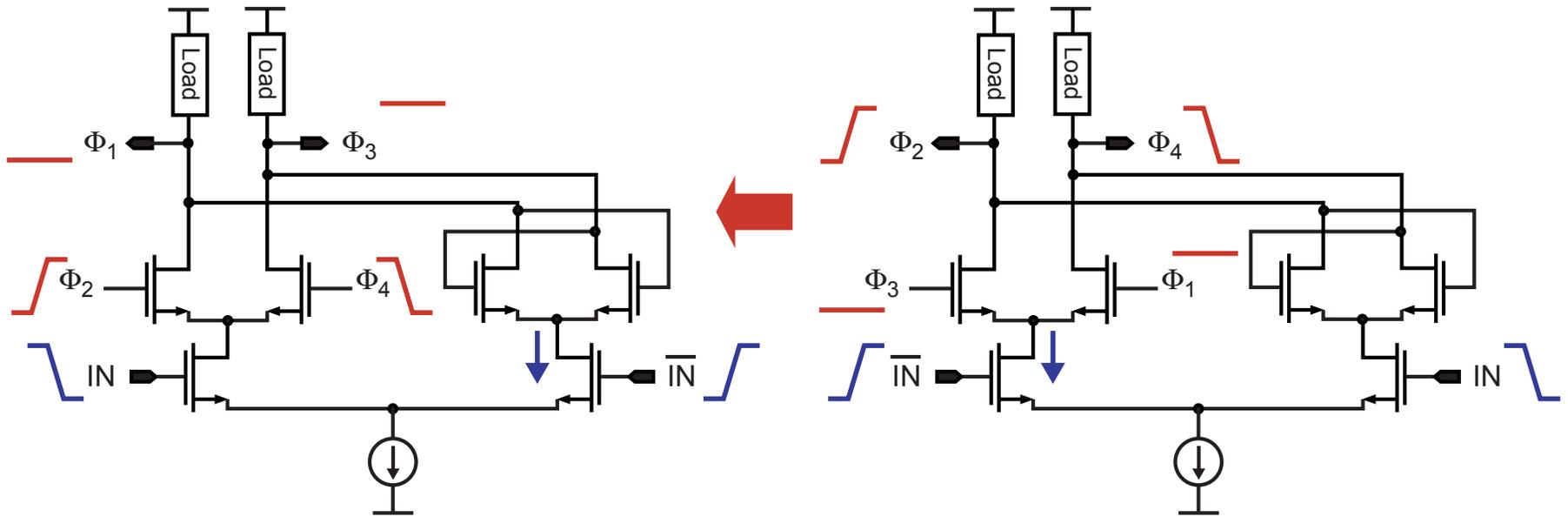Explanation of SCL Topology Operation (Part 2)




- **Left latch**

- **Current is directed into cross-coupled pair**
 - Latch output voltage retained

- **Right latch**

- **Current is directed into differential amp**
 - Latch output voltage follows input from left latch

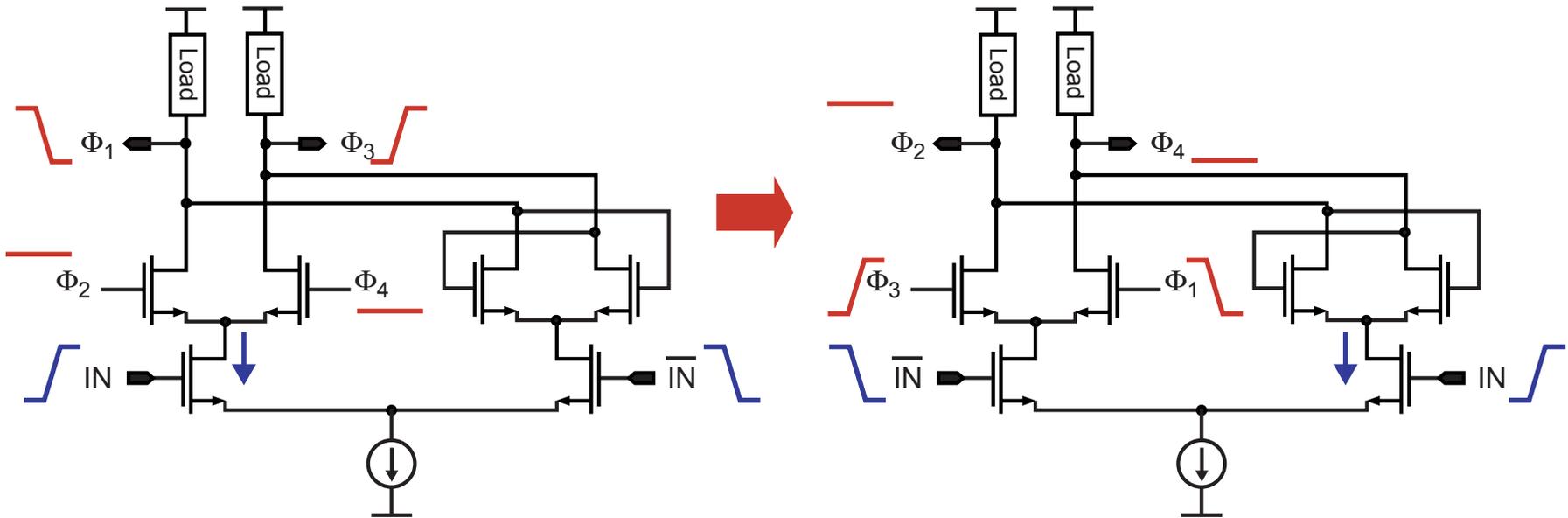Explanation of SCL Topology Operation (Part 3)



- Same process repeats on left side
 - Voltage polarity is now flipped

Advantages and Disadvantages of SCL Topology

■ **Advantages**


- **Very fast – no PMOS at all, signal goes through only two gates per cycle**
- **Smaller input swing for input clock than previous approaches**
 - Much easier to satisfy at high frequencies

■ **Disadvantages**

- **Static power**
- **Differential signals required**
- **Large area compared to previous approaches**
- **Biasing sources required**


- **Note: additional speedup can be obtained by adding using inductor peaking as described for amplifiers in Lecture 6**

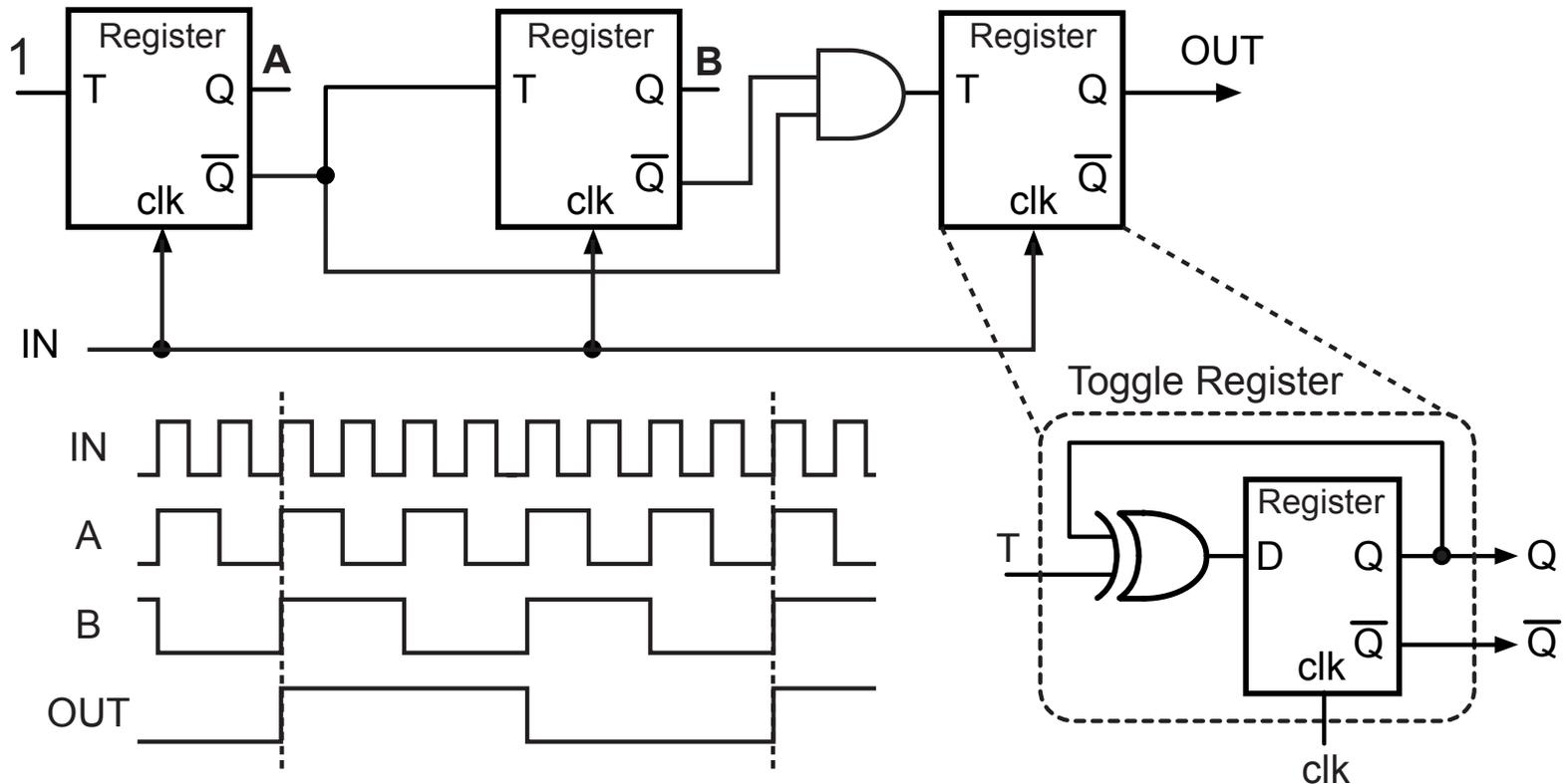Creating Higher Divide Values (Synchronous Approach)




- **Cascades toggle registers and logic to perform division**
 - **Advantage: low jitter (explained shortly)**
 - **Problems: high power (all registers run at high frequency), high loading on clock (IN signal drives *all* registers)**

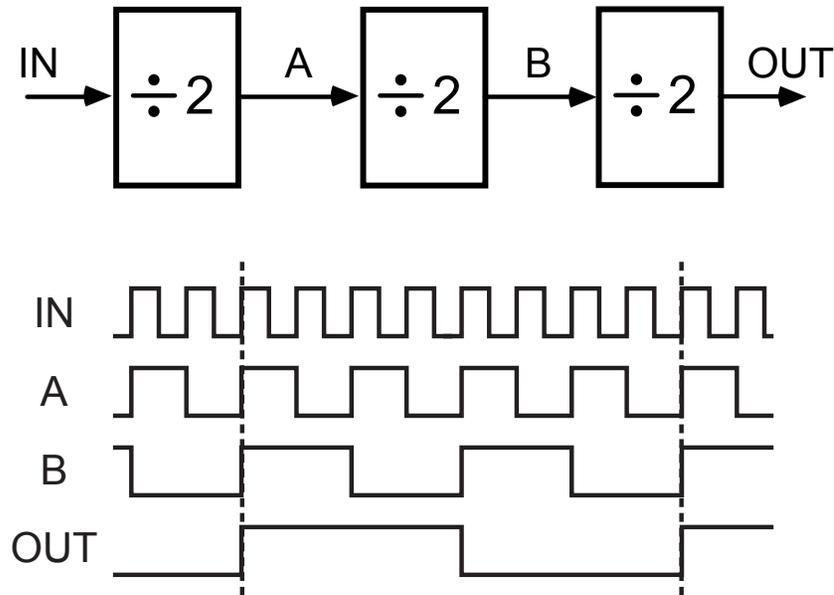Creating Higher Divide Values (Asynchronous Approach)




- Higher division achieved by simply cascading divide-by-2 stages
- Advantages over synchronous approach
 - Lower power: each stage runs at a lower frequency, allowing power to be correspondingly reduced
 - Less loading of input: IN signal only drives first stage
- Disadvantage: jitter is larger

Jitter in Asynchronous Designs

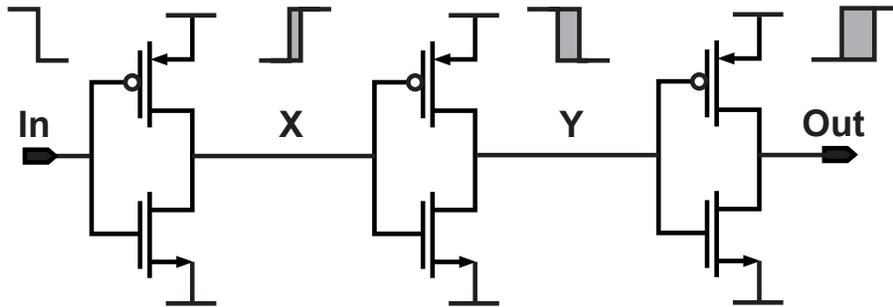


- Each logic stage adds jitter to its output
 - Jitter accumulates as it passes through more and more gates

Jitter in Synchronous Designs

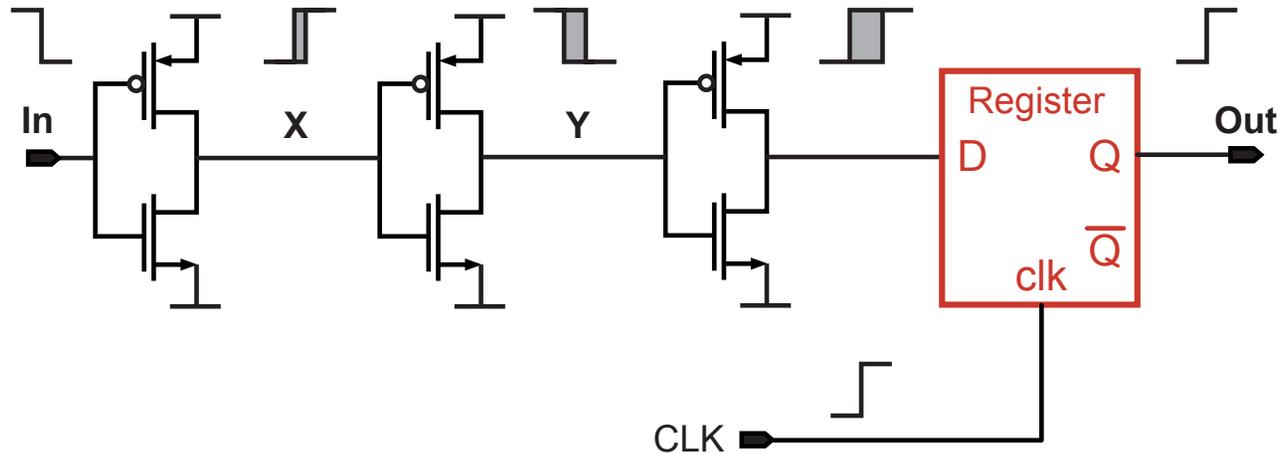


- Transition time of register output is set by the clock, not the incoming data input
 - Synchronous circuits have jitter performance corresponding to their clock
 - Jitter does not accumulate as signal travels through synchronous stages

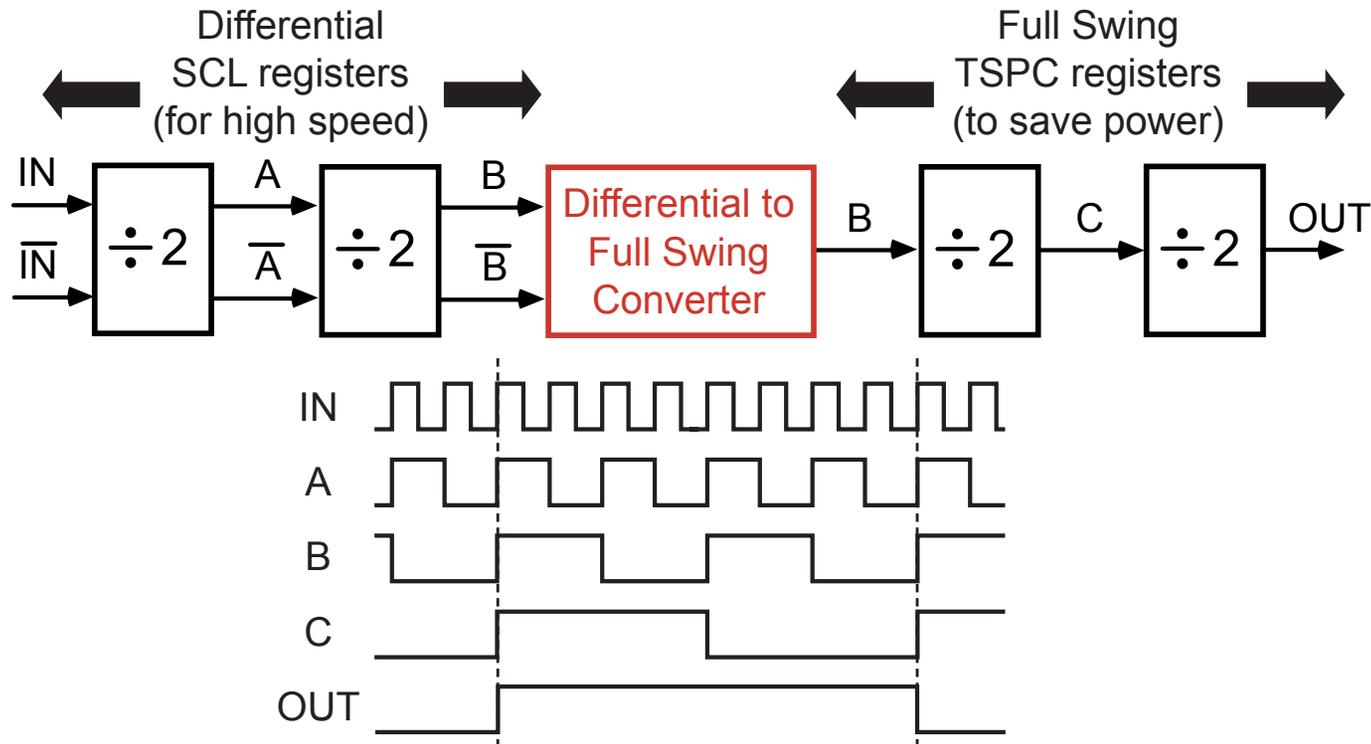High Speed, Low Power Asynchronous Dividers




- Highest speed achieved with differential SCL registers
 - Static power consumption not an issue for high speed sections, but wasteful in low speed sections
- Lower power achieved by using full swing logic for low speed sections

Differential to Full Swing Converter

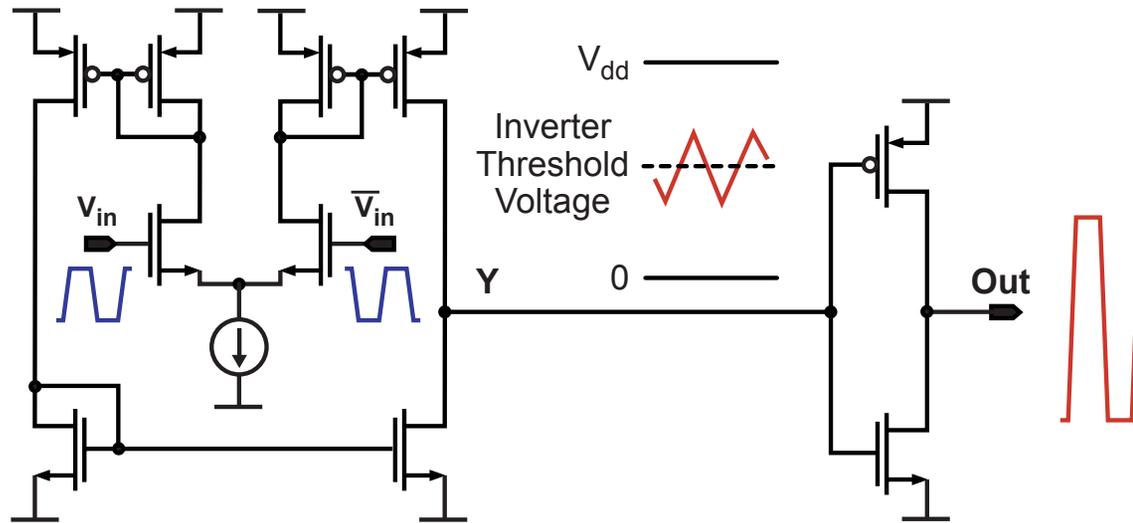


- Use an opamp style circuit to translate differential input voltage to a single-ended output
- Use an inverter to amplify the single-ended output to full swing level

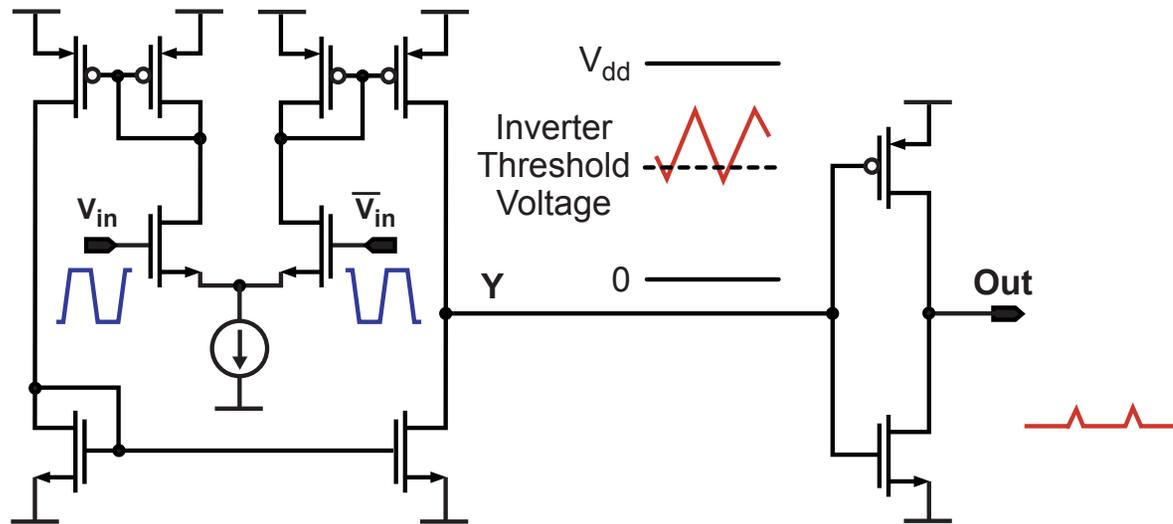Issue: Architecture Very Sensitive to DC Offset




- Opamp style circuit has very high DC gain from V_{in} to node Y
- DC offset will cause signal to rise above or fall below inverter threshold
 - Output signal rails rather than pulsing

Use Resistor Feedback to Reduce DC Gain

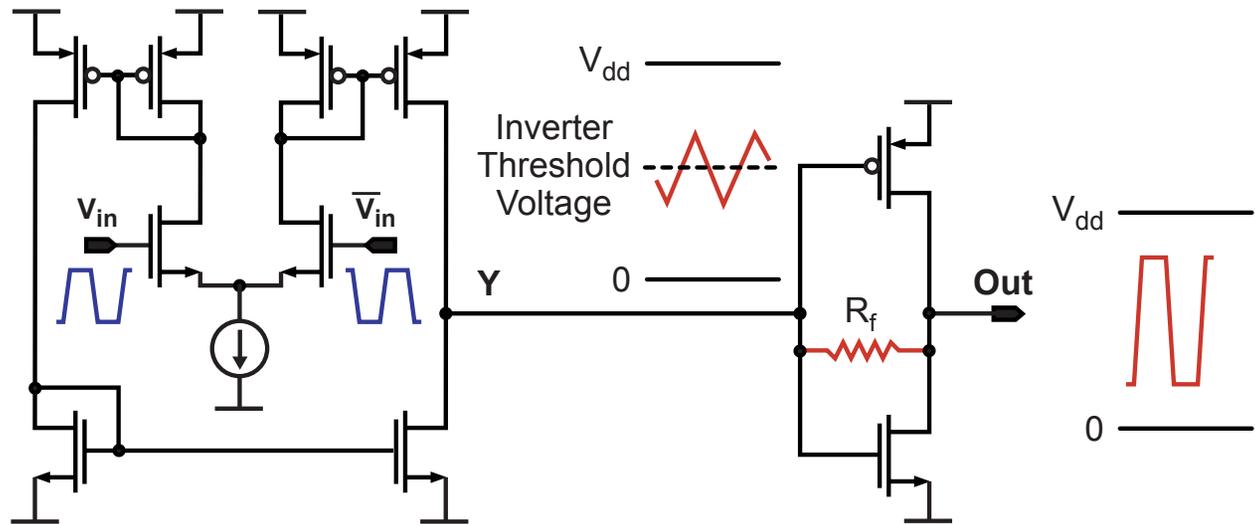


- **Idea: create transresistance amplifier rather than voltage amplifier out of inverter by using feedback resistor**
 - Presents a low impedance to node Y
 - Current from opamp style circuit is shunted through resistor
 - DC offset at input shifts output waveform slightly, but not node Y (to first order)
- **Circuit is robust against DC offset!**

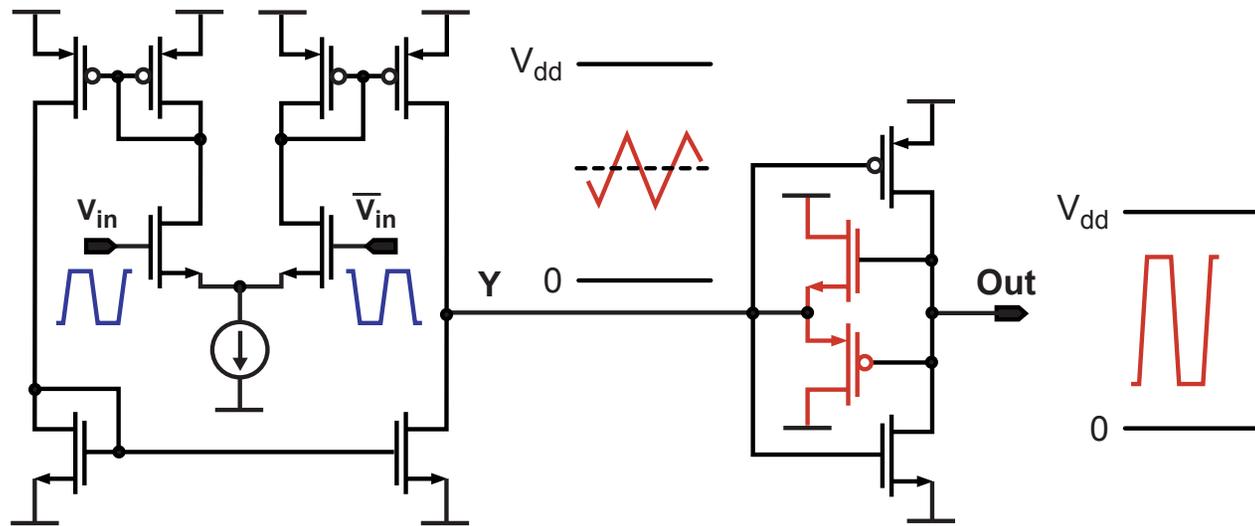Alternate Implementation of Inverter Feedback




- **Nonlinear feedback using MOS devices can be used in place of resistor**
 - Smaller area than resistor implementation
- **Analysis done by examining impact of feedback when output is high or low**

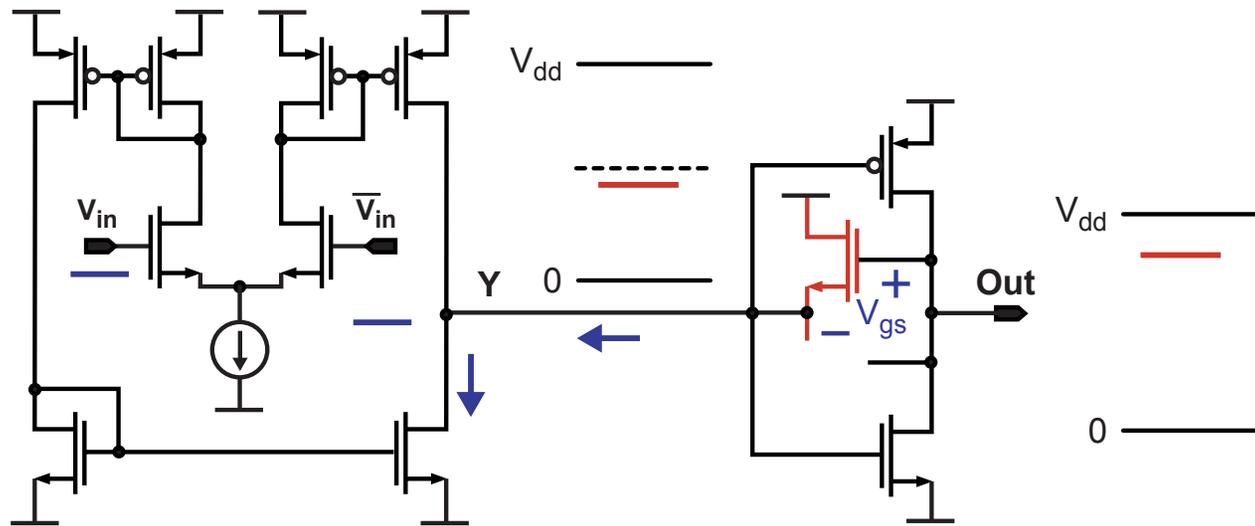Impact of Nonlinear Feedback When Output is High




- Corresponds to case where current flows into node Y
 - NMOS device acts like source follower
 - PMOS device is shut off
- Output is approximately set to V_{gs} of NMOS feedback device away from inverter threshold voltage
 - Inverter input is set to a value that yields that output voltage
 - High DC gain of inverter insures it is close to inverter threshold

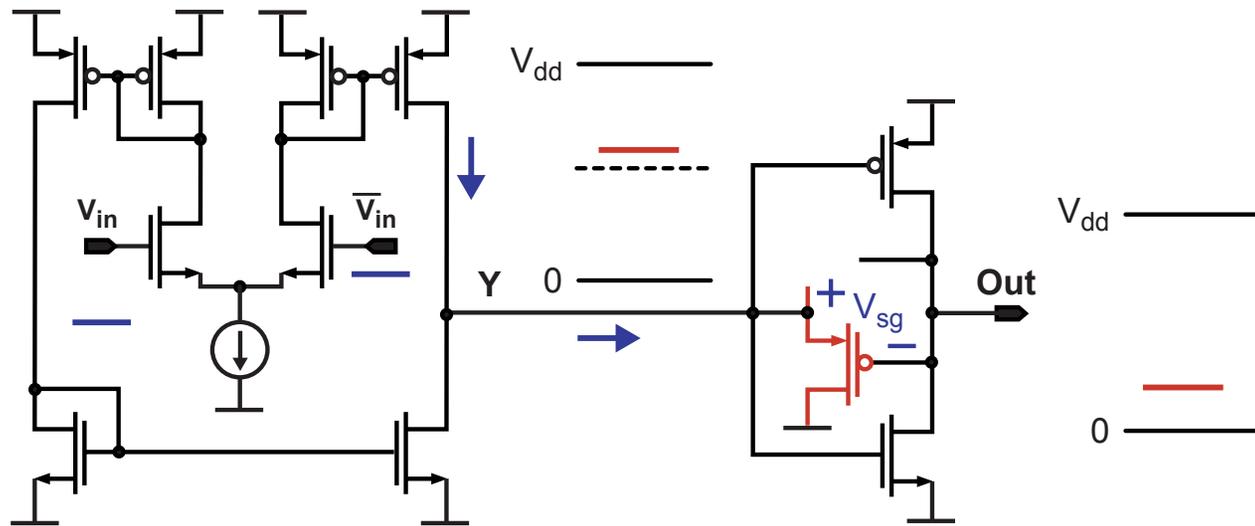Impact of Nonlinear Feedback When Output is Low





- Corresponds to case where current flows out of node Y
 - NMOS device is shut off
 - PMOS device acts like source follower
- Output is approximately set to V_{gs} of PMOS feedback device away from inverter threshold voltage
 - Inverter input is set to a value that yields that output voltage
 - High DC gain of inverter insures it is close to inverter threshold

Variable Frequency Division

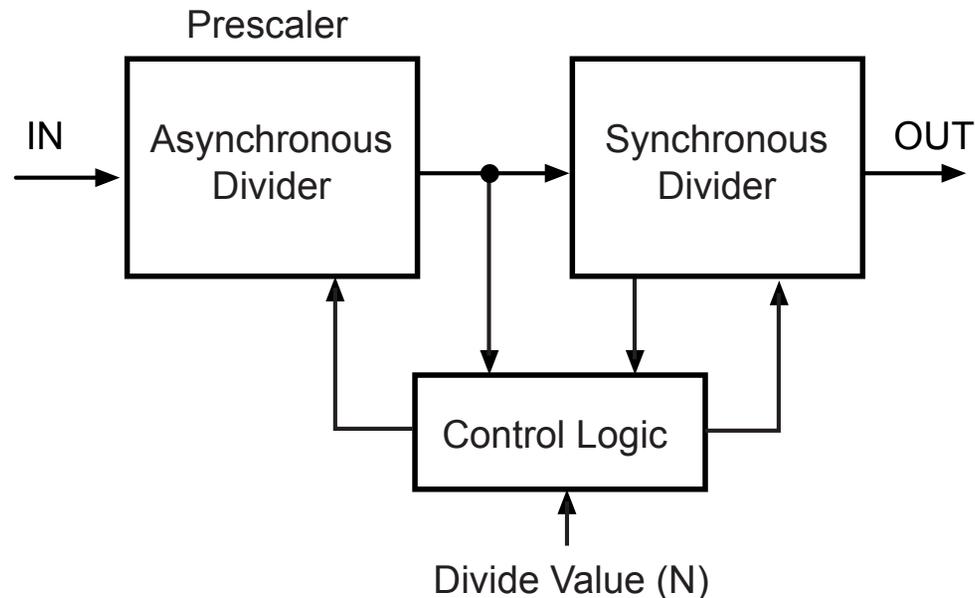


- **Classical design partitions variable divider into two sections**
 - **Asynchronous section (called a prescaler) is fast**
 - Often supports a limited range of divide values
 - **Synchronous section has no jitter accumulation and a wide range of divide values**
 - **Control logic coordinates sections to produce a wide range of divide values**

Dual Modulus Prescalers

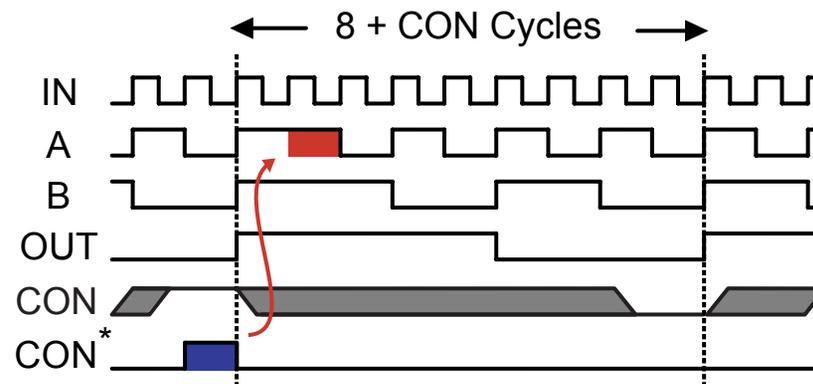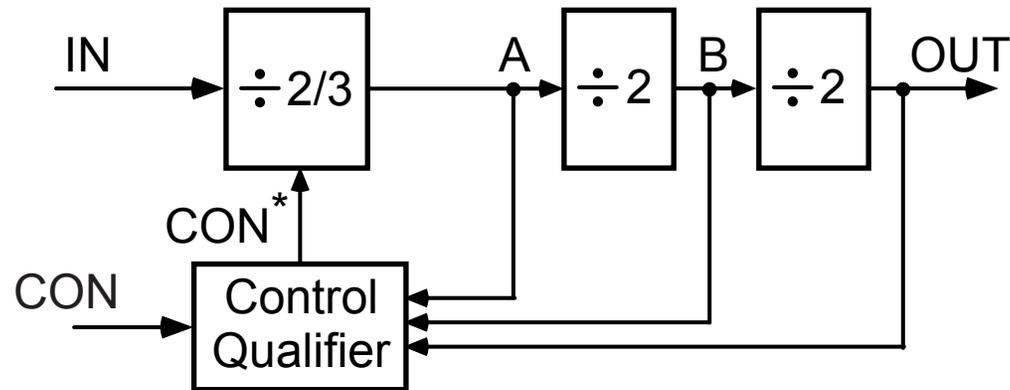


- Dual modulus design supports two divide values
 - In this case, divide-by-8 or 9 according to CON signal
- One cycle resolution achieved with front-end “2/3” divider

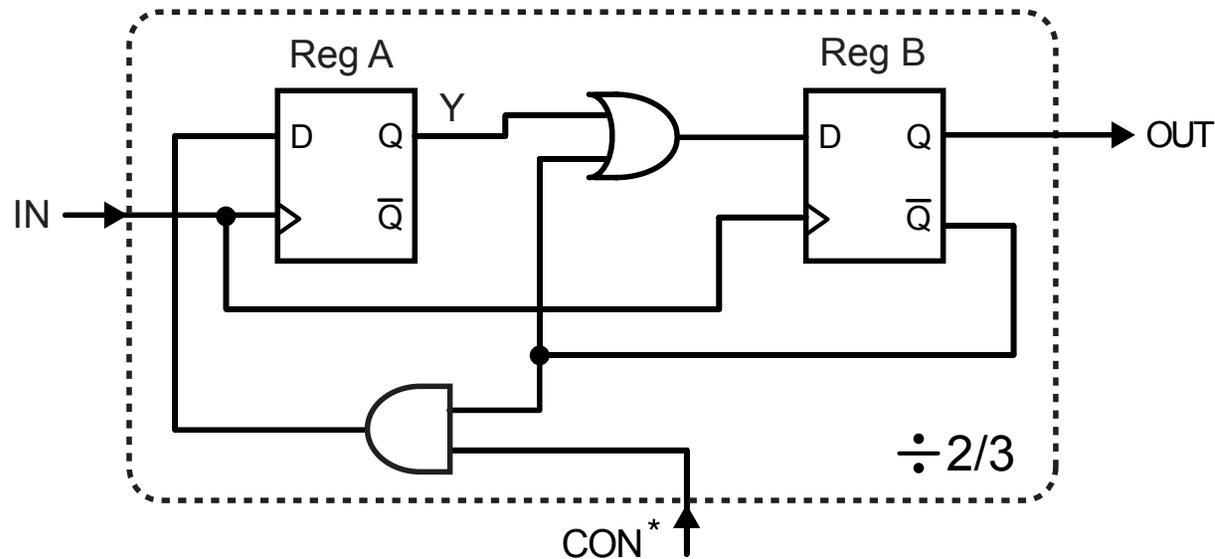Divide-by-2/3 Design (Classical Approach)




- **Normal mode of operation: $CON^* = 0 \Rightarrow Y = 0$**
 - Register B acts as divide-by-2 circuit
- **Divide-by-3 operation: $CON^* = 1 \Rightarrow Y = 1$**
 - Reg B remains high for an extra cycle
 - Causes Y to be set back to 0 \Rightarrow Reg B toggles again
 - CON^* must be set back to 0 before Reg B toggles to prevent extra pulses from being swallowed

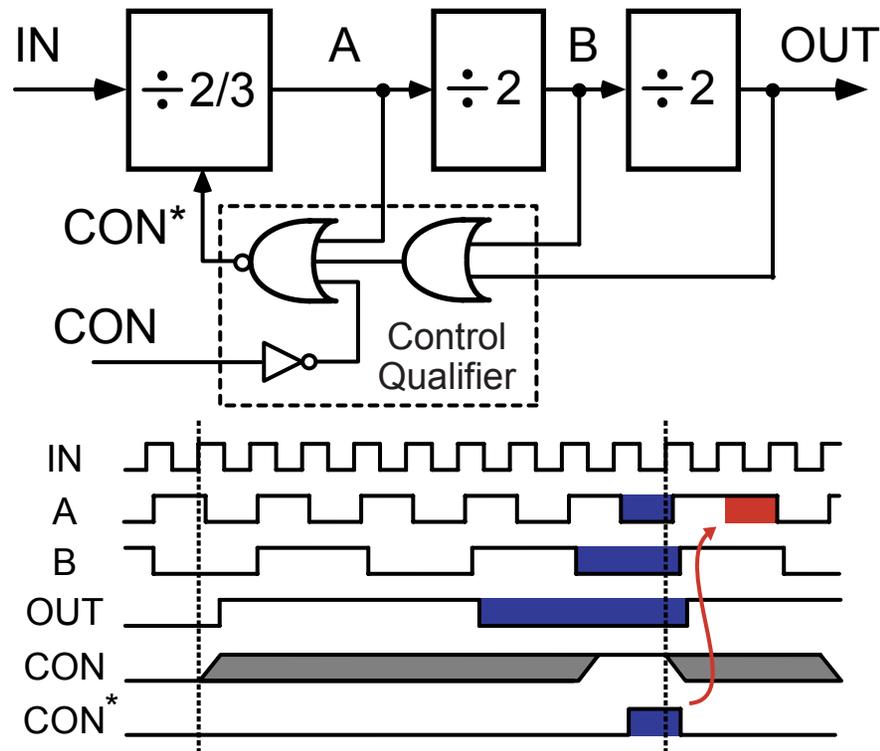Control Qualifier Design (Classical Approach)




- **Must align CON signal to first “2/3” divider stage**
 - CON signal is based on logic clocked by divider output
 - There will be skew between “2/3” divider timing and CON
- **Classical approach cleverly utilizes outputs from each section to “gate” the CON signal to “2/3” divider**

Multi-Modulus Prescalers

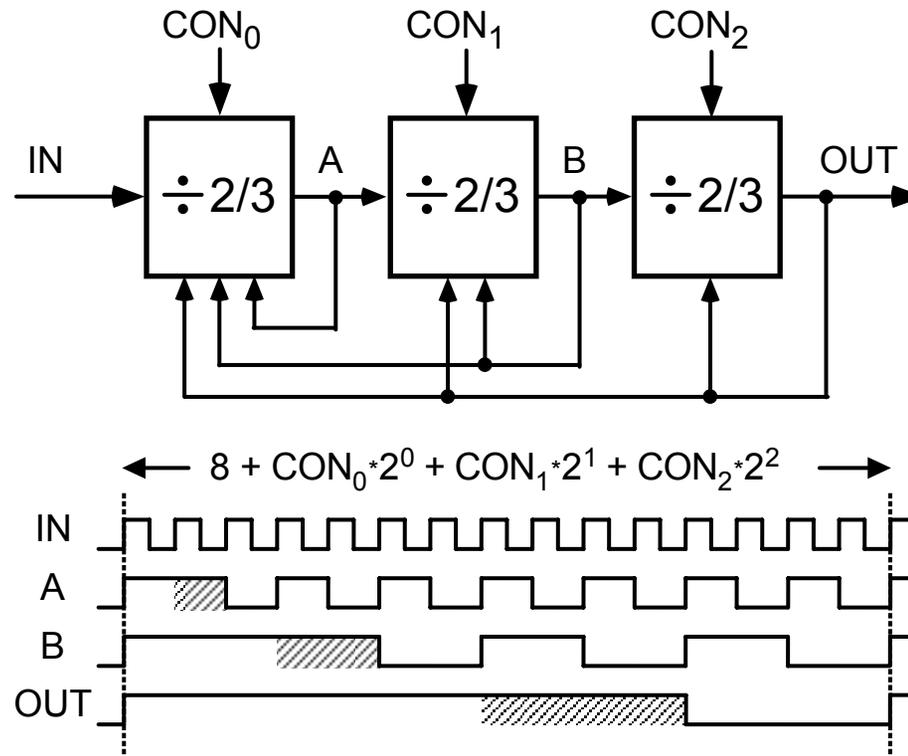


- Cascaded $2/3$ sections achieves a range of 2^n to $2^{n+1}-1$
 - Above example is 8/ ... /15 divider
- Asynchronous design allows high speed and low power operation to be achieved
 - Only negative is jitter accumulation

A More Modular Design

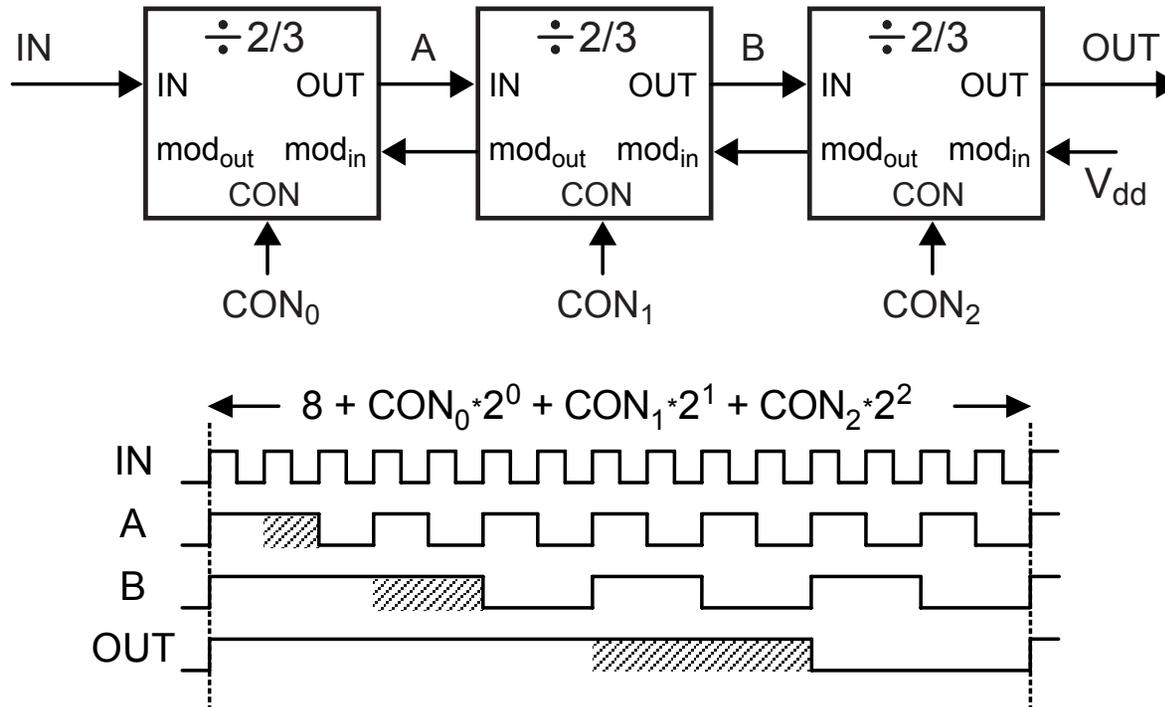


- Perform control qualification by synchronizing within each stage before passing to previous one
 - Compare to previous slide in which all outputs required for qualification of first 2/3 stage
- See Vaucher et. al., “A Family of Low-Power Truly Modular Programmable Dividers ...”, JSSC, July 2000

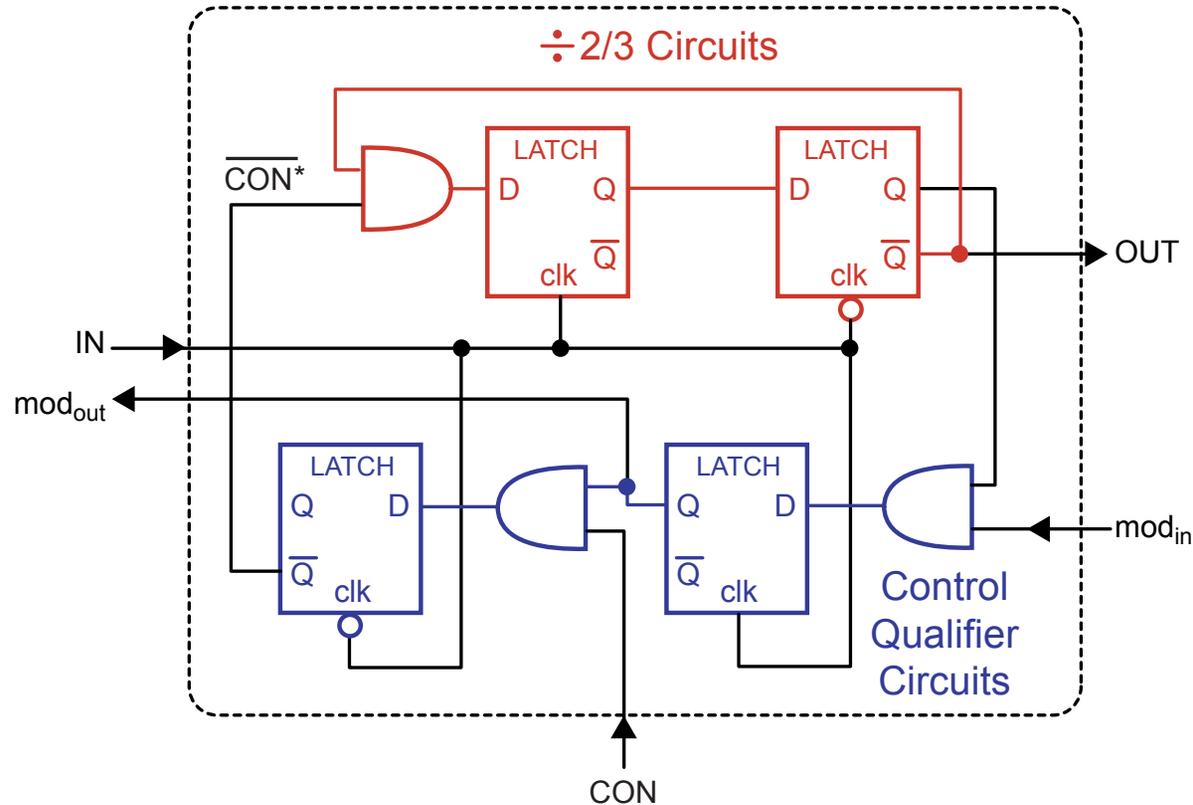Implementation of 2/3 Sections in Modular Approach



- Approach has similar complexity to classical design
 - Consists of two registers with accompanying logic gates
- Cleverly utilizes “gating” register to pass synchronized control qualifying clk signal to the previous stage

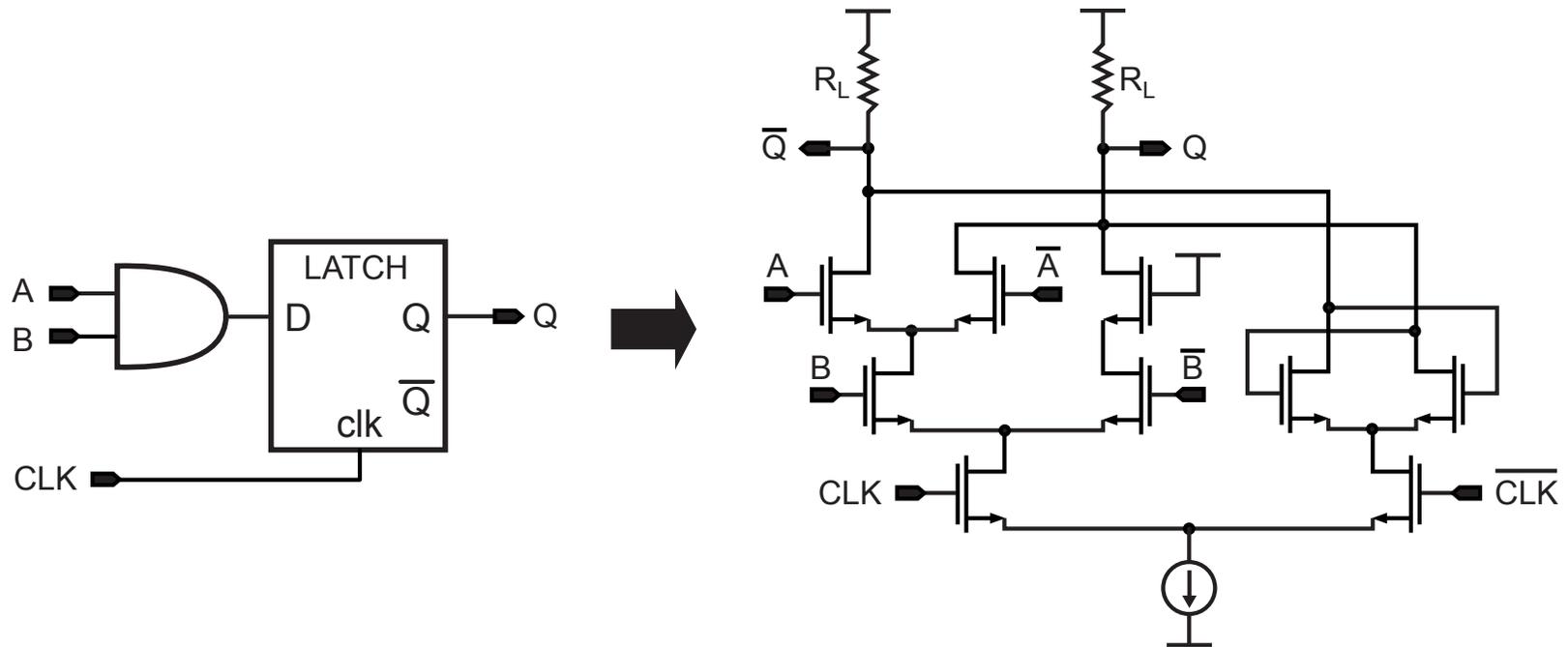
Implementation of Latch and And Gate in 2/3 Section



- Combine AND gate and latch for faster speed and lower power dissipation
- Note that all primitives in 2/3 Section on previous slide consist of this combination or just a straight latch

Can We Go Even Faster?


Speed Limitations of Divide-by-2 Circuit

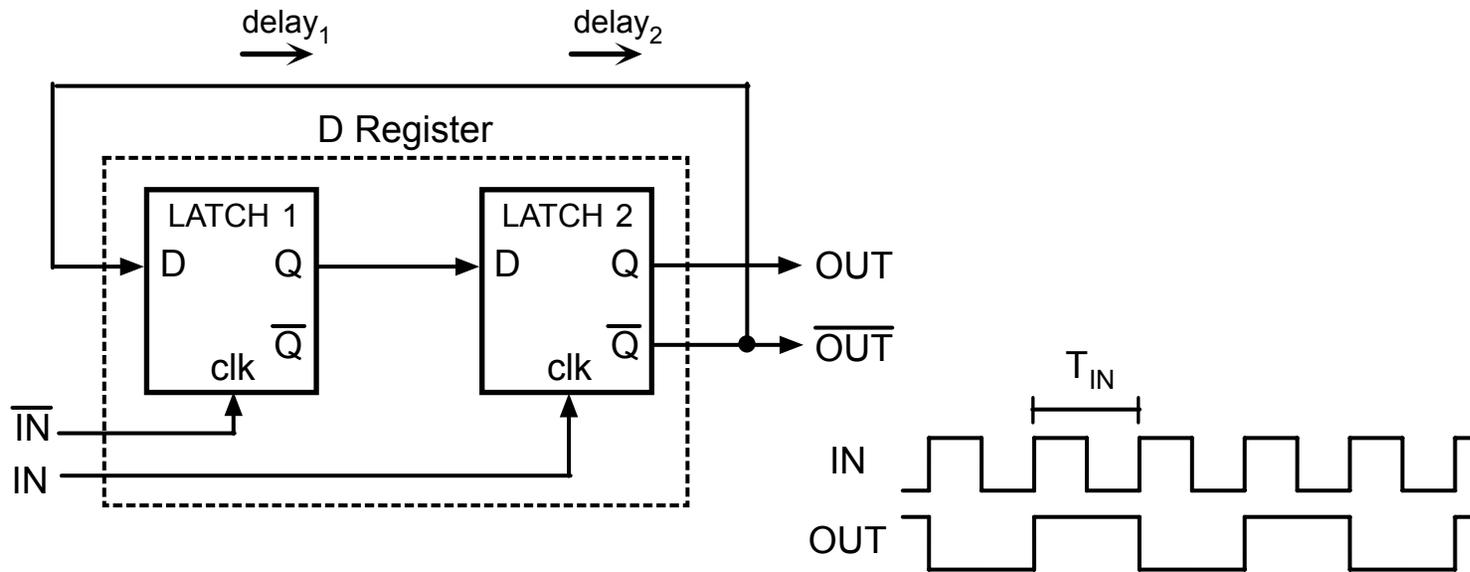

- Maximum speed limited only by propagation delay ($delay_1$, $delay_2$) of latches and setup time of latches (T_s)

$$\frac{T_{IN}}{2} > delay_1 + T_s, \quad \frac{T_{IN}}{2} > delay_2 + T_s$$

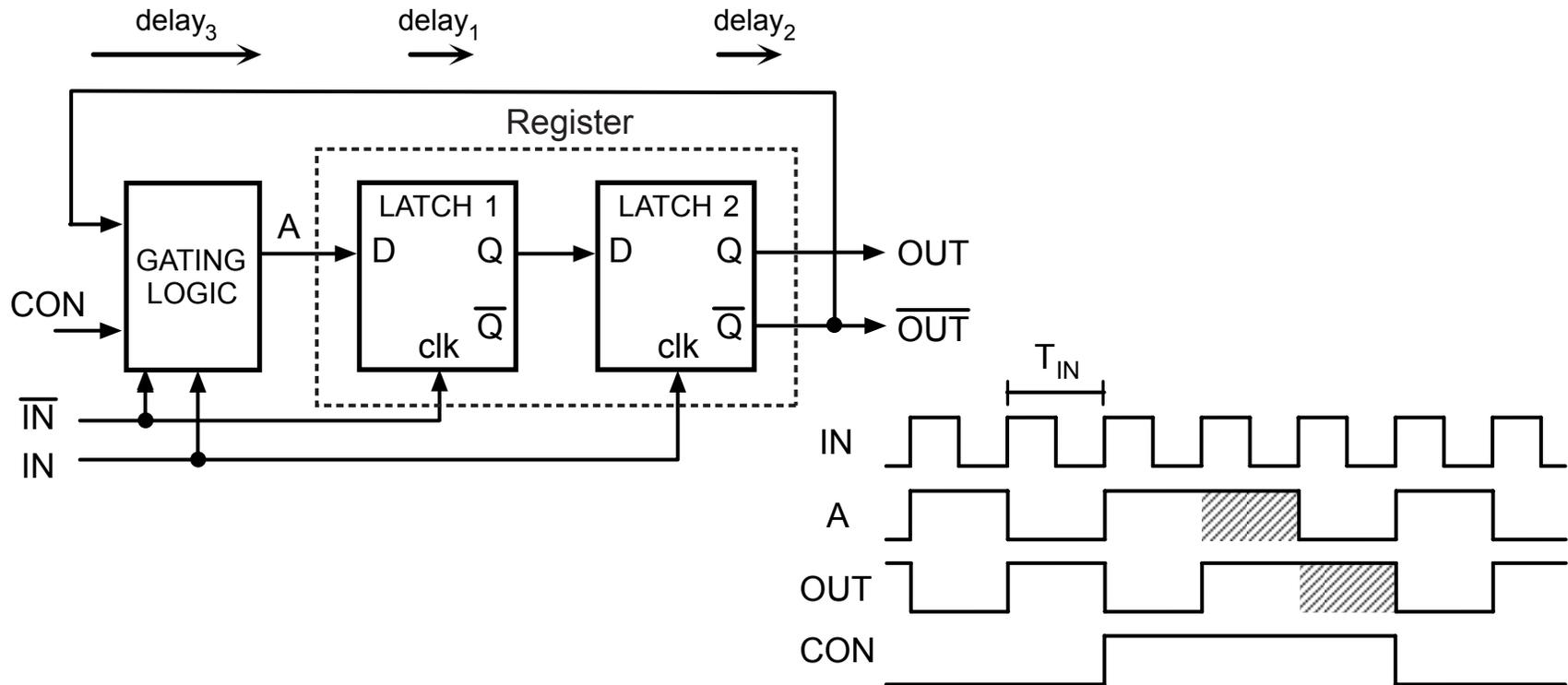Speed Limitations of Gated Divide-by-2/3 Circuit





- Maximum speed limited by latch *plus* gating logic

$$\frac{T_{IN}}{2} > delay_2 + delay_3 + T_s$$

- Gated divide-by-2/3 *fundamentally* slower than divide-by-2

Divide-by-2/3 Using Phase Shifting

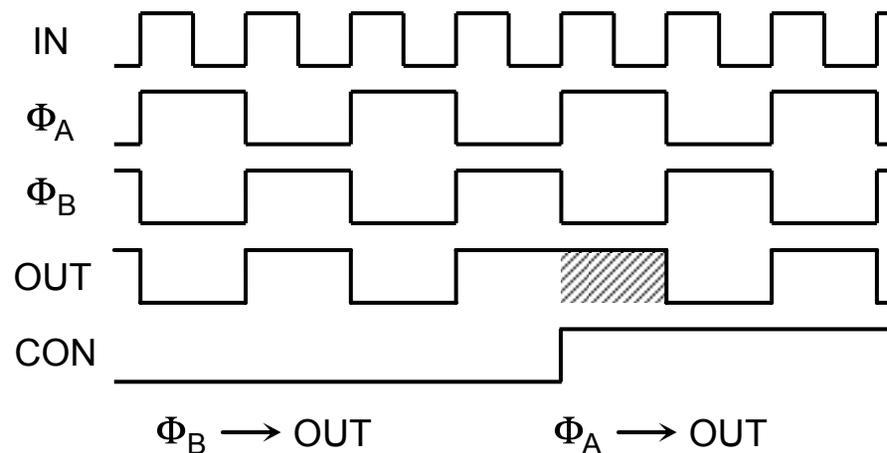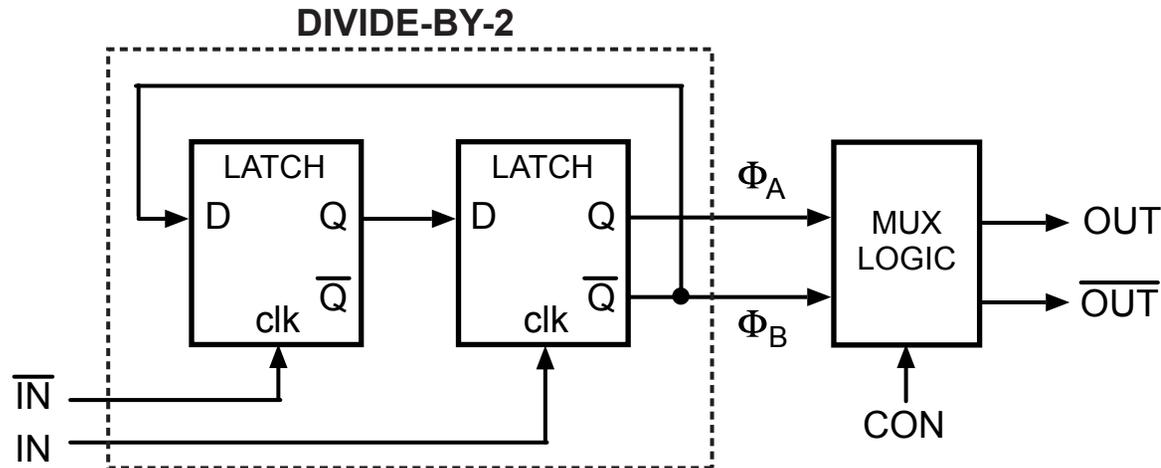


- Achieves speed of divide-by-2 circuits!
 - MUX logic runs at half the input clock speed

Implementation Challenges to Phase Shifting


- **Avoiding glitches**
 - **By assumption of sine wave characteristics**
 - Craninckx et. al., “A 1.75 GHz/3 V Dual-Modulus Divide-by-128/129 Prescaler ...”, JSSC, July 1996
 - **By make-before-break switching**
 - My thesis: <http://www-mtl.mit.edu/~perrott/>
 - **Through re-timed multiplexor**
 - Krishnapura et. al, “A 5.3 GHz Programmable Divider for HiPerLan in 0.25 μ m CMOS”, JSSC, July 2000
- **Avoiding jitter due to mismatch in phases**
 - **Through calibration**
 - Park et. al., “A 1.8-GHz Self-Calibrated Phase-Locked Loop with Precise I/Q Matching”, JSSC, May 2001

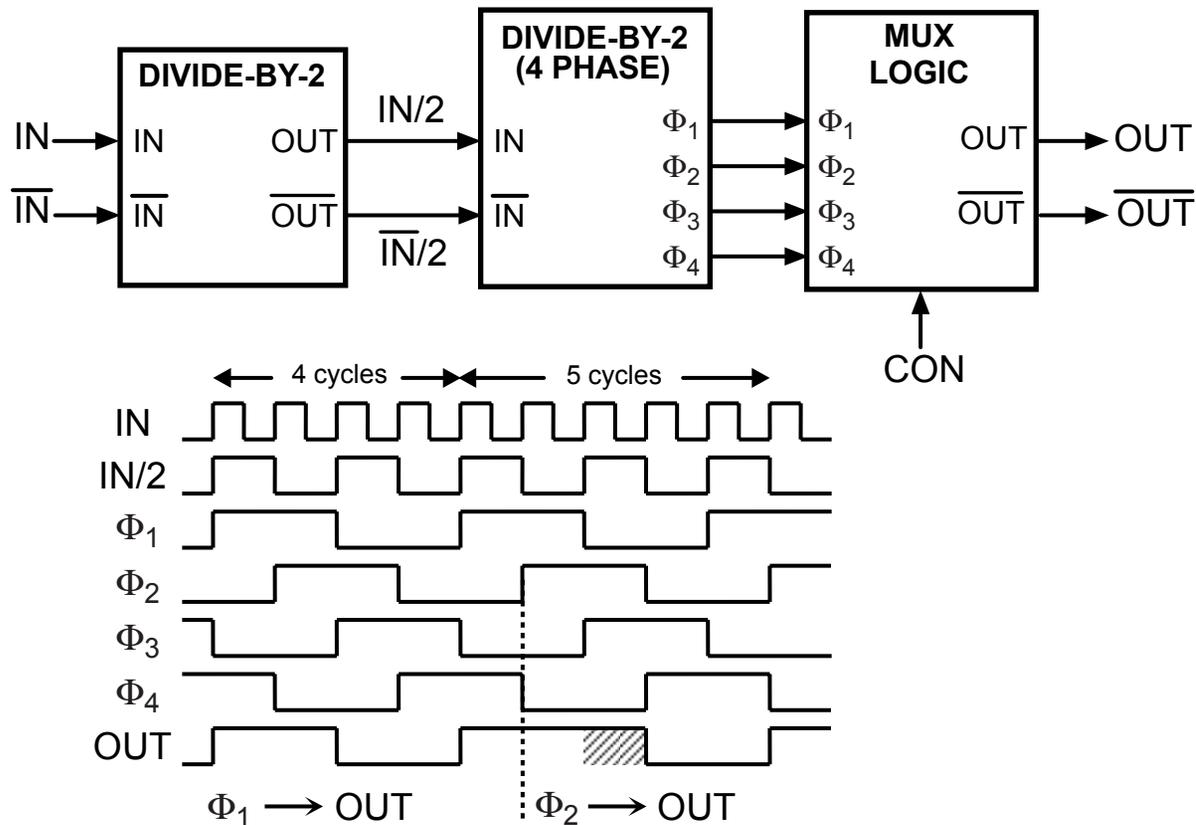Further Reduction of MUX Operating Frequency




- Leverage the fact that divide-by-2 circuit has 4 phases
 - Create divide-by-4/5 by cascading two divide-by-2 circuits
 - Note that single cycle pulse swallowing still achieved
 - Mux operates at one fourth the input frequency!

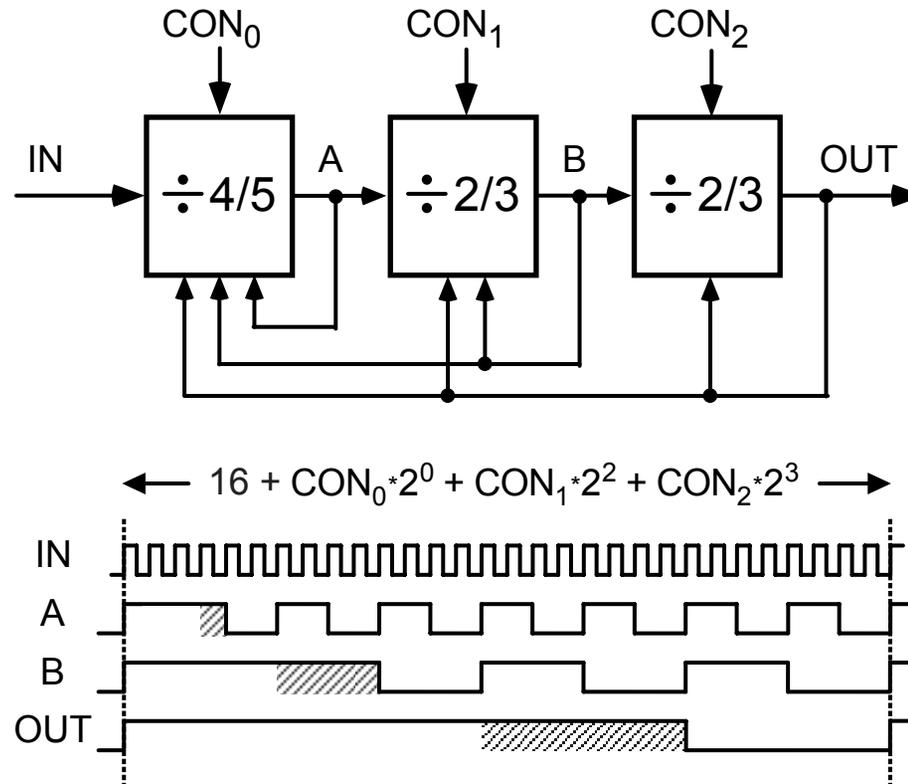Impact of Divide-by-4/5 in Multi-Modulus Prescaler




- Issue – gaps are created in divide value range
 - Divide-by-4/5 lowers swallowing resolution of following stage

Method to “Fill In” Divide Value Range

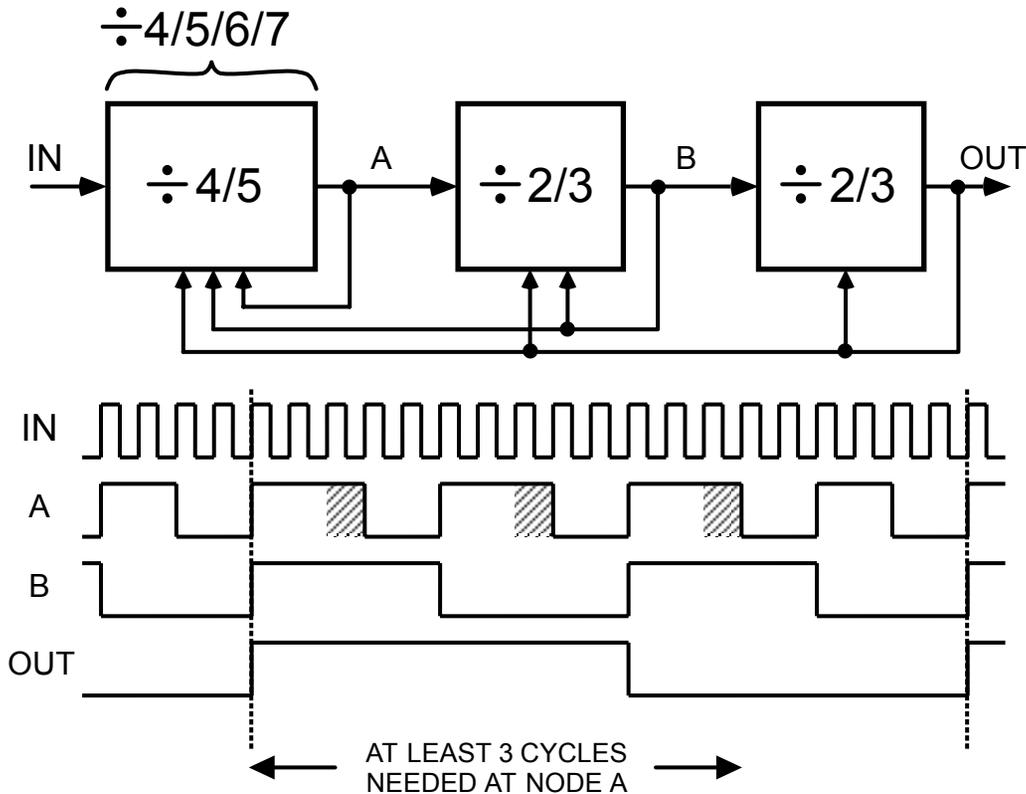

- Allow divide-by-4/5 to swallow more than one input cycle per OUT period
 - Divide-by-4/5 changed to Divide-by-4/5/6/7
- Note: at least two divide-by-2/3 sections must follow

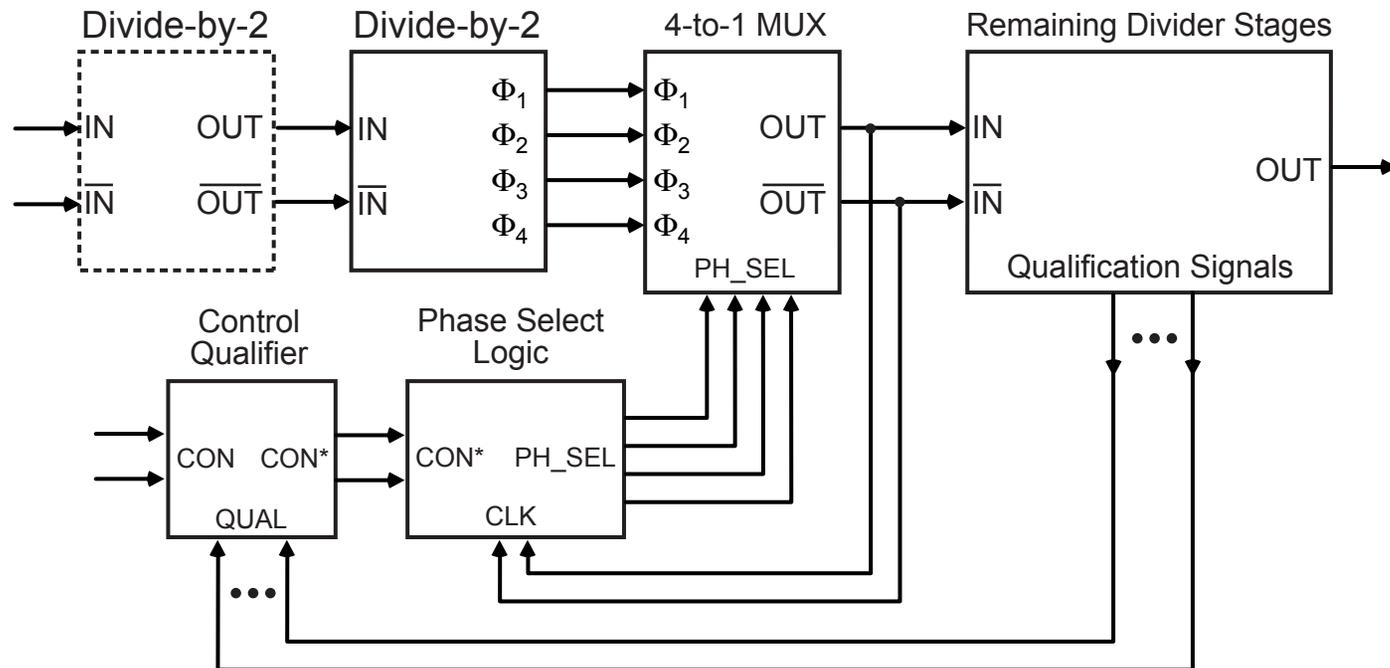Example Architecture for a Phase-Shifted Divider



- Phase shifting in first divide-by-4/5/6/7 stage to achieve high speed
- Remaining stages correspond to gated divide-by-2/3 cells
- For details, see my thesis
 - <http://www-mtl.mit.edu/~perrott/>