



6.976


*High Speed Communication Circuits and Systems  
Lecture 4*

*Generalized Reflection Coefficient, Smith Chart,  
Integrated Passive Components*

Michael Perrott  
Massachusetts Institute of Technology


Copyright © 2003 by Michael H. Perrott
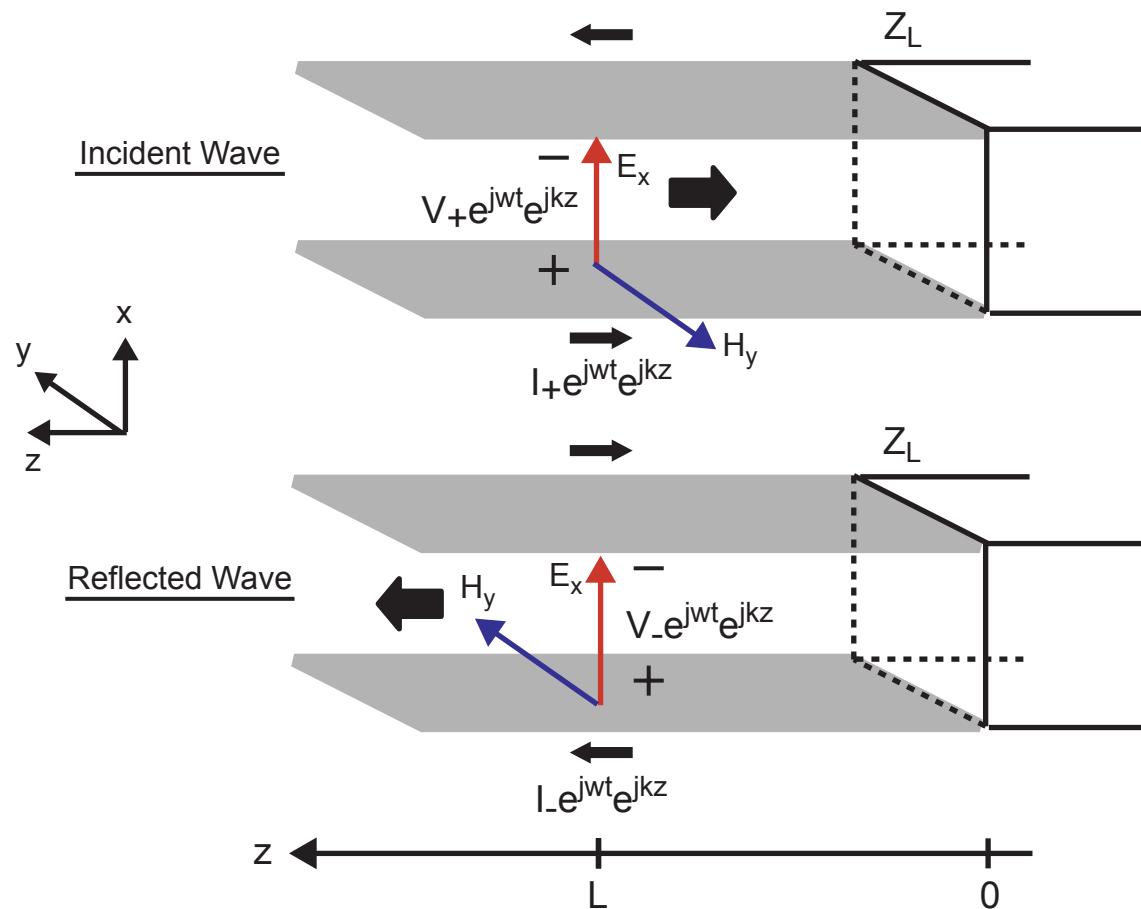
# Determine Voltage and Current At Different Positions



- Incident and reflected waves must be added together
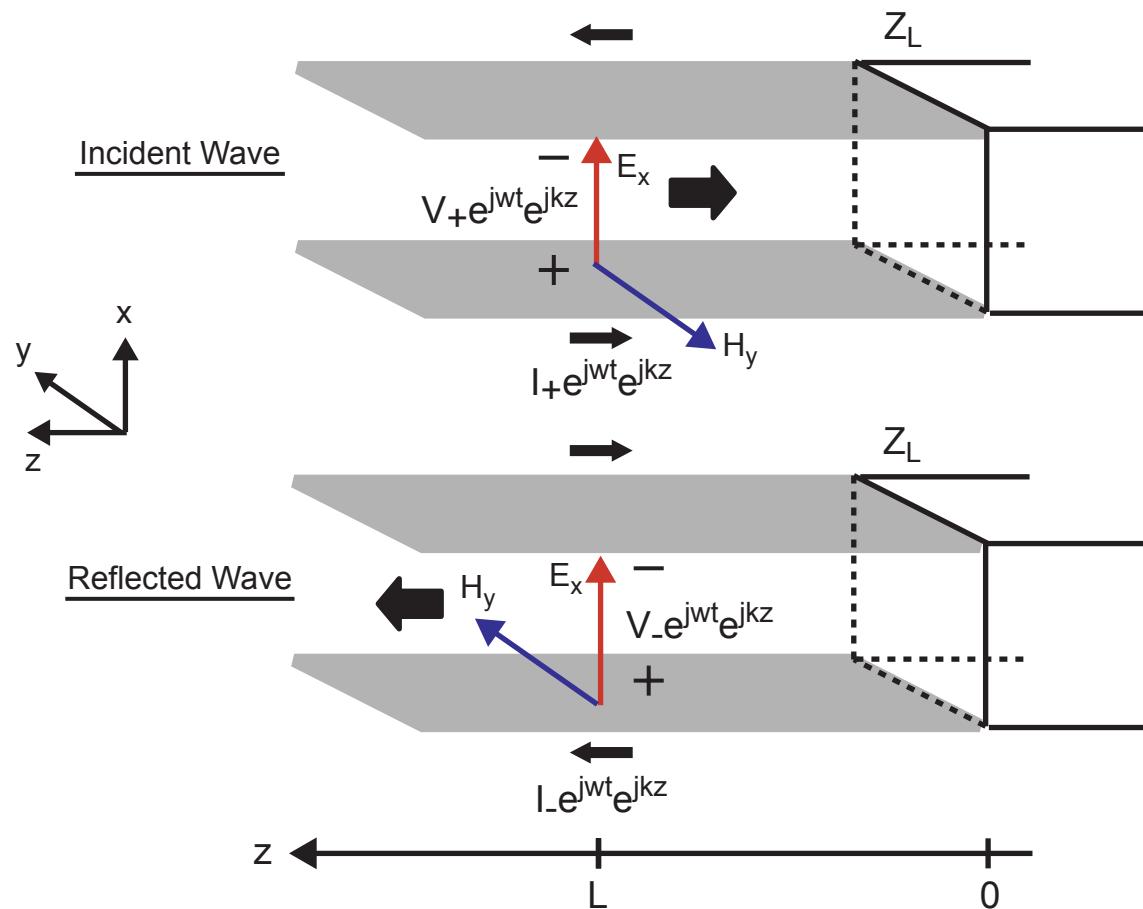
# Determine Voltage and Current At Different Positions



$$V(z, t) = V_+ e^{j\omega t} e^{jkz} + V_- e^{j\omega t} e^{-jkz}$$
$$I(z, t) = I_+ e^{j\omega t} e^{jkz} - I_- e^{j\omega t} e^{-jkz}$$

## **Define Generalized Reflection Coefficient**

---

$$V(z, t) = V_+ e^{j \omega t} e^{j k z} + V_- e^{j \omega t} e^{-j k z}$$

$$I(z, t) = I_+ e^{j \omega t} e^{j k z} - I_- e^{j \omega t} e^{-j k z}$$

---

$$V(z, t) = V_+ e^{j \omega t} e^{j k z} \left( 1 + \frac{V_-}{V_+} e^{-2 j k z} \right)$$



$$V(z, t) = V_+ e^{j \omega t} e^{j k z} \left( 1 + \Gamma_L e^{-2 j k z} \right)$$



$$V(z, t) = V_+ e^{j \omega t} e^{j k z} (1 + \Gamma(z))$$

**Similarly:**  $I(z, t) = I_+ e^{j \omega t} e^{j k z} (1 - \Gamma(z))$

$$\Rightarrow \Gamma(z) = \Gamma_L e^{-2 j k z}$$

## A Closer Look at $\Gamma(z)$

- Recall  $\Gamma_L$  is


$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o}$$

Note:  $|\Gamma_L| \leq 1$

for  $Re\{Z_L/Z_o\} \geq 0$

- We can view  $\Gamma(z)$  as a complex number that rotates clockwise as  $z$  (distance from the load) increases

$$\Gamma(z) = \Gamma_L e^{-2jkz}$$

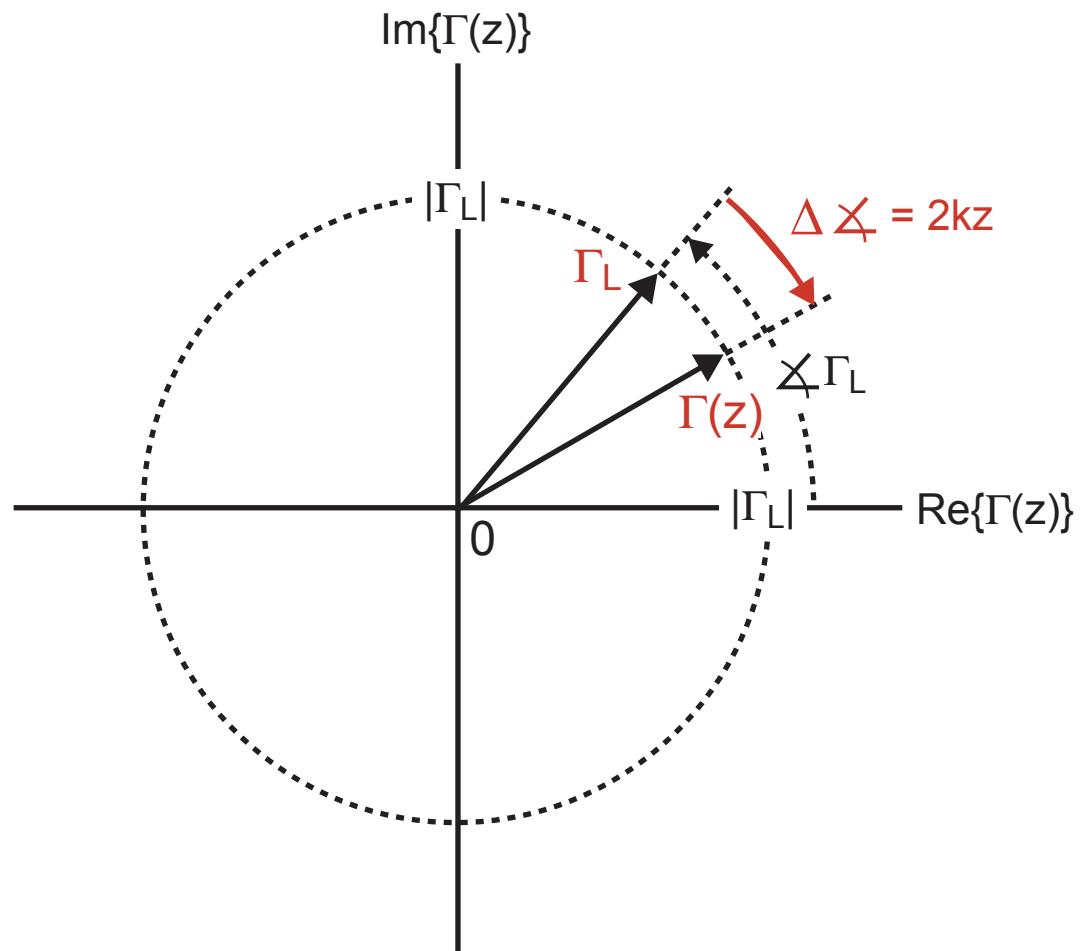

## **Calculate $|V_{max}|$ and $|V_{min}|$ Across The Transmission Line**

---

- We found that

$$V(z, t) = V_+ e^{j\omega t} e^{jkz} (1 + \Gamma(z))$$

- So that the max and min of  $V(z,t)$  are calculated as


$$\Rightarrow V_{max} = \max |V(z, t)| = |V_+| \max |1 + \Gamma(z)|$$

$$\Rightarrow V_{min} = \min |V(z, t)| = |V_+| \min |1 + \Gamma(z)|$$

- We can calculate this geometrically!

# A Geometric View of $|1 + \Gamma(z)|$

---

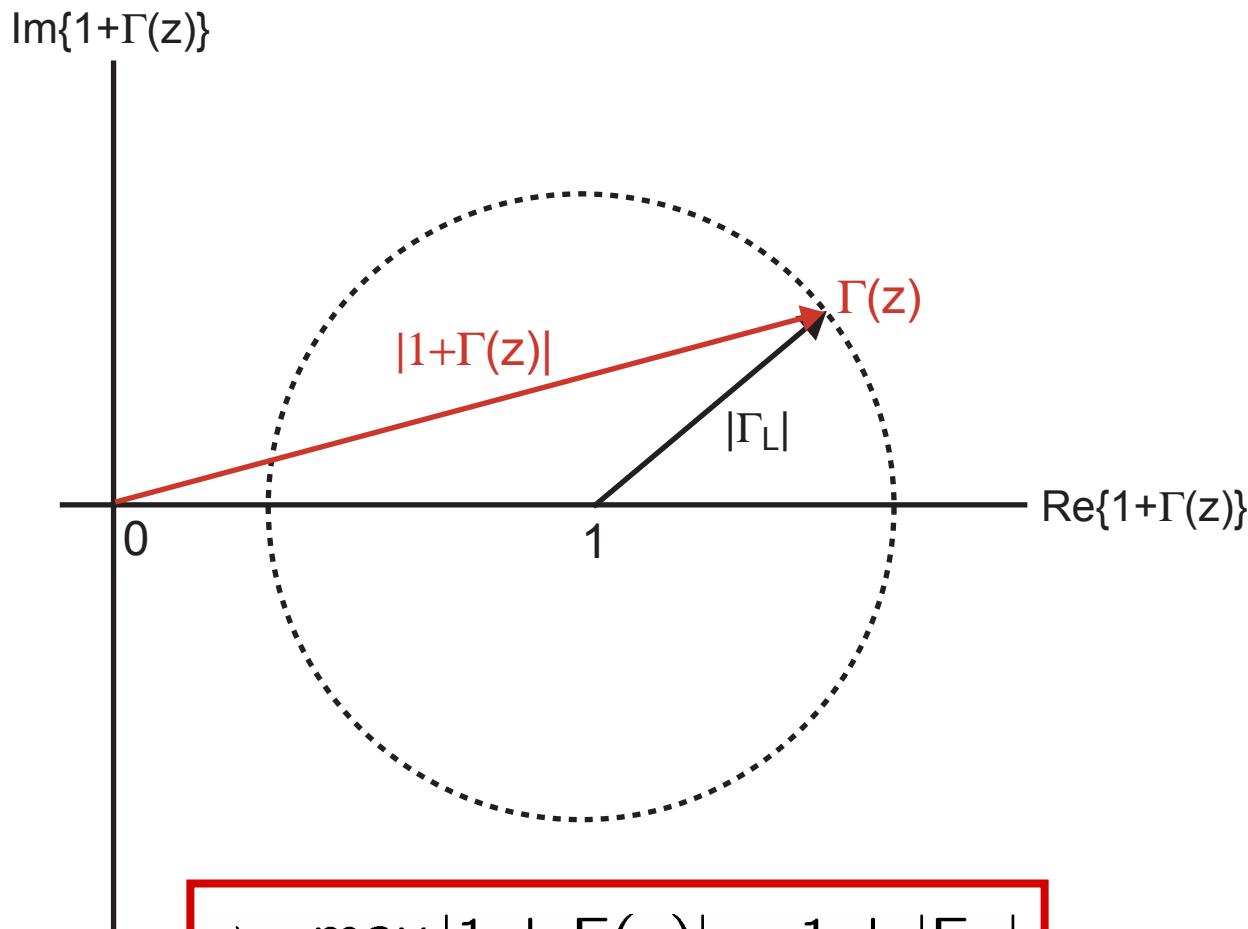


$$\Rightarrow \max |1 + \Gamma(z)| = 1 + |\Gamma_L|$$

$$\Rightarrow \min |1 + \Gamma(z)| = 1 - |\Gamma_L|$$

## Reflections Cause Amplitude to Vary Across Line

- **Equation:**  $V(z, t) = V_+ e^{j\omega t} e^{jkz} |1 + \Gamma(z)| e^{j\angle(1+\Gamma(z))}$
- **Graphical representation:**

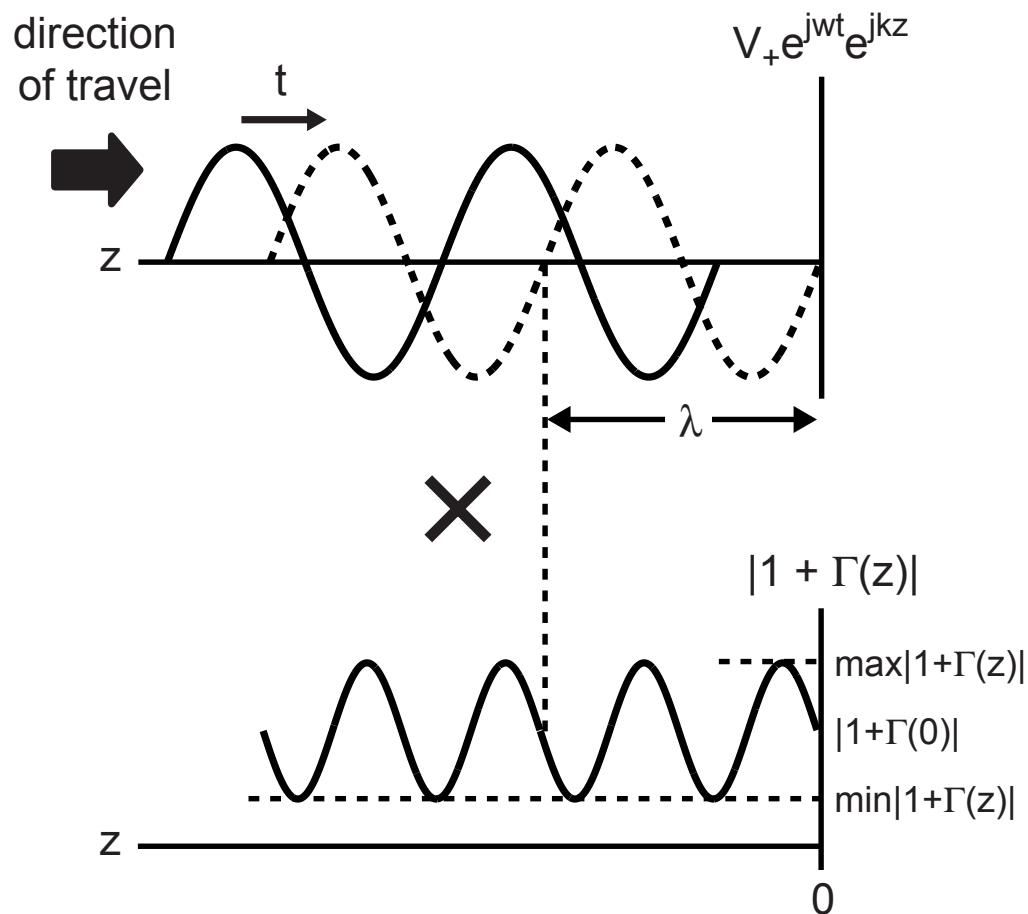

# **Voltage Standing Wave Ratio (VSWR)**

---

- **Definition**

$$\text{VSWR} = \frac{V_{max}}{V_{min}} = \frac{|V_+|(1 + |\Gamma_L|)}{|V_+|(1 - |\Gamma_L|)} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$

- **For passive load (and line)**

$$|\Gamma_L| \leq 1 \Rightarrow 1 \leq \text{VSWR} \leq \infty$$

$\uparrow \qquad \qquad \qquad \uparrow$

$$|\Gamma_L| = 0 \qquad \qquad |\Gamma_L| = 1$$

- **We can infer the magnitude of the reflection coefficient based on VSWR**

$$|\Gamma_L| = \frac{\text{VSWR} - 1}{\text{VSWR} + 1}$$

## Reflections Influence Impedance Across The Line

- **From Slide 4**

$$V(z, t) = V_+ e^{j\omega t} e^{jkz} (1 + \Gamma(z))$$

$$I(z, t) = I_+ e^{j\omega t} e^{jkz} (1 - \Gamma(z))$$

$$\Rightarrow Z(z, t) = \frac{V_+ (1 + \Gamma(z))}{I_+ (1 - \Gamma(z))} = Z_o \frac{1 + \Gamma(z)}{1 - \Gamma(z)}$$

- Note: not a function of time! (only of distance from load)


- **Alternatively**

$$Z(z) = Z_o \frac{1 + \Gamma_L e^{-2jkz}}{1 - \Gamma_L e^{-2jkz}}$$

- **From Lecture 2:**  $\lambda = \frac{T}{\sqrt{\mu\epsilon}} = \frac{wT}{w\sqrt{\mu\epsilon}} = \frac{2\pi f T}{k} = \frac{2\pi}{k}$

$$Z(z) = Z_o \frac{1 + \Gamma_L e^{-j(4\pi/\lambda)z}}{1 - \Gamma_L e^{-j(4\pi/\lambda)z}}$$
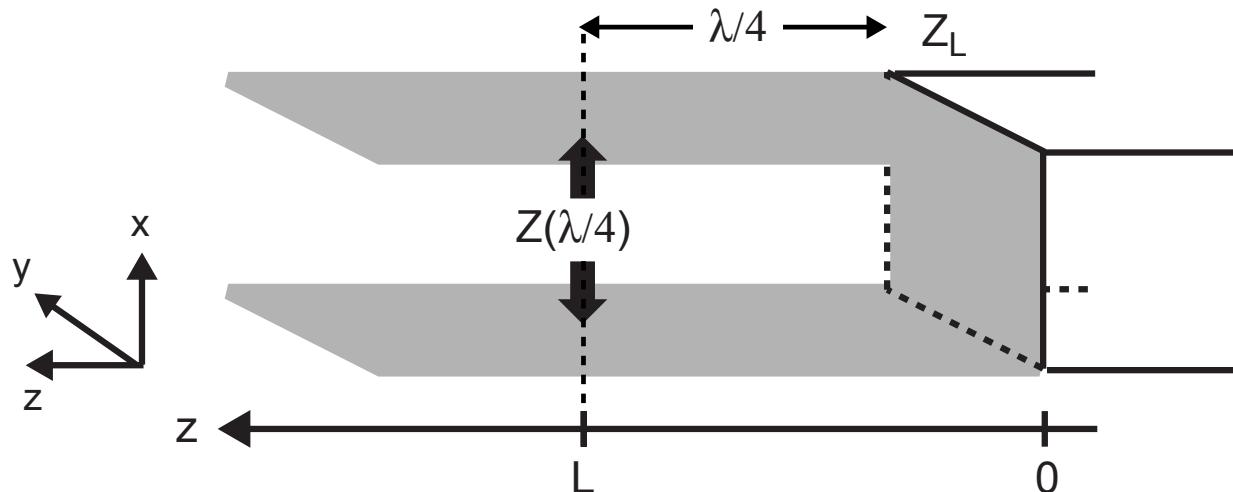
## **Example: $Z(\lambda/4)$ with Shorted Load**



- Calculate reflection coefficient

$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = \frac{0 - Z_o}{0 + Z_o} = -1$$

- Calculate generalized reflection coefficient

$$\Gamma(\lambda/4) = \Gamma_L e^{-j(4\pi/\lambda)(\lambda/4)} = \Gamma_L e^{-j\pi} = -\Gamma_L = 1$$

- Calculate impedance

$$Z(\lambda/4) = Z_o \frac{1 + \Gamma(z)}{1 - \Gamma(z)} = \infty !$$

# **Generalize Relationship Between $Z(\lambda/4)$ and $Z(0)$**

---

- **General formulation**

$$Z(z) = Z_o \frac{1 + \Gamma_L e^{-j(4\pi/\lambda)z}}{1 - \Gamma_L e^{-j(4\pi/\lambda)z}}$$

- **At load ( $z=0$ )**

$$Z_L = Z(0) = Z_o \frac{1 + \Gamma_L}{1 - \Gamma_L}$$

- **At quarter wavelength away ( $z = \lambda/4$ )**

$$Z(\lambda/4) = Z_o \frac{1 - \Gamma_L}{1 + \Gamma_L} = \frac{Z_o^2}{Z_L}$$

- **Impedance is inverted!**

- Shorts turn into opens
    - Capacitors turn into inductors

## Now Look At $Z(\Delta)$ (*Impedance Close to Load*)

---

- **Impedance formula ( $\Delta$  very small)**

$$Z(\Delta) = Z_o \frac{1 + \Gamma_L e^{-2jk\Delta}}{1 - \Gamma_L e^{-2jk\Delta}}$$

- **A useful approximation:**  $e^{-jx} \approx 1 - jx$  for  $x \ll 1$

$$\Rightarrow e^{-2jk\Delta} \approx 1 - 2jk\Delta$$


- **Recall from Lecture 2:**  $k = w\sqrt{LC}$ ,  $Z_o = \sqrt{\frac{L}{C}}$

- **Overall approximation:**

$$Z(\Delta) \approx \left( \sqrt{\frac{L}{C}} \right) \frac{1 + \Gamma_L(1 - 2jw\sqrt{LC}\Delta)}{1 - \Gamma_L(1 - 2jw\sqrt{LC}\Delta)}$$

## Example: Look At $Z(\Delta)$ With Load Shorted

---

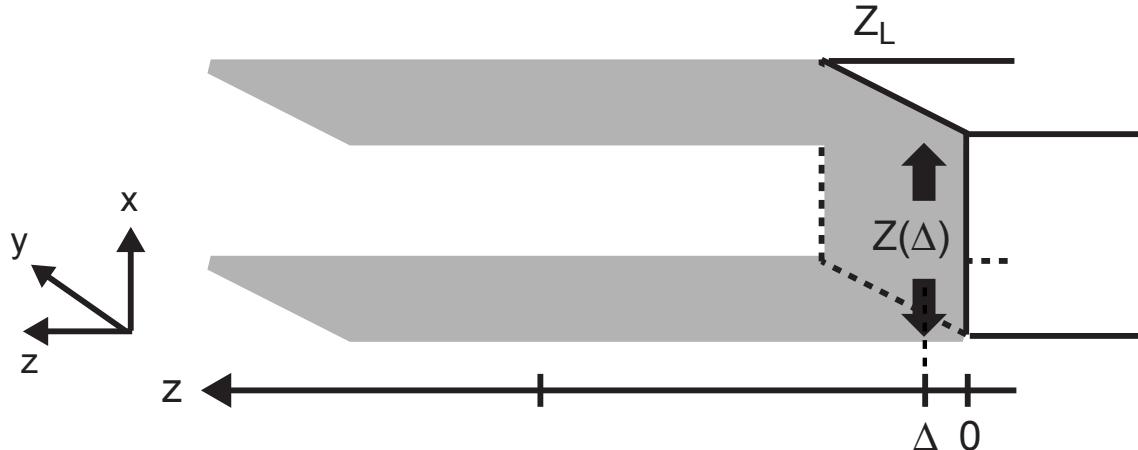

$$Z(\Delta) \approx \left( \sqrt{\frac{L}{C}} \right) \frac{1 + \Gamma_L (1 - 2jw\sqrt{LC}\Delta)}{1 - \Gamma_L (1 - 2jw\sqrt{LC}\Delta)}$$


---

- **Reflection coefficient:**  $\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = \frac{0 - Z_o}{0 + Z_o} = -1$
- **Resulting impedance looks inductive!**

$$Z(\Delta) \approx \left( \sqrt{\frac{L}{C}} \right) \frac{1 - (1 - 2jw\sqrt{LC}\Delta)}{1 + (1 - 2jw\sqrt{LC}\Delta)} \approx jwL\Delta$$

## Example: Look At $Z(\Delta)$ With Load Open

---

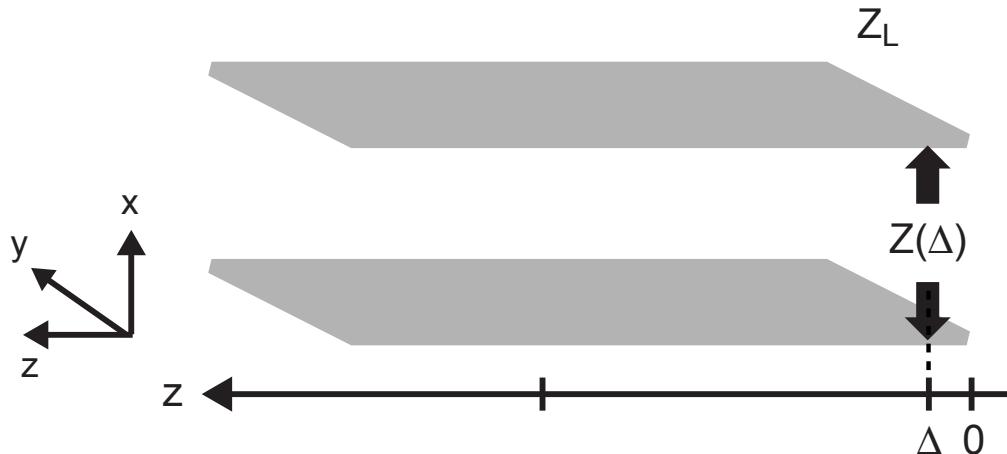


$$Z(\Delta) \approx \left( \sqrt{\frac{L}{C}} \right) \frac{1 + \Gamma_L (1 - 2jw\sqrt{LC}\Delta)}{1 - \Gamma_L (1 - 2jw\sqrt{LC}\Delta)}$$

---

- **Reflection coefficient:**  $\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = \frac{\infty - Z_o}{\infty + Z_o} = 1$
- **Resulting impedance looks capacitive!**

$$Z(\Delta) \approx \left( \sqrt{\frac{L}{C}} \right) \frac{1 + (1 - 2jw\sqrt{LC}\Delta)}{1 - (1 - 2jw\sqrt{LC}\Delta)} \approx \frac{1}{jwC\Delta}$$

## Consider an Ideal LC Tank Circuit

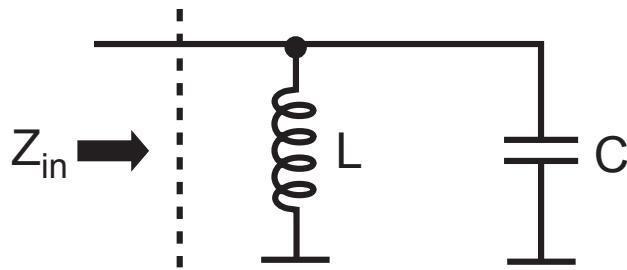

$$Z_{in}(w) = \frac{1}{jwC} || jwL = \frac{jwL}{1 - w^2LC}$$


- Calculate input impedance about resonance

Consider  $w = w_o + \Delta w$ , where  $w_o = \frac{1}{\sqrt{LC}}$

$$\begin{aligned} Z_{in}(\Delta w) &= \frac{j(w_o + \Delta w)L}{1 - (w_o + \Delta w)^2LC} \\ &= \frac{j(w_o + \Delta w)L}{\underline{1 - w_o^2LC} - 2\Delta w(w_oLC) - \underline{\Delta w^2LC}} \\ &\quad = 0 \qquad \text{negligible} \end{aligned}$$

$$\Rightarrow Z_{in}(\Delta w) \approx \frac{j(w_o + \Delta w)L}{-2\Delta w(w_oLC)} \approx \frac{jw_oL}{-2\Delta w(w_oLC)} = -\frac{j}{2} \sqrt{\frac{L}{C}} \left( \frac{w_o}{\Delta w} \right)$$
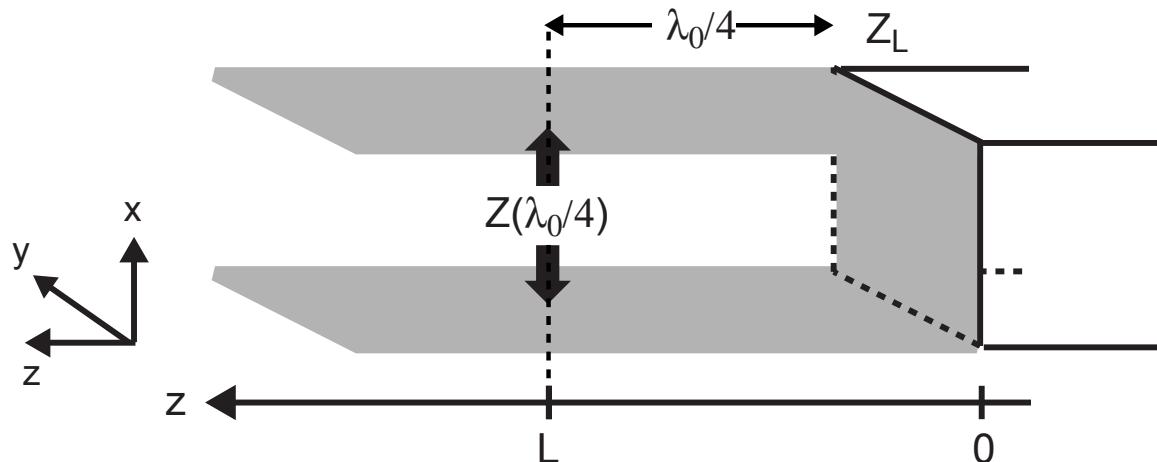
## Transmission Line Version: $Z(\lambda_0/4)$ with Shorted Load



- As previously calculated

$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o} = \frac{0 - Z_o}{0 + Z_o} = -1$$


- Impedance calculation

$$Z(z) = Z_o \frac{1 + \Gamma(z)}{1 - \Gamma(z)}, \text{ where } \Gamma(z) = \Gamma_L e^{-j(4\pi/\lambda)z}$$

- Relate  $\lambda$  to frequency

$$\lambda = \frac{1}{f \sqrt{\mu \epsilon}} = \frac{1}{(f_o + \Delta f) \sqrt{\mu \epsilon}}$$

## Calculate $Z(\Delta f)$ – Step 1

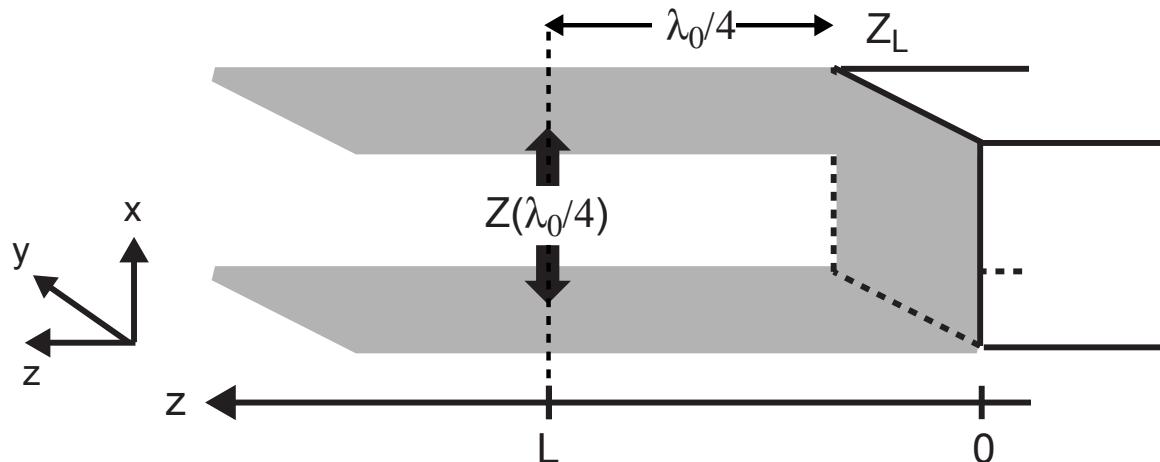

- **Wavelength as a function of  $\Delta f$**


$$\lambda = \frac{1}{(f_o + \Delta f) \sqrt{\mu\epsilon}} = \frac{1}{f_o \sqrt{\mu\epsilon} (1 + \Delta f / f_o)} = \frac{\lambda_o}{1 + \Delta f / f_o}$$

- **Generalized reflection coefficient**

$$\Gamma(\lambda_o/4) = \Gamma_L e^{-j(4\pi/\lambda)\lambda_o/4} = \Gamma_L e^{-j\pi\lambda_o/\lambda} = \Gamma_L e^{-j\pi\lambda_o/\lambda}$$

$$\Rightarrow \Gamma(\lambda_o/4) = \Gamma_L e^{-j\pi(1 + \Delta f / f_o)} = -\Gamma_L e^{-j\pi\Delta f / f_o}$$

## Calculate $Z(\Delta f)$ – Step 2

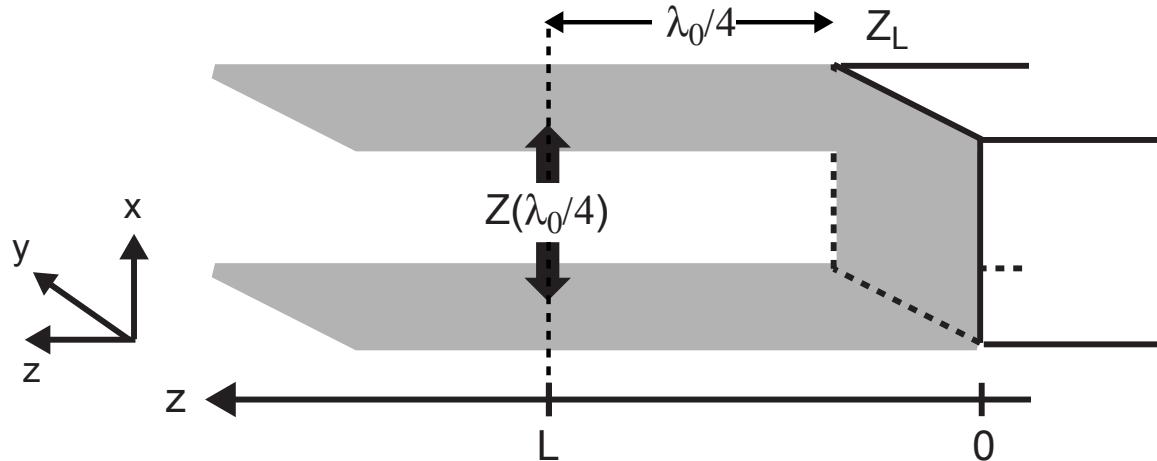

### ■ Impedance calculation

$$Z(\lambda_0/4) = Z_o \frac{1 - \Gamma_L e^{-j\pi\Delta f/f_o}}{1 + \Gamma_L e^{-j\pi\Delta f/f_o}} = Z_o \frac{1 + e^{-j\pi\Delta f/f_o}}{1 - e^{-j\pi\Delta f/f_o}}$$

### ■ Recall $e^{-j\pi\Delta f/f_o} \approx 1 - j\pi\Delta f/f_o$

$$\Rightarrow Z(z) \approx Z_o \frac{1 + 1 - j\pi\Delta f/f_o}{1 - 1 + j\pi\Delta f/f_o} \approx Z_o \frac{2}{j\pi\Delta f/f_o} = -j \frac{2}{\pi} \sqrt{\frac{L}{C}} \left( \frac{w_o}{\Delta w} \right)$$

– Looks like LC tank circuit about frequency  $w_o$ !

## Smith Chart

---

- Define normalized impedance

$$Z_n = \frac{Z_L}{Z_o}$$

- Mapping from normalized impedance to  $\Gamma$  is one-to-one


$$Z_n = \frac{1 + \Gamma_L}{1 - \Gamma_L}$$

- Consider working in coordinate system based on  $\Gamma$
- Key relationship between  $Z_n$  and  $\Gamma$

$$Re\{Z_n\} + jIm\{Z_n\} = \frac{1 + Re\{\Gamma_L\} + jIm\{\Gamma_L\}}{1 - (Re\{\Gamma_L\} + jIm\{\Gamma_L\})}$$


- Equate real and imaginary parts to get Smith Chart
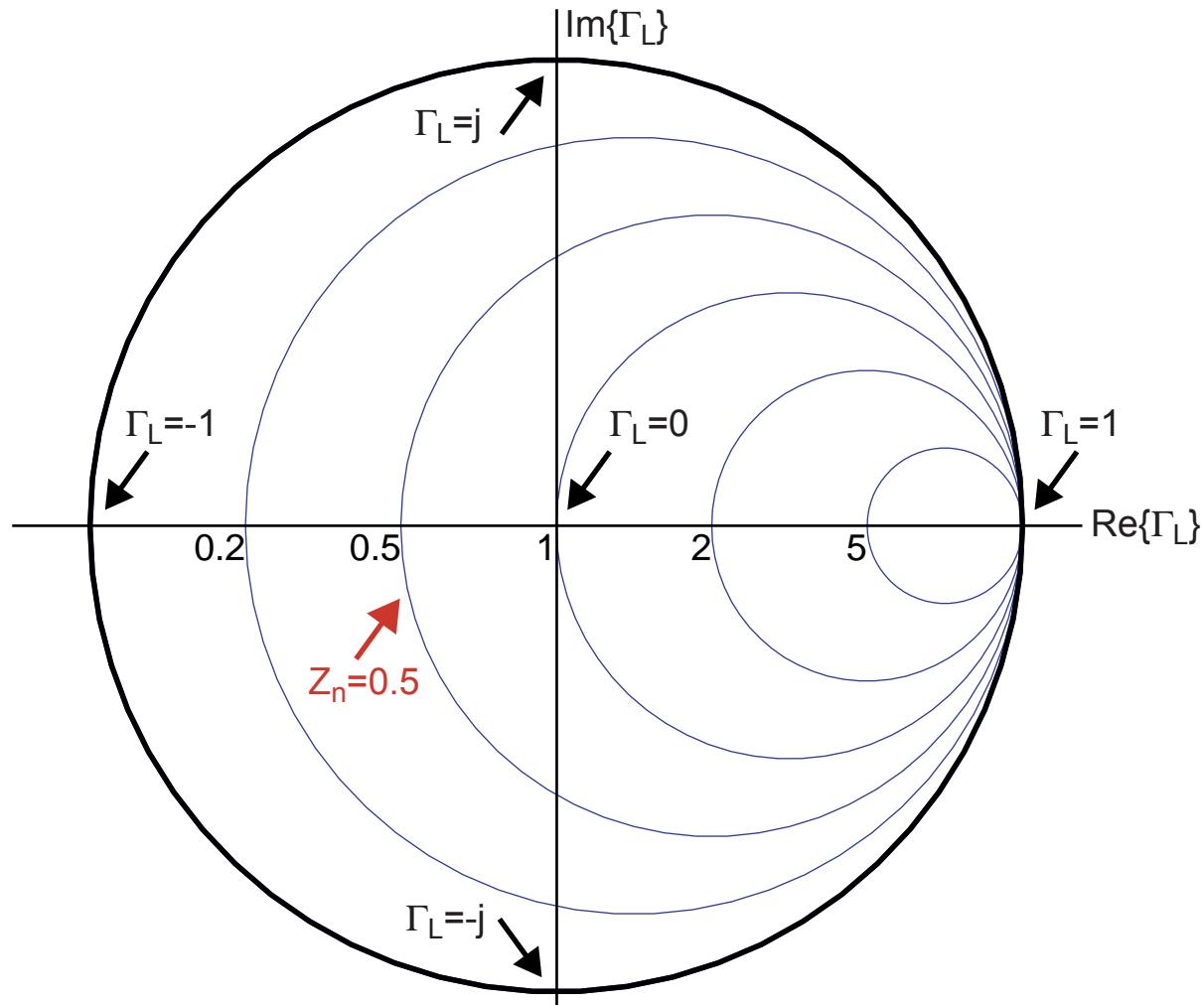
## Real Impedance in $\Gamma$ Coordinates (Equate Real Parts)



$$\left( \text{Re}\{\Gamma_L\} - \frac{\text{Re}\{Z_n\}}{1 + \text{Re}\{Z_n\}} \right)^2 + (\text{Im}\{\Gamma_L\})^2 = \left( \frac{1}{1 + \text{Re}\{Z_n\}} \right)^2$$
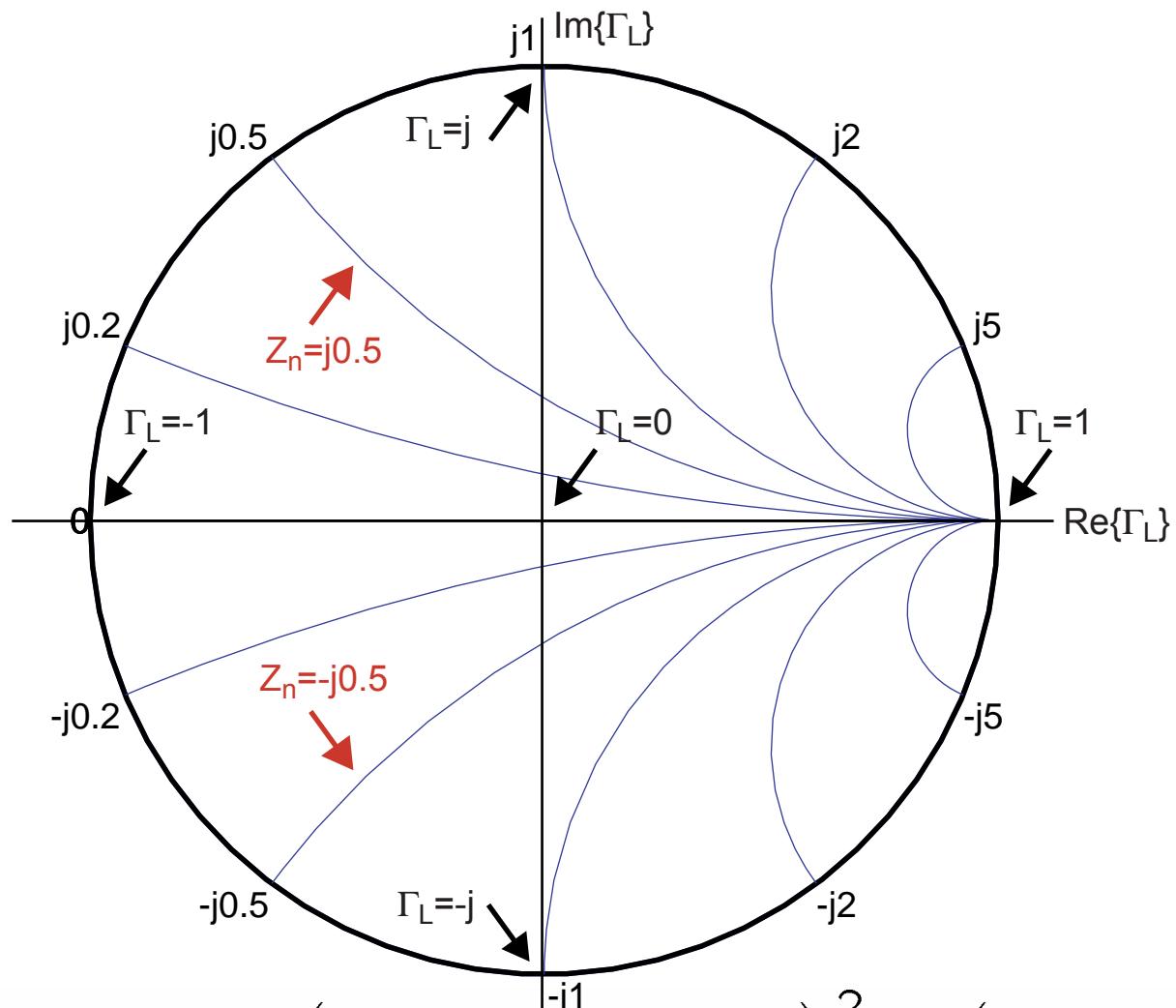
## Imag. Impedance in $\Gamma$ Coordinates (Equate Imag. Parts)



$$(Re\{\Gamma_L\} - 1)^2 + \left( Im\{\Gamma_L\} - \frac{1}{Im\{Z_n\}} \right)^2 = \left( \frac{1}{Im\{Z_n\}} \right)^2$$

# *What Happens When We Invert the Impedance?*

---

- **Fundamental formulas**

$$Z_n = \frac{1 + \Gamma_L}{1 - \Gamma_L} \Rightarrow \Gamma_L = \frac{Z_n - 1}{Z_n + 1}$$

- **Impact of inverting the impedance**

$$Z_n \rightarrow 1/Z_n \Rightarrow \Gamma_L \rightarrow -\Gamma_L$$

- **Derivation:**

$$\frac{1/Z_n - 1}{1/Z_n + 1} = \frac{1 - Z_n}{1 + Z_n} = -\left(\frac{Z_n - 1}{Z_n + 1}\right)$$

- **We can invert complex impedances in  $\Gamma$  plane by simply changing the sign of  $\Gamma$  !**

- **How can we best exploit this?**

# *The Smith Chart as a Calculator for Matching Networks*


---

- Consider constructing both impedance and admittance curves on Smith chart


$$Z_n \rightarrow 1/Z_n \Rightarrow \Gamma_L \rightarrow -\Gamma_L$$

- Conductance curves derived from resistance curves
- Susceptance curves derived from reactance curves
- For series circuits, work with impedance
  - Impedances add for series circuits
- For parallel circuits, work with admittance
  - Admittances add for parallel circuits
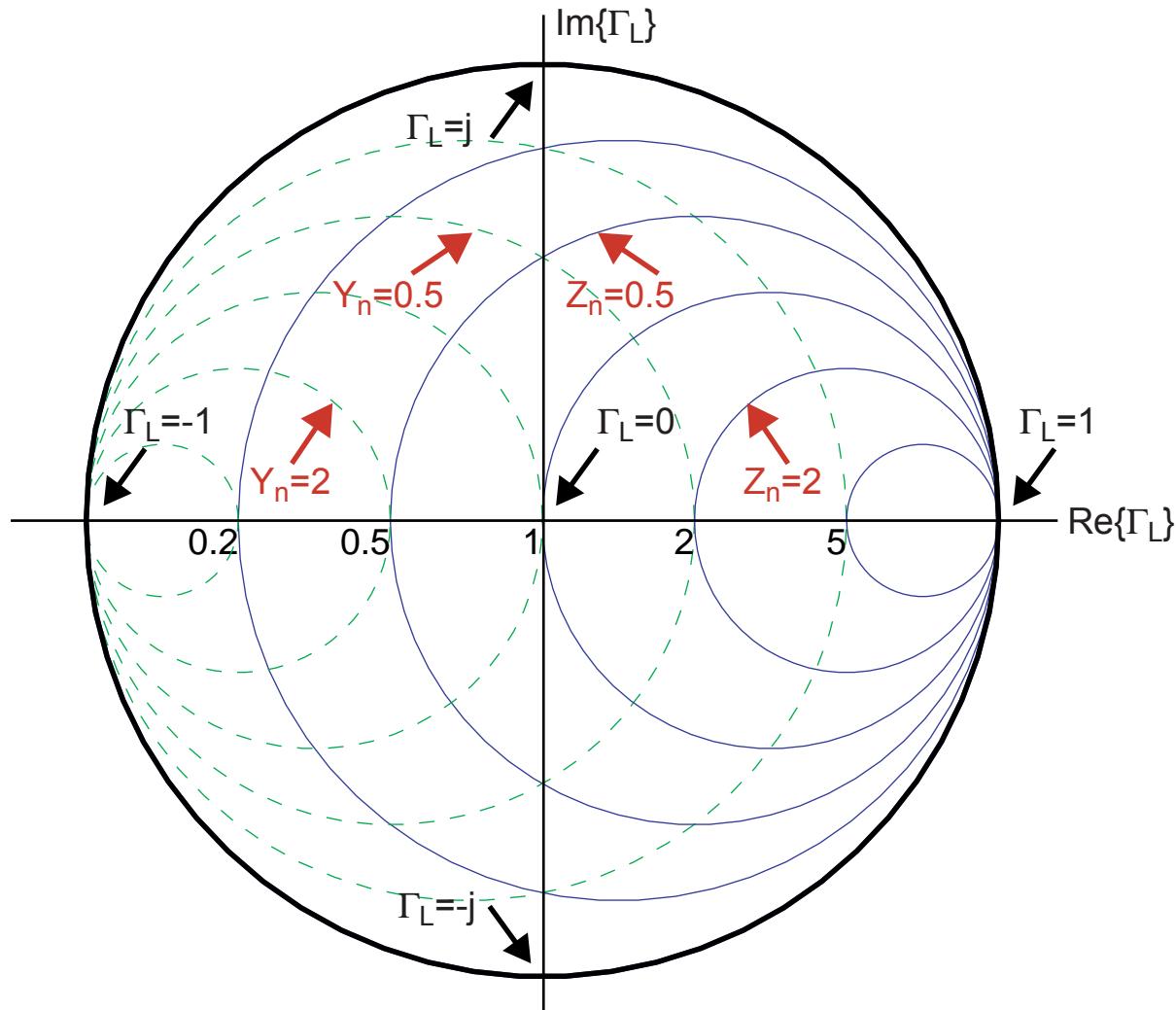
# Resistance and Conductance on the Smith Chart



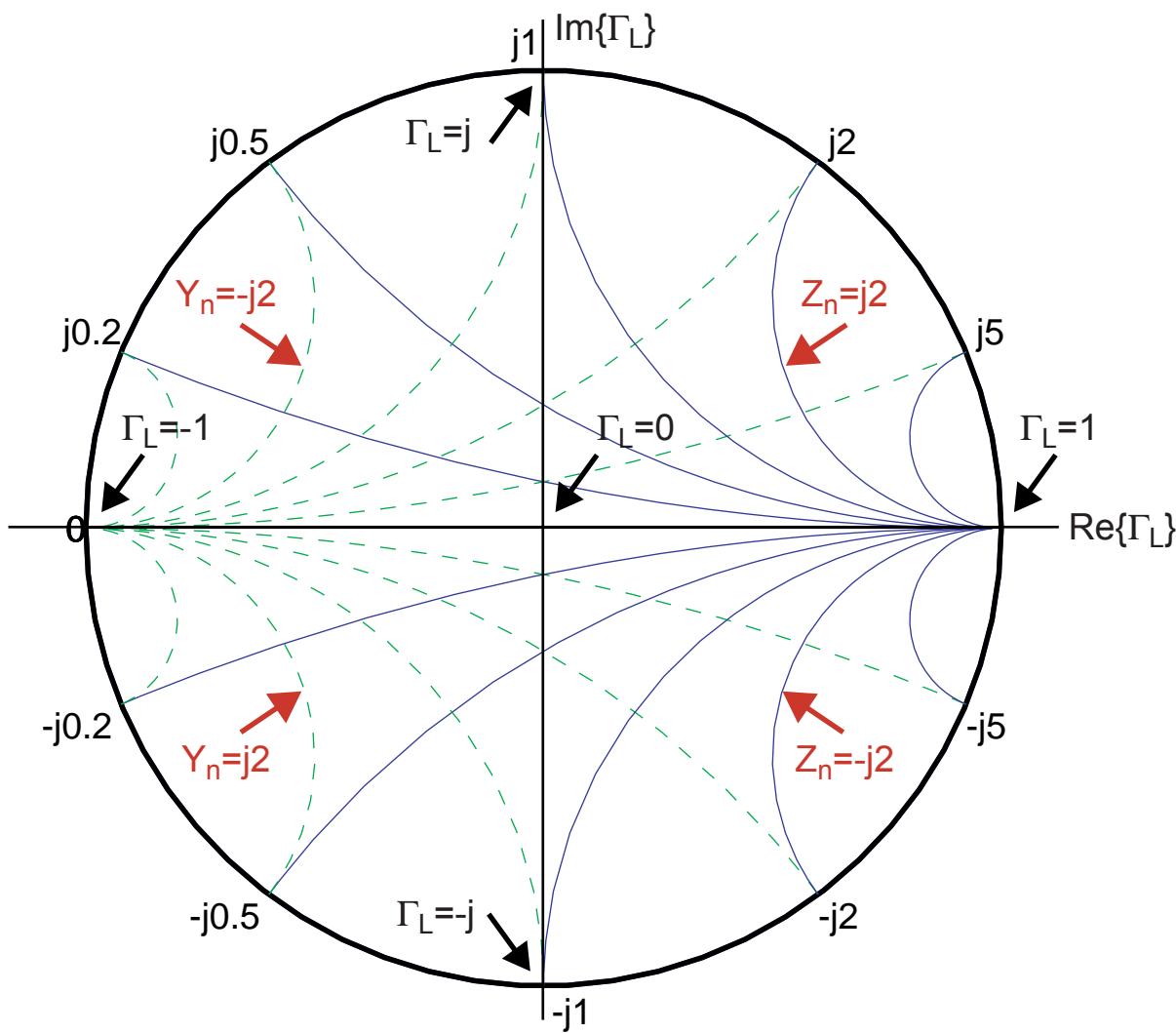
# Reactance and Susceptance on the Smith Chart




# *Overall Smith Chart*

---

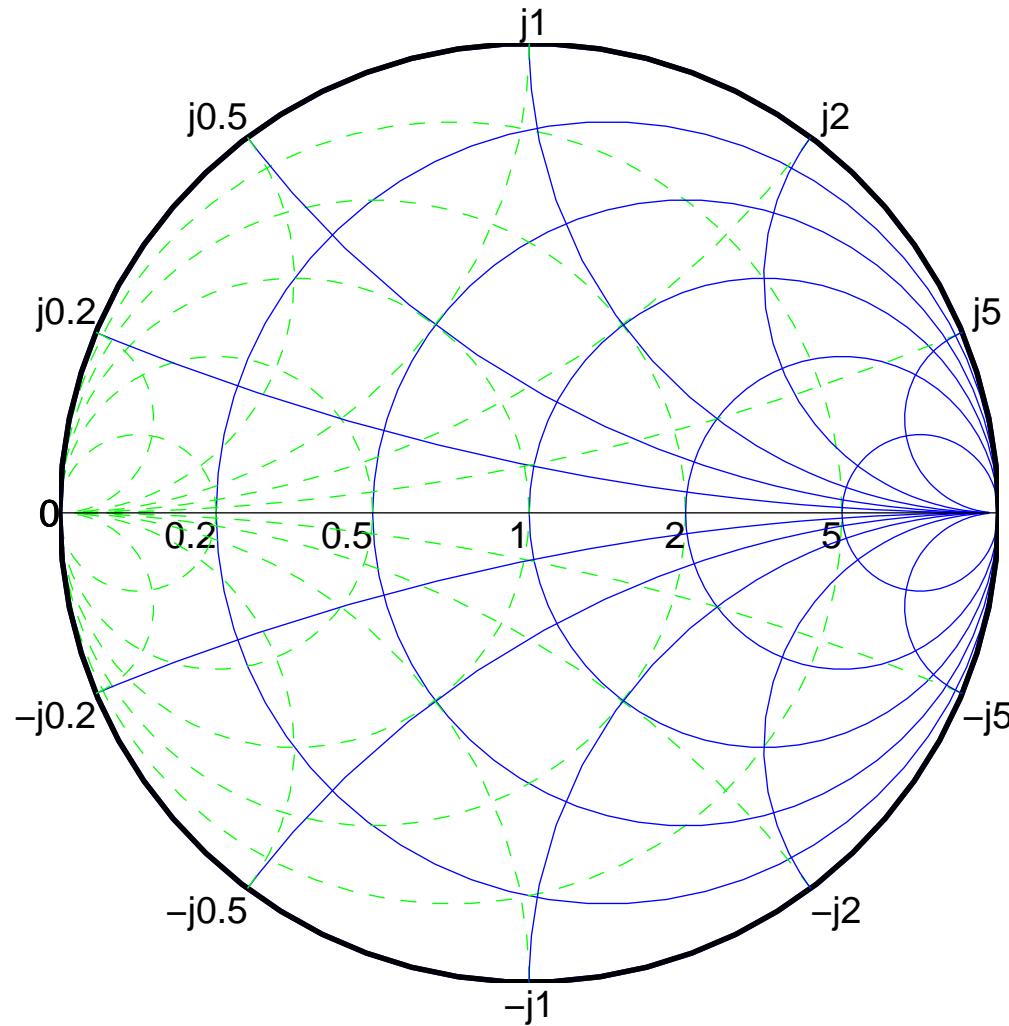

## Example – Match RC Network to 50 Ohms at 2.5 GHz

- Circuit

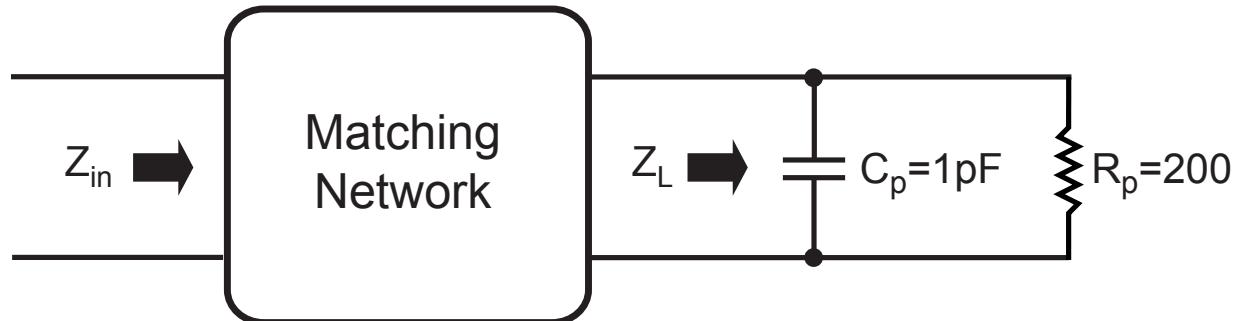


- Step 1: Calculate  $Z_{Ln}$

$$\begin{aligned}Z_{Ln} &= \frac{Z_L}{Z_o} = \frac{R_L || (1/jwC)}{50} = \frac{1}{50(1/R_L + jwC)} \\&= \frac{1}{50(1/200 + j2\pi(2.5e9)10^{-12})} = \frac{1}{0.25 + j.7854}\end{aligned}$$


- Step 2: Plot  $Z_{Ln}$  on Smith Chart (use admittance,  $Y_{Ln}$ )
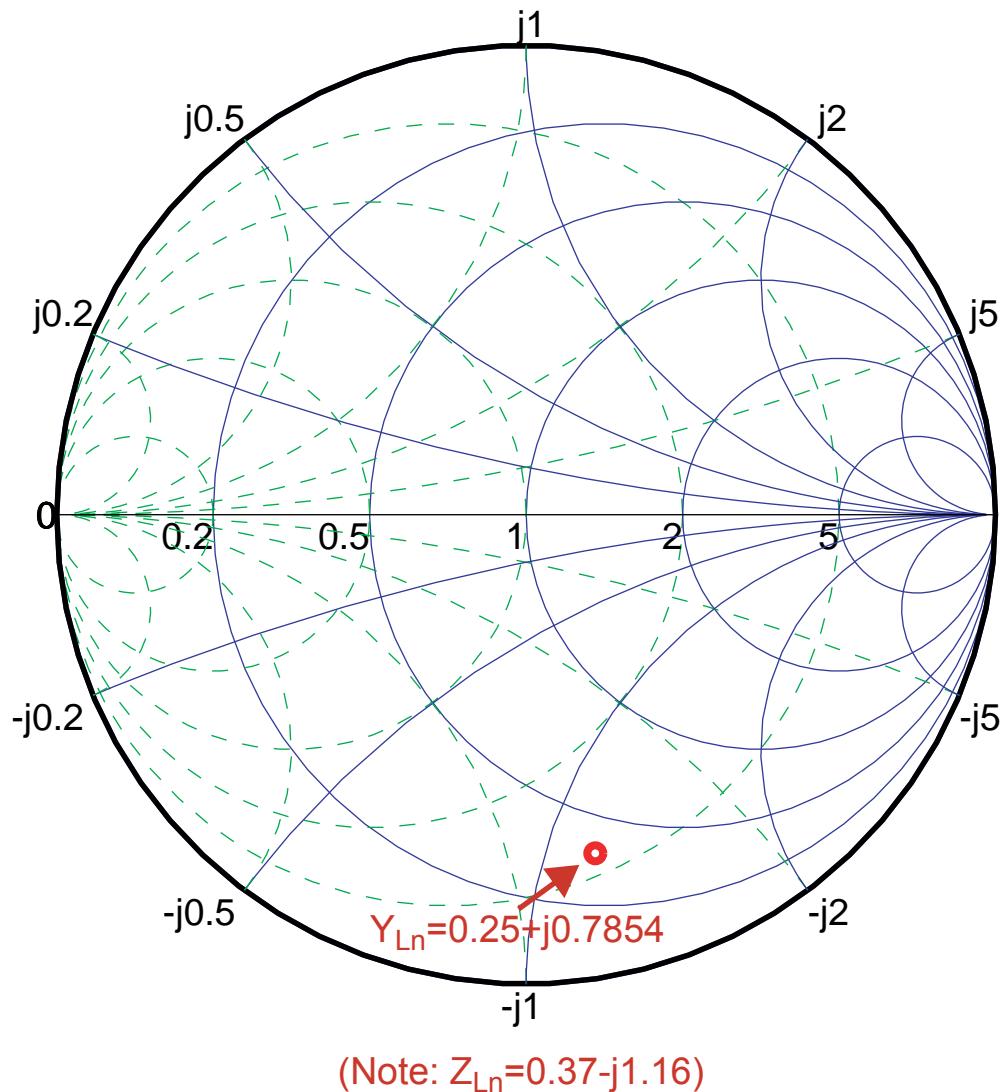
# Plot Starting Impedance (Admittance) on Smith Chart


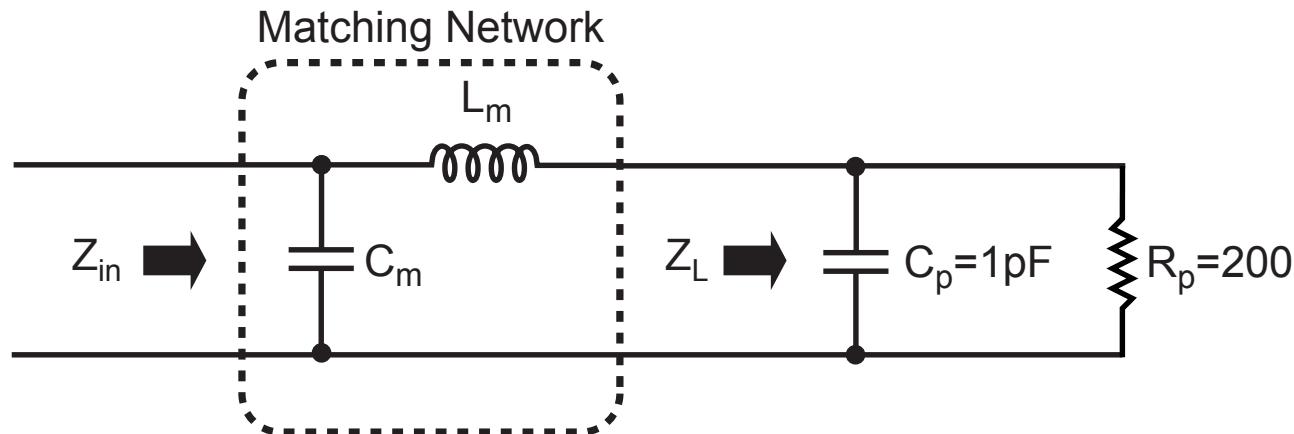
## Develop Matching “Game Plan” Based on Smith Chart


- By inspection, we see that the following matching network can bring us to  $Z_{in} = 50 \text{ Ohms}$  (center of Smith chart)



- Use the Smith chart to come up with component values
  - Inductance  $L_m$  shifts impedance up along reactance curve
  - Capacitance  $C_m$  shifts impedance down along susceptance curve

## Add Reactance of Inductor $L_m$

---

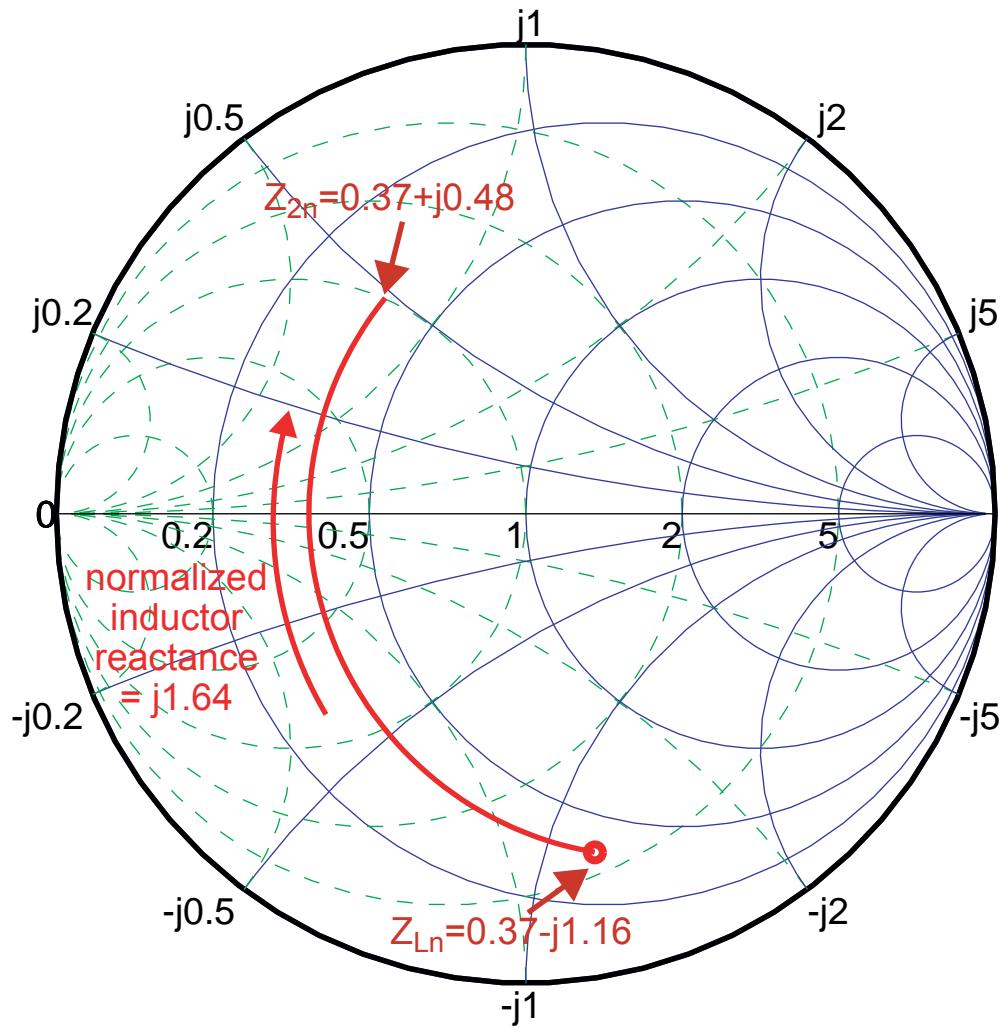

## *Inductor Value Calculation Using Smith Chart*

---


- From Smith chart, we found that the desired normalized inductor reactance is

$$\frac{jwL_m}{Z_o} = \frac{jwL_m}{50} = j1.64$$

- Required inductor value is therefore

$$\Rightarrow L_m = \frac{50(1.64)}{2\pi 2.5e9} = 5.2nH$$
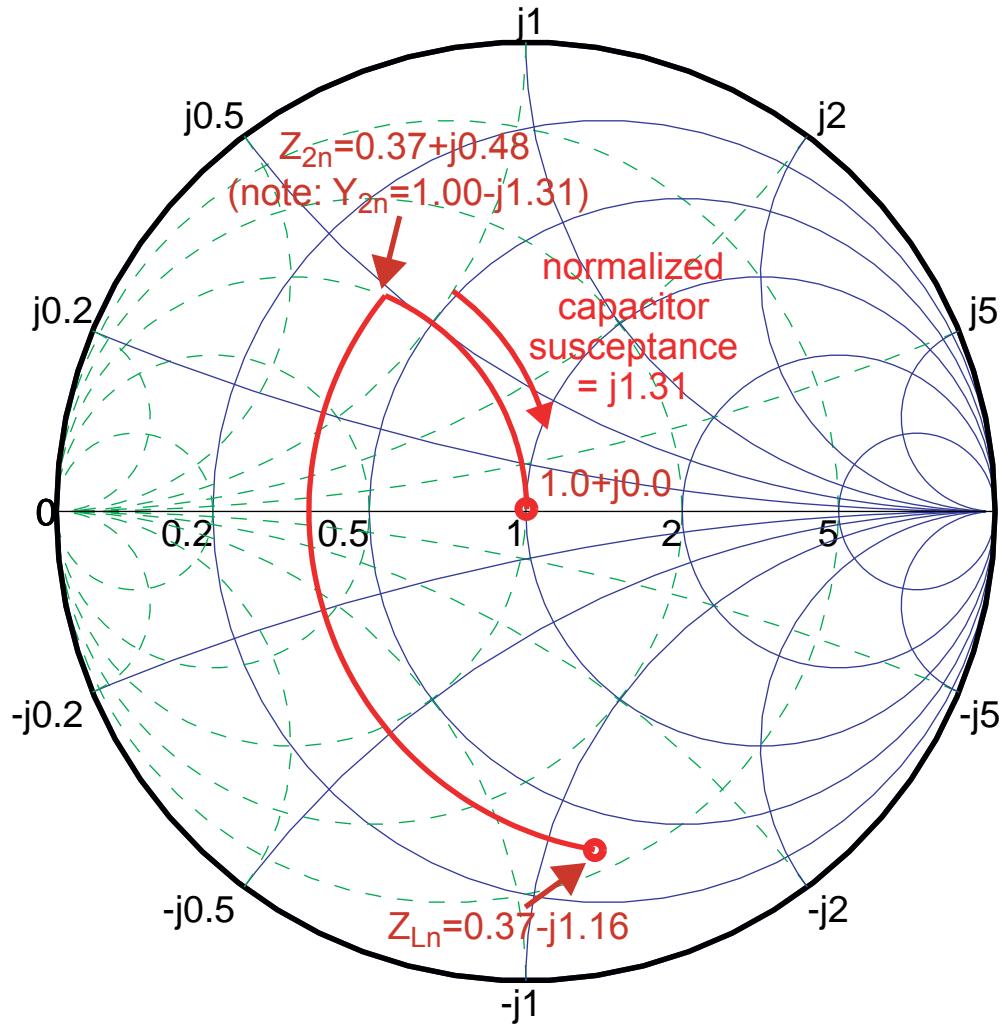
## Add Susceptance of Capacitor $C_m$ (Achieves Match!)



## **Capacitor Value Calculation Using Smith Chart**

---

- From Smith chart, we found that the desired normalized capacitor susceptance is

$$Z_o j w C_m = 50 j w C_m = j 1.31$$

- Required capacitor value is therefore

$$\Rightarrow C_m = \frac{1.31}{50(2\pi 2.5e9)} = 1.67 pF$$

## *Just For Fun*

---

- Play the “matching game” at

<http://contact.tm.agilent.com/Agilent/tmo/an-95-1/classes/imatch.html>


- Allows you to graphically tune several matching networks
- Note: game is set up to match source to load impedance rather than match the load to the source impedance
  - Same results, just different viewpoint

# *Passives*
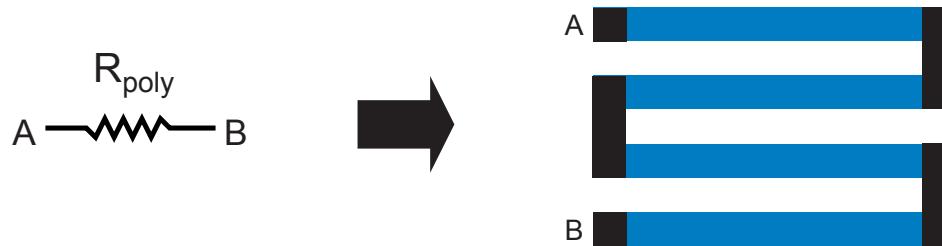
# Polysilicon Resistors

---

- Use unsilicided polysilicon to create resistor




- Key parameters
  - Resistance (usually 100- 200 Ohms per square)
  - Parasitic capacitance (usually small)
    - Appropriate for high speed amplifiers
  - Linearity (quite linear compared to other options)
  - Accuracy (usually can be set within  $\pm 15\%$ )

# MOS Resistors

---

- Bias a MOS device in its triode region

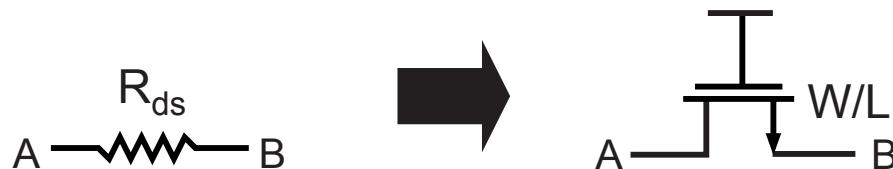


$$R_{ds} \approx \frac{1}{\mu C_{ox} W/L ((V_{gs} - V_T) - V_{DS})}$$

- High resistance values can be achieved in a small area (MegaOhms within tens of square microns)
- Resistance is quite nonlinear
  - Appropriate for small swing circuits
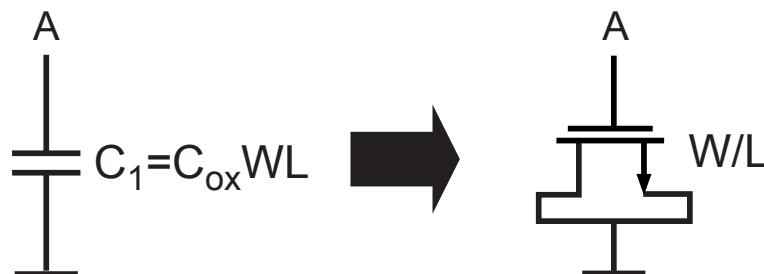
# High Density Capacitors (*Biasing, Decoupling*)

---


- MOS devices offer the highest capacitance per unit area
  - Limited to a one terminal device
  - Voltage must be high enough to invert the channel



- Key parameters
  - Capacitance value
    - Raw cap value from MOS device is  $6.1 \text{ fF}/\mu \text{m}^2$  for  $0.24\mu$  CMOS
  - Q (i.e., amount of series resistance)
    - Maximized with minimum L (tradeoff with area efficiency)
- See pages 39-40 of Tom Lee's book
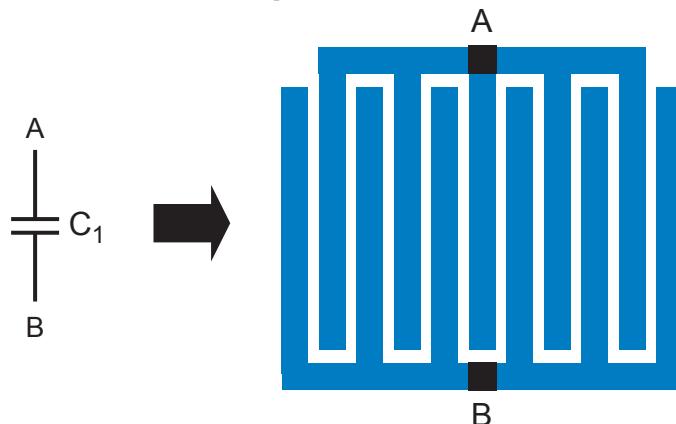
## High Q Capacitors (Signal Path)

- Lateral metal capacitors offer high Q and reasonably large capacitance per unit area
  - Stack many levels of metal on top of each other (best layers are the top ones), via them at maximum density




- Accuracy often better than  $\pm 10\%$
- Parasitic side cap is symmetric, less than 10% of cap value
- Example:  $C_T = 1.5 \text{ fF}/\mu\text{m}^2$  for  $0.24\mu\text{m}$  process with 7 metals,  $L_{\min} = W_{\min} = 0.24\mu\text{m}$ ,  $t_{\text{metal}} = 0.53\mu\text{m}$ 
  - See “Capacity Limits and Matching Properties of Integrated Capacitors”, Aparicio et. al., JSSC, Mar 2002
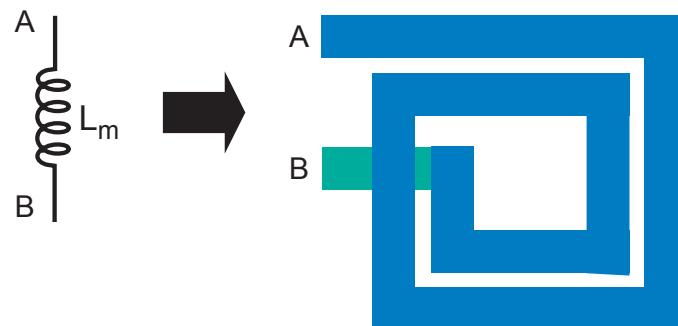
## Spiral Inductors

---


- Create integrated inductor using spiral shape on top level metals (may also want a patterned ground shield)



- Key parameters are Q (< 10), L (1-10 nH), self resonant freq.
- Usually implemented in top metal layers to minimize series resistance, coupling to substrate
- Design using Mohan et. al, “Simple, Accurate Expressions for Planar Spiral Inductances, JSSC, Oct, 1999, pp 1419-1424
- Verify inductor parameters (L, Q, etc.) using ASITIC  
<http://formosa.eecs.berkeley.edu/~niknejad/asitic.html>
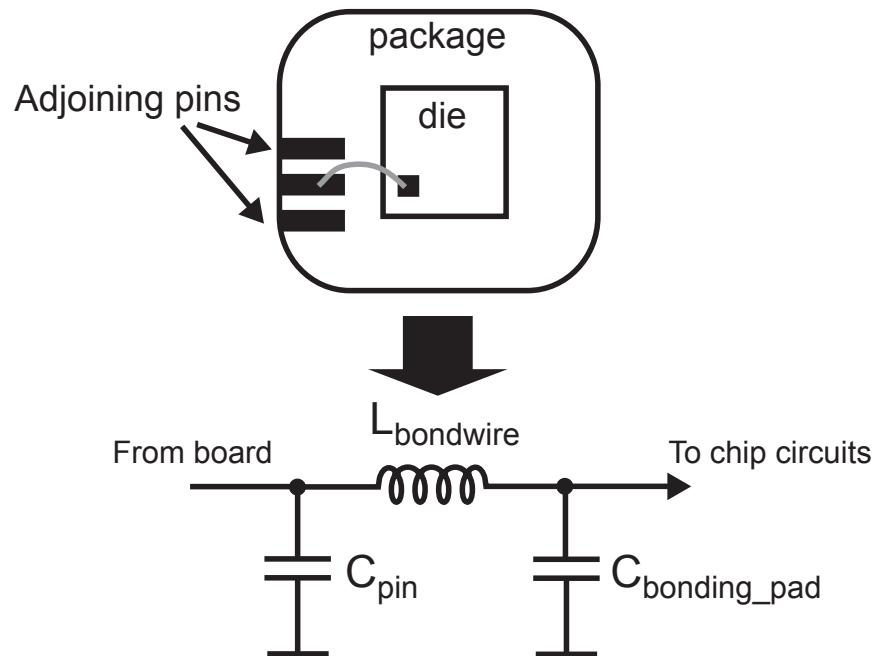
# Bondwire Inductors



- Used to bond from the package to die
  - Can be used to advantage



- Key parameters
  - Inductance ( $\approx 1 \text{ nH/mm}$  – usually achieve 1-5 nH)
  - Q (much higher than spiral inductors – typically  $> 40$ )
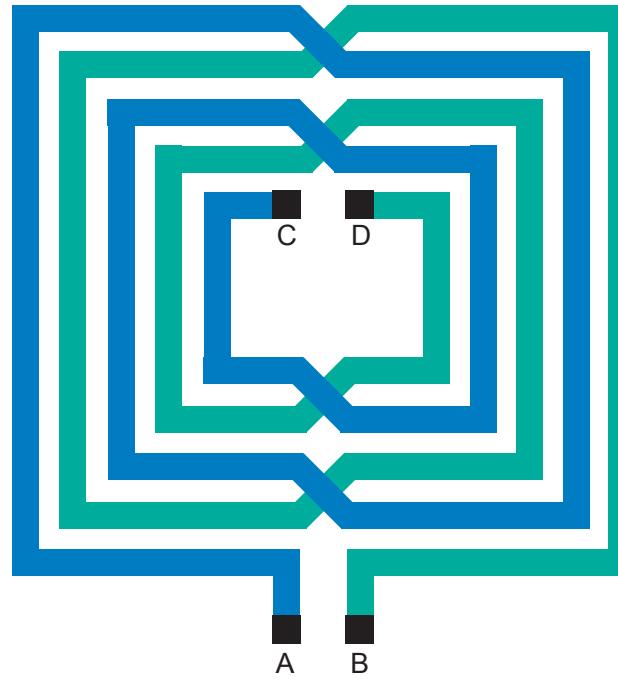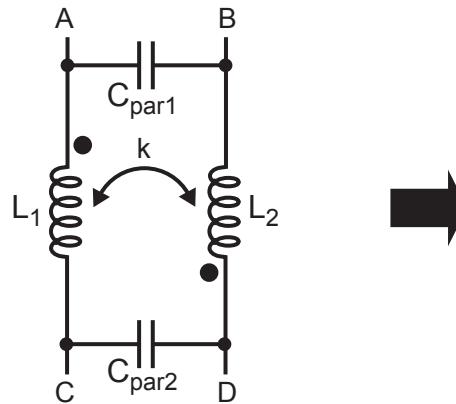
# *Integrated Transformers*

- Utilize magnetic coupling between adjoining wires




- Key parameters
  - L (self inductance for primary and secondary windings)
  - k (coupling coefficient between primary and secondary)

Note:  $k = \frac{M}{\sqrt{L_1 L_2}}$  where M = mutual inductance

- Design – ASITIC, other CAD packages
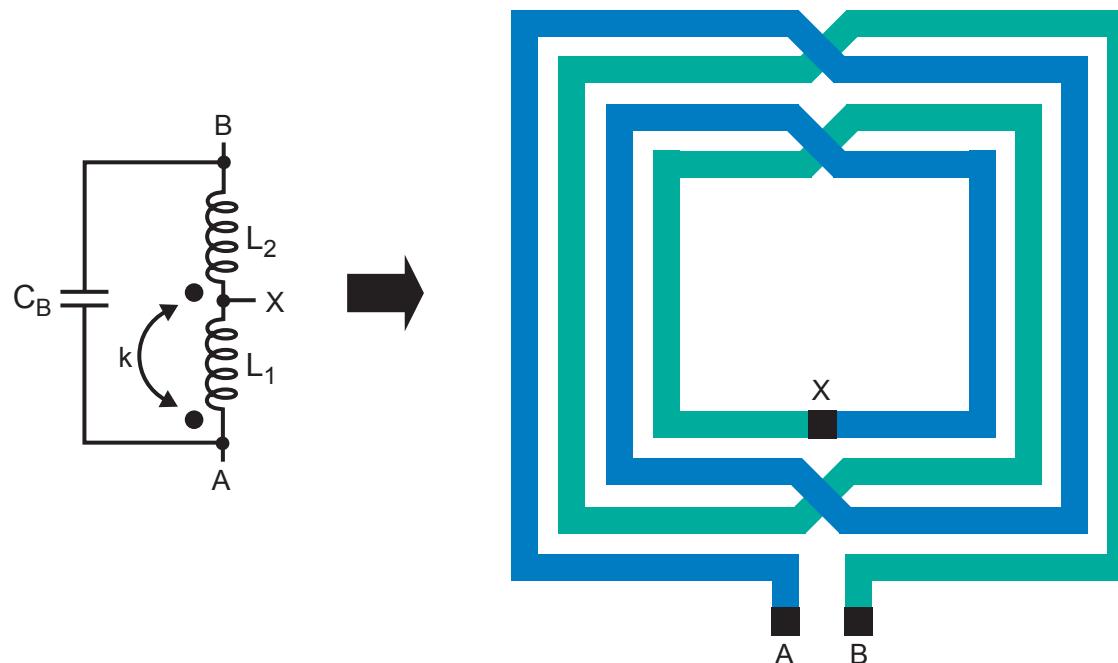
## High Speed Transformer Example – A T-Coil Network

- A T-coil consists of a center-tapped inductor with mutual coupling between each inductor half



- Used for bandwidth enhancement
  - See S. Galal, B. Ravazi, “10 Gb/s Limiting Amplifier and Laser/Modulator Driver in 0.18 $\mu$  CMOS”, ISSCC 2003, pp 188-189 and “Broadband ESD Protection ...”, pp. 182-183